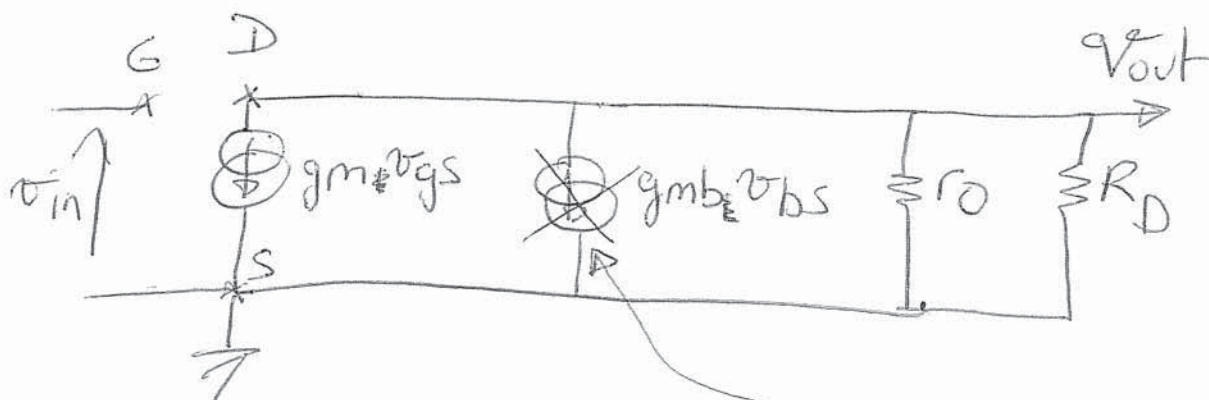


Problem 1:

1) small-signal gain  $A_v = \frac{v_{out}}{v_{in}}$



$$v_b = v_s = 0 \quad g_{mb} v_{bs} = 0 \quad (1)$$

$$v_g = v_{in} \Rightarrow v_{gs} = v_{in} \quad (2)$$


$$v_{out} = -g_m v_{gs} (r_o // R_D) \quad (3)$$

(2)  $\Rightarrow$  (3):  $v_{out} = -g_m v_{in} (r_o // R_D)$


$$\Rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_m \frac{r_o R_D}{r_o + R_D}$$

2) input impedance looking into the gate is  $R_{in} = \infty$  since no current can flow into the gate.

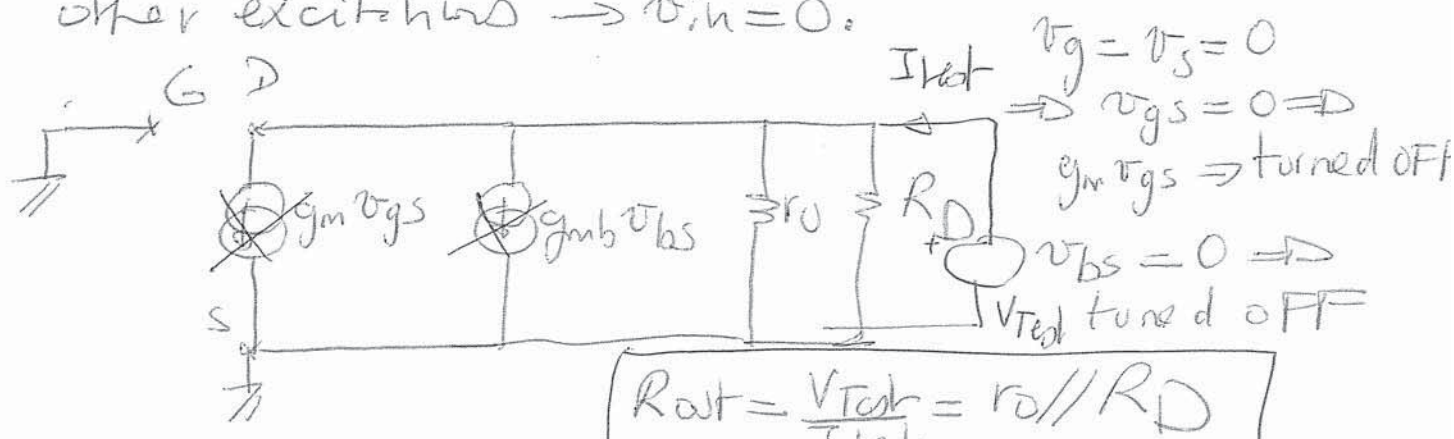3) To determine output impedance, Apply  $V_{Test}$  at the output, measure  $I_{Test}$ . Remove all other excitations  $\rightarrow v_{in} = 0$ .



### Problem 2:

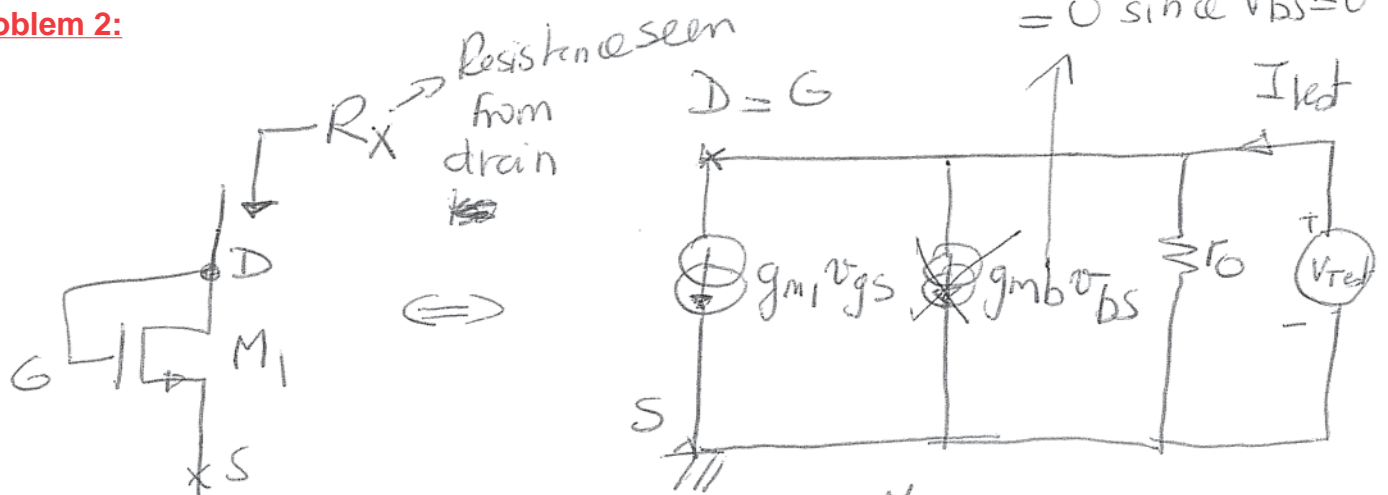

Apply  $V_{test} \Rightarrow$  Measle I test  
 $\rightarrow$  between chain and ground

$$R_X = ? \quad R_X = \frac{V_{\text{Test}}}{I_{\text{Test}}}$$


~~1st 2nd 3rd 4th~~

KCL:

$$I_{red} = \frac{V_{kck}}{r_D} + g_{m1} v_{gs}$$

$$= \frac{V_{Tst}}{r_o} + g_{m1} V_{Tst}$$
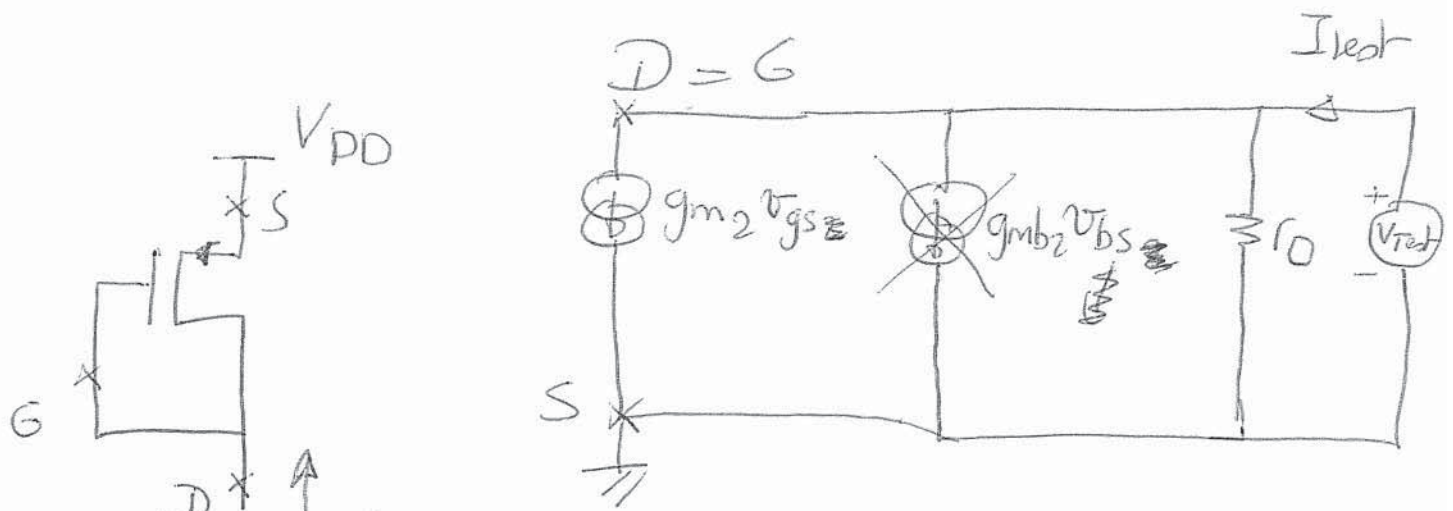
$$R_x = \frac{V_{test}}{I_{test}} = \frac{r_o}{1 + g_{m1}r_o} = r_o \parallel \frac{1}{g_{m1}}$$



$R_y \rightarrow$  resistance  
seen from  
drain

$v_{bs} = 0$  since  
 $V_{bulk} = V_{DD}$  } dc  
 and  $V_s = V_{DD}$   
~~drain is connected to ground~~

KCL:


$$I_{test} = g_{m2} v_{gs} + \frac{V_{test}}{r_o}$$

since  $v_{gs} = V_{test}$

$$\rightarrow R_y = \frac{V_{test}}{I_{test}} = \frac{r_o}{1 + g_{m2} r_o} = r_o \parallel \frac{1}{g_{m2}}$$
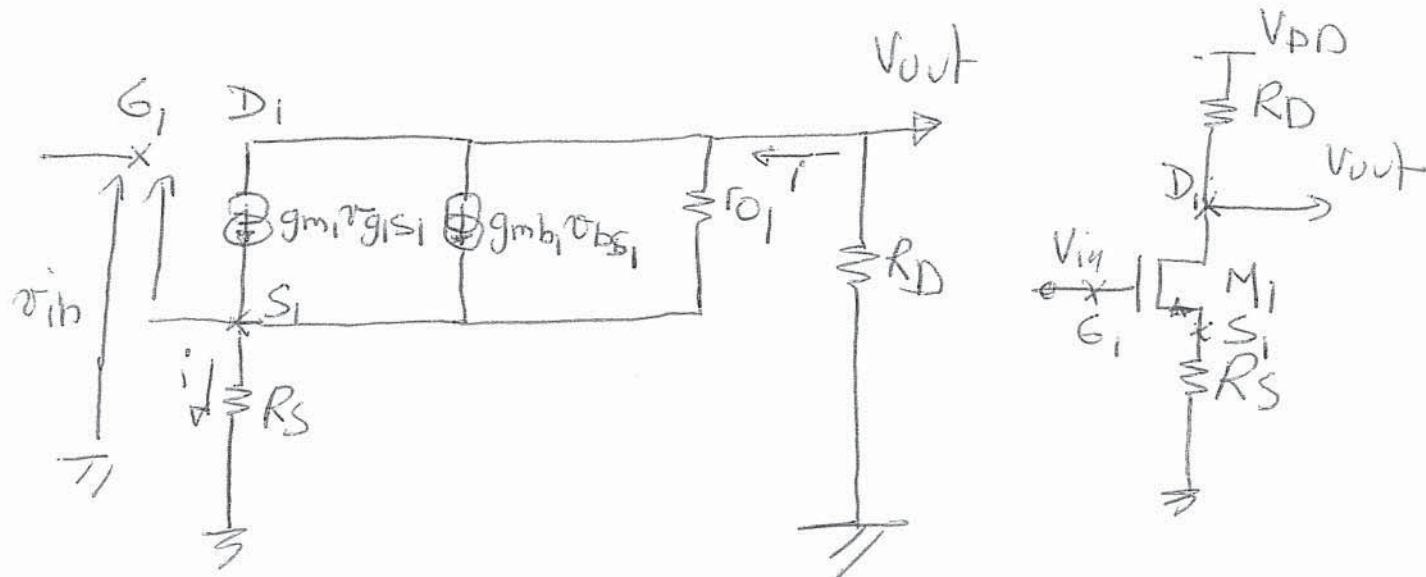
### Problem 3:

small-signal gain  $A_v = \frac{v_{out}}{v_{in}} ?$



$$v_{bs1} = 0 - v_{s1} = -v_{s1}.$$

$$v_{gs1} = v_{in} - v_{s1}.$$

$$v_{s1} = R_S i = -R_S \frac{v_{out}}{R_D} \quad (1)$$

$$\text{KCL in } S_1 \Rightarrow \cancel{g_{m1} v_{gs1}} \quad g_{m1} v_{gs1} + g_{mb1} v_{bs1} + \frac{v_{out} - v_{s1}}{r_{o1}} = \frac{v_{s1}}{R_S}$$

$$\Rightarrow g_{m1} (v_{in} - v_{s1}) + g_{mb1} (-v_{s1}) + \frac{v_{out} - v_{s1}}{r_{o1}} = \frac{v_{s1}}{R_S}$$

$$\Rightarrow g_{m1} v_{in} = -\frac{v_{out}}{r_{o1}} + v_{s1} \left( \frac{1}{R_S} + \frac{1}{r_{o1}} + g_{mb1} + g_{m1} \right) \quad (2)$$


$$(1) \text{ in } (2) \Rightarrow g_{m1} v_{in} = -\frac{v_{out}}{r_{o1}} - \frac{R_S}{R_D} v_{out} \left( \frac{1}{R_S} + \frac{1}{r_{o1}} + g_{mb1} + g_{m1} \right)$$

$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1} \cdot \frac{1}{\frac{1}{r_{o1}} + \frac{1}{R_D} + \frac{R_S}{r_{o1} R_D} + \frac{R_S}{R_D} (g_{m1} + g_{mb1})}$$

$$A_v = -g_{m1} \cdot \frac{r_{o1} R_D}{r_{o1} + R_D + R_S + r_{o1} R_S (g_{m1} + g_{mb1})}$$



Resistance looking into the drain:

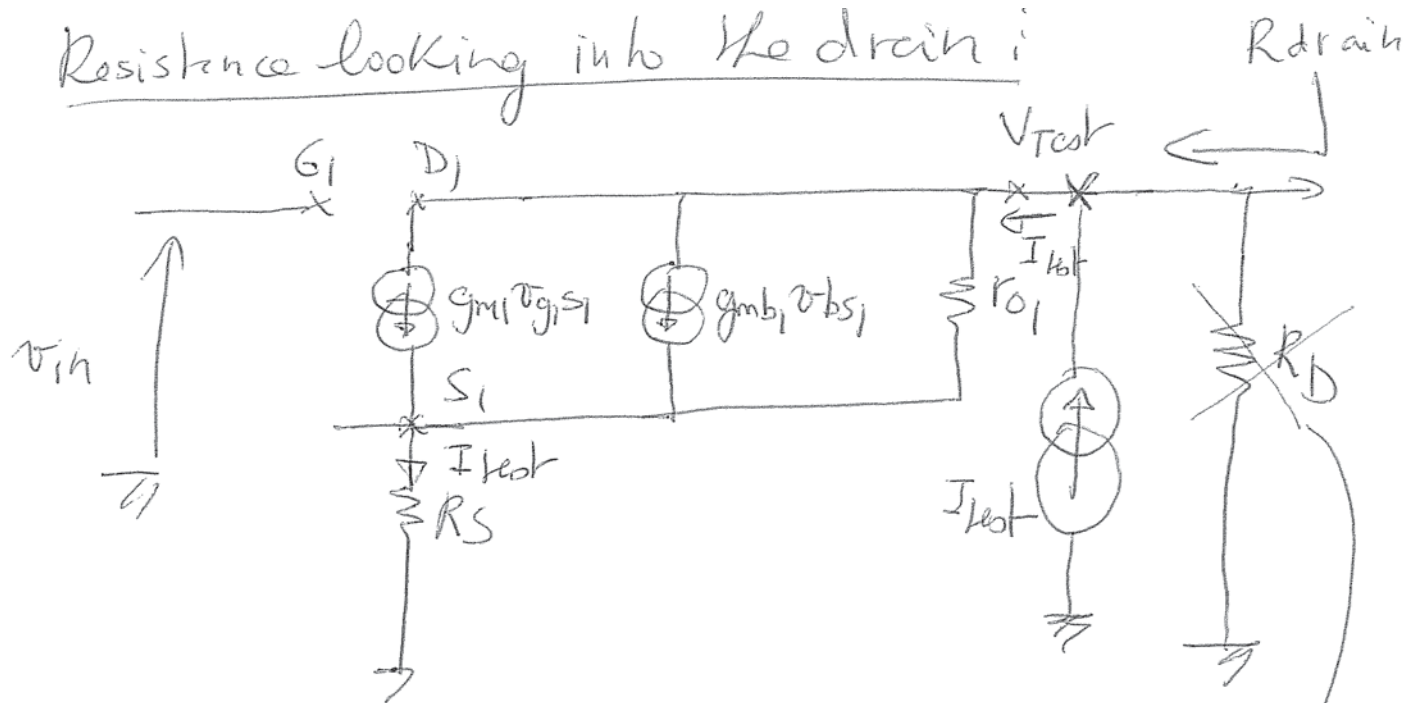

$$R_{\text{drain}} = R_D // R_{\text{Test}}$$

so we Apply here  $I_{\text{Test}}$  and determine  $V_{\text{Test}}$ .

$v_{\text{in}} = 0$  during this experiment.

$$v_{G1} = 0 \Rightarrow v_{g1s1} = -V_{S1} \quad (1)$$

$$v_{bs1} = -V_{S1} \quad (2)$$

$$\text{with } V_{S1} = R_S I_{\text{Test}} \quad (3)$$

~~Minimum  $V_{\text{Test}} = V_{S1}$~~

~~$V_{\text{Test}} = V_{S1}$~~

$$\text{KCL in } S_1: g_{m1} v_{gs1} + g_{mb1} v_{bs1} + \frac{v_{\text{Test}} - v_{S1}}{r_{o1}} = \frac{v_{S1}}{R_S} \quad (4)$$

$$(1)(2)(3) \text{ into } (4) \text{ gives: } -g_{m1} v_{S1} - g_{mb1} v_{S1} + \frac{v_{\text{Test}} - v_{S1}}{r_{o1}} = \frac{v_{S1}}{R_S}$$

$$\frac{v_{\text{Test}}}{r_{o1}} = R_S I_{\text{Test}} \left( \frac{1}{R_S} + (g_{m1} + g_{mb1}) + \frac{1}{r_{o1}} \right)$$


$$\boxed{\text{So } R_{\text{Test}} = \frac{v_{\text{Test}}}{I_{\text{Test}}} = r_{o1} R_S (g_{m1} + g_{mb1}) + r_{o1} + R_S}$$

# Resistance looking into the source:

$$R_{\text{source}} = R_S \parallel R_{\text{Test}}$$

~~with~~ with  $R_{\text{Test}}$  resistance measured at the source of the transistor, with  $V_{\text{in}} = 0$ .

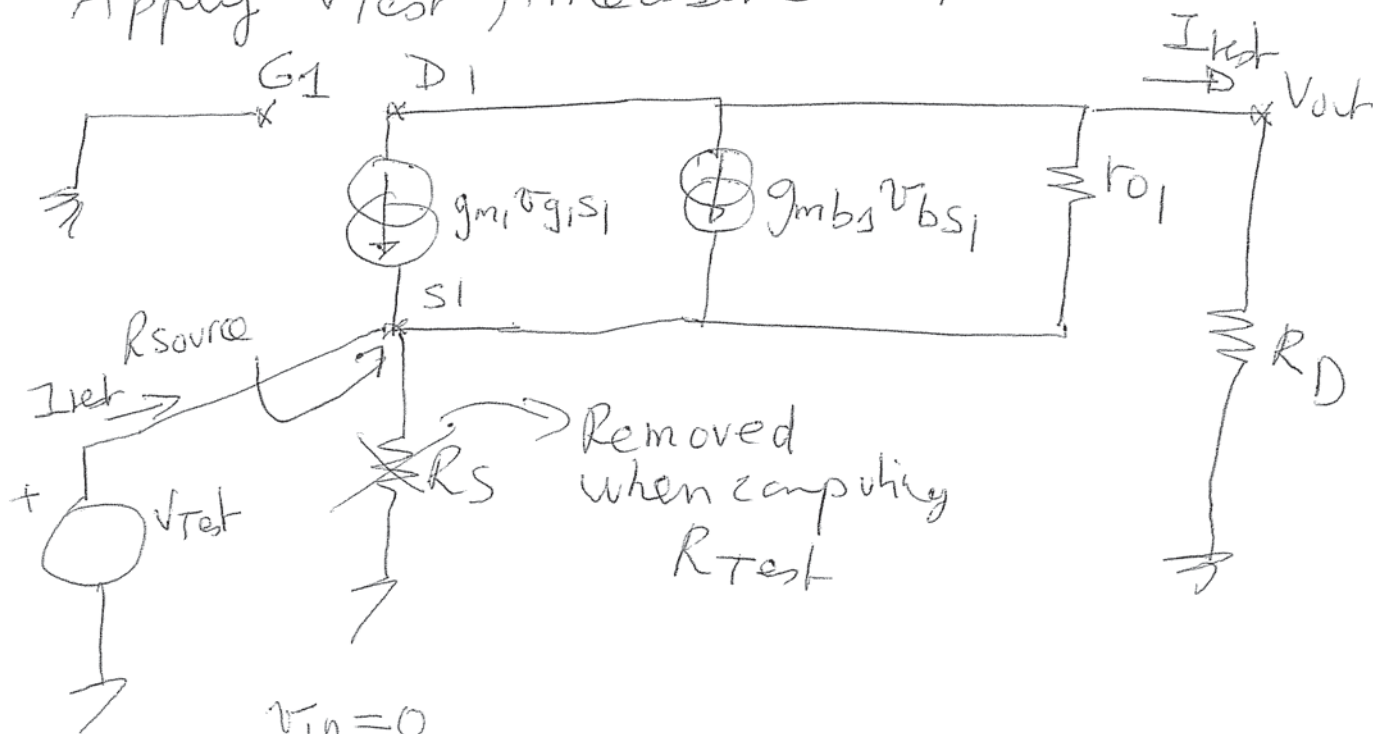Apply  $V_{\text{Test}}$ , measure  $I_{\text{Test}}$ .



$$V_{\text{in}} = 0$$

$$v_{g1s1} = v_{s1} \text{ and } v_{b1s1} = -v_{s1} \quad (1)$$

$$v_{s1} = V_{\text{Test}} \quad (2)$$



$$\text{KCL in } S1 \Rightarrow I_{\text{Test}} + g_{m1} v_{g1s1} + g_{mb1} v_{b1s1} + \frac{V_{\text{out}} - V_{\text{Test}}}{r_{o1}} = 0$$

$$\text{given that } V_{\text{out}} = R_D I_{\text{Test}} \text{ and } v_{s1} = V_{\text{Test}}$$

$$\Rightarrow I_{\text{Test}} \left( 1 + \frac{R_D}{r_{o1}} \right) = V_{\text{Test}} \left( g_{m1} + g_{mb1} + \frac{1}{r_{o1}} \right)$$

$$R_{\text{Test}} = \frac{V_{\text{Test}}}{I_{\text{Test}}} = \frac{r_{o1} + R_D}{1 + r_{o1}(g_{m1} + g_{mb1})}$$

# Problem 4:

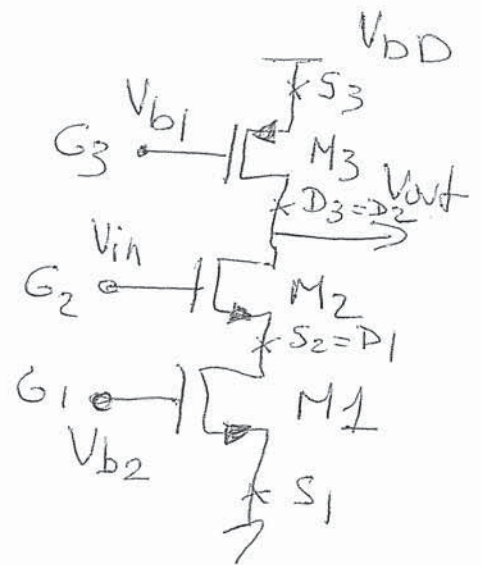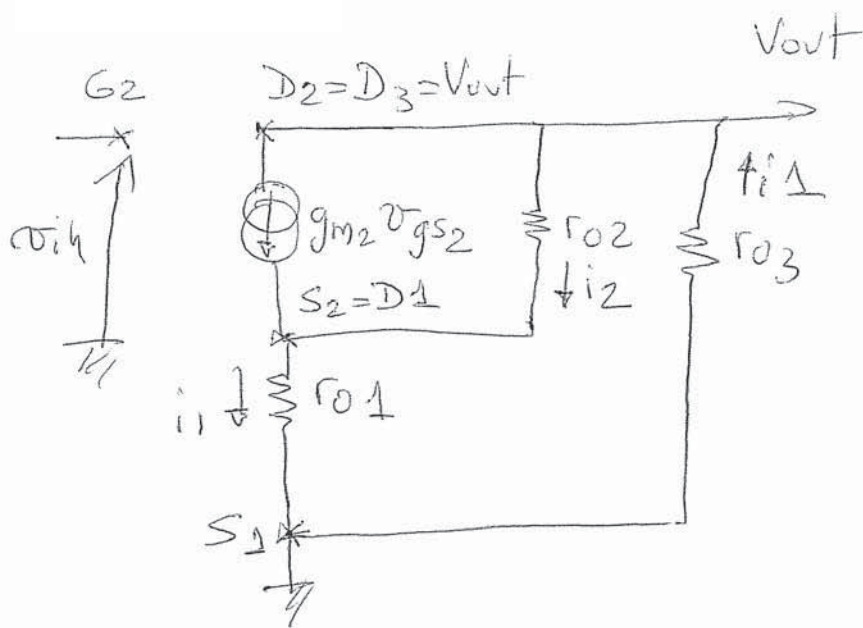

$V_{DD}, V_{b1}$  and  $V_{b2}$  dc values  $\Rightarrow v_{s3} = v_{G1} = v_{G3} = 0$  in small-signal analysis

$$v_{gs3} = v_{gs1} = 0$$

$$v_{gs2} = v_{in} - v_{s2}$$

$$\text{KCL in } S_2: g_{m2}(v_{in} - v_{s2}) + \frac{V_{out} - v_{s2}}{r_{o2}} = \frac{v_{s2}}{r_{o1}} \quad (1)$$

$$\text{Ohm's law: } V_{out} = -r_{o3} i_1 = -r_{o3} \frac{v_{s2}}{r_{o1}}$$

$$\rightarrow \boxed{v_{s2} = -\frac{r_{o1}}{r_{o3}} v_{out}} \quad (2)$$

$$(2) \text{ in } (1) \Rightarrow g_{m2}\left(v_{in} + \frac{r_{o1}}{r_{o3}} v_{out}\right) + \frac{v_{out}}{r_{o2}} + \frac{r_{o1}}{r_{o3} r_{o2}} v_{out} = -\frac{r_{o1} v_{out}}{r_{o3} r_{o1}}$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = -g_{m2} \cdot \frac{r_{o3} r_{o2}}{r_{o3} + r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}}$$

$$\boxed{A_v = -g_{m2} \cdot \frac{r_{o3} r_{o2}}{r_{o3} + r_{o1} + r_{o2}(1 + g_{m2} r_{o1})}}$$