

Tutorial 8 Bipolar junction transistor (Basic concept)

Question 1

A BJT has $I_C=1$ mA and $I_B=10$ μ A. What are I_E , β_F and α_F ?

Solution:


$$I_E = I_C + I_B = 1\text{mA} + 10\mu\text{A} = 1.01\text{mA}$$

$$\beta_F = \frac{I_C}{I_B} = \frac{1\text{mA}}{10\mu\text{A}} = 100$$

$$\alpha_F = \frac{I_C}{I_E} = \frac{1\text{mA}}{1.01\text{mA}} = 0.9901$$

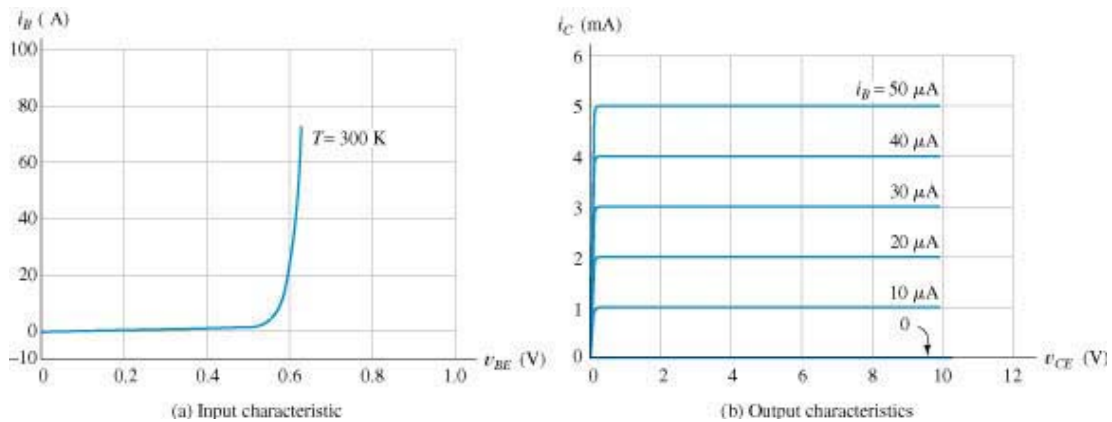Question 2

Using Device Curves of a bipolar junction transistor to determine its α and β .



Solution:

For example:


at $v_{CE}=4$ V and $i_B=30$ μ A; $i_C=3$ mA;

$$\beta = \frac{i_C}{i_B} = \frac{3\text{ mA}}{30\mu\text{A}} = 100$$

$$\alpha = \frac{\beta}{\beta + 1} = 0.99$$

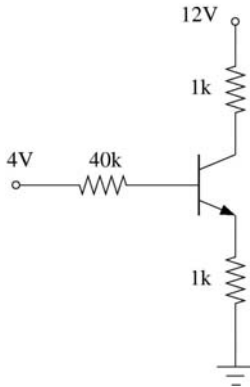Question 3

Compute transistor parameters I_B , I_C , V_{BE} , V_{CE} (Si BJT with $\beta = 100$).



Solution:

$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} + 10^3 i_E$$

$$\text{CE-KVL: } 12 = 10^3 i_C + v_{CE} + 10^3 i_E$$

Assume Cut-off: $i_B = 0$, $i_C = 0$ and $v_{BE} < V_{D0} = 0.7 \text{ V}$

$$i_E = i_B + i_C = 0$$

$$\text{BE-KVL: } 4 = 40 \times 10^3 \times 0 + v_{BE} + 10^3 \times 0 \rightarrow v_{BE} = 4 \text{ V}$$

$v_{BE} = 4 \text{ V} > V_{D0} = 0.7 \text{ V} \rightarrow$ Assumption incorrect

Because BE-KVL depends on i_E (there is a resistor in the emitter circuit), i_B would depend on the state of transistor (active or saturation)

$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} + 10^3 i_E$$

$$\text{CE-KVL: } 12 = 10^3 i_C + v_{CE} + 10^3 i_E$$

Assume Active: $i_C = \beta i_B$ and $v_{CE} \geq V_{D0} = 0.7 \text{ V}$

BE ON: $v_{BE} = V_{D0} = 0.7 \text{ V}$ and $i_B \geq 0$

$$i_E = i_B + i_C = (\beta + 1) i_B = 101 i_B$$

$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} + 10^3 \times 101 i_B$$

$$4 = (40 + 101) \times 10^3 i_B + 0.7 \rightarrow i_B = 23.4 \mu\text{A}$$

$$i_C = \beta i_B = 100 \times 23.4 \times 10^{-6} = 2.34 \text{ mA}$$

$$i_E = i_B + i_C = 2.36 \text{ mA}$$

$$\text{CE-KVL: } 12 = 10^3 \times 2.34 \times 10^{-3} + v_{CE} + 10^3 \times 2.36 \times 10^{-3} \rightarrow v_{CE} = 7.3 \text{ V}$$

$v_{CE} = 7.3 \text{ V} > V_{D0} = 0.7 \text{ V} \rightarrow$ Assumption correct

It is a very good approximation to set $i_E \approx i_C$ in the active mode!