

Tutorial 7 solutions


Problem 1:

The condition required for the transistor to be ON is $|V_{GS}| \geq |V_T|$. It follows that:


- For an NMOS to be ON requires $V_{GS} > V_T$, since V_{GS} and V_T are positive for NMOS.
- For a PMOS to be ON requires $V_{GS} < V_T$, since V_{GS} and V_T are negative for PMOS.

In order to find the operating mode of a transistor and to determine the current I_D , we must proceed as follow:

For NMOS transistor:

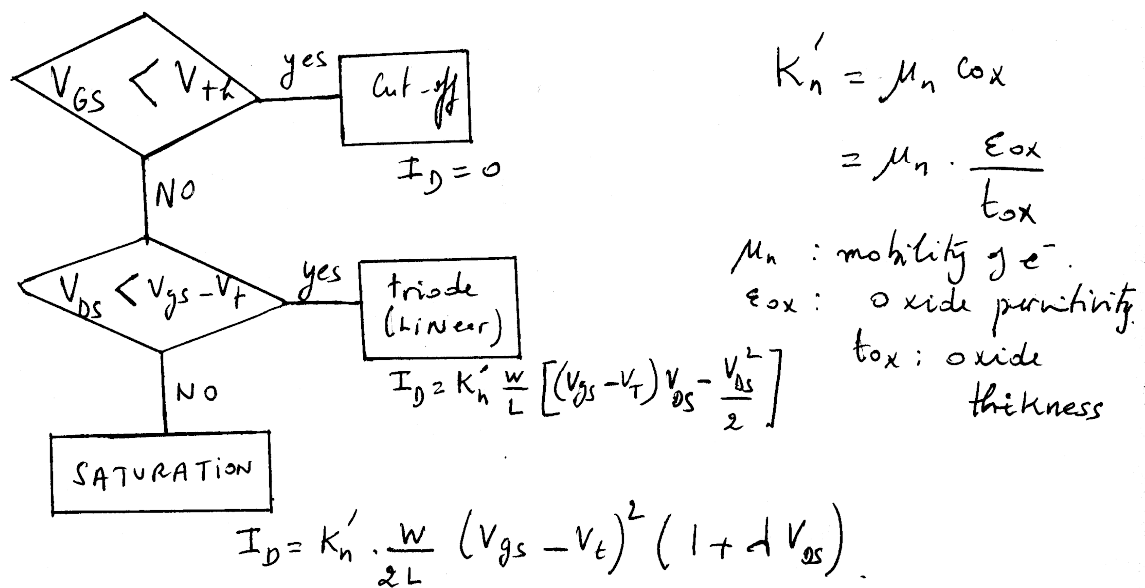

For PMOS

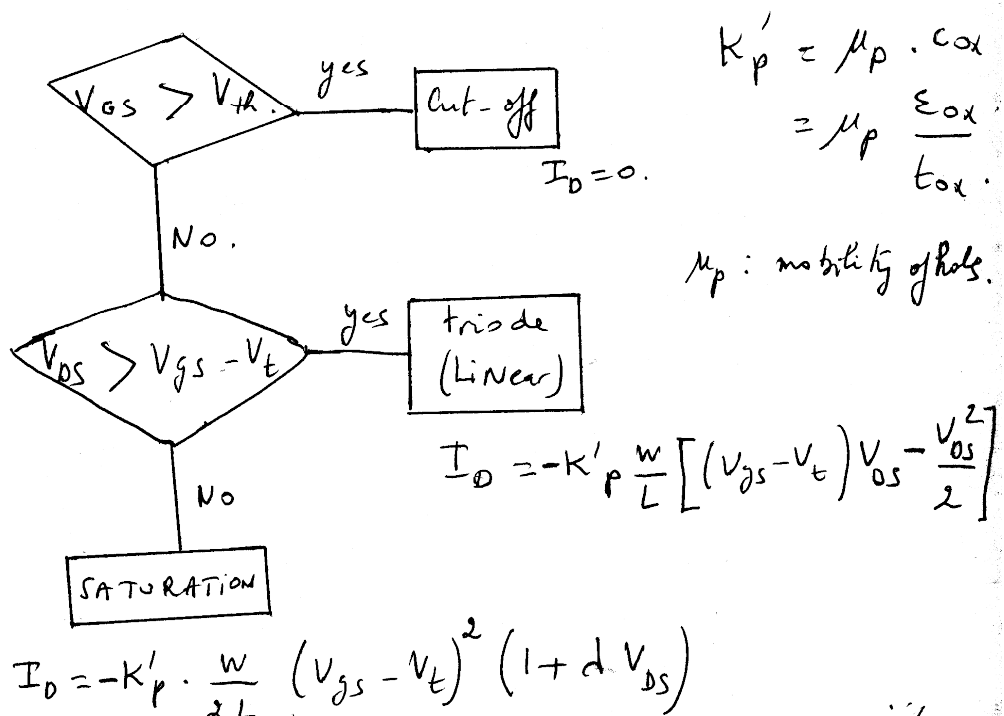

Case (a) : $V_{gs} = 3.3 \text{ V} > V_{th} \Rightarrow$ Transistor is ON
NMOS :

$$V_{ds} = 3.3 \text{ V} > V_{gs} - V_{th} = 3.3 - 0.7 = 2.6$$

\Rightarrow Transistor in the SATURATION Mode.

$$I_{D_{SN}} = \frac{k'_n}{2} \cdot \frac{W}{L} (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$$

$$= \frac{60 \mu\text{A}}{\text{V}^2} \cdot \frac{1}{2} \times 1 (3.3 - 0.7)^2 (1 + 0.1 \times 3.3)$$

$$\boxed{I_{D_{SN}} = 269.8 \mu\text{A}}$$

PMOS :

$$V_{gs} = -0.5 \text{ V} > V_{To} = -0.8 \text{ V}$$

$$\Rightarrow \text{PMOS is Cut-off} \quad \boxed{I_{D_{SP}} = 0}$$

Case (b)

NMOS : $V_{gs} = 3.3 \text{ V} > V_{th} = 0.7 \Rightarrow$ ON.

$$V_{ds} = 2.2 \text{ V} < V_{gs} - V_{th} = 3.3 - 0.7 = 2.6$$

\Rightarrow Transistor in the Triode Mode.

$$I_{D_S} = k'_n \cdot \frac{W}{L} \left[(V_{gs} - V_{th}) \cdot V_{ds} - \frac{V_{ds}^2}{2} \right]$$

$$\boxed{I_{D_{SN}} = 198 \mu\text{A}}$$

PMOS : $V_{gs} = -3.3 \text{ V} < -0.8 \text{ V} \Rightarrow$ ON

$$V_{ds} = -2.6 < V_{gs} - V_{th} = -3.3 \text{ V} - (-0.8) = -2.5 \text{ V}$$

\Rightarrow Transistor is in the SATURATION Mode

..
..

$$I_{Dsp} = -K_p' \cdot \frac{w}{2L} \left[(V_{gs} - V_t)^2 (1 + \lambda V_{ds}) \right]$$

$$= -\frac{20}{2} \left[(-2.5)^2 (1 + 0.1(-2.6)) \right]$$

$$I_{Dsp} = -78.75 \mu A$$

Case (c): NMOS:

$$V_{gs} = 0.6 V \quad V_{ds} = 0.1 V$$

$$V_{gs} = 0.6 < V_{th} = 0.7 V \Rightarrow \text{Transistor is off}$$

$$\boxed{I_{Ds} = 0}$$

pmos: $V_{gs} = -3.3 V \quad V_{ds} = -0.5 V$

$$V_{gs} < V_{th} \Rightarrow \text{on}$$

$$V_{ds} = -0.5 V > V_{gs} - V_{th} = -3.3 V + 0.8$$

$$= -2.5 V$$

\Rightarrow transistor is in the triode mode.

$$I_{Dsp} = -K_p' \cdot \frac{w}{L} \left[(V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2} \right]$$

$$= -20 \left[(-2.5) \cdot (-0.5) - \frac{(-0.5)^2}{2} \right]$$

$$\boxed{I_{Dsp} = -22.5 \mu A}$$

Problem 2:

Transistor	V_S	V_G	V_D	I_D	type	mode	$\mu C_{ox} \frac{W}{L}$	V_t
1	0	2	5	100	N	Sat.	200	1
1	0	3	5	400	N	Sat.	200	1
2	5	3	-4.5	50	P	Sat.	400	-1.5
2	5	2	-0.5	450	P	Sat.	400	-1.5
3	5	3	4	200	P	Sat.	400	-1
3	5	2	0	800	P	Sat.	400	-1
4	-2	0	0	72	N	Sat.	100	0.8
4	-4	0	-3	270	N	Triode	100	0.8

Case a) transistor 1: $V_{GS} = 2V$ $V_{DS} = 5V$ $I_D = 100\mu A$
 This must be an NMOS operating in Saturation

$$I_D = 100 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (2 - V_t)^2$$

 when $V_{GS} = 3V$: $400 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (3 - V_t)^2 \Rightarrow 4 = \frac{(3 - V_t)^2}{(2 - V_t)^2}$

$$\Rightarrow 2(2 - V_t) = 3 - V_t \Rightarrow V_t = 1V, \mu_n C_{ox} \frac{W}{L} = \frac{200\mu A}{V^2}$$

Case b) transistor 2: $V_{GS} = 3 - 5 = -2V$ $V_{DS} = -9.5V$
 Therefore $V_{DS} < V_{GS} - V_t$ regardless of value of V_t ,
 and the device operates in saturation. (PMOS)

$$I_D = 50 = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (-2 - V_t)^2$$

$$450 = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (-3 - V_t)^2 \Rightarrow 9 = \frac{(3 + V_t)^2}{(2 + V_t)^2}$$

$$\Rightarrow 3(2 + V_t) = 3 + V_t \Rightarrow V_t = -1.5V, \mu_p C_{ox} \frac{W}{L} = \frac{400\mu A}{V^2}$$

case c) transistor 3: $V_{GS} = -2V$ $V_{DS} = -1V \Rightarrow$ PMOS
 This device can be either in saturation or triode region. First, we assume saturation region:

$$I_D = 200 = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (-2 - V_t)^2$$

$$800 = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (-3 - V_t)^2 \Rightarrow 4 = \frac{(3 + V_t)^2}{(2 + V_t)^2}$$

$$\Rightarrow 2(2 + V_t) = 3 + V_t \Rightarrow V_t = -1V, \mu_p C_{ox} \frac{W}{L} = \frac{400\mu A}{V^2}$$

 So our assumption was right:

$$(V_{DS} = -1V) < (V_{GS} - V_t) = -2 + 1 = -1V$$

edge of saturation

Case d) transistor 4: $V_{GS} = 2V$ $V_{DS} = 2V \Rightarrow$ NMOS

So $V_{DS} > V_{GS} - V_t \Rightarrow$ Saturation region

$$\textcircled{1} I_D = 72 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (2 - V_t)^2$$

But for $V_{GS} = 4V$, $V_{DS} = 1V$ and considering that $V_t < 2V$, then the device is in triode region:

$$270 = \mu_n C_{ox} \frac{W}{L} \left[(4 - V_t) \times 1 - \frac{1}{2} \times 1 \right]$$



$$\textcircled{2} 270 = \mu_n C_{ox} \frac{W}{L} (3.5 - V_t)$$

$$\textcircled{1,2} \Rightarrow V_t = 0.8V \quad \mu_n C_{ox} \frac{W}{L} = 100 \mu A/V^2$$

Problem 3

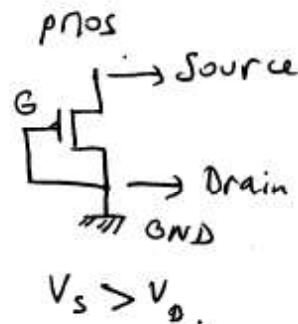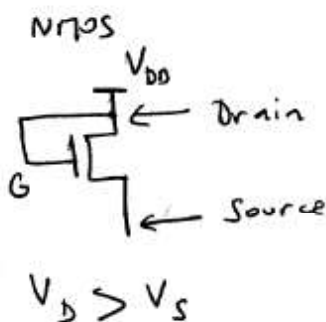a) before finding out the operating mode of the transistors, we need to figure out the drain and the source terminals of the transistor.

Remember ! - The source of an NMOS is at Lower voltage compared to the drain $V_S < V_D$ for NMOS
and - the source of a PMOS is at Higher voltage compared to the drain $V_S > V_D$ for PMOS.



for both transistors the gate is connected to the drain
 $\Rightarrow V_{GS} = V_{DS}$.

For the NMOS transistor $V_g = V_{DD} \Rightarrow$ Transistor is ON when $V_{GS} > V_{thn} \Rightarrow V_g - V_S > V_{thn}$

$$\Rightarrow V_{DD} - V_S > V_{thn} \Rightarrow \boxed{V_S < V_{DD} - V_{thn}} \rightarrow \text{ON.}$$

When the NMOS is ON $V_{DS} > V_{GS} - V_{thn}$ is always true.
 \Rightarrow SATURATION. because $V_{DS} = V_{GS}$

So For $V_S < V_{DD} - V_{thN}$ the transistor is SATURATED
 For $V_S > V_{DD} - V_{thN}$ the transistor is Cut-off

For the PMOS transistor $V_g = 0 \Rightarrow$ transistor is ON when $V_{gs} < V_{th}$ $\Rightarrow V_g - V_S < V_{thp}$
 $\Rightarrow V_S > -V_{thp}$ (with $V_{thp} < 0$)

when the NMOS is ON $V_{DS} < V_{gs} - V_{thp}$
 is always true because $V_{DS} = V_{gs}$
 \Rightarrow SATURATION.


So For the PMOS

For $V_S > -V_{thp}$ SATURATION


$V_S < -V_{thp}$ the transistor is Cut-off.

To Summarize :

For NMOS

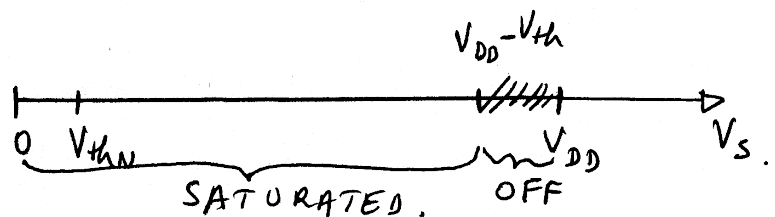

For PMOS.

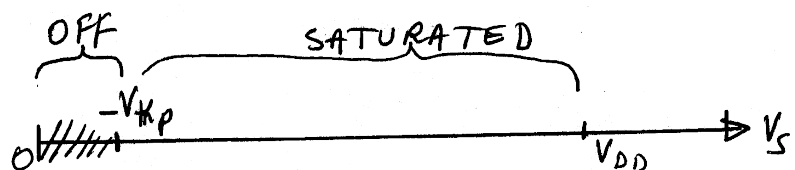

b) For $V_s = \frac{V_{dd}}{2}$ both transistors are saturated. (3)

NMOS: $\Rightarrow I_{D_{sN}} = \frac{K'_n}{2} \frac{W}{L} (V_{gs} - V_t)^2 (1 + \lambda V_{ds})$.

$$V_{gs} = V_g - V_s = V_{dd} - \frac{V_{dd}}{2} = \frac{V_{dd}}{2} = 2.5V$$

$$V_{ds} = V_d - V_s = V_{dd} - \frac{V_{dd}}{2} = \frac{V_{dd}}{2} = 2.5V$$

$$I_{D_{sN}} = \frac{60 \mu A/V^2}{2} \cdot 1 \cdot (2.5 - 0.7)^2 (1 + 0.1 \times 2.5)$$

$$\boxed{I_{D_s} = 121.5 \mu A.}$$

PMOS: $I_{D_{sP}} = -\frac{K'_p}{2} \frac{W}{L} (V_{gs} - V_t)^2 (1 + \lambda V_{ds})$.


$$V_{gs} = V_g - V_s = 0 - \frac{V_{dd}}{2} = -2.5V.$$

$$V_{ds} = V_d - V_s = 0 - \frac{V_{dd}}{2} = -2.5V$$

$$I_{D_{sP}} = -\frac{20 \mu A/V^2}{2} \cdot 1 \cdot (-2.5 - (-0.8))^2 (1 - 0.1 \cdot (-2.5))$$

$$\boxed{I_{D_{sP}} = -36.125 \mu A}$$

Problem 4:

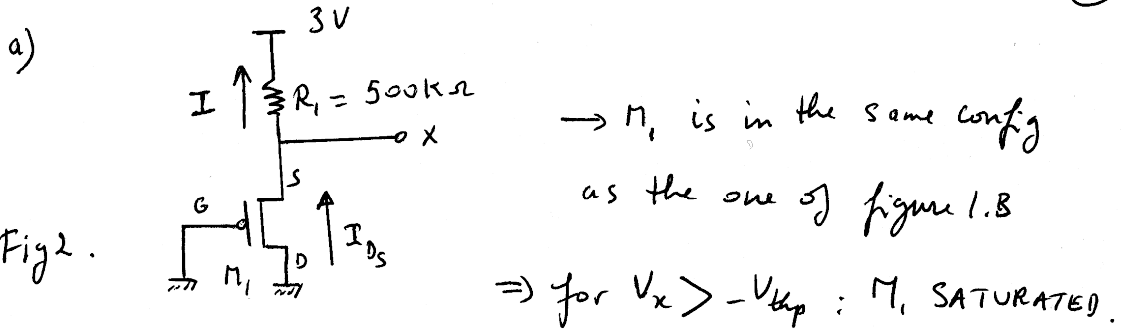

$$I_{Ds} = -\frac{k_p'}{2} \cdot \frac{W}{L} \cdot (V_{gs} - V_{thp})^2 (1 + \lambda V_{Ds})$$

$$V_{gs} = V_g - V_s = 0 - V_x$$

$$V_{Ds} = V_d - V_s = 0 - V_x$$

$$I_{Ds} = -\frac{k_p'}{2} \cdot \frac{W}{L} (-V_x - V_{thp})^2 (1 - \lambda V_x)$$

$$V_{thp} \text{ is negative } \Rightarrow V_{thp} = -|V_{thp}|$$

$$\Rightarrow I_{Ds} = -\frac{k_p'}{2} \cdot \frac{W}{L} (-V_x - |V_{thp}|)^2 (1 - \lambda V_x)$$

$$I_{Ds} = \ominus \frac{k_p'}{2} \cdot \frac{W}{L} (V_x - |V_{thp}|)^2 (1 - \lambda V_x)$$

b) Voltage V_x = ?

From figure 2, we can write that $I_{Ds} = I$

$$I = \ominus \frac{3V - V_x}{R} = I_{Ds} = -\frac{k_p'}{2} \cdot \frac{W}{L} (V_x - |V_{thp}|)^2 (1 - \lambda V_x)$$

$$\text{For } \lambda = 0 \Rightarrow (3V - V_x) = \frac{R}{2} k_p' \cdot \frac{W}{L} (V_x - |V_{thp}|)^2$$

c) The required width of the transistor : W .

$$\frac{3 - V_x}{R} = \frac{k'_p}{2} \cdot \frac{W}{L} (V_x - |V_{thp}|)^2$$

$$\Rightarrow \frac{1.5V}{500k\Omega} = \frac{5.4 \cdot 10^{-6} \text{ MA/V}^2}{2} \cdot \frac{W}{L} (1.5 - |V_{thp}|)^2$$

$$\text{for } L = 1.2\mu\text{m} \quad \text{and} \quad |V_{thp}| = 0.739$$

$$\Rightarrow \boxed{W = 2.3\mu\text{m}}$$