

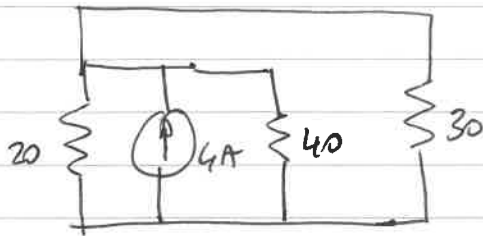


TENSC 3021 2019 TUTORIAL Questions 1A.

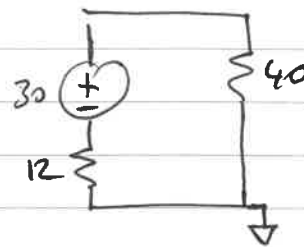
Q1 use superposition to find voltage across resistor  
 Power =  $P = VI = V^2/R$ .





$$V_{1a} = 36.923V$$

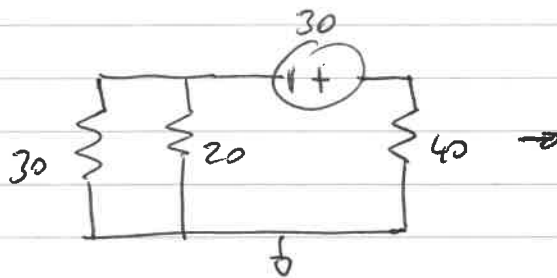

$$V_{1b} = 23.077V$$

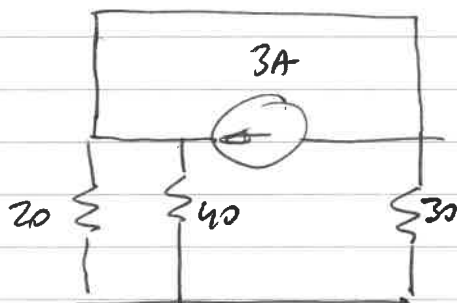
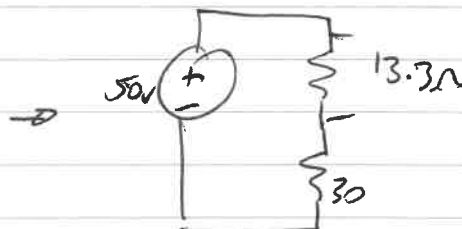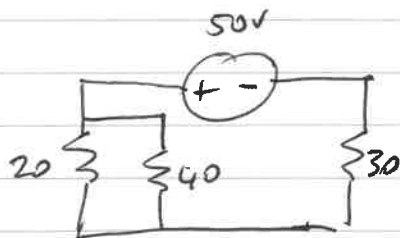
$$V_{1c} = 0V \quad \text{as current source is shorted.}$$




$$V_{1d} = 15.385V$$

$$V_1 = V_{1a} + V_{1b} + V_{1c} + V_{1d} = 75.385$$


$$\text{Power} = 75.385^2 / 40 = \underline{142 \text{ watts}}$$

Q2

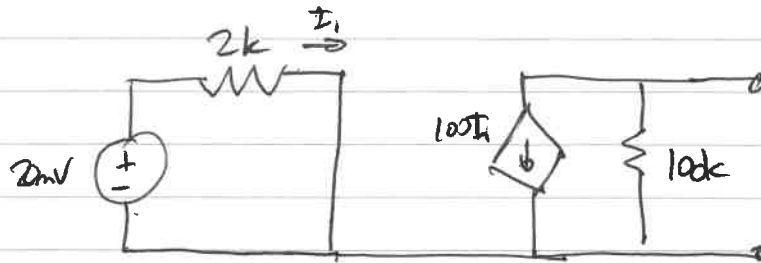


$$I_1 = \frac{2\text{mV}}{2\text{k}} = 10\mu\text{A} \quad \Rightarrow \quad 100 I_1 = 1\text{mA}$$

So Norton equivalent:

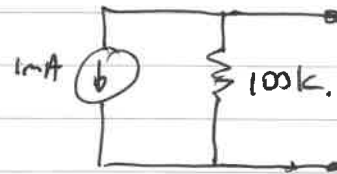


Thevenin equivalent:

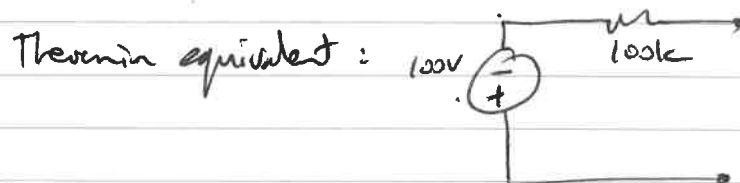

Note the open circuit voltage will be -100V, and resistance looking in 100k when independent sources removed as  $I_1 = 0$  in that case.

Q3. Use Superposition again, with nodal analysis at each node to solve for the voltage.

Step 1  
Just the  
voltage  
source

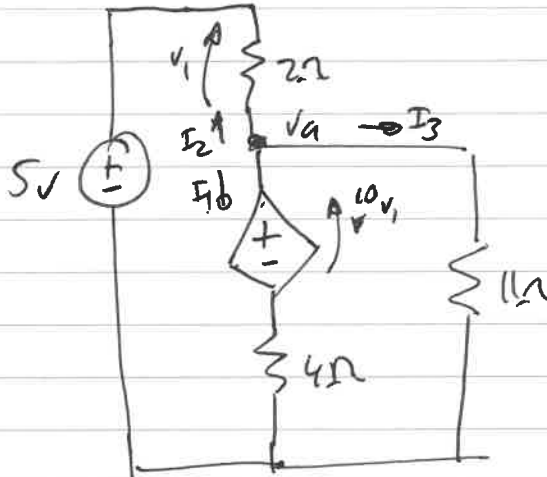

note  $V_1 = 5 - V_a$

$$I_1 + I_2 + I_3 = 0$$

$$I_3 = \frac{V_a}{11} \quad I_2 = \frac{V_a - 5}{2}$$

to find  $I_1$  go around the loop on the left with KVL

$$5 = 11V_1 + 4I_1 \quad V_1 = 5 - V_a$$


$$5 = 11(5 - V_a) + 4I_1$$

$$I_1 = \frac{1}{4}(11V_a - 50)$$

$$\frac{V_a}{11} + \frac{V_a - 5}{2} + \frac{1}{4}(11V_a - 50) = 0$$

$$\Rightarrow \underline{\underline{V_{a1} = 4.48979 \text{ V}}}$$

Step 2 Just the current source.

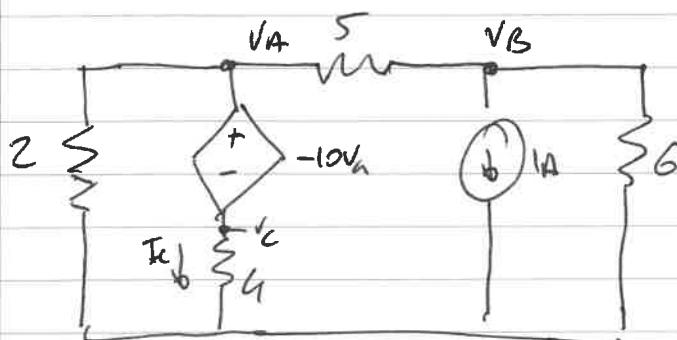

KCL at node B:

$$\frac{V_B - V_A}{5} + 1 + \frac{V_B}{6} = 0 \quad (1)$$

KCL at node A:

$$\frac{V_A}{2} + \frac{V_A - V_B}{5} + I_1 = 0$$

$$I_1 = V_c/4, \quad \text{KVL around left loop gives } V_c = 11V_a$$


$$\Rightarrow \left(\frac{1}{2} + \frac{1}{5} + \frac{11}{4}\right)V_a = \frac{V_B}{5} \quad (2)$$

Solving ① + ② gives  $V_{a2} = -0.1633 \text{ V}$

$$V_a = V_{a1} + V_{a2} = 4.327 \text{ V} \Rightarrow$$

$$\boxed{V_1 = 5 - 4.327 = 0.673 \text{ V}}$$

Q4. First find open circuit voltage

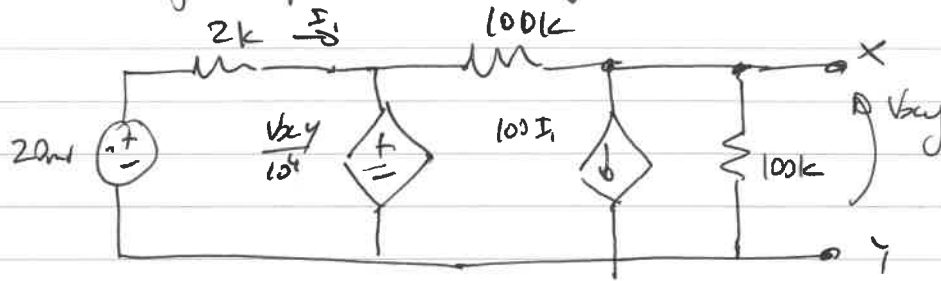

$$i_1 = \frac{20\text{mV} - V_{xy}}{2\text{k}}$$


KCL at node X:  $100i_1 + \frac{V_{xy}}{10^5} + \frac{V_{xy} - V_{xy}}{10^5} = 0$

$$\frac{1.9999 V_{xy}}{10^5} + \frac{100}{2000} \left( \frac{20 \times 10^{-3}}{2000} - \frac{V_{xy}}{10^5} \right) = 0$$


$$\Rightarrow \boxed{V_{xy} = -66.67\text{V}}$$

~~Now circuit is with independent~~

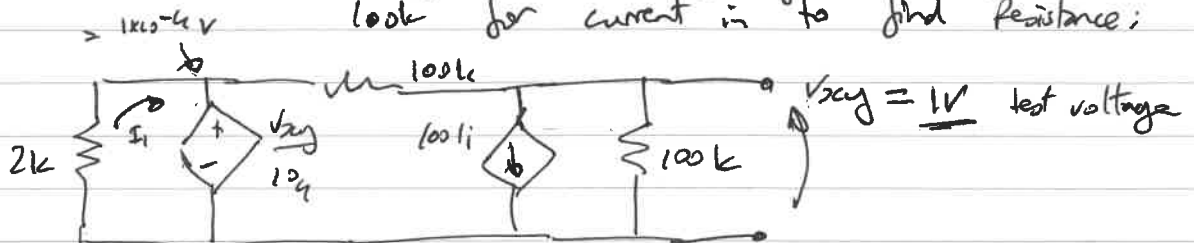Now equivalent resistance looking in when independent source removed:  
 - Apply a test voltage of 1V @ xy and look for current in to find resistance;


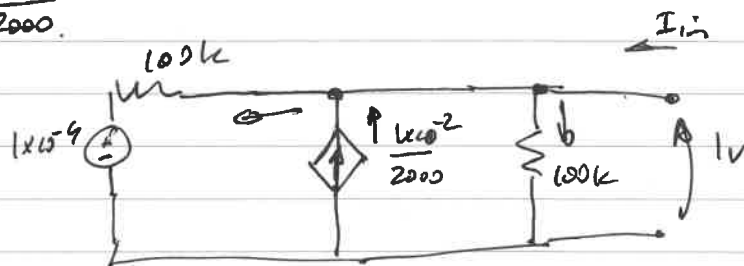
$$i_1 = - \frac{1 \times 10^{-4}}{2000}$$



KCL @ node X:  $\frac{1 \times 10^{-2}}{2000} - \frac{1 - 1 \times 10^{-4}}{10^5} - \frac{1}{10^5} + i_{in} = 0$

$$5\mu\text{A} - 10\mu\text{A} - 10\mu\text{A} + i_{in} = 0 \Rightarrow i_{in} = 15\mu\text{A}$$

$$R_{th} = \frac{1\text{V}}{15\mu\text{A}} = \boxed{66.67\text{k}\Omega}$$

$$\boxed{V_{th} = -66.67\text{V}}$$