

Q.1 Reduce the following Boolean expressions to the required number of literals.

(a) $ABC + \overline{A}\overline{B}C + \overline{A}BC + AB\overline{C} + \overline{A}\overline{B}\overline{C}$ to five literals

$$\begin{aligned}
 (a) \quad & ABC + \overline{A}\overline{B}C + \overline{A}BC + AB\overline{C} + \overline{A}\overline{B}\overline{C} \\
 &= BC(\cancel{A+\overline{A}}) + \overline{A}\overline{B}(\cancel{C+\overline{C}}) + AB\overline{C} \\
 &= BC + \overline{A}\overline{B} + AB\overline{C} \\
 &= B(C + A\overline{C}) + \overline{A}\overline{B} \\
 &= B(C + A)(\cancel{C+\overline{C}}) + \overline{A}\overline{B} \\
 &= B(A + C) + \overline{A}\overline{B}
 \end{aligned}$$

(b) $\overline{[(\overline{CD}) + A]} + A + CD + AB$ to three literals

$$\begin{aligned}
 (b) \quad & \overline{[(\overline{CD}) + A]} + A + CD + AB \\
 &= CD\overline{A} + A + CD + AB \\
 &= CD(\cancel{\overline{A}+1}) + A(\cancel{1+B}) \\
 &= CD + A
 \end{aligned}$$

(c) $(A+C+D)(A+C+\bar{D})(A+\bar{C}+D)(A+\bar{B})$ to four literals.

$$\begin{aligned}
 & (c) \quad (A+C+D)(A+C+\bar{D})(A+\bar{C}+D)(A+\bar{B}) \\
 &= \left[(A+C)(A+C) + (A+C)\bar{D} + (A+C)D + \cancel{D\bar{D}} \right] (A+\bar{C}+D)(A+\bar{B}) \\
 &= (A+C) \underbrace{\left[(A+C) + \underbrace{\bar{D}+D}_1 \right]}_1 (A+\bar{C}+D)(A+\bar{B}) \\
 &= (A+C)(A+\bar{C}+D)(A+\bar{B}) \\
 &= (AA + A\bar{C} + AD + CA + \cancel{C\bar{C}} + CD)(A+\bar{B}) \\
 &= \left[A \underbrace{\left[A + D + \underbrace{\bar{C}+C}_1 \right]}_1 + CD \right] (A+\bar{B}) \\
 &= (A+CD) \underbrace{(A+\bar{B})}_1 = A + \bar{B}CD \\
 & \quad \text{(since } A + ACD + A\bar{B} = A)
 \end{aligned}$$

Q.2 For each of the problems in Q.1, draw up a truth table and show that the simplified expressions are equivalent to the original Boolean expressions.

(a)

A	B	C	ABC	$\bar{A}\bar{B}C$	$\bar{A}B\bar{C}$	$A\bar{B}\bar{C}$	$\bar{A}\bar{B}\bar{C}$	OUTPUT
0	0	0	0	0	0	0	1	1
0	0	1	0	1	0	0	0	1
0	1	0	0	0	0	0	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	1	0	1
1	1	1	1	0	0	0	0	1

A	B	C	$B(A+C)$	$\bar{A}\bar{B}$	OUTPUT
0	0	0	0	1	1
0	0	1	0	1	1
0	1	0	0	0	0
0	1	1	1	0	1
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	1	0	1
1	1	1	1	0	1

Thus $B(A+C) + \bar{A}\bar{B}$

$$= ABC + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$$

(b)

ABCD	$\overline{CD} + A$	A	CD	AB	Z	CD	A	Z*
0000	0	0	0	0	0	0	0	0
0001	0	0	0	0	0	0	0	0
0010	0	0	0	0	0	0	0	0
0011	1	0	1	0	1	1	0	1
0100	0	0	0	0	0	0	0	0
0101	0	0	0	0	0	0	0	0
0110	0	0	0	0	0	0	0	0
0111	1	0	1	0	1	1	0	1
1000	0	1	0	0	1	0	1	1
1001	0	1	0	0	1	0	1	1
1010	0	1	0	0	1	0	1	1
1011	0	1	1	0	1	1	1	1
1100	0	1	0	1	1	0	1	1
1101	0	1	0	1	1	0	1	1
1110	0	1	0	1	1	0	1	1
1111	0	1	1	1	1	1	1	1

$$Z = \overline{CD} + A + A + CD + AB$$

$$Z^* = \overline{CD} + A$$

By the truth table, $Z = Z^*$

(c)


ABCD	$A + C + D$	$A + C + \overline{D}$	$A + \overline{C} + D$	$A + \overline{B}$	Z	A	$\overline{B}CD$	Z*
0000	0	1	1	1	0	0	0	0
0001	1	0	1	1	0	0	0	0
0010	1	1	0	1	0	0	0	0
0011	1	1	1	1	1	0	1	1
0100	0	1	1	1	0	0	0	0
0101	1	0	1	0	0	0	0	0
0110	1	1	0	0	0	0	0	0
0111	1	1	1	0	0	0	0	0
1000	1	1	1	1	1	1	0	1
1001	1	1	1	1	1	1	0	1
1010	1	1	1	1	1	1	0	1
1011	1	1	1	1	1	1	0	1
1100	1	1	1	1	1	1	0	1
1101	1	1	1	1	1	1	0	1
1110	1	1	1	1	1	1	0	1
1111	1	1	1	1	1	1	0	1

$$Z = (A + C + D)(A + C + \overline{D})(A + \overline{C} + D)(A + \overline{B}), \quad Z^* = A + \overline{B}CD$$


Again $Z = Z^*$

Q.3 For each of the problems in Q.1, draw a logic circuit implementation of the simplified expressions using AND, OR and NOT gates.


a)

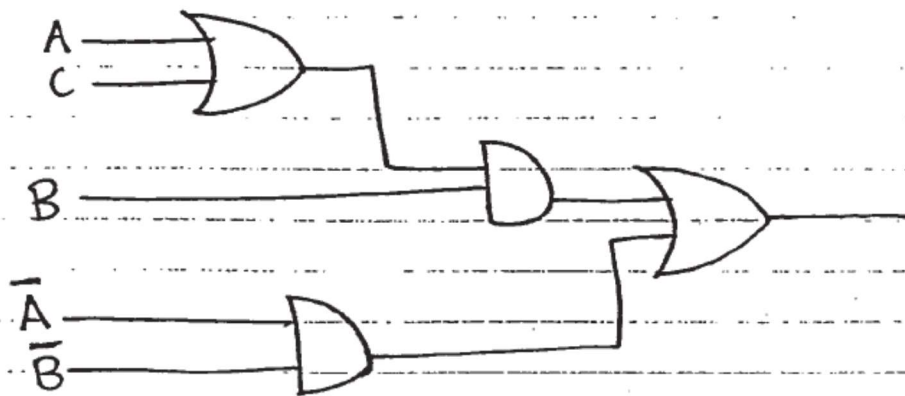

b)

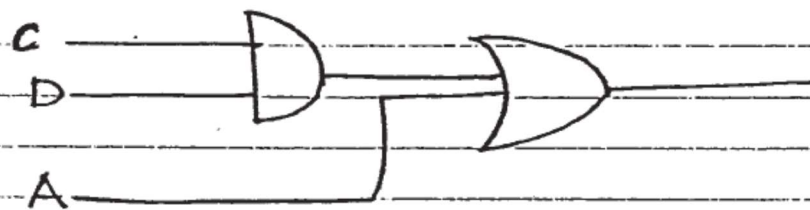

c)

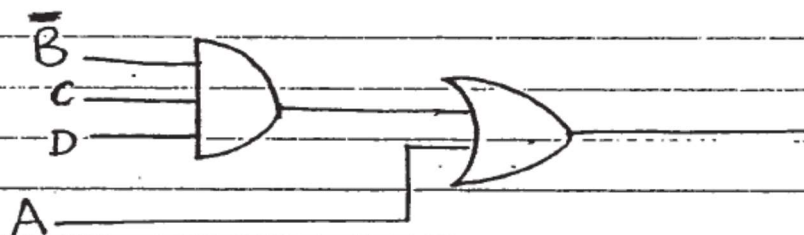

Q4. Use Karnaugh maps to simplify the following Boolean function in:

- (a) Sum-of-products, and
- (b) Product-of-sums form.

$$F = \bar{W} (\bar{X}Y + \bar{X}\bar{Y} + XYZ) + \bar{X}\bar{Z} (Y + W)$$

$$\text{"don't care"} = \bar{W}X (\bar{Y}Z + Y\bar{Z}) + WYZ$$

$$F = \bar{W}(\bar{X}Y + \bar{X}\bar{Y} + XYZ) + \bar{X}\bar{Z}(Y+W)$$


$$d = \bar{W}X(\bar{Y}Z + Y\bar{Z}) + WYZ$$

(a)

		YZ			
WX		00	01	11	10
00		1	1	1	1
01			X	1	X
11				X	
10		1		X	1

$\bar{X}\bar{Z}$ (points to the group of 1s in the first column, WX=00)
 $\bar{W}Z$ (points to the group of 1s in the first and fifth columns, WX=00 and WX=10)

$$F = \bar{X}\bar{Z} + \bar{W}Z$$

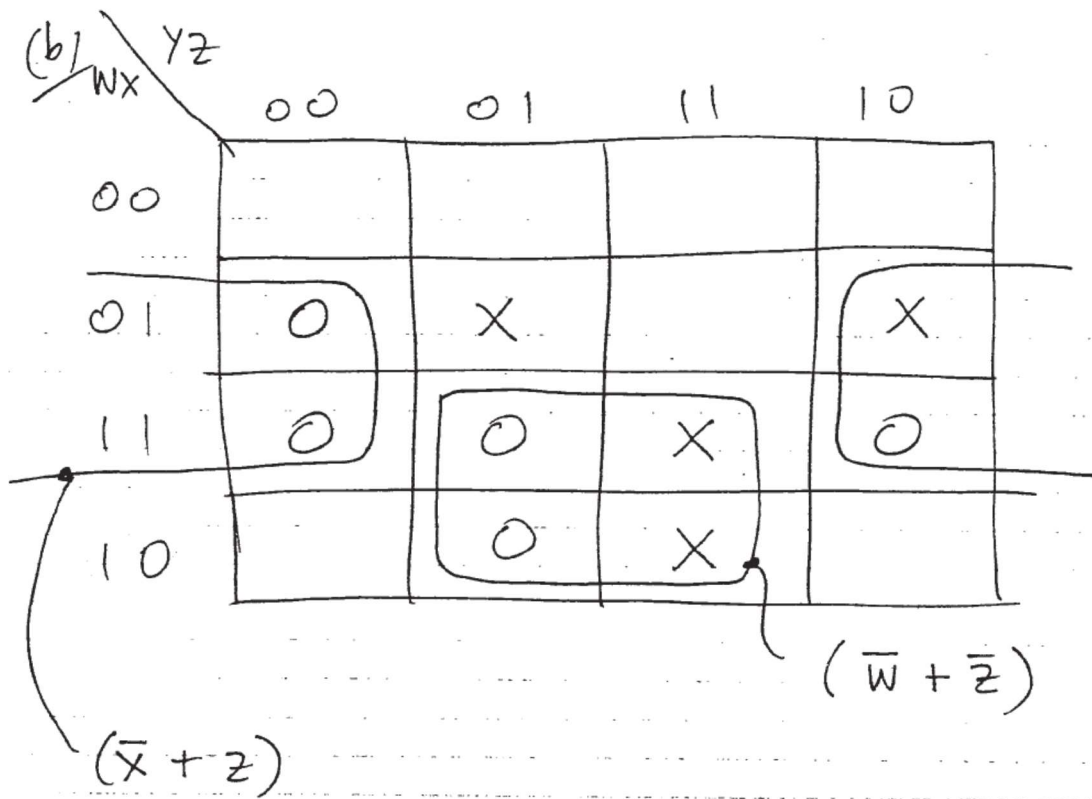

$$F = (\bar{w} + \bar{z})(\bar{x} + z)$$