

Solution 14.1

Find the transfer function $\mathbf{I}_o/\mathbf{I}_i$ of the RL circuit in Fig. 14.68. Express the transfer function using $\omega_o = R/L$.

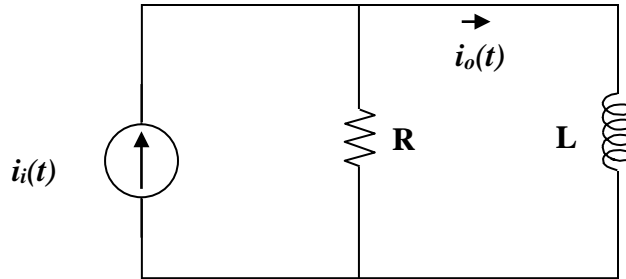


Figure 14.68
For Prob. 14.1.


Solution

$$\mathbf{H}(\omega) = \mathbf{I}_o/\mathbf{I}_i = [Rj\omega L/(R+j\omega L)]/(j\omega L) = 1/(1+j\omega L/R)$$

If we let $\omega_o = R/L$ we get $\mathbf{H}(\omega) = 1/(1+j\omega/\omega_o)$.

$$H = |\mathbf{H}(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_o}\right)^2}} \quad \text{and} \quad \theta = \angle \mathbf{H}(\omega) = -\tan^{-1}(\omega/\omega_o)$$

This is a highpass filter. The frequency response is the same as that for P.P.14.1 except that $\omega_o = R/L$. Thus, the sketches of H and ϕ are shown below.

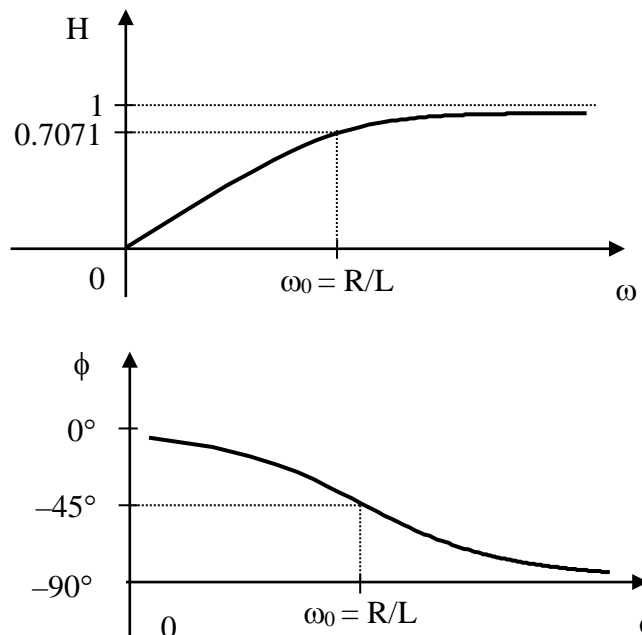

Solution 14.2

Using Fig. 14.69, design a problem to help other students to better understand how to determine transfer functions.

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

Obtain the transfer function V_o/V_i of the circuit in Fig. 14.66.

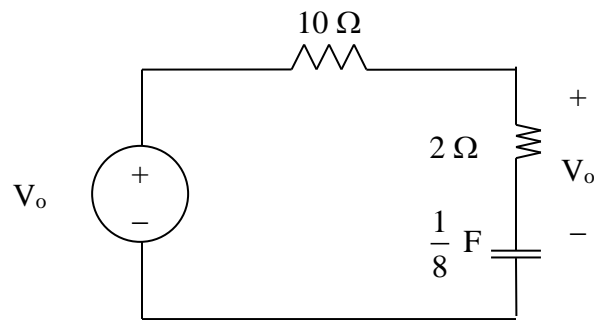


Figure 14.66

For Prob. 14.2.

Solution

$$H(s) = \frac{V_o}{V_i} = \frac{2 + \frac{1}{s/8}}{10 + 20 + \frac{1}{s/8}} = \frac{2 + 8/s}{12 + 8/s} = \frac{1}{6} \frac{s + 4}{s + 0.6667}$$

Solution 14.3

For the circuit shown in Fig. 14.67, find $\mathbf{H}(s) = \mathbf{V}_o(s)/\mathbf{I}_i(s)$.


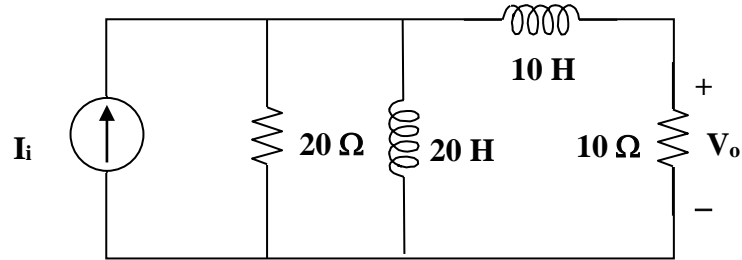


Figure 14.67
For Prob. 14.3.

Solution

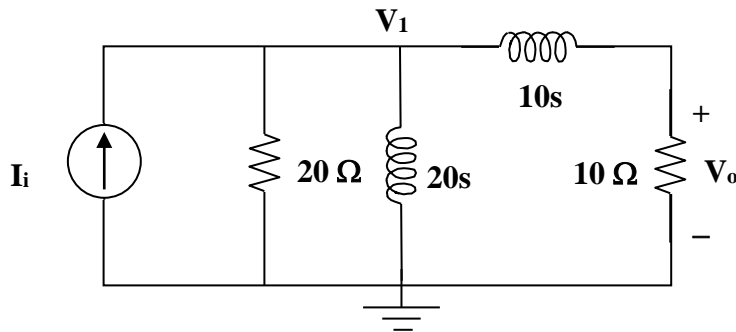Step 1. We can transform this circuit into the s-domain where $10\ \text{H}$ becomes $10s$ and $20\ \text{H}$ becomes $20s$. This leads to the following circuit,



We can use nodal analysis to solve this problem. Clearly we can write the following nodal equation.

$$-\mathbf{I}_i + [(\mathbf{V}_1 - 0)/20] + [(\mathbf{V}_1 - 0)/(20s)] + [(\mathbf{V}_1 - 0)/(10s + 10)] = 0. \text{ Finally, } \mathbf{V}_o = [(\mathbf{V}_1 - 0)/(10s + 10)]10.$$

Step 2. $[0.05 + (0.05/s) + 0.1/(s+1)]\mathbf{V}_1 = 0.05[(s^2 + s + s + 1 + 2s)/(s(s+1))]\mathbf{V}_1 = \mathbf{I}_i$ and $\mathbf{V}_1 = 20[s(s+1)/(s^2 + 4s + 1)]\mathbf{I}_i$. Finally,

$$\mathbf{V}_o = \mathbf{V}_1/(s+1) = [20s/(s^2 + 4s + 1)]\mathbf{I}_i \text{ or}$$

$$\mathbf{H}(s) = \mathbf{V}_o(s)/\mathbf{I}_i(s) = 20s/(s^2 + 4s + 1).$$

Solution 14.4

Find the transfer function $\mathbf{H(s)} = \mathbf{V_o/V_i}$ of the circuit shown in Fig. 14.71.


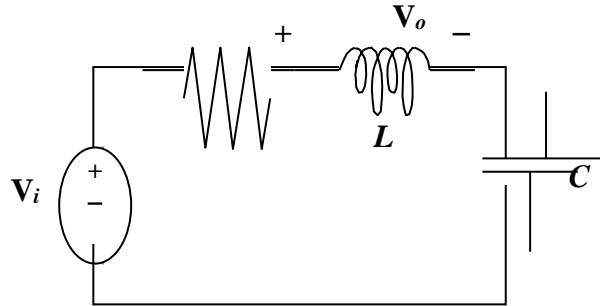


Figure 14.71
For Prob. 14.4.

Solution

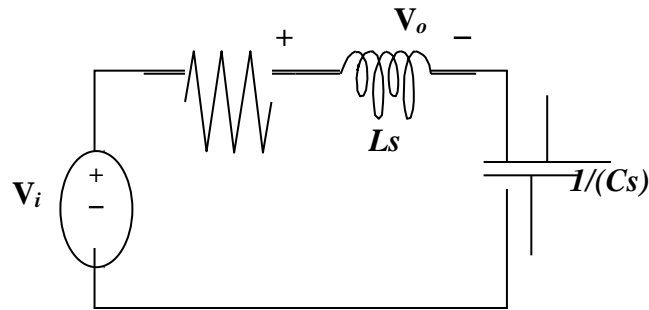Step 1. First we convert the circuit into the s-domain where the capacitor becomes $1/(Cs)$ and the inductor becomes Ls . Now we redraw the circuit as follows,



We can write a mesh equation, $-\mathbf{V_i} + \mathbf{RI} + \mathbf{LsI} + [1/(Cs)]\mathbf{I} = 0$ and note that $\mathbf{V_o} = \mathbf{LsI}$. This now leads to $\mathbf{V_o/V_i}$.

Step 2. $[\mathbf{R+Ls+1/(Cs)}]\mathbf{I} = \mathbf{V_i}$ or $\mathbf{I} = [\mathbf{Cs/(CLs^2+CRs+1)}]\mathbf{V_i}$. Thus,
 $\mathbf{V_o} = \mathbf{LsI}$ or

$$\mathbf{H(s)} = \mathbf{V_o/V_i} = \mathbf{LCs^2/(CLs^2+CRs+1)}.$$

Solution 14.5

For the circuit shown in Fig. 14.72, find $\mathbf{H}(s) = \mathbf{V}_o/\mathbf{I}_s$.


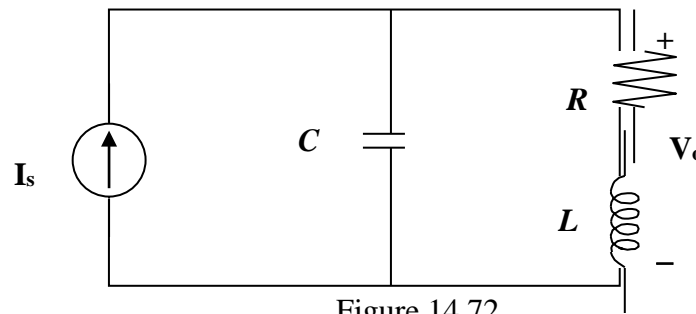


Figure 14.72
For Prob. 14.5.

Solution

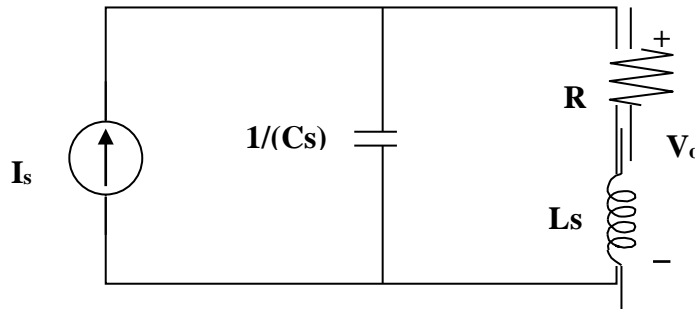Step 1. Let the capacitor be represented by $1/(Cs)$ and the inductor by Ls . Then convert the circuit into the s-domain.



Very simply by current division we can represent \mathbf{V}_o as,
 $\mathbf{I}_o = [1/(Cs)][\mathbf{I}_s/((1/(Cs))+R+Ls)]$ which leads to $\mathbf{V}_o = (Ls+R)\mathbf{I}_o$.

Step 2. $\mathbf{I}_o = \mathbf{I}_s/[1+RCs+LCs^2]$ or $\mathbf{V}_o = (Ls+R)\mathbf{I}_s/(LCs^2+RCs+1)$ or

$$\mathbf{H}(s) = \mathbf{V}_o/\mathbf{I}_s = (Ls+R)/(LCs^2+RCs+1).$$

Solution 14.6

For the circuit in Fig. 14.73, find $\mathbf{H}(s) = \mathbf{V}_o(s)/\mathbf{V}_s(s)$.


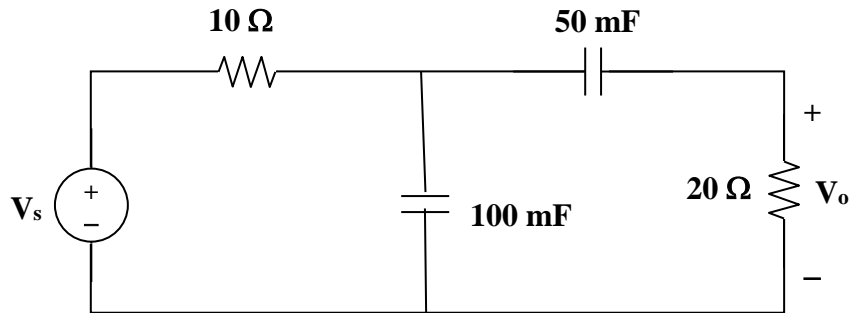


Figure 14.73
For Prob. 14.6.

Solution

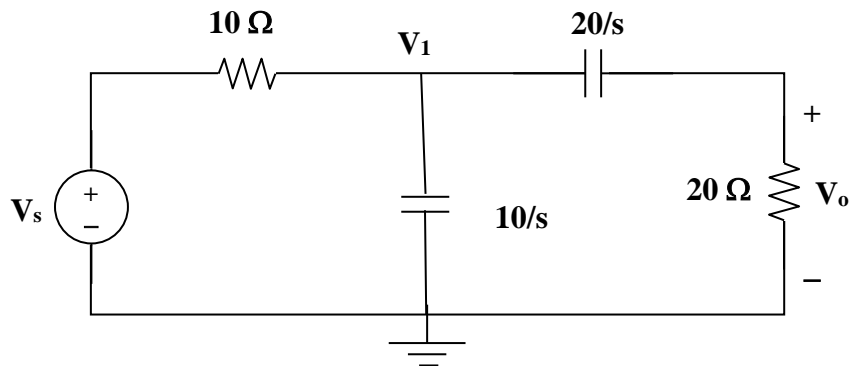Step 1. The 50 mF capacitor becomes $20/s$ and the 100 mF capacitor becomes $10/s$. Now we convert the circuit into the s-domain and using nodal analysis we can solve for \mathbf{V}_o .



$$[(\mathbf{V}_1 - \mathbf{V}_s)/10] + [(\mathbf{V}_1 - 0)/(10/s)] + [(\mathbf{V}_1 - 0)/(20 + 20/s)] = 0 \text{ and } \mathbf{V}_o = \mathbf{V}_1/(20 + 20/s).$$

Step 2. $[(0.1 + 0.1s + 0.05s)/(s+1)]\mathbf{V}_1 = 0.1\mathbf{V}_s$ or $[(s+1+s^2+s+0.5s)/(s+1)]\mathbf{V}_1 = \mathbf{V}_s$ or $\mathbf{V}_1 = [(s+1)/(s^2+2.5s+1)]\mathbf{V}_s$ which then gives us $\mathbf{V}_o = [(s+1)/(s^2+2.5s+1)][0.05s/(s+1)]\mathbf{V}_s$.

$$\mathbf{H}(s) = \mathbf{V}_o(s)/\mathbf{V}_s(s) = \mathbf{0.05s/(s^2+2.5s+1)}.$$

Solution 14.7

Calculate $|\mathbf{H}|$ if H_{dB} equals

- (a) 0.1 dB
- (b) -5 dB
- (c) 215 dB

Solution

- (a) $0.1 \text{ dB} = 20\log_{10}|\mathbf{H}|$, thus, $|\mathbf{H}| = \mathbf{1.0116}$
- (b) $-5 \text{ dB} = 20\log_{10}|\mathbf{H}|$, thus, $|\mathbf{H}| = \mathbf{0.5623}$
- (c) $215 \text{ dB} = 20\log_{10}|\mathbf{H}|$, thus, $|\mathbf{H}| = \mathbf{5.623 \times 10^{10}}$

Solution 14.8

Design a problem to help other students to better calculate the magnitude in dB and phase in degrees of a variety of transfer functions at a single value of ω .

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

Determine the magnitude (in dB) and the phase (in degrees) of $\mathbf{H}(\omega)$ at $\omega = 1$ if $\mathbf{H}(\omega)$ equals

- (a) 0.05
- (b) 125
- (c) $\frac{10j\omega}{2 + j\omega}$
- (d) $\frac{3}{1 + j\omega} + \frac{6}{2 + j\omega}$

Solution

- (a) $H = 0.05$
 $H_{\text{dB}} = 20\log_{10} 0.05 = \mathbf{-26.02}$, $\phi = \mathbf{0^\circ}$
- (b) $H = 125$
 $H_{\text{dB}} = 20\log_{10} 125 = \mathbf{41.94}$, $\phi = \mathbf{0^\circ}$
- (c) $H(1) = \frac{j10}{2 + j} = 4.472 \angle 63.43^\circ$
 $H_{\text{dB}} = 20\log_{10} 4.472 = \mathbf{13.01}$, $\phi = \mathbf{63.43^\circ}$
- (d) $H(1) = \frac{3}{1 + j} + \frac{6}{2 + j} = 3.9 - j2.7 = 4.743 \angle -34.7^\circ$
 $H_{\text{dB}} = 20\log_{10} 4.743 = \mathbf{13.521}$, $\phi = \mathbf{-34.7^\circ}$


Solution 14.9

$$\mathbf{H}(\omega) = \frac{10}{10(1 + j\omega)(1 + j\omega/10)}$$

$$H_{dB} = 20 \log_{10}|1| - 20 \log_{10}|1 + j\omega| - 20 \log_{10}|1 + j\omega/10|$$

$$\phi = -\tan^{-1}(\omega) - \tan^{-1}(\omega/10)$$

The magnitude and phase plots are shown below.

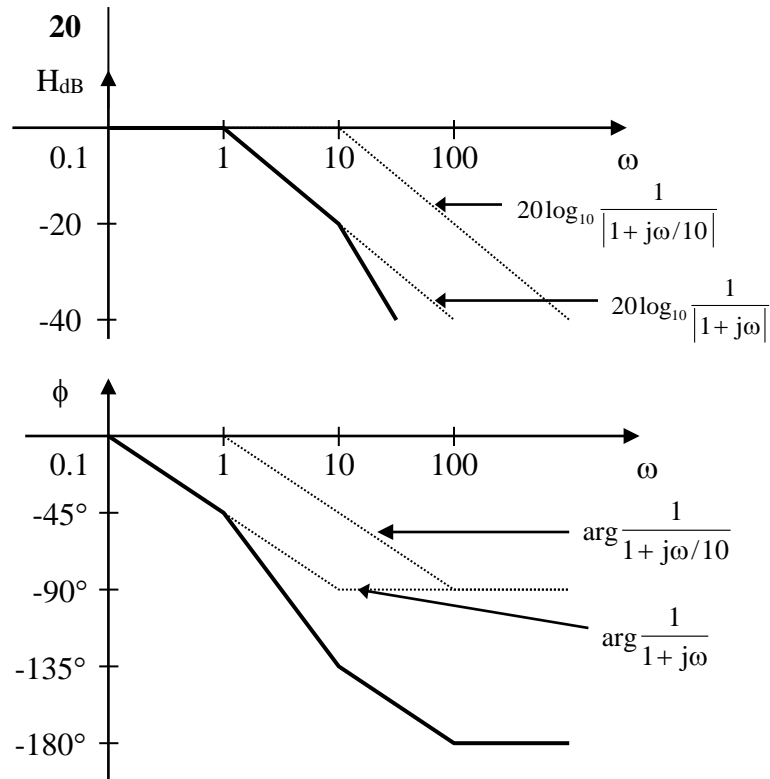

Solution 14.10

Design a problem to help other students to better understand how to determine the Bode magnitude and phase plots of a given transfer function in terms of $j\omega$.

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.


Problem

Sketch the Bode magnitude and phase plots of:

$$H(j\omega) = \frac{50}{j\omega(5 + j\omega)}$$

Solution

$$H(j\omega) = \frac{50}{j\omega(5 + j\omega)} = \frac{10}{1j\omega\left(1 + \frac{j\omega}{5}\right)}$$

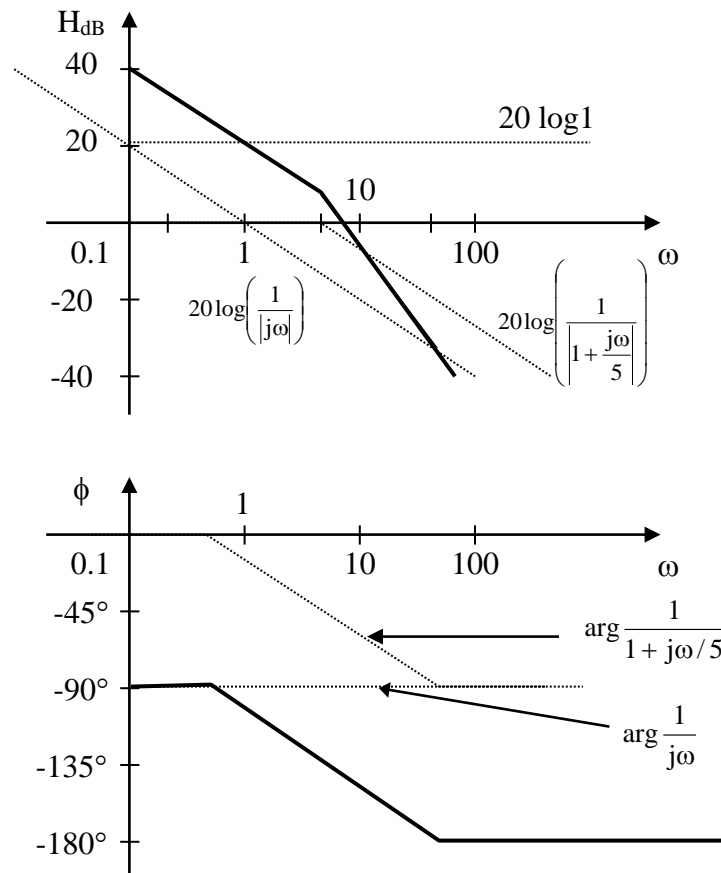


Solution 14.11

$$\mathbf{H}(\omega) = \frac{0.2 \times 10(1 + j\omega/10)}{2[j\omega(1 + j\omega/2)]}$$

$$H_{dB} = 20\log_{10} 1 + 20\log_{10} |1 + j\omega/10| - 20\log_{10} |j\omega| - 20\log_{10} |1 + j\omega/2|$$

$$\phi = -90^\circ + \tan^{-1} \omega/10 - \tan^{-1} \omega/2$$

The magnitude and phase plots are shown below.

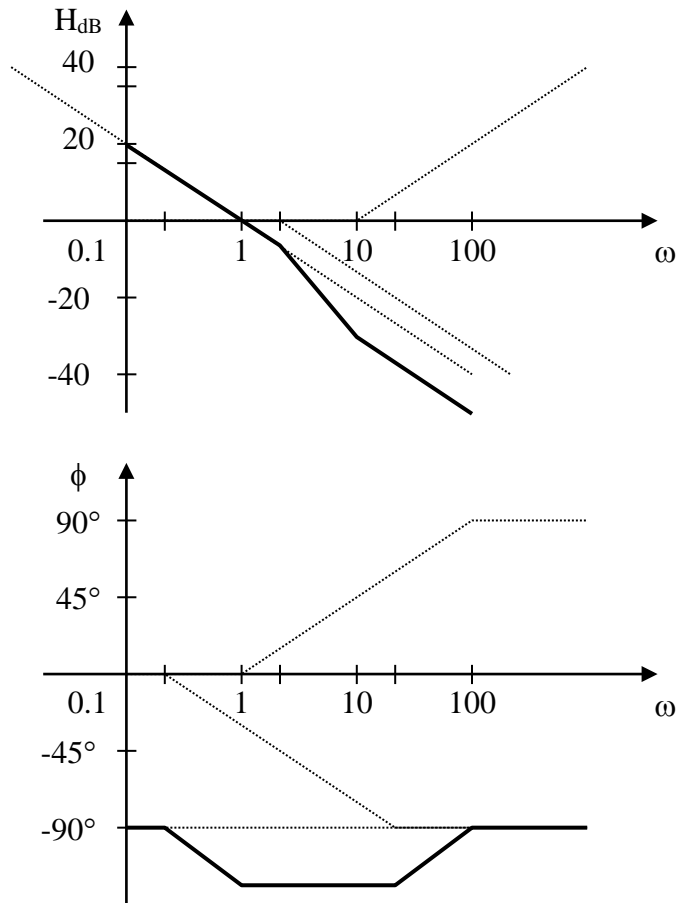


Solution 14.12

$$T(\omega) = \frac{10(1 + j\omega)}{j\omega(1 + j\omega/10)}$$

To sketch this we need $20\log_{10} |T(\omega)| = 20\log_{10} |10| + 20\log_{10} |1+j\omega| - 20\log_{10} |j\omega| - 20\log_{10} |1+j\omega/10|$ and the phase is equal to $\tan^{-1}(\omega) - 90^\circ - \tan^{-1}(\omega/10)$.

The plots are shown below.

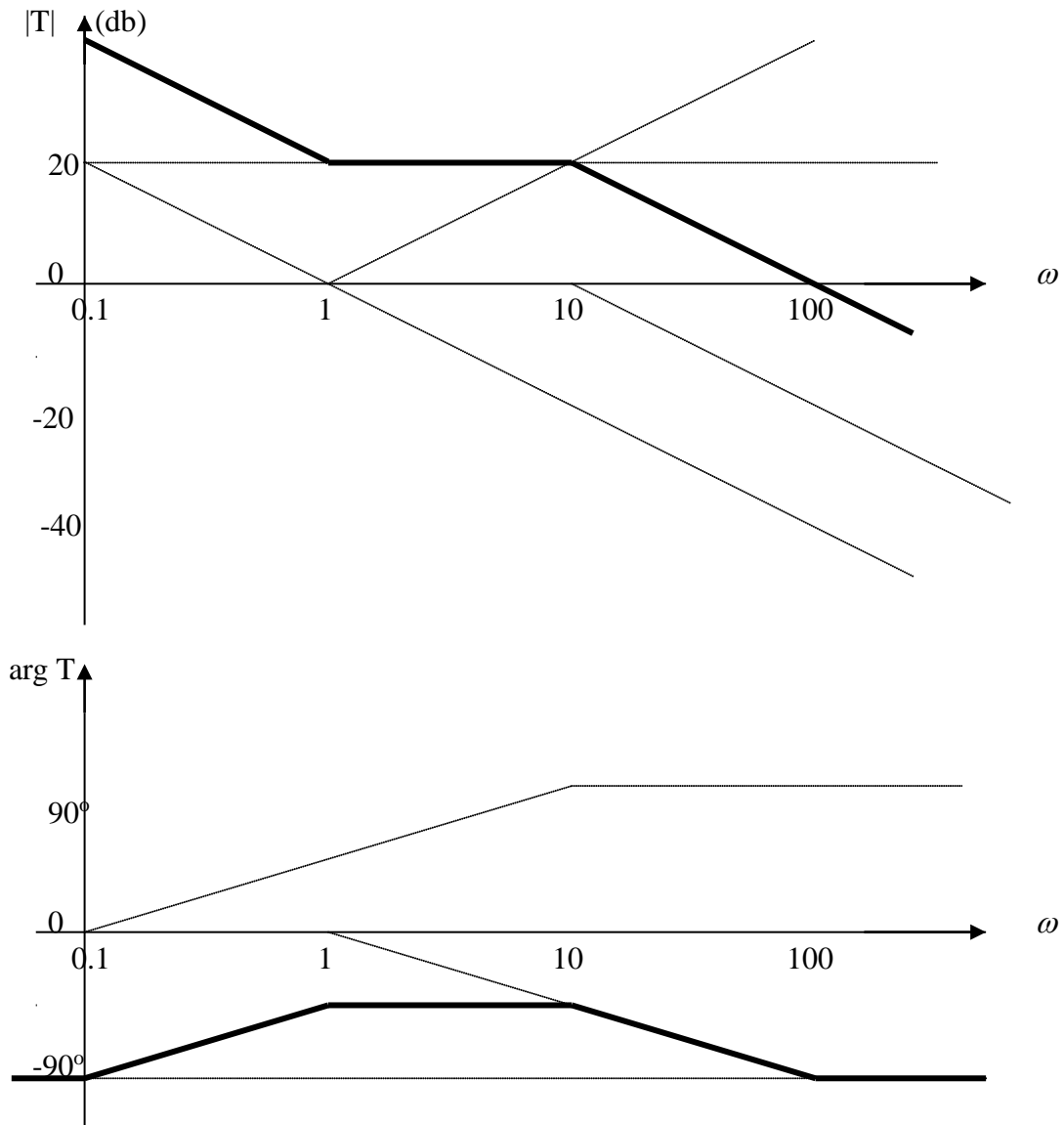


Solution 14.13

$$\mathbf{G}(\omega) = \frac{0.1(1 + j\omega)}{(j\omega)^2(10 + j\omega)} = \frac{(1/100)(1 + j\omega)}{(j\omega)^2(1 + j\omega/10)}$$

$$G_{dB} = -40 + 20\log_{10}|1 + j\omega| - 40\log_{10}|j\omega| - 20\log_{10}|1 + j\omega/10|$$

$$\phi = -180^\circ + \tan^{-1}\omega - \tan^{-1}\omega/10$$

The magnitude and phase plots are shown below.

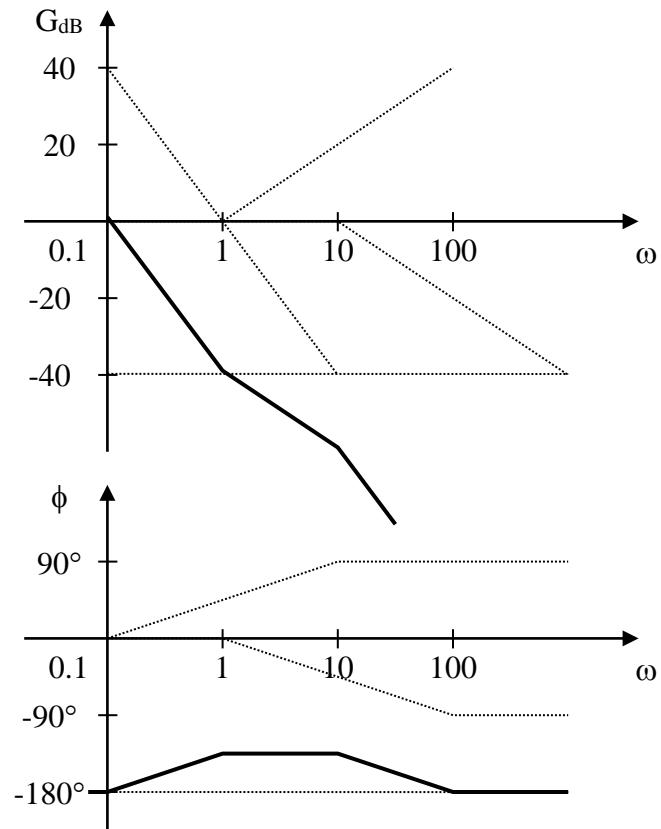


Solution 14.14

$$\mathbf{H}(\omega) = \frac{250}{25} \frac{1 + j\omega}{j\omega \left(1 + \frac{j\omega 10}{25} + \left(\frac{j\omega}{5} \right)^2 \right)}$$

$$H_{dB} = 20 \log_{10} 10 + 20 \log_{10} |1 + j\omega| - 20 \log_{10} |j\omega| \\ - 20 \log_{10} \left| 1 + j\omega 2/5 + (j\omega/5)^2 \right|$$

$$\phi = -90^\circ + \tan^{-1} \omega - \tan^{-1} \left(\frac{\omega 10/25}{1 - \omega^2/5} \right)$$

The magnitude and phase plots are shown below.

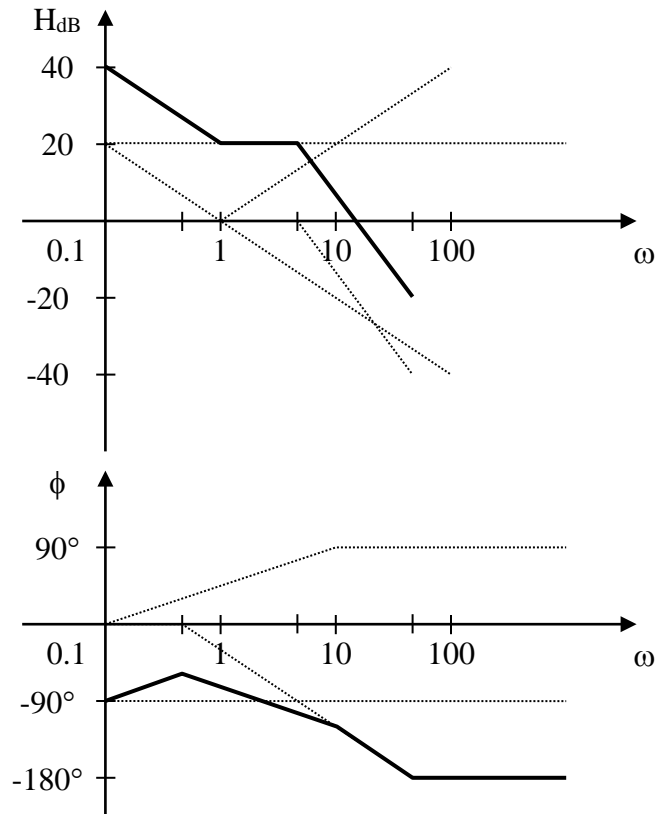


Solution 14.15

$$\mathbf{H}(\omega) = \frac{2(1 + j\omega)}{(2 + j\omega)(10 + j\omega)} = \frac{0.1(1 + j\omega)}{(1 + j\omega/2)(1 + j\omega/10)}$$

$$H_{dB} = 20\log_{10} 0.1 + 20\log_{10}|1 + j\omega| - 20\log_{10}|1 + j\omega/2| - 20\log_{10}|1 + j\omega/10|$$

$$\phi = \tan^{-1} \omega - \tan^{-1} \omega/2 - \tan^{-1} \omega/10$$

The magnitude and phase plots are shown below.

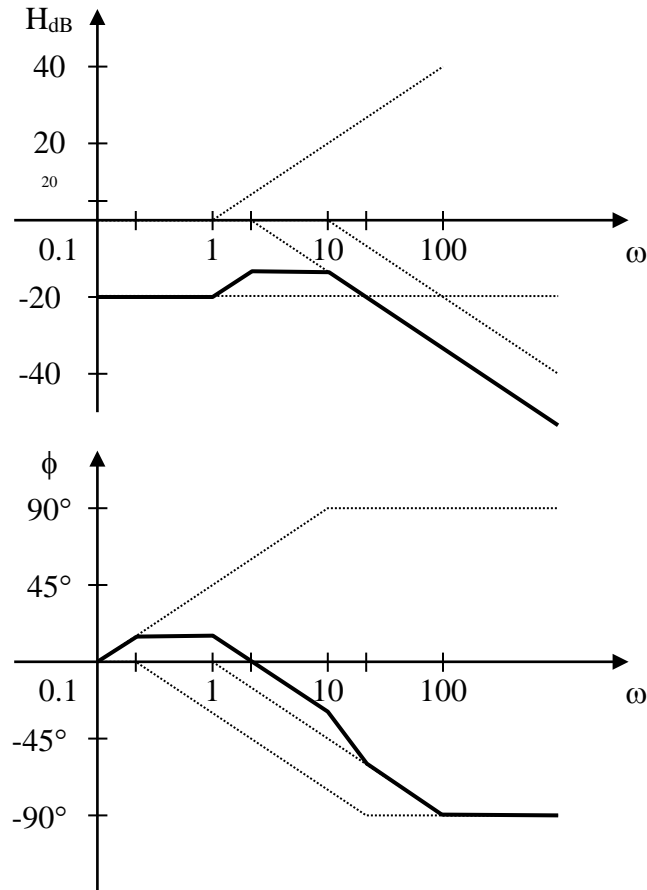


Solution 14.16

$$H(\omega) = \frac{\frac{1.6}{16}}{j\omega \left[1 + j\omega + \left(\frac{j\omega}{4} \right)^2 \right]} = \frac{0.1}{j\omega \left[1 + j\omega + \left(\frac{j\omega}{4} \right)^2 \right]}$$

$$H_{db} = 20\log_{10}|0.1| - 20\log_{10}|j\omega| - 20\log_{10}|1 + j\omega + (j\omega/4)^2|$$

The magnitude and phase plots are shown below.

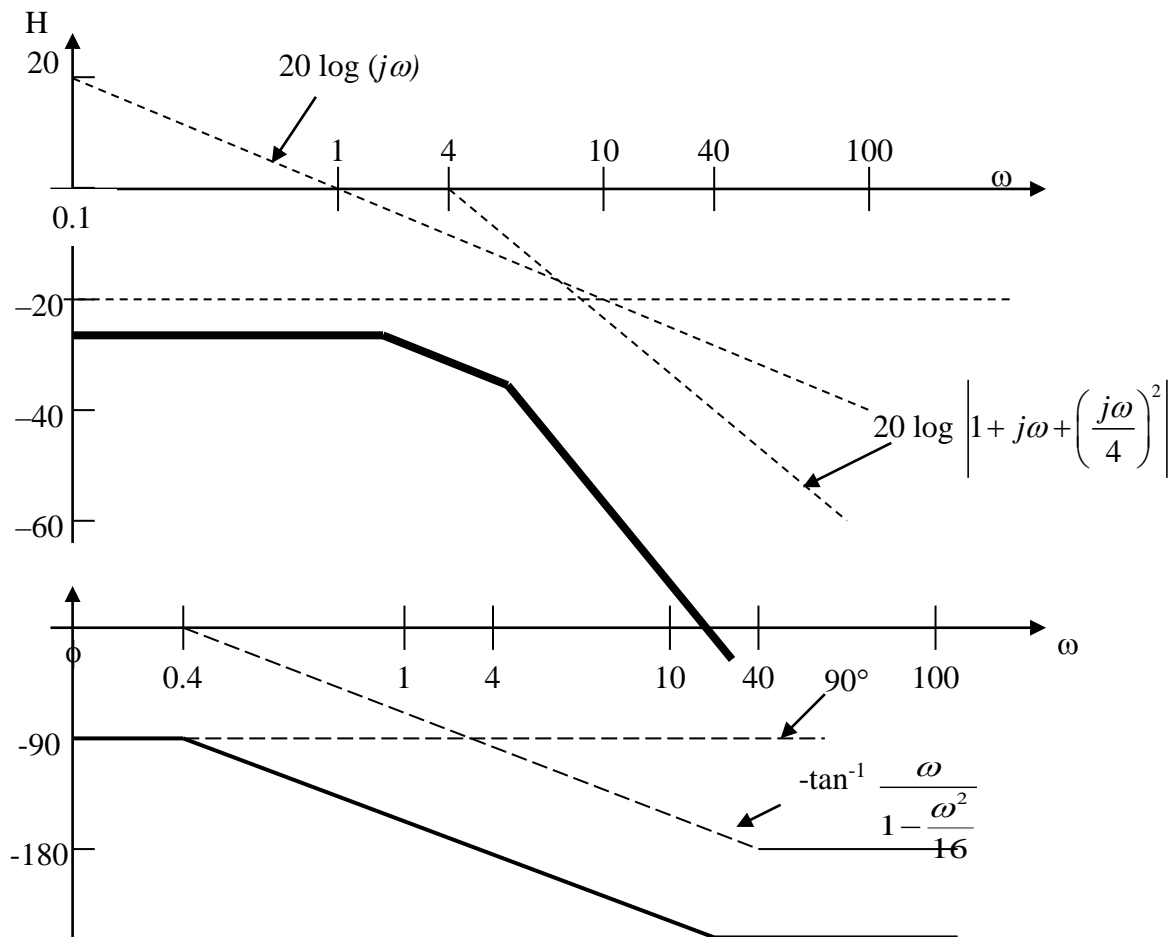


Solution 14.17

$$G(\omega) = \frac{(1/4)j\omega}{(1+j\omega)(1+j\omega/2)^2}$$

$$G_{dB} = -20\log_{10} 4 + 20\log_{10} |j\omega| - 20\log_{10} |1+j\omega| - 40\log_{10} |1+j\omega/2|$$

$$\phi = -90^\circ - \tan^{-1}\omega - 2 \tan^{-1} \omega/2$$


The magnitude and phase plots are shown below.

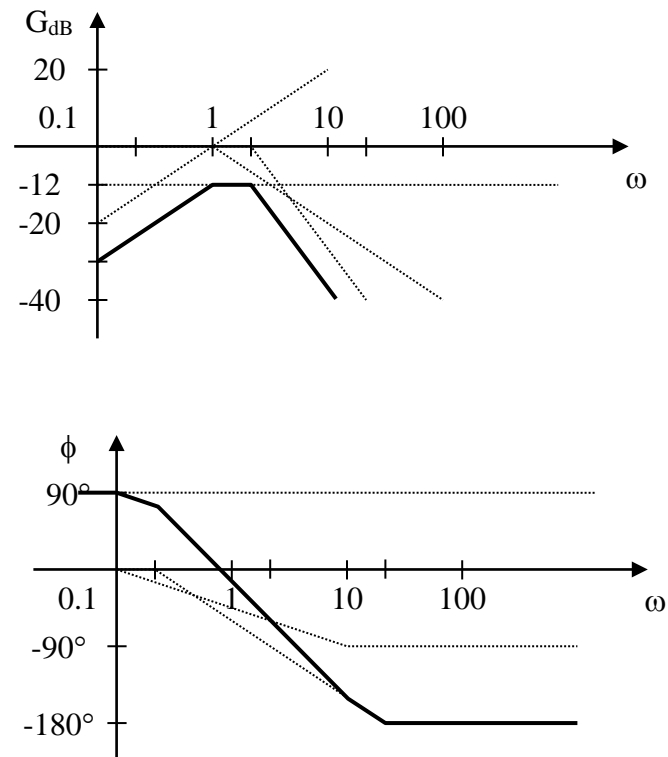

Solution 14.18


The MATLAB code is shown below.
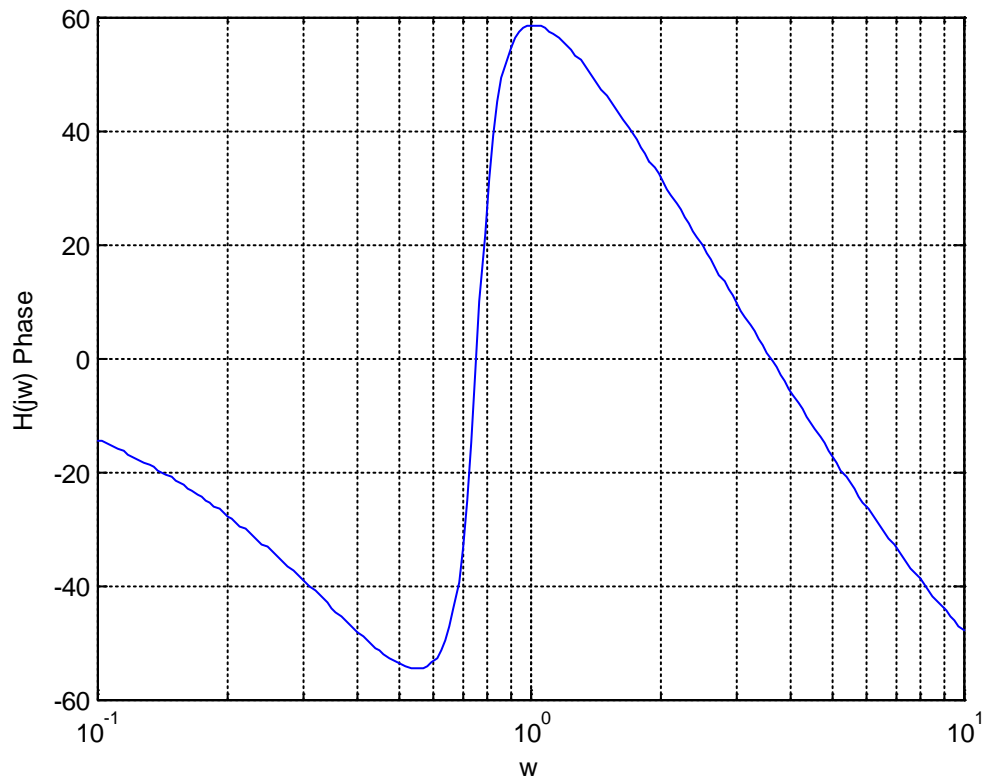
```
>> w=logspace(-1,1,200);  
>> s=i*w;  
>> h=(7*s.^2+s+4)./(s.^3+8*s.^2+14*s+5);  
>> Phase=unwrap(angle(h))*57.23;  
>> semilogx(w,Phase)  
>> grid on
```



Now for the magnitude, we need to add the following to the above,

```
>> H=abs(h);  
>> HdB=20*log10(H);  
>> semilogx(w,HdB);  
>> grid on
```

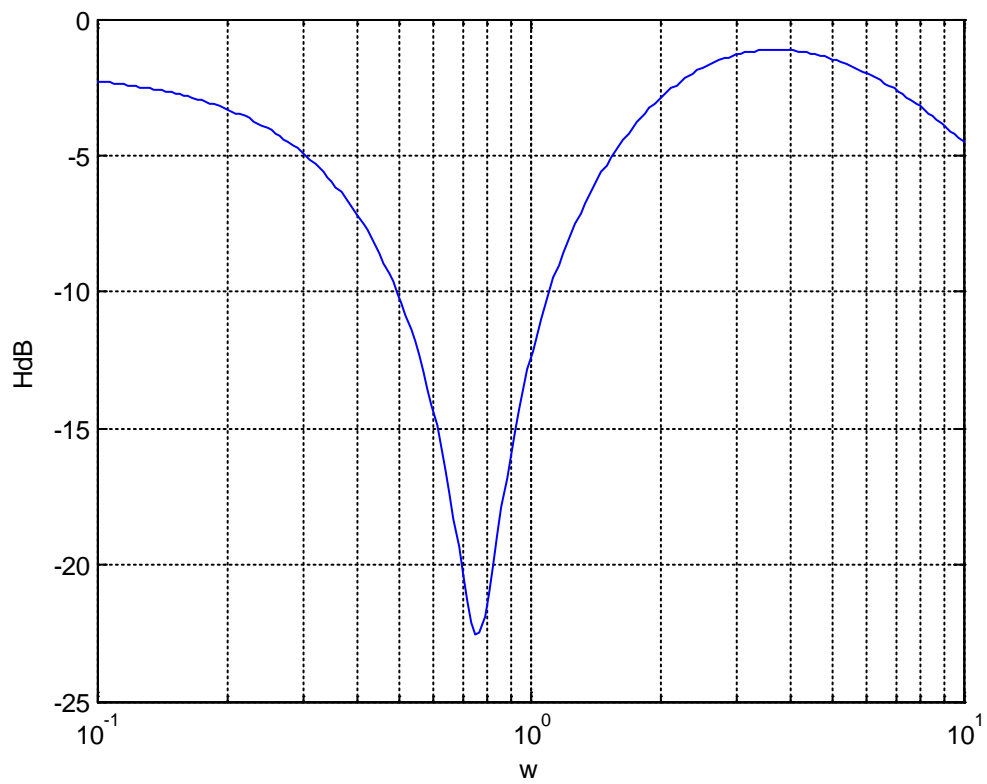


Solution 14.19

$$H(\omega) = 80j\omega / [(10+j\omega)(20+j\omega)(40+j\omega)]$$

$$= [80/(10 \times 20 \times 40)](j\omega) / [(1+j\omega/10)(1+j\omega/20)(1+j\omega/40)]$$

$$H_{db} = 20\log_{10}|0.01| + 20\log_{10}|j\omega| - 20\log_{10}|1+j\omega/10| - 20\log_{10}|1+j\omega/20| - 20\log_{10}|1+j\omega/40|$$

The magnitude and phase plots are shown below.

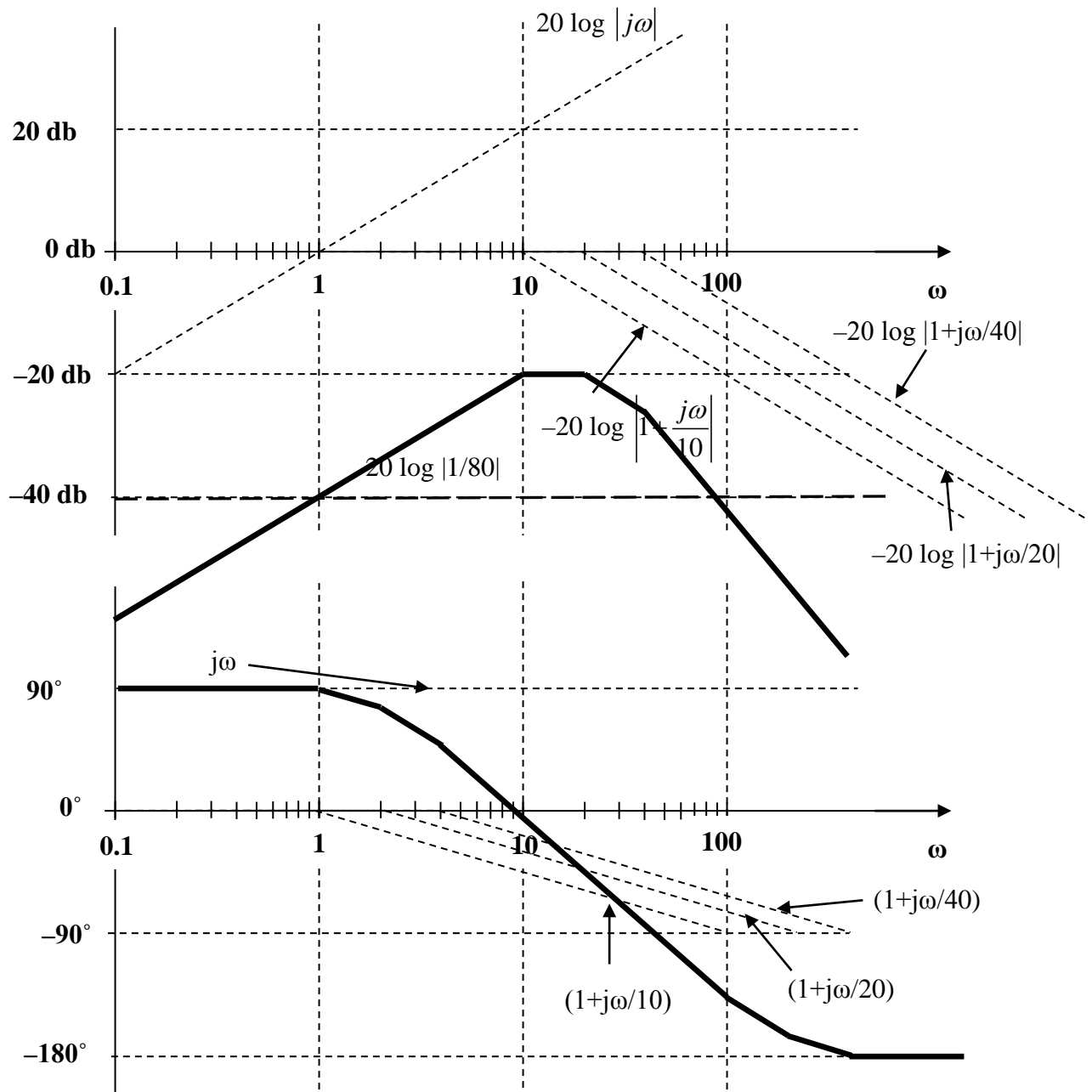

Solution 14.20

Design a more complex problem than given in Prob. 14.10, to help other students to better understand how to determine the Bode magnitude and phase plots of a given transfer function in terms of $j\omega$. Include at least a second order repeated root.

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

Sketch the magnitude phase Bode plot for the transfer function

$$H(\omega) = \frac{25j\omega}{(j\omega + 1)(j\omega + 5)^2(j\omega + 10)}$$


Solution

$$H(\omega) = \frac{\left(\frac{1}{100}\right)j\omega}{(1 + j\omega)\left(1 + \frac{j\omega}{5}\right)^2\left(1 + \frac{j\omega}{10}\right)}$$

$$20\log(1/100) = -40$$

For the plots, see the next page.

The magnitude and phase plots are shown below.

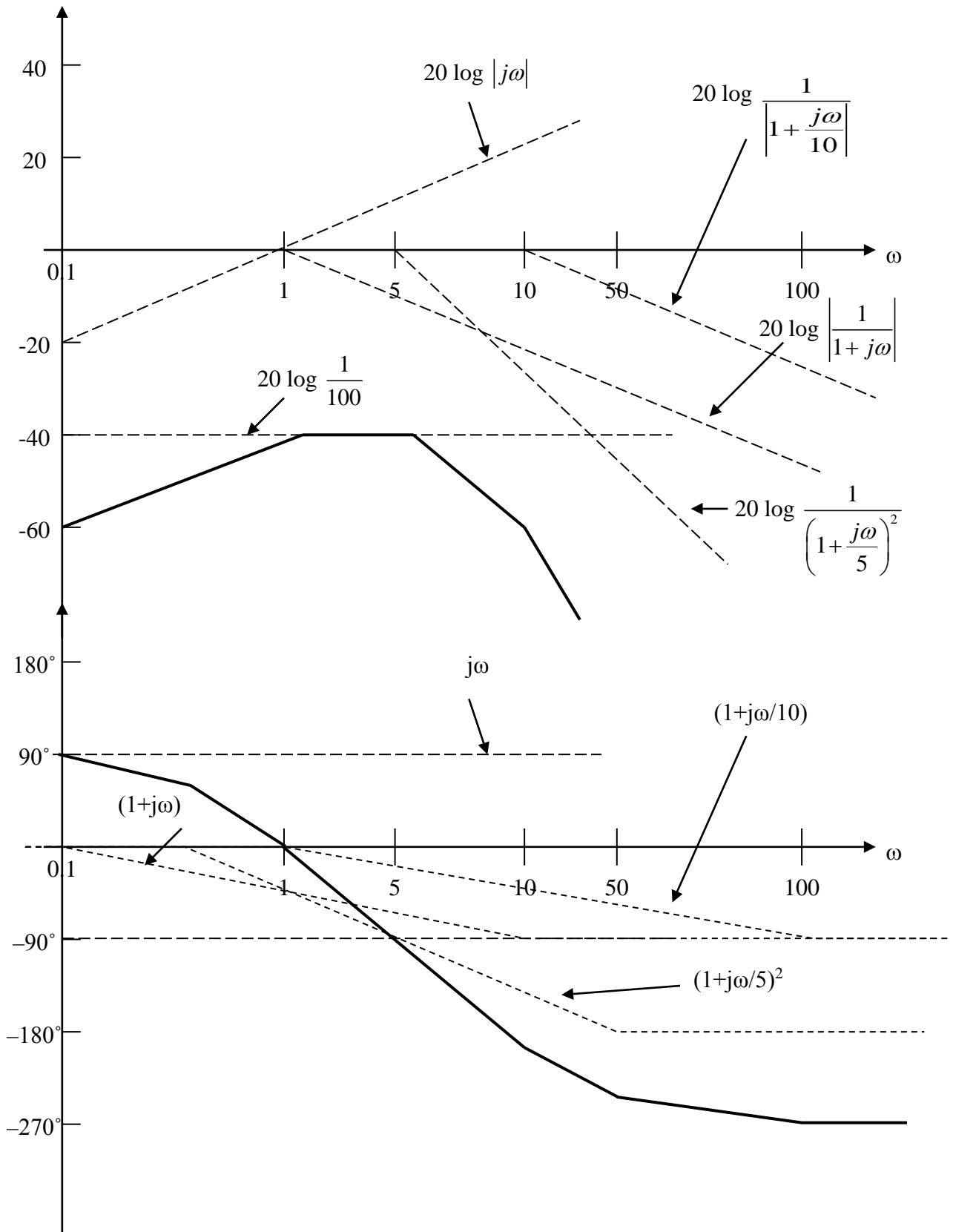


Solution 14.21

$$H(\omega) = 10(j\omega)(20+j\omega)/[(1+j\omega)(400+60j\omega-\omega^2)]$$

$$= [10 \times 20 / 400](j\omega)(1+j\omega/20)/[(1+j\omega)(1+(3j\omega/20)+(j\omega/20)^2)]$$

$$H_{dB} = 20\log(0.5) + 20\log|j\omega| + 20\log\left|1 + \frac{j\omega}{20}\right| - 20\log|1 + j\omega| - 20\log\left|1 + \frac{j3\omega}{20} + \left(\frac{j\omega}{20}\right)^2\right|$$

The magnitude plot is as sketched below. $20\log_{10}|0.5| = -6 \text{ db}$

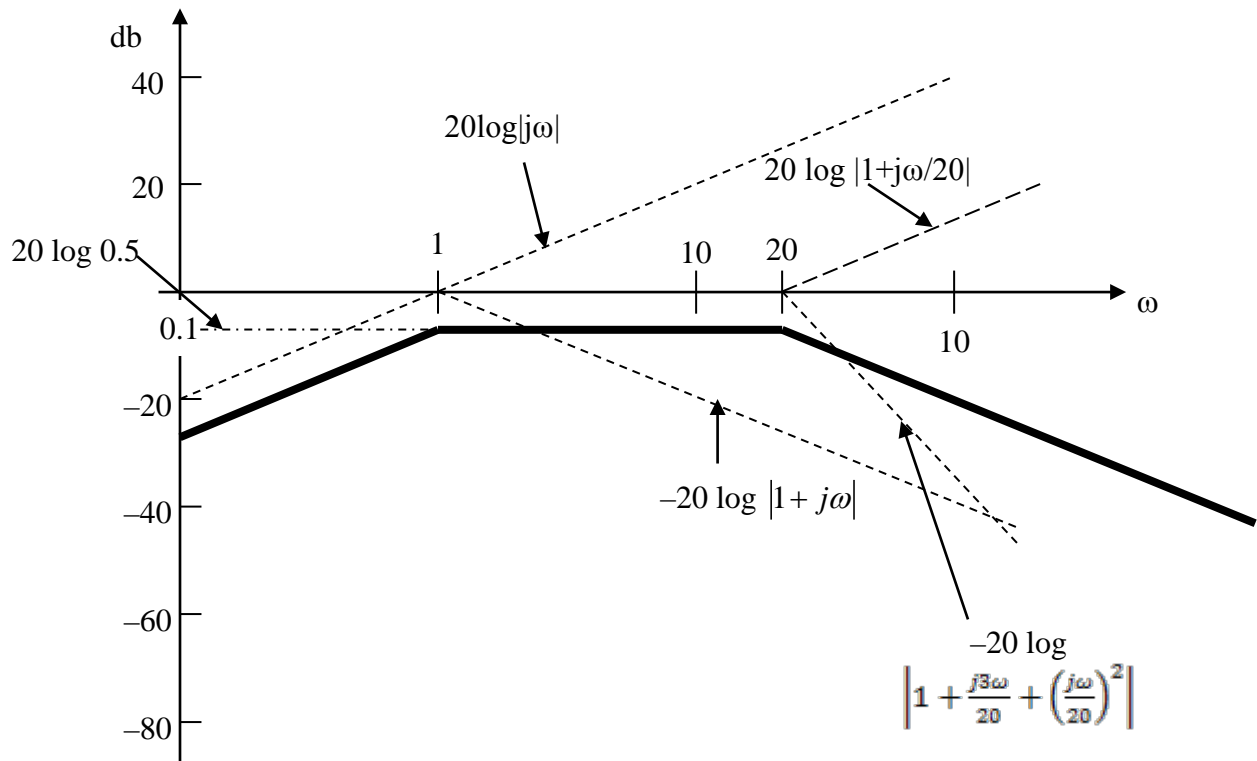

Solution 14.22

Find the transfer function $\mathbf{H}(\omega)$ with the Bode magnitude plot shown in Fig. 14.74.

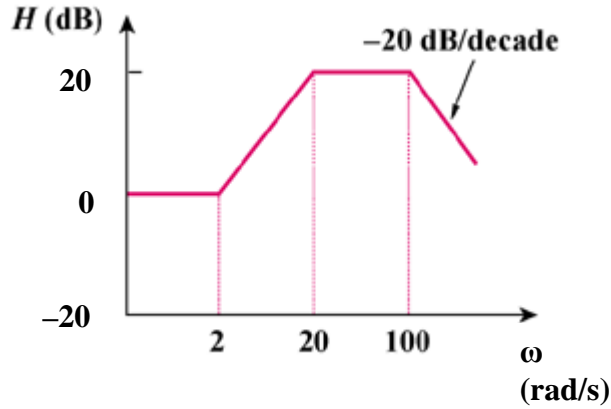


Figure 14.74
For Prob. 14.22.

Solution

$$0 = 20 \log_{10} k \longrightarrow k = 1$$

$$\text{A zero of slope } +20 \text{ dB/dec at } \omega = 2 \longrightarrow 1 + j\omega/2$$

$$\text{A pole of slope } -20 \text{ dB/dec at } \omega = 20 \longrightarrow \frac{1}{1 + j\omega/20}$$

$$\text{A pole of slope } -20 \text{ dB/dec at } \omega = 100 \longrightarrow \frac{1}{1 + j\omega/100}$$

Hence,

$$\mathbf{H}(\omega) = \frac{1(1 + j\omega/2)}{(1 + j\omega/20)(1 + j\omega/100)} = \frac{1,000(2 + j\omega)}{(20 + j\omega)(100 + j\omega)}$$

Solution 14.23

The Bode magnitude plot of $\mathbf{H}(\omega)$ is shown in Fig. 14.75. Find $\mathbf{H}(\omega)$.

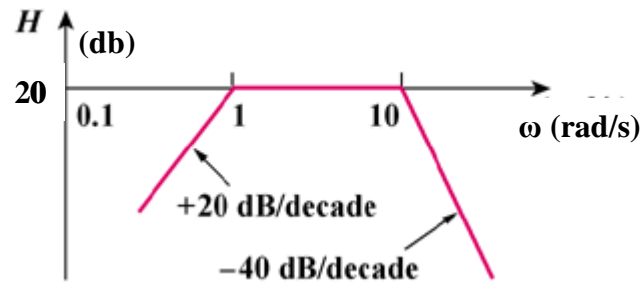


Figure 14.75
For Prob. 14.23.

Solution

The initial slope indicates we have $j\omega$ in the numerator. Our approach to plotting requires the plot of $j\omega$ to cross 0db at $\omega = 1$ rad/s. Since it crosses at 20db, that indicates that the overall gain is 20db or,

$20 = 20\log_{10}|\text{gain}|$ the gain has to be 10.

A zero of slope + 20 dB / dec at the origin $\longrightarrow j\omega$

A pole of slope - 20 dB / dec at $\omega = 1$ $\longrightarrow \frac{1}{1 + j\omega/1}$

A pole of slope - 40 dB / dec at $\omega = 10$ $\longrightarrow \frac{1}{(1 + j\omega/10)^2}$

Hence,

$$\mathbf{H}(\omega) = \frac{10 j\omega}{(1 + j\omega)(1 + j\omega/10)^2}$$

$$\mathbf{H}(\omega) = \frac{1,000 j\omega}{(1 + j\omega)(10 + j\omega)^2}$$

(It should be noted that this function could also have a minus sign out in front and still be correct. The magnitude plot does not contain this information. It can only be obtained from the phase plot.)

Solution 14.24

The magnitude plot in Fig. 14.76 represents the transfer function of a preamplifier. Find $H(s)$.

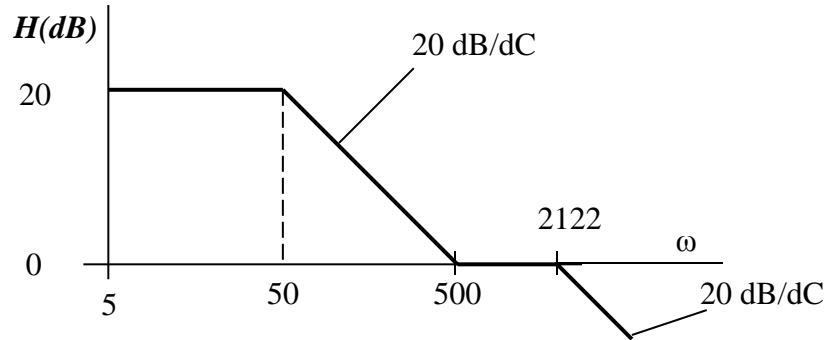


Figure 14.76
For Prob. 14.24.

Solution

$20 = 20\log_{10}|\text{gain}|$ or $\text{gain} = 10$.

There is a pole at $\omega=50$ giving $1/(1+j\omega/50)$

There is a zero at $\omega=500$ giving $(1 + j\omega/500)$.

There is another pole at $\omega=2122$ giving $1/(1 + j\omega/2122)$.

Thus,

$$H(j\omega) = 10(1+j\omega/500)/[(1+j\omega/50)(1+j\omega/2122)]$$

$$= [10(50 \times 2122)/500](j\omega+500)/[(j\omega+50)(j\omega+2122)]$$

or

$$H(s) = \mathbf{2,122(s+500)/[(s+50)(s+2122)]}.$$

Solution 14.25

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(40 \times 10^{-3})(1 \times 10^{-6})}} = 5 \text{ krad/s}$$

$$\mathbf{Z}(\omega_0) = \mathbf{R} = \mathbf{2 \text{ k}\Omega}$$

$$\mathbf{Z}(\omega_0/4) = \mathbf{R} + \mathbf{j} \left(\frac{\omega_0}{4} \mathbf{L} - \frac{4}{\omega_0 \mathbf{C}} \right)$$

$$\mathbf{Z}(\omega_0/4) = 2000 + \mathbf{j} \left(\frac{5 \times 10^3}{4} \cdot 40 \times 10^{-3} - \frac{4}{(5 \times 10^3)(1 \times 10^{-6})} \right)$$

$$\mathbf{Z}(\omega_0/4) = 2000 + \mathbf{j}(50 - 4000/5)$$

$$\mathbf{Z}(\omega_0/4) = \mathbf{2 - j0.75 \text{ k}\Omega}$$

$$\mathbf{Z}(\omega_0/2) = \mathbf{R} + \mathbf{j} \left(\frac{\omega_0}{2} \mathbf{L} - \frac{2}{\omega_0 \mathbf{C}} \right)$$

$$\mathbf{Z}(\omega_0/2) = 2000 + \mathbf{j} \left(\frac{(5 \times 10^3)}{2} (40 \times 10^{-3}) - \frac{2}{(5 \times 10^3)(1 \times 10^{-6})} \right)$$

$$\mathbf{Z}(\omega_0/2) = 200 + \mathbf{j}(100 - 2000/5)$$

$$\mathbf{Z}(\omega_0/2) = \mathbf{2 - j0.3 \text{ k}\Omega}$$

$$\mathbf{Z}(2\omega_0) = \mathbf{R} + \mathbf{j} \left(2\omega_0 \mathbf{L} - \frac{1}{2\omega_0 \mathbf{C}} \right)$$

$$\mathbf{Z}(2\omega_0) = 2000 + \mathbf{j} \left((2)(5 \times 10^3)(40 \times 10^{-3}) - \frac{1}{(2)(5 \times 10^3)(1 \times 10^{-6})} \right)$$

$$\mathbf{Z}(2\omega_0) = \mathbf{2 + j0.3 \text{ k}\Omega}$$

$$\mathbf{Z}(4\omega_0) = \mathbf{R} + \mathbf{j} \left(4\omega_0 \mathbf{L} - \frac{1}{4\omega_0 \mathbf{C}} \right)$$

$$\mathbf{Z}(4\omega_0) = 2000 + \mathbf{j} \left((4)(5 \times 10^3)(40 \times 10^{-3}) - \frac{1}{(4)(5 \times 10^3)(1 \times 10^{-6})} \right)$$

$$\mathbf{Z}(4\omega_0) = \mathbf{2 + j0.75 \text{ k}\Omega}$$

Solution 14.26

Design a problem to help other students to better understand ω_o , Q , and B at resonance in series RLC circuits.


Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

A coil with resistance $3\ \Omega$ and inductance 100 mH is connected in series with a capacitor of 50 pF , a resistor of $6\ \Omega$, and a signal generator that gives 110V-rms at all frequencies. Calculate ω_o , Q , and B at resonance of the resultant series RLC circuit.

Solution

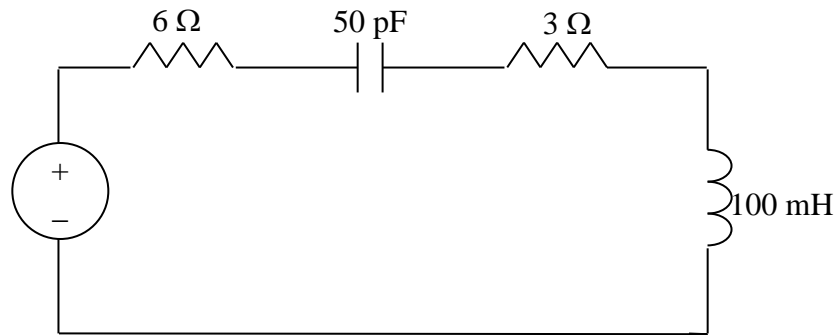Consider the circuit as shown below. This is a series RLC resonant circuit.



$$R = 6 + 3 = 9\ \Omega$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{100 \times 10^{-3} \times 50 \times 10^{-12}}} = \underline{447.21\text{ krad/s}}$$

$$Q = \frac{\omega_o L}{R} = \frac{447.21 \times 10^3 \times 100 \times 10^{-3}}{9} = \underline{4969}$$

$$B = \frac{\omega_o}{Q} = \frac{447.21 \times 10^3}{4969} = \underline{90\text{ rad/s}}$$

Solution 14.27

$$\omega_o = \frac{1}{\sqrt{LC}} = 40 \quad \longrightarrow \quad LC = \frac{1}{40^2}$$

$$B = \frac{R}{L} = 10 \quad \longrightarrow \quad R = 10L$$

If we select $R = \mathbf{1\ \Omega}$, then $L = R/10 = \mathbf{100\ mH}$ and

$$C = \frac{1}{40^2 L} = \frac{1}{40^2 \times 0.1} = \underline{\underline{6.25\ mF}}$$

Solution 14.28

Design a series *RLC* circuit with $B = 20$ rad/s and $\omega_0 = 1,000$ rad/s. Find the circuit's Q .
Let $R = 10\ \Omega$.

Solution

$$R = 10\ \Omega.$$

$$L = \frac{R}{B} = \frac{10}{20} = 0.5\ \text{H}$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(1000)^2 (0.5)} = 2\ \mu\text{F}$$


$$Q = \frac{\omega_0}{B} = \frac{1000}{20} = 50$$

Therefore, if $R = 10\ \Omega$ then

$$L = \mathbf{500\ mH}, \quad C = \mathbf{2\ \mu F}, \quad Q = \mathbf{50}$$

Solution 14.29

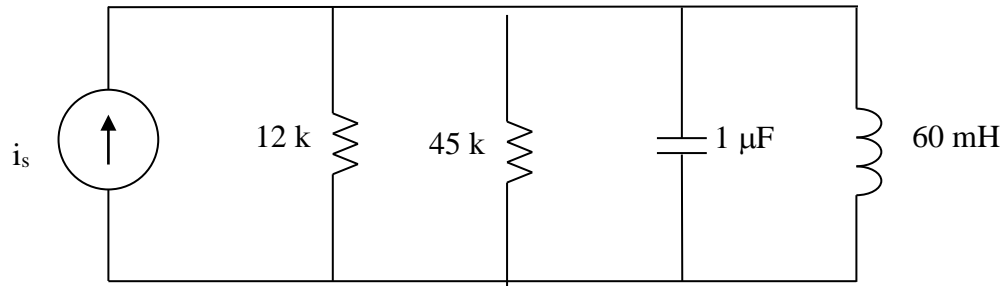We convert the voltage source to a current source as shown below.



$$i_s = \frac{20}{12} \cos \omega t, \quad R = 12 // 45 = \frac{12 \times 45}{57} = 9.4737\text{ k}\Omega$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{60 \times 10^{-3} \times 1 \times 10^{-6}}} = \underline{4.082\text{ krad/s}} = \mathbf{4.082\text{ krad/s}}$$

$$B = \frac{1}{RC} = \frac{1}{9.4737 \times 10^3 \times 10^{-6}} = \underline{105.55\text{ rad/s}} = \mathbf{105.55\text{ rad/s}}$$

$$Q = \frac{\omega_o}{B} = \frac{4082}{105.55} = \underline{38.674} = \mathbf{38.67}$$

4.082 krad/s, 105.55 rad/s, 38.67

Solution 14.30

(a) $f_o = 15,000$ Hz leads to $\omega_o = 2\pi f_o = 94.25$ krad/s = $1/(LC)^{0.5}$ or

$$LC = 1/8.883 \times 10^9 \text{ or } C = 1/(8.883 \times 10^9 \times 10^{-2}) = 11.257 \times 10^{-9} \text{ F} = \mathbf{11.257 \text{ pF}}.$$

(b) since the capacitive reactance cancels out the inductive reactance at resonance, the current through the series circuit is given by

$$I = 120/20 = \mathbf{6 \text{ A}}.$$

$$(c) Q = \omega_o L/R = 94.25 \times 10^3 (0.01)/20 = \mathbf{47.12}.$$

Solution 14.31

Design a parallel resonant *RLC* circuit with $\omega_0 = 100$ krad/s and a bandwidth of 10 krad/s.

Additionally what is the value of Q ?

Solution

Step 1. We note that,

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{LC}} \\ Q &= R/(\omega_0 L) = \omega_0 RC \\ B &= \omega_0/Q.\end{aligned}$$

Since this is a design problem, we need to find out where to start. Let us pick a value of $L = \mathbf{10\text{ mH}}$. Now all we need to do is to solve for Q , R , and C and make sure we meet the design criterion.

Step 2. $Q = 100/10 = \mathbf{10}$. Next

$$R/L = \omega_0 Q = 10^5 \times 10 = 10^6 \text{ and } RC = Q/\omega_0 = 10/10^5 = 10^{-4}$$

Since $L = 10\text{ mH}$ we get $R = \omega_0 QL = 10^6 \times 0.01 = \mathbf{10\text{ k}\Omega}$. Next we get,

$$C = 10^{-4}/R = 10^{-4}/10^4 = 10^{-8} = \mathbf{10\text{ nF}}.$$

Solution 14.32

Design a problem to help other students to better understand the quality factor, the resonant frequency, and bandwidth of a parallel *RLC* circuit.

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

A parallel RLC circuit has the following values:

$$R = 60 \, \Omega, \quad L = 1 \, \text{mH}, \quad \text{and} \quad C = 50 \, \mu\text{F}$$

Find the quality factor, the resonant frequency, and the bandwidth of the RLC circuit.

Solution

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 50 \times 10^{-6}}} = \underline{4.472 \, \text{krad/s}}$$

$$B = \frac{1}{RC} = \frac{1}{60 \times 50 \times 10^{-6}} = \underline{333.33 \, \text{rad/s}}$$

$$Q = \frac{\omega_o}{B} = \frac{4472}{333.33} = \underline{13.42}$$

Solution 14.33

A parallel resonant circuit has a bandwidth of 40 krad/s and the half power frequencies are $\omega_1 = 4.98$ Mrad/s and $\omega_2 = 5.02$ Mrad/s, calculate the quality factor and resonant frequency.

Solution

Since $\omega_1 = \omega_o - B/2$ then $\omega_o = (4.98+5.02)/2$ M = **5 Mrad/s**. Since $B = \omega_o/Q$ then $Q = 5 \text{ M}/0.04 \text{ M} = \mathbf{125}$.

Solution 14.34

A parallel RLC circuit has an $R = 100\text{ k}\Omega$, $L = 100\text{ mH}$, and a $C = 10\text{ }\mu\text{F}$, determine the value of Q , the resonant frequency, and the bandwidth. If $R = 200\text{ k}\Omega$, how does that effect the values of Q , resonant frequency, and the bandwidth?

Solution

Since,

$$\omega_o = \frac{1}{\sqrt{LC}}$$
$$Q = R/(\omega_o L) = \omega_o RC$$
$$B = \omega_o/Q.$$

$$\omega_o = 1/\sqrt{0.1 \times 10^{-5}} = \mathbf{1,000\text{ rad/s}}$$
 and $Q = \omega_o RC = 10^3 \times 10^5 \times 10^{-5} = \mathbf{1,000}$. Finally,

$$B = \omega_o/Q = 1,000/1,000 = \mathbf{1\text{ rad/s}}.$$

When $R = 200\text{ k}\Omega$ the value of ω_o **does not change** since it is only dependent on L and C .

$$Q = \omega_o RC = 1,000 \times 2 \times 10^5 \times 10^{-5} = 2,000 \text{ and } B = 1,000/2,000 = \mathbf{0.5}.$$

Solution 15.35

A parallel RLC circuit has an $R = 10 \text{ k}\Omega$, an $L = 100 \text{ mH}$, and a resonant frequency of 200 krad/s , calculate the value of C , the value of the quality factor, and the bandwidth.

Solution

Since,

$$\omega_o = \frac{1}{\sqrt{LC}} \text{ or } LC = 1/(\omega_o)^2$$
$$Q = R/(\omega_o L) = \omega_o RC$$
$$B = \omega_o/Q$$

we get $C = 1/(4 \times 10^{10} \times 0.1) = 0.25 \times 10^{-9} = \mathbf{0.25 \text{ nF}}$ and $Q = 2 \times 10^5 \times 10^4 \times 0.25 \times 10^{-9} = \mathbf{0.5}$.

Finally, $B = 200\text{k}/0.5 = \mathbf{400 \text{ krad/s}}$. Note, since the bandwidth is equal to 400 krad/s , the lower frequency must be equal to 0 Hz ! Clearly the bandwidth goes from DC to 400 krad/s .

Solution 14.36

It is expected that a parallel RLC resonant circuit has a midband admittance of $25 \times 10^{-3} \text{ S}$, quality factor of 120, and a resonant frequency of 200 krad/s. Calculate the values of R , L , and C . Find the bandwidth and the half-power frequencies.

Solution

At resonance,

$$Y = \frac{1}{R} \longrightarrow R = \frac{1}{Y} = \frac{1}{25 \times 10^{-3}} = \mathbf{40 \, \Omega}$$

$$Q = \omega_0 RC \longrightarrow C = \frac{Q}{\omega_0 R} = \frac{120}{(200 \times 10^3)(40)} = \mathbf{15 \, \mu\text{F}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \longrightarrow L = \frac{1}{\omega_0^2 C} = \frac{1}{(4 \times 10^{10})(15 \times 10^{-6})} = \mathbf{1.6667 \, \mu\text{H}}$$

$$B = \frac{\omega_0}{Q} = \frac{200 \times 10^3}{120} = \mathbf{1.6667 \, \text{krad/s}}$$

$$\omega_1 = \omega_0 - \frac{B}{2} = 200 - 0.8333 = \mathbf{199.167 \, \text{krad/s}}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 200 + 0.8333 = \mathbf{200.833 \, \text{krad/s}}$$

Solution 4.37

$$\omega_0 = \frac{1}{\sqrt{LC}} = 5000 \text{ rad/s}$$

$$\mathbf{Y}(\omega_0) = \frac{1}{R} \longrightarrow \mathbf{Z}(\omega_0) = R = \mathbf{2 \text{ k}\Omega}$$

$$\mathbf{Y}(\omega_0/4) = \frac{1}{R} + j \left(\frac{\omega_0}{4} C - \frac{4}{\omega_0 L} \right) = 0.5 - j18.75 \text{ mS}$$

$$\mathbf{Z}(\omega_0/4) = \frac{1}{0.0005 - j0.01875} = \mathbf{(1.4212 + j53.3) \Omega}$$

$$\mathbf{Y}(\omega_0/2) = \frac{1}{R} + j \left(\frac{\omega_0}{2} C - \frac{2}{\omega_0 L} \right) = 0.5 - j7.5 \text{ mS}$$

$$\mathbf{Z}(\omega_0/2) = \frac{1}{0.0005 - j0.0075} = \mathbf{(8.85 + j132.74) \Omega}$$

$$\mathbf{Y}(2\omega_0) = \frac{1}{R} + j \left(2\omega_0 L - \frac{1}{2\omega_0 C} \right) = 0.5 + j7.5 \text{ mS}$$

$$\mathbf{Z}(2\omega_0) = \mathbf{(8.85 - j132.74) \Omega}$$

$$\mathbf{Y}(4\omega_0) = \frac{1}{R} + j \left(4\omega_0 L - \frac{1}{4\omega_0 C} \right) = 0.5 + j18.75 \text{ mS}$$

$$\mathbf{Z}(4\omega_0) = \mathbf{(1.4212 - j53.3) \Omega}$$

Solution 14.38

Find the resonant frequency of the circuit in Fig. 14.78.

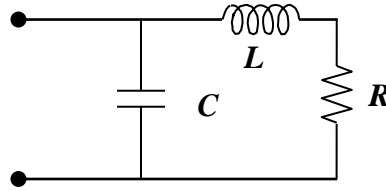


Figure 14.78
For Prob. 14.38.

Solution

$$\begin{aligned}
 Z &= (1/(j\omega C))(R+j\omega L)/[(1/(j\omega C))+R+j\omega L] = (R+j\omega L)/(1+j\omega RC-\omega^2 LC) \\
 &= (R+j\omega L)(1-\omega^2 LC-j\omega RC)/[(1-\omega^2 LC)^2+(\omega RC)^2] \\
 &= [R-\omega^2 RLC+\omega^2 RLC+j(\omega L-\omega^3 L^2 C-\omega R^2 C)]/[(1-\omega^2 LC)^2+(\omega RC)^2]
 \end{aligned}$$

To find the resonant frequency all we need to do is to set the imaginary part to zero.

Thus, $(\omega L-\omega^3 L^2 C-\omega R^2 C) = 0 = (L-\omega^2 L^2 C-R^2 C)$ gives us $(\omega_o)^2 = (L-R^2 C)/(L^2 C)$ or

$$\omega_o = \sqrt{\frac{L-R^2 C}{L^2 C}} \text{ rad/s}$$

Solution 4.39

$$Y = \frac{1}{R + j\omega L} + j\omega C = j\omega C + \frac{R - j\omega L}{R^2 + \omega^2 L^2}$$

At resonance, $\text{Im}(\mathbf{Y}) = 0$, i.e.

$$\omega_0 C - \frac{\omega_0 L}{R^2 + \omega_0^2 L^2} = 0$$

$$R^2 + \omega_0^2 L^2 = \frac{L}{C}$$

$$\omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = \sqrt{\frac{1}{(40 \times 10^{-3})(1 \times 10^{-6})} - \left(\frac{50}{40 \times 10^{-3}}\right)^2}$$

$$\omega_0 = \mathbf{4.841 \text{ krad/s}}$$

Solution 14.40

$$(a) \quad B = \omega_2 - \omega_1 = 2\pi(f_2 - f_1) = 2\pi(90 - 86) \times 10^3 = 8\pi \text{ krad/s}$$

$$\omega_o = \frac{1}{2}(\omega_1 + \omega_2) = 2\pi(88) \times 10^3 = 176\pi \times 10^3$$

$$B = \frac{1}{RC} \longrightarrow C = \frac{1}{BR} = \frac{1}{8\pi \times 10^3 \times 2 \times 10^3} = \underline{19.89 \text{ nF}}$$

$$(b) \quad \omega_o = \frac{1}{\sqrt{LC}} \longrightarrow L = \frac{1}{\omega_o^2 C} = \frac{1}{(176\pi \times 10^3)^2 \times 19.89 \times 10^{-9}} = \mathbf{164.45 \text{ } \mu\text{H}}$$

$$(c) \quad \omega_o = 176\pi = \underline{552.9 \text{ krad/s}}$$

$$(d) \quad B = 8\pi = \underline{25.13 \text{ krad/s}}$$

$$(e) \quad Q = \frac{\omega_o}{B} = \frac{176\pi}{8\pi} = \underline{22}$$

Solution 14.41

Using Fig. 14.80, design a problem to help other students to better understand the quality factor, the resonant frequency, and bandwidth of an *RLC* circuit.

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in Example 14.9.

Problem

For the circuits in Fig. 14.80, find the resonant frequency ω_0 , the quality factor Q , and the bandwidth B . Let $C = 0.1$ F, $R_1 = 10\ \Omega$, $R_2 = 2\ \Omega$, and $L = 2$ H.

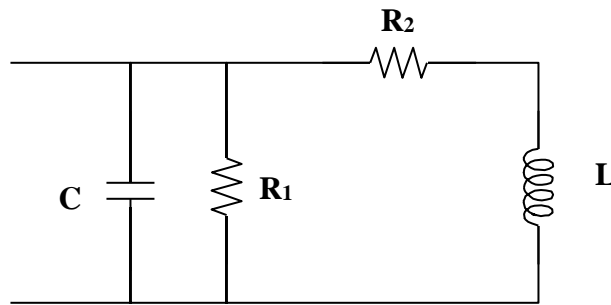


Figure 14.80
For Prob. 14.41.

Solution

To find ω_0 , we need to find the input impedance or input admittance and set imaginary component equal to zero. Finding the input admittance seems to be the easiest approach.

$$\mathbf{Y} = j\omega 0.1 + 0.1 + 1/(2 + j\omega 2) = j\omega 0.1 + 0.1 + [2/(4 + 4\omega^2)] - [j\omega 2/(4 + 4\omega^2)]$$

At resonance,

$$0.1\omega = 2\omega/(4 + 4\omega^2) \text{ or } 4\omega^2 + 4 = 20 \text{ or } \omega^2 = 4 \text{ or } \omega_0 = \mathbf{2 \text{ rad/s}}$$

and,

$$\mathbf{Y} = 0.1 + 2/(4 + 16) = 0.1 + 0.1 = 0.2 \text{ S}$$

The bandwidth is define as the two values of ω such that $|\mathbf{Y}| = 1.4142(0.2) = 0.28284 \text{ S}$.

I do not know about you, but I sure would not want to solve this analytically. So how about using MATLAB or excel to solve for the two values of ω ?

Using Excel, we get $\omega_1 = 1.414$ rad/s and $\omega_2 = 3.741$ rad/s or $B = \mathbf{2.327}$ rad/s

We can now use the relationship between ω_o and the bandwidth.

$$Q = \omega_o/B = 2/2.327 = \mathbf{0.8595}$$

Solution 14.42

(a) This is a series RLC circuit.

$$R = 2 + 6 = 8 \, \Omega, \quad L = 1 \, \text{H}, \quad C = 0.4 \, \text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.4}} = \mathbf{1.5811 \, \text{rad/s}}$$

$$Q = \frac{\omega_0 L}{R} = \frac{1.5811}{8} = \mathbf{0.1976}$$

$$B = \frac{R}{L} = \mathbf{8 \, \text{rad/s}}$$

(b) This is a parallel RLC circuit.

$$3 \, \mu\text{F} \text{ and } 6 \, \mu\text{F} \longrightarrow \frac{(3)(6)}{3+6} = 2 \, \mu\text{F}$$

$$C = 2 \, \mu\text{F}, \quad R = 2 \, \text{k}\Omega, \quad L = 20 \, \text{mH}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2 \times 10^{-6})(20 \times 10^{-3})}} = \mathbf{5 \, \text{krad/s}}$$

$$Q = \frac{R}{\omega_0 L} = \frac{2 \times 10^3}{(5 \times 10^3)(20 \times 10^{-3})} = \mathbf{20}$$

$$B = \frac{1}{RC} = \frac{1}{(2 \times 10^3)(2 \times 10^{-6})} = \mathbf{250 \, \text{rad/s}}$$

Solution 14.43

$$(a) \quad \mathbf{Z}_{in} = (1/j\omega C) \parallel (R + j\omega L)$$

$$\mathbf{Z}_{in} = \frac{\frac{R + j\omega L}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} = \frac{R + j\omega L}{1 - \omega^2 LC + j\omega RC}$$

$$\mathbf{Z}_{in} = \frac{(R + j\omega L)(1 - \omega^2 LC - j\omega RC)}{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}$$

At resonance, $\text{Im}(\mathbf{Z}_{in}) = 0$, i.e.

$$0 = \omega_0 L(1 - \omega_0^2 LC) - \omega_0 R^2 C$$

$$\omega_0^2 L^2 C = L - R^2 C$$

$$\omega_0 = \sqrt{\frac{L - R^2 C}{L^2 C}} = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$(b) \quad \mathbf{Z}_{in} = R \parallel (j\omega L + 1/j\omega C)$$

$$\mathbf{Z}_{in} = \frac{R(j\omega L + 1/j\omega C)}{R + j\omega L + 1/j\omega C} = \frac{R(1 - \omega^2 LC)}{(1 - \omega^2 LC) + j\omega RC}$$

$$\mathbf{Z}_{in} = \frac{R(1 - \omega^2 LC)[(1 - \omega^2 LC) - j\omega RC]}{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}$$

At resonance, $\text{Im}(\mathbf{Z}_{in}) = 0$, i.e.


$$0 = R(1 - \omega^2 LC)\omega RC$$

$$1 - \omega^2 LC = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Solution 14.44

Consider the circuit below.

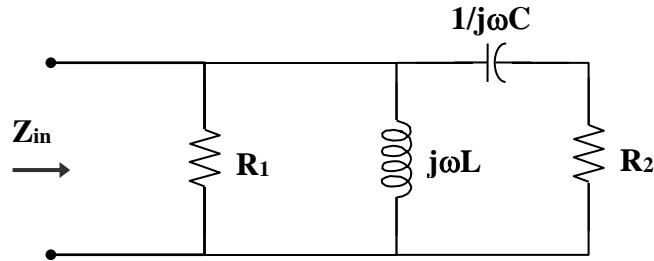

$$(a) \quad Z_{in} = (R_1 \parallel j\omega L) \parallel (R_2 + 1/j\omega C)$$

$$Z_{in} = \left(\frac{R_1 j\omega L}{R_1 + j\omega L} \right) \parallel \left(R_2 + \frac{1}{j\omega C} \right)$$

$$Z_{in} = \frac{\frac{j\omega R_1 L}{R_1 + j\omega L} \cdot \left(R_2 + \frac{1}{j\omega C} \right)}{R_2 + \frac{1}{j\omega C} + \frac{jR_1 \omega L}{R_1 + j\omega L}}$$

$$Z_{in} = \frac{j\omega R_1 L (1 + j\omega R_2 C)}{(R_1 + j\omega L)(1 + j\omega R_2 C) - \omega^2 L C R_1}$$

$$Z_{in} = \frac{-\omega^2 R_1 R_2 L C + j\omega R_1 L}{R_1 - \omega^2 L C R_1 - \omega^2 L C R_2 + j\omega (L + R_1 R_2 C)}$$

$$Z_{in} = \frac{(-\omega^2 R_1 R_2 L C + j\omega R_1 L)[R_1 - \omega^2 L C R_1 - \omega^2 L C R_2 - j\omega (L + R_1 R_2 C)]}{(R_1 - \omega^2 L C R_1 - \omega^2 L C R_2)^2 + \omega^2 (L + R_1 R_2 C)^2}$$

At resonance, $\text{Im}(Z_{in}) = 0$, i.e.

$$0 = \omega^3 R_1 R_2 L C (L + R_1 R_2 C) + \omega R_1 L (R_1 - \omega^2 L C R_1 - \omega^2 L C R_2)$$

$$0 = \omega^3 R_1^2 R_2^2 L C^2 + R_1^2 \omega L - \omega^3 R_1^2 L^2 C$$

$$0 = \omega^2 R_2^2 C^2 + 1 - \omega^2 L C$$

$$\omega^2 (L C - R_2^2 C^2) = 1$$

$$\omega_0 = \frac{1}{\sqrt{L C - R_2^2 C^2}}$$

$$\omega_0 = \frac{1}{\sqrt{(0.02)(9 \times 10^{-6}) - (0.1)^2 (9 \times 10^{-6})^2}}$$

$$\omega_0 = \mathbf{2.357 \text{ krad/s}}$$

(b) At $\omega = \omega_0 = 2.357 \text{ krad/s}$,
 $j\omega L = j(2.357 \times 10^3)(20 \times 10^{-3}) = j47.14$

$$R_1 \parallel j\omega L = \frac{j47.14}{1 + j47.14} = 0.9996 + j0.0212$$

$$R_2 + \frac{1}{j\omega C} = 0.1 + \frac{1}{j(2.357 \times 10^3)(9 \times 10^{-6})} = 0.1 - j47.14$$


$$\mathbf{Z}_{in}(\omega_0) = (R_1 \parallel j\omega L) \parallel (R_2 + 1/j\omega C)$$

$$\mathbf{Z}_{in}(\omega_0) = \frac{(0.9996 + j0.0212)(0.1 - j47.14)}{(0.9996 + j0.0212) + (0.1 - j47.14)}$$

$$\mathbf{Z}_{in}(\omega_0) = \mathbf{1\Omega}$$

Solution 14.45

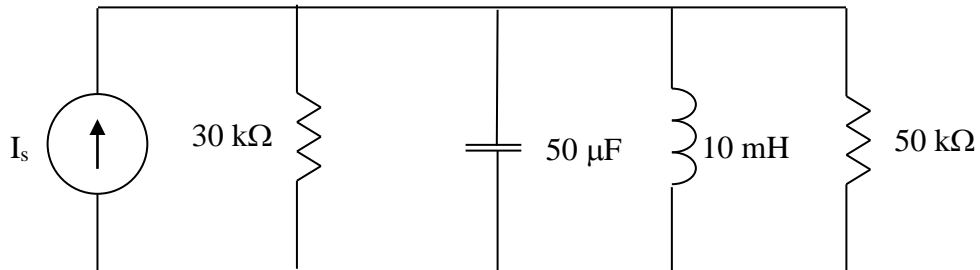Convert the voltage source to a current source as shown below.



$$R = 30//50 = 30 \times 50 / 80 = 18.75\text{ k}\Omega$$

This is a parallel resonant circuit.

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \times 10^{-3} \times 50 \times 10^{-6}}} = \underline{447.21\text{ rad/s}}$$

$$B = \frac{1}{RC} = \frac{1}{18.75 \times 10^3 \times 50 \times 10^{-6}} = \underline{1.067\text{ rad/s}}$$


$$Q = \frac{\omega_o}{B} = \frac{447.21}{1.067} = \underline{419.13}$$

447.2 rad/s, 1.067 rad/s, 419.1

Solution 14.46

$$(a) \quad 1 \parallel j\omega = \frac{j\omega}{1+j\omega}, \quad 1 \parallel \frac{1}{j\omega} = \frac{1/j\omega}{1+1/j\omega} = \frac{1}{1+j\omega}$$

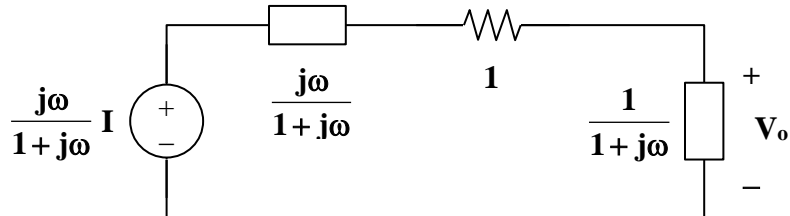Transform the current source gives the circuit below.



$$V_o = \frac{\frac{1}{1+j\omega}}{1 + \frac{1}{1+j\omega} + \frac{j\omega}{1+j\omega}} \cdot \frac{j\omega}{1+j\omega} I$$

$$H(\omega) = \frac{V_o}{I} = \frac{j\omega}{2(1+j\omega)^2}$$

$$(b) \quad H(1) = \frac{1}{2(1+j)^2}$$

$$|H(1)| = \frac{1}{2(\sqrt{2})^2} = 0.25$$

Solution 14.47

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{\mathbf{R}}{\mathbf{R} + j\omega\mathbf{L}} = \frac{1}{1 + j\omega\mathbf{L}/\mathbf{R}}$$

$H(0) = 1$ and $H(\infty) = 0$ showing that this circuit is a lowpass filter.

At the corner frequency, $|H(\omega_c)| = \frac{1}{\sqrt{2}}$, i.e.

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega_c \mathbf{L}}{\mathbf{R}}\right)^2}} \longrightarrow 1 = \frac{\omega_c \mathbf{L}}{\mathbf{R}} \quad \text{or} \quad \omega_c = \frac{\mathbf{R}}{\mathbf{L}}$$

Hence,

$$\omega_c = \frac{\mathbf{R}}{\mathbf{L}} = 2\pi f_c$$

$$f_c = \frac{1}{2\pi} \cdot \frac{\mathbf{R}}{\mathbf{L}} = \frac{1}{2\pi} \cdot \frac{10 \times 10^3}{2 \times 10^{-3}} = \mathbf{796 \text{ kHz}}$$

Solution 14.48

Find the transfer function $\mathbf{V}_o/\mathbf{V}_s$ of the circuit in Fig. 14.86. Show that the circuit is a lowpass filter.

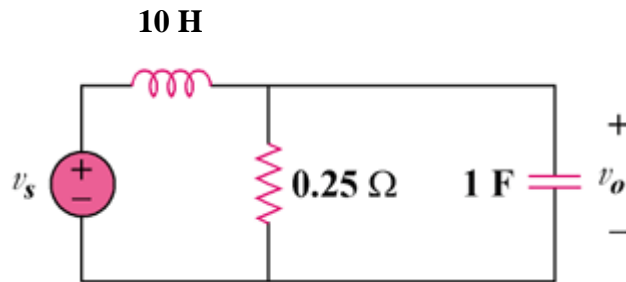


Figure 14.86
For Prob. 14.48.

Solution

$$\begin{aligned}\mathbf{H}(\omega) &= \frac{\mathbf{R} \parallel \frac{1}{j\omega\mathbf{C}}}{j\omega\mathbf{L} + \mathbf{R} \parallel \frac{1}{j\omega\mathbf{C}}} \\ \mathbf{H}(\omega) &= \frac{\frac{R/j\omega C}{R + 1/j\omega C}}{j\omega L + \frac{R/j\omega C}{R + 1/j\omega C}} = \frac{\frac{R}{1 + j\omega RC}}{j\omega L + \frac{R}{1 + j\omega RC}} = \frac{R}{R + j\omega L + \frac{R/j\omega C}{R + 1/j\omega C}} \\ \mathbf{H}(\omega) &= \frac{0.25}{(0.25 - \omega^2 2.5) + j\omega 10}\end{aligned}$$

$\mathbf{H}(0) = 1$ and $\mathbf{H}(\infty) = 0$ showing that **this circuit is a lowpass filter.**

Solution 14.49

Design a problem to help other students to better understand lowpass filters described by transfer functions.

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

Determine the cutoff frequency of the lowpass filter described by

$$H(\omega) = \frac{4}{2 + j\omega 10}$$

Find the gain in dB and phase of $\mathbf{H}(\omega)$ at $\omega = 2$ rad/s.

Solution

$$\text{At dc, } H(0) = \frac{4}{2} = 2.$$

$$\text{Hence, } |H(\omega)| = \frac{1}{\sqrt{2}} H(0) = \frac{2}{\sqrt{2}}$$

$$\frac{2}{\sqrt{2}} = \frac{4}{\sqrt{4 + 100\omega_c^2}}$$

$$4 + 100\omega_c^2 = 8 \longrightarrow \omega_c = 0.2$$

$$H(2) = \frac{4}{2 + j20} = \frac{2}{1 + j10}$$

$$|H(2)| = \frac{2}{\sqrt{101}} = 0.199$$

$$\text{In dB, } 20\log_{10}|H(2)| = \mathbf{-14.023}$$

$$\arg H(2) = -\tan^{-1}10 = -84.3^\circ \text{ or } \omega_c = \mathbf{1.4713 \text{ rad/sec.}}$$

Solution 14.50

Determine what type of filter is in Fig. 14.87. Calculate the corner frequency f_c .

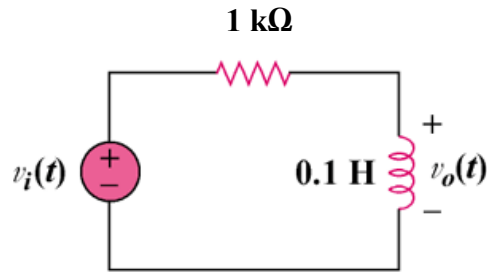


Figure 14.87
For Prob. 14.50.

Solution

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{j\omega L}{R + j\omega L}$$

$H(0) = 0$ and $H(\infty) = 1$ showing that **this circuit is a highpass filter**.


$$|\mathbf{H}(\omega_c)| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega_c L}\right)^2}} \longrightarrow 1 = \frac{R}{\omega_c L}$$

or $\omega_c = \frac{R}{L} = 2\pi f_c$

$$f_c = \frac{1}{2\pi} \cdot \frac{R}{L} = \frac{1}{2\pi} \cdot \frac{1,000}{0.1} = \mathbf{1.5915 \text{ kHz}}.$$

Solution 14.51

The lowpass RL filter is shown below.

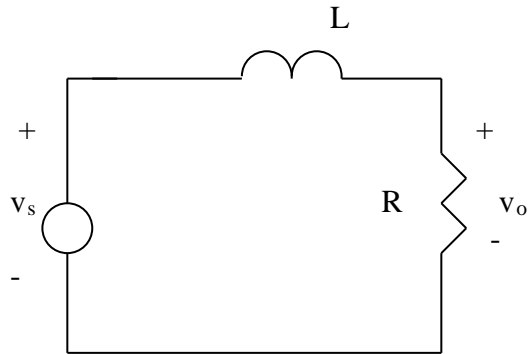

$$H = \frac{V_o}{V_s} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega L/R}$$

$$\omega_c = \frac{R}{L} = 2\pi f_c \quad \longrightarrow \quad R = 2\pi f_c L = 2\pi \times 5 \times 10^3 \times 40 \times 10^{-3} = \underline{\underline{1.256 \text{ k}\Omega}}$$

Solution 14.52

Design a problem to help other students to better understand passive highpass filters.

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

In a highpass RL filter with a cutoff frequency of 100 kHz, $L = 40$ mH. Find R .

Solution

$$\omega_c = \frac{R}{L} = 2\pi f_c$$

$$R = 2\pi f_c L = (2\pi)(10^5)(40 \times 10^{-3}) = \mathbf{25.13 \text{ k}\Omega}$$

Solution 14.53

$$\omega_1 = 2\pi f_1 = 20\pi \times 10^3$$

$$\omega_2 = 2\pi f_2 = 22\pi \times 10^3$$

$$B = \omega_2 - \omega_1 = 2\pi \times 10^3$$

$$\omega_0 = \frac{\omega_2 + \omega_1}{2} = 21\pi \times 10^3$$

$$Q = \frac{\omega_0}{B} = \frac{21\pi}{2\pi} = \mathbf{10.5}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \longrightarrow L = \frac{1}{\omega_0^2 C}$$

$$L = \frac{1}{(21\pi \times 10^3)^2 (80 \times 10^{-12})} = \mathbf{2.872 \text{ H}}$$

$$B = \frac{R}{L} \longrightarrow R = BL$$

$$R = (2\pi \times 10^3)(2.872) = \mathbf{18.045 \text{ k}\Omega}$$

Solution 14.54

We start with a series RLC circuit and use the equations related to the circuit and the values for a bandstop filter.

$$Q = \omega_o L/R = 1/(\omega_o CR) = 20; \quad B = R/L = \omega_o/Q = 10/20 = 0.5; \quad \omega_o = 1/(LC)^{0.5} = 10$$

$$(LC)^{0.5} = 0.1 \text{ or } LC = 0.01. \text{ Pick } L = \mathbf{10 \text{ H}} \text{ then } C = \mathbf{1 \text{ mF}}.$$

$$Q = 20 = \omega_o L/R = 10 \times 10/R \text{ or } R = 100/20 = \mathbf{5 \text{ } \Omega}.$$

Solution 14.55

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(25 \times 10^{-3})(0.4 \times 10^{-6})}} = 10 \text{ krad/s}$$

$$B = \frac{R}{L} = \frac{10}{25 \times 10^{-3}} = 0.4 \text{ krad/s}$$

$$Q = \frac{10}{0.4} = \mathbf{25}$$

$$\omega_1 = \omega_o - B/2 = 10 - 0.2 = 9.8 \text{ krad/s} \quad \text{or} \quad f_1 = \frac{9.8}{2\pi} = 1.56 \text{ kHz}$$

$$\omega_2 = \omega_o + B/2 = 10 + 0.2 = 10.2 \text{ krad/s} \quad \text{or} \quad f_2 = \frac{10.2}{2\pi} = 1.62 \text{ kHz}$$

Therefore,

$$\mathbf{1.56 \text{ kHz} < f < 1.62 \text{ kHz}}$$

Solution 14.56

(a) From Eq. 14.54,

$$\mathbf{H}(s) = \frac{R}{R + sL + \frac{1}{sC}} = \frac{sRC}{1 + sRC + s^2LC} = \frac{s \frac{R}{L}}{s^2 + s \frac{R}{L} + \frac{1}{LC}}$$

Since $B = \frac{R}{L}$ and $\omega_0 = \frac{1}{\sqrt{LC}}$,

$$\mathbf{H}(s) = \frac{sB}{s^2 + sB + \omega_0^2}$$


(b) From Eq. 14.56,

$$\mathbf{H}(s) = \frac{sL + \frac{1}{sC}}{R + sL + \frac{1}{sC}} = \frac{s^2 + \frac{1}{LC}}{s^2 + s \frac{R}{L} + \frac{1}{LC}}$$

$$\mathbf{H}(s) = \frac{s^2 + \omega_0^2}{s^2 + sB + \omega_0^2}$$

Solution 14.57

(a) Consider the circuit below.

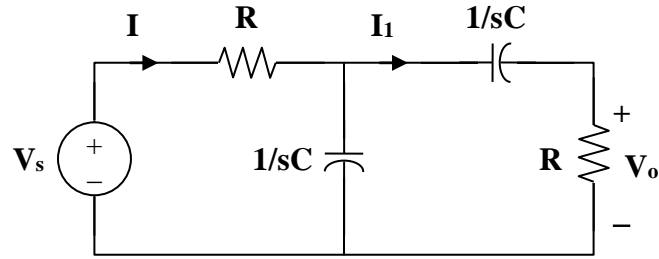

$$Z(s) = R + \frac{1}{sC} \parallel \left(R + \frac{1}{sC} \right) = R + \frac{\frac{1}{sC} \left(R + \frac{1}{sC} \right)}{R + \frac{2}{sC}}$$

$$Z(s) = R + \frac{1 + sRC}{sC(2 + sRC)}$$

$$Z(s) = \frac{1 + 3sRC + s^2 R^2 C^2}{sC(2 + sRC)}$$

$$I = \frac{V_s}{Z}$$

$$I_1 = \frac{1/sC}{2/sC + R} I = \frac{V_s}{Z(2 + sRC)}$$

$$V_o = I_1 R = \frac{R V_s}{2 + sRC} \cdot \frac{sC(2 + sRC)}{1 + 3sRC + s^2 R^2 C^2}$$

$$H(s) = \frac{V_o}{V_s} = \frac{sRC}{1 + 3sRC + s^2 R^2 C^2}$$

$$H(s) = \frac{1}{3} \left[\frac{\frac{3}{RC} s}{s^2 + \frac{3}{RC} s + \frac{1}{R^2 C^2}} \right]$$

$$\text{Thus, } \omega_0^2 = \frac{1}{R^2 C^2} \quad \text{or} \quad \omega_0 = \frac{1}{RC} = \mathbf{1 \text{ rad/s}}$$

$$B = \frac{3}{RC} = \mathbf{3 \text{ rad/s}}$$

(b) Similarly,

$$\mathbf{Z}(s) = sL + R \parallel (R + sL) = sL + \frac{R(R + sL)}{2R + sL}$$

$$\mathbf{Z}(s) = \frac{R^2 + 3sRL + s^2L^2}{2R + sL}$$

$$\mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}}, \quad \mathbf{I}_1 = \frac{R}{2R + sL} \mathbf{I} = \frac{R \mathbf{V}_s}{\mathbf{Z}(2R + sL)}$$

$$\mathbf{V}_o = \mathbf{I}_1 \cdot sL = \frac{sLR \mathbf{V}_s}{2R + sL} \cdot \frac{2R + sL}{R^2 + 3sRL + s^2L^2}$$

$$\mathbf{H}(s) = \frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{sRL}{R^2 + 3sRL + s^2L^2} = \frac{\frac{1}{3} \left(\frac{3R}{L} s \right)}{s^2 + \frac{3R}{L} s + \frac{R^2}{L^2}}$$

$$\text{Thus, } \omega_0 = \frac{R}{L} = \mathbf{1 \text{ rad/s}}$$

$$B = \frac{3R}{L} = \mathbf{3 \text{ rad/s}}$$

Solution 14.58

The circuit parameters for a series RLC bandstop filter are $R = 250\ \Omega$, $L = 1\ \text{mH}$, $C = 40\ \text{pF}$. Calculate:

- (a) the center frequency
- (b) the half-power frequencies
- (c) the quality factor.

Solution

$$(a) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.001)(40 \times 10^{-12})}} = \mathbf{5\ \text{Mrad/s}}$$

$$(b) \quad B = \frac{R}{L} = \frac{250}{0.001} = 0.25 \times 10^6\ \text{rad/s}$$

$$Q = \frac{\omega_0}{B} = \frac{5 \times 10^6}{0.25 \times 10^6} = 20$$

As a high Q (Q greater than 10) circuit,


$$\omega_1 = \omega_0 - \frac{B}{2} = 10^6 (5 - 0.125) = \mathbf{4.875\ \text{Mrad/s}}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 10^6 (5 + 0.125) = \mathbf{5.125\ \text{Mrad/s}}$$

$$(c) \quad \text{As seen in part (b),} \quad Q = \mathbf{20}$$

Solution 14.59

Consider the circuit below.

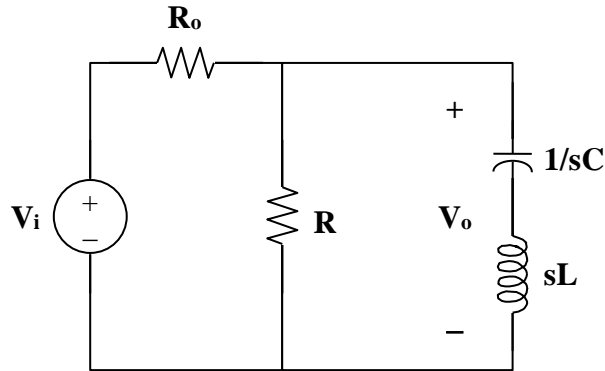

where $L = 1 \text{ mH}$, $C = 4 \text{ } \mu\text{F}$, $R_o = 6 \text{ } \Omega$, and $R = 4 \text{ } \Omega$.

$$\mathbf{Z}(s) = R \parallel \left(sL + \frac{1}{sC} \right) = \frac{R(sL + 1/sC)}{R + sL + 1/sC}$$

$$\mathbf{Z}(s) = \frac{R(1 + s^2LC)}{1 + sRC + s^2LC}$$

$$\mathbf{H} = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{\mathbf{Z}}{\mathbf{Z} + R_o} = \frac{R(1 + s^2LC)}{R_o + sRR_oC + s^2LCR_o + R + s^2LCR}$$

$$\mathbf{Z}_{in} = R_o + \mathbf{Z} = R_o + \frac{R(1 + s^2LC)}{1 + sRC + s^2LC}$$

$$\mathbf{Z}_{in} = \frac{R_o + sRR_oC + s^2LCR_o + R + s^2LCR}{1 + sRC + s^2LC}$$

$$s = j\omega$$

$$\mathbf{Z}_{in} = \frac{R_o + j\omega RR_oC - \omega^2LCR_o + R - \omega^2LCR}{1 - \omega^2LC + j\omega RC}$$

$$\mathbf{Z}_{in} = \frac{(R_o + R - \omega^2LCR_o - \omega^2LCR + j\omega RR_oC)(1 - \omega^2LC - j\omega RC)}{(1 - \omega^2LC)^2 + (\omega RC)^2}$$

$\text{Im}(\mathbf{Z}_{in}) = 0$ implies that

$$-\omega RC[R_o + R - \omega^2LCR_o - \omega^2LCR] + \omega RR_oC(1 - \omega^2LC) = 0$$

$$R_o + R - \omega^2 LCR_o - \omega^2 LCR - R_o + \omega^2 LCR_o = 0$$

$$\omega^2 LCR = R$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1 \times 10^{-3})(4 \times 10^{-6})}} = \mathbf{15.811 \text{ krad/s}}$$

$$\mathbf{H} = \frac{R(1 - \omega^2 LC)}{R_o + j\omega RR_o C + R - \omega^2 LCR_o - \omega^2 LCR}$$

$$H_{\max} = H(0) = \frac{R}{R_o + R}$$

$$\text{or } H_{\max} = H(\infty) = \lim_{\omega \rightarrow \infty} \frac{R\left(\frac{1}{\omega^2} - LC\right)}{\frac{R_o + R}{\omega^2} + j\frac{RR_o C}{\omega} - LC(R + R_o)} = \frac{R}{R + R_o}$$

$$\text{At } \omega_1 \text{ and } \omega_2, |\mathbf{H}| = \frac{1}{\sqrt{2}} H_{\max}$$

$$\frac{R}{\sqrt{2}(R_o + R)} = \left| \frac{R(1 - \omega^2 LC)}{R_o + R - \omega^2 LC(R_o + R) + j\omega RR_o C} \right|$$

$$\frac{1}{\sqrt{2}} = \frac{(R_o + R)(1 - \omega^2 LC)}{\sqrt{(\omega RR_o C)^2 + (R_o + R - \omega^2 LC(R_o + R))^2}}$$

$$\frac{1}{\sqrt{2}} = \frac{10(1 - \omega^2 \cdot 4 \times 10^{-9})}{\sqrt{(96 \times 10^{-6} \omega)^2 + (10 - \omega^2 \cdot 4 \times 10^{-8})^2}}$$

$$0 = \frac{10(1 - \omega^2 \cdot 4 \times 10^{-9})}{\sqrt{(96 \times 10^{-6} \omega)^2 + (10 - \omega^2 \cdot 4 \times 10^{-8})^2}} - \frac{1}{\sqrt{2}}$$

$$(10 - \omega^2 \cdot 4 \times 10^{-8})(\sqrt{2}) - \sqrt{(96 \times 10^{-6} \omega)^2 + (10 - \omega^2 \cdot 4 \times 10^{-8})^2} = 0$$

$$(2)(10 - \omega^2 \cdot 4 \times 10^{-8})^2 = (96 \times 10^{-6} \omega)^2 + (10 - \omega^2 \cdot 4 \times 10^{-8})^2$$

$$(96 \times 10^{-6} \omega)^2 - (10 - \omega^2 \cdot 4 \times 10^{-8})^2 = 0$$

$$1.6 \times 10^{-15} \omega^4 - 8.092 \times 10^{-7} \omega^2 + 100 = 0$$

$$\omega^4 - 5.058 \times 10^8 + 6.25 \times 10^{16} = 0$$

$$\omega^2 = \begin{cases} 2.9109 \times 10^8 \\ 2.1471 \times 10^8 \end{cases}$$

Hence,

$$\omega_1 = 14.653 \text{ krad/s}$$

$$\omega_2 = 17.061 \text{ krad/s}$$

$$B = \omega_2 - \omega_1 = 17.061 - 14.653 = \mathbf{2.408 \text{ krad/s}}$$

Solution 14.60

Obtain the transfer function of a highpass filter with a passband gain of 100 and a cutoff frequency of 40 rad/s.

Solution

$$\mathbf{H}'(\omega) = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\omega}{j\omega + 1/RC} \quad (\text{from Eq. 14.52})$$

This has a unity passband gain, i.e. $H(\infty) = 1$.

$$\frac{1}{RC} = \omega_c = 40$$

$$\mathbf{H}^{\wedge}(\omega) = 100\mathbf{H}'(\omega) = \frac{j100\omega}{40 + j\omega}$$

$$\mathbf{H}(\omega) = \mathbf{j100\omega/(40+j\omega)}$$

Solution 14.61

$$(a) \quad \mathbf{V}_+ = \frac{1/j\omega C}{R + 1/j\omega C} \mathbf{V}_i, \quad \mathbf{V}_- = \mathbf{V}_o$$

Since $\mathbf{V}_+ = \mathbf{V}_-$,

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1}{1 + j\omega RC}$$

$$(b) \quad \mathbf{V}_+ = \frac{R}{R + 1/j\omega C} \mathbf{V}_i, \quad \mathbf{V}_- = \mathbf{V}_o$$

Since $\mathbf{V}_+ = \mathbf{V}_-$,

$$\frac{j\omega RC}{1 + j\omega RC} \mathbf{V}_i = \mathbf{V}_o$$

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{j\omega RC}{1 + j\omega RC}$$

Solution 14.62

This is a highpass filter.

$$\mathbf{H}(\omega) = \frac{j\omega RC}{1 + j\omega RC} = \frac{1}{1 - j/\omega RC}$$

$$\mathbf{H}(\omega) = \frac{1}{1 - j\omega_c/\omega}, \quad \omega_c = \frac{1}{RC} = 2\pi(1000)$$

$$\mathbf{H}(\omega) = \frac{1}{1 - jf_c/f} = \frac{1}{1 - j1000/f}$$

$$(a) \quad \mathbf{H}(f = 200 \text{ Hz}) = \frac{1}{1 - j5} = \frac{\mathbf{V}_o}{\mathbf{V}_i}$$

$$|\mathbf{V}_o| = \frac{120 \text{ mV}}{|1 - j5|} = \mathbf{23.53 \text{ mV}}$$

$$(b) \quad \mathbf{H}(f = 2 \text{ kHz}) = \frac{1}{1 - j0.5} = \frac{\mathbf{V}_o}{\mathbf{V}_i}$$

$$|\mathbf{V}_o| = \frac{120 \text{ mV}}{|1 - j0.5|} = \mathbf{107.3 \text{ mV}}$$

$$(c) \quad \mathbf{H}(f = 10 \text{ kHz}) = \frac{1}{1 - j0.1} = \frac{\mathbf{V}_o}{\mathbf{V}_i}$$

$$|\mathbf{V}_o| = \frac{120 \text{ mV}}{|1 - j0.1|} = \mathbf{119.4 \text{ mV}}$$

Solution 14.63

For an active highpass filter,

$$H(s) = -\frac{sC_i R_f}{1 + sC_i R_i} \quad (1)$$

But

$$H(s) = -\frac{10s}{1 + s/10} \quad (2)$$

Comparing (1) and (2) leads to:

$$C_i R_f = 10 \quad \longrightarrow \quad R_f = \frac{10}{C_i} = \underline{10\text{M}\Omega}$$

$$C_i R_i = 0.1 \quad \longrightarrow \quad R_i = \frac{0.1}{C_i} = \underline{100\text{k}\Omega}$$

Solution 14.64

$$Z_f = R_f \parallel \frac{1}{j\omega C_f} = \frac{R_f}{1 + j\omega R_f C_f}$$

$$Z_i = R_i + \frac{1}{j\omega C_i} = \frac{1 + j\omega R_i C_i}{j\omega C_i}$$

Hence,

$$H(\omega) = \frac{V_o}{V_i} = \frac{-Z_f}{Z_i} = \frac{-j\omega R_f C_i}{(1 + j\omega R_f C_f)(1 + j\omega R_i C_i)}$$

This is a bandpass filter. $H(\omega)$ is similar to the product of the transfer function of a lowpass filter and a highpass filter.

Solution 14.65

$$\mathbf{V}_+ = \frac{\mathbf{R}}{\mathbf{R} + 1/j\omega\mathbf{C}} \mathbf{V}_i = \frac{j\omega\mathbf{RC}}{1 + j\omega\mathbf{RC}} \mathbf{V}_i$$

$$\mathbf{V}_- = \frac{\mathbf{R}_i}{\mathbf{R}_i + \mathbf{R}_f} \mathbf{V}_o$$

Since $\mathbf{V}_+ = \mathbf{V}_-$,

$$\frac{\mathbf{R}_i}{\mathbf{R}_i + \mathbf{R}_f} \mathbf{V}_o = \frac{j\omega\mathbf{RC}}{1 + j\omega\mathbf{RC}} \mathbf{V}_i$$

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \left(1 + \frac{\mathbf{R}_f}{\mathbf{R}_i}\right) \left(\frac{j\omega\mathbf{RC}}{1 + j\omega\mathbf{RC}}\right)$$

It is evident that as $\omega \rightarrow \infty$, the gain is $1 + \frac{\mathbf{R}_f}{\mathbf{R}_i}$ and that the corner frequency is $\frac{1}{\mathbf{RC}}$.

Solution 14.66

(a) **Proof**

(b) When $\mathbf{R}_1\mathbf{R}_4 = \mathbf{R}_2\mathbf{R}_3$,

$$\mathbf{H}(s) = \frac{\mathbf{R}_4}{\mathbf{R}_3 + \mathbf{R}_4} \cdot \frac{s}{s + 1/\mathbf{R}_2\mathbf{C}}$$

(c) When $\mathbf{R}_3 \rightarrow \infty$,

$$\mathbf{H}(s) = \frac{-1/\mathbf{R}_1\mathbf{C}}{s + 1/\mathbf{R}_2\mathbf{C}}$$

Solution 14.67

$$\text{DC gain} = \frac{R_f}{R_i} = \frac{1}{4} \longrightarrow R_i = 4R_f$$

$$\text{Corner frequency} = \omega_c = \frac{1}{R_f C_f} = 2\pi(500) \text{ rad/s}$$

If we select $R_f = 20 \text{ k}\Omega$, then $R_i = 80 \text{ k}\Omega$ and

$$C = \frac{1}{(2\pi)(500)(20 \times 10^3)} = 15.915 \text{ nF}$$

Therefore, if $R_f = \mathbf{20 \text{ k}\Omega}$, then $R_i = \mathbf{80 \text{ k}\Omega}$ and $C = \mathbf{15.915 \text{ nF}}$

Solution 14.68

Design a problem to help other students to better understand the design of active highpass filters when specifying a high-frequency gain and a corner frequency.

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

Design an active highpass filter with a high-frequency gain of 5 and a corner frequency of 200 Hz.

Solution

$$\text{High frequency gain} = 5 = \frac{R_f}{R_i} \longrightarrow R_f = 5R_i$$

$$\text{Corner frequency} = \omega_c = \frac{1}{R_i C_i} = 2\pi(200) \text{ rad/s}$$

If we select $R_i = 20 \text{ k}\Omega$, then $R_f = 100 \text{ k}\Omega$ and

$$C = \frac{1}{(2\pi)(200)(20 \times 10^3)} = 39.8 \text{ nF}$$

Therefore, if $R_i = \mathbf{20 \text{ k}\Omega}$, then $R_f = \mathbf{100 \text{ k}\Omega}$ and $C = \mathbf{39.8 \text{ nF}}$

Solution 14.69

This is a highpass filter with $f_c = 2 \text{ kHz}$.

$$\omega_c = 2\pi f_c = \frac{1}{RC}$$
$$RC = \frac{1}{2\pi f_c} = \frac{1}{4\pi \times 10^3}$$

10^8 Hz may be regarded as high frequency. Hence the high-frequency gain is

$$\frac{-R_f}{R} = \frac{-10}{4} \quad \text{or} \quad R_f = 2.5R$$

If we let $R = \mathbf{10 \text{ k}\Omega}$, then $R_f = \mathbf{25 \text{ k}\Omega}$, and $C = \frac{1}{4000\pi \times 10^4} = \mathbf{7.96 \text{ nF}}$.

Solution 14.70

$$(a) \quad \mathbf{H}(s) = \frac{\mathbf{V}_o(s)}{\mathbf{V}_i(s)} = \frac{\mathbf{Y}_1 \mathbf{Y}_2}{\mathbf{Y}_1 \mathbf{Y}_2 + \mathbf{Y}_4 (\mathbf{Y}_1 + \mathbf{Y}_2 + \mathbf{Y}_3)}$$

where $\mathbf{Y}_1 = \frac{1}{\mathbf{R}_1} = \mathbf{G}_1$, $\mathbf{Y}_2 = \frac{1}{\mathbf{R}_2} = \mathbf{G}_2$, $\mathbf{Y}_3 = s\mathbf{C}_1$, $\mathbf{Y}_4 = s\mathbf{C}_2$.

$$\mathbf{H}(s) = \frac{\mathbf{G}_1 \mathbf{G}_2}{\mathbf{G}_1 \mathbf{G}_2 + s\mathbf{C}_2 (\mathbf{G}_1 + \mathbf{G}_2 + s\mathbf{C}_1)}$$

$$(b) \quad \mathbf{H}(0) = \frac{\mathbf{G}_1 \mathbf{G}_2}{\mathbf{G}_1 \mathbf{G}_2} = 1, \quad \mathbf{H}(\infty) = 0$$

showing that **this circuit is a lowpass filter.**

Solution 14.71

$R = 50\ \Omega$, $L = 40\ \text{mH}$, $C = 1\ \mu\text{F}$

$$L' = \frac{K_m}{K_f} L \longrightarrow 1 = \frac{K_m}{K_f} \cdot (40 \times 10^{-3})$$

$$25K_f = K_m \quad (1)$$

$$C' = \frac{C}{K_m K_f} \longrightarrow 1 = \frac{10^{-6}}{K_m K_f}$$

$$10^6 K_f = \frac{1}{K_m} \quad (2)$$

Substituting (1) into (2),

$$10^6 K_f = \frac{1}{25K_f}$$

$$K_f = 2 \times 10^{-4}$$

$$K_m = 25K_f = 5 \times 10^{-3}$$

Solution 14.72

Design a problem to help other students to better understand magnitude and frequency scaling.

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

What values of K_m and K_f will scale a 4-mH inductor and a 20- μ F capacitor to 1 H and 2 F respectively?

Solution

$$L'C' = \frac{LC}{K_f^2} \longrightarrow K_f^2 = \frac{LC}{L'C'}$$

$$K_f^2 = \frac{(4 \times 10^{-3})(20 \times 10^{-6})}{(1)(2)} = 4 \times 10^{-8}$$

$$K_f = 2 \times 10^{-4}$$

$$\frac{L'}{C'} = \frac{L}{C} K_m^2 \longrightarrow K_m^2 = \frac{L'}{C'} \cdot \frac{C}{L}$$

$$K_m^2 = \frac{(1)(20 \times 10^{-6})}{(2)(4 \times 10^{-3})} = 2.5 \times 10^{-3}$$

$$K_m = 5 \times 10^{-2}$$

Solution 14.73

$$R' = K_m R = (12)(800 \times 10^3) = \mathbf{9.6 \text{ M}\Omega}$$

$$L' = \frac{K_m}{K_f} L = \frac{800}{1000} (40 \times 10^{-6}) = \mathbf{32 \text{ }\mu\text{F}}$$

$$C' = \frac{C}{K_m K_f} = \frac{300 \times 10^{-9}}{(800)(1000)} = \mathbf{0.375 \text{ pF}}$$

Solution 14.74

$$\mathbf{R'_1 = K_m R_1 = 3 \times 100 = \underline{300 \Omega}}$$

$$\mathbf{R'_2 = K_m R_2 = 10 \times 100 = \underline{1 \text{ k}\Omega}}$$

$$\mathbf{L' = \frac{K_m}{K_f} L = \frac{10^2}{10^6} (2) = \underline{200 \mu\text{H}}}$$

$$\mathbf{C' = \frac{C}{K_m K_f} = \frac{1}{10^8} = \underline{1 \text{ nF}}}$$

Solution 14.75

$$\mathbf{R' = K_m R = 20 \times 10 = \underline{200 \, \Omega}}$$

$$\mathbf{L' = \frac{K_m}{K_f} L = \frac{10}{10^5} (4) = \underline{400 \, \mu\text{H}}}$$

$$\mathbf{C' = \frac{C}{K_m K_f} = \frac{1}{10 \times 10^5} = \underline{1 \, \mu\text{F}}}$$

Solution 14.76

$$R' = K_m R = 500 \times 5 \times 10^3 = \underline{25 \text{ M}\Omega}$$

$$L' = \frac{K_m}{K_f} L = \frac{500}{10^5} (10 \text{ mH}) = \underline{50 \text{ }\mu\text{H}}$$

$$C' = \frac{C}{K_m K_f} = \frac{20 \times 10^{-6}}{500 \times 10^5} = \underline{0.4 \text{ pF}}$$

Solution 14.77

L and C are needed before scaling.

$$B = \frac{R}{L} \longrightarrow L = \frac{R}{B} = \frac{10}{5} = 2 \text{ H}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \longrightarrow C = \frac{1}{\omega_0^2 L} = \frac{1}{(1600)(2)} = 312.5 \text{ } \mu\text{F}$$

$$(a) \quad L' = K_m L = (600)(2) = \mathbf{1.200 \text{ kH}}$$

$$C' = \frac{C}{K_m} = \frac{3.125 \times 10^{-4}}{600} = \mathbf{0.5208 \text{ } \mu\text{F}}$$

$$(b) \quad L' = \frac{L}{K_f} = \frac{2}{10^3} = \mathbf{2 \text{ mH}}$$

$$C' = \frac{C}{K_f} = \frac{3.125 \times 10^{-4}}{10^3} = \mathbf{312.5 \text{ nF}}$$

$$(c) \quad L' = \frac{K_m}{K_f} L = \frac{(400)(2)}{10^5} = \mathbf{8 \text{ mH}}$$

$$C' = \frac{C}{K_m K_f} = \frac{3.125 \times 10^{-4}}{(400)(10^5)} = \mathbf{7.81 \text{ pF}}$$


Solution 14.78

$$R' = K_m R = (1000)(1) = 1 \text{ k}\Omega$$

$$L' = \frac{K_m}{K_f} L = \frac{10^3}{10^4} (1) = 0.1 \text{ H}$$


$$C' = \frac{C}{K_m K_f} = \frac{1}{(10^3)(10^4)} = 0.1 \text{ }\mu\text{F}$$

The new circuit is shown below.

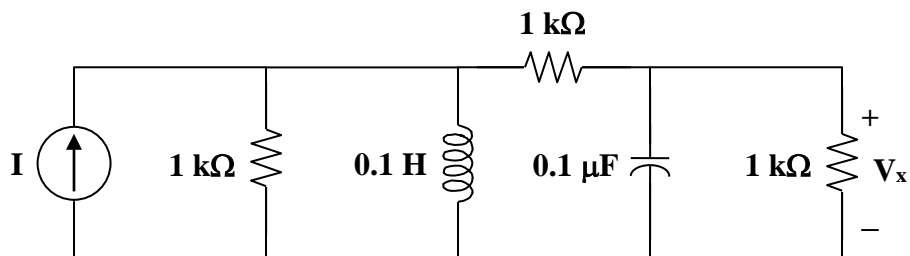

Solution 14.79

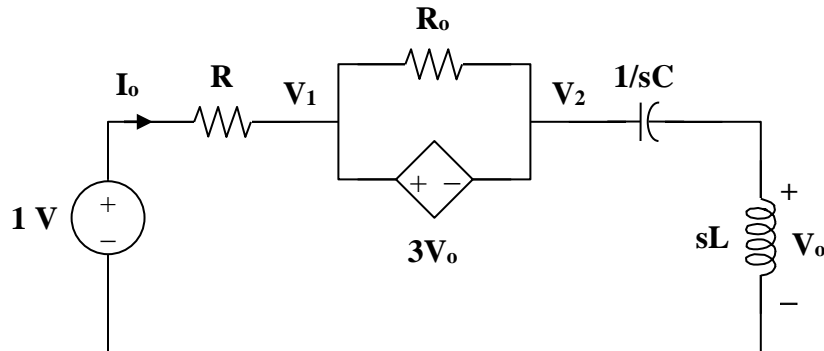- (a) Insert a 1-V source at the input terminals.



There is a supernode.

$$\frac{1 - V_1}{R} = \frac{V_2}{sL + 1/sC} \quad (1)$$

$$\text{But } V_1 = V_2 + 3V_o \longrightarrow V_2 = V_1 - 3V_o \quad (2)$$

$$\text{Also, } V_o = \frac{sL}{sL + 1/sC} V_2 \longrightarrow \frac{V_o}{sL} = \frac{V_2}{sL + 1/sC} \quad (3)$$

Combining (2) and (3)

$$\begin{aligned} V_2 &= V_1 - 3V_o = \frac{sL + 1/sC}{sL} V_o \\ V_o &= \frac{s^2 LC}{1 + 4s^2 LC} V_1 \end{aligned} \quad (4)$$

Substituting (3) and (4) into (1) gives

$$\begin{aligned} \frac{1 - V_1}{R} &= \frac{V_o}{sL} = \frac{sC}{1 + 4s^2 LC} V_1 \\ 1 &= V_1 + \frac{sRC}{1 + 4s^2 LC} V_1 = \frac{1 + 4s^2 LC + sRC}{1 + 4s^2 LC} V_1 \\ V_1 &= \frac{1 + 4s^2 LC}{1 + 4s^2 LC + sRC} \end{aligned}$$

$$I_o = \frac{1 - V_1}{R} = \frac{sRC}{R(1 + 4s^2 LC + sRC)}$$

$$Z_{in} = \frac{1}{I_o} = \frac{1 + sRC + 4s^2 LC}{sC}$$

$$\mathbf{Z_{in}} = 4sL + R + \frac{1}{sC} \quad (5)$$

When $R = 5$, $L = 2$, $C = 0.1$,

$$\mathbf{Z_{in}}(s) = \mathbf{8s + 5 + \frac{10}{s}}$$

At resonance,

$$\text{Im}(\mathbf{Z_{in}}) = 0 = 4\omega L - \frac{1}{\omega C}$$

$$\text{or } \omega_0 = \frac{1}{2\sqrt{LC}} = \frac{1}{2\sqrt{(0.1)(2)}} = \mathbf{1.118 \text{ rad/s}}$$

(b) After scaling,

$$R' \longrightarrow K_m R$$

$$4 \Omega \longrightarrow 40 \Omega$$

$$5 \Omega \longrightarrow 50 \Omega$$

$$L' = \frac{K_m}{K_f} L = \frac{10}{100} (2) = 0.2 \text{ H}$$

$$C' = \frac{C}{K_m K_f} = \frac{0.1}{(10)(100)} = 10^{-4}$$

From (5),

$$\mathbf{Z_{in}}(s) = \mathbf{0.8s + 50 + \frac{10^4}{s}}$$

$$\omega_0 = \frac{1}{2\sqrt{LC}} = \frac{1}{2\sqrt{(0.2)(10^{-4})}} = \mathbf{111.8 \text{ rad/s}}$$


Solution 14.80

(a) $R' = K_m R = (200)(2) = 400 \Omega$


$$L' = \frac{K_m L}{K_f} = \frac{(200)(1)}{10^4} = 20 \text{ mH}$$

$$C' = \frac{C}{K_m K_f} = \frac{0.5}{(200)(10^4)} = 0.25 \mu\text{F}$$

The new circuit is shown below.

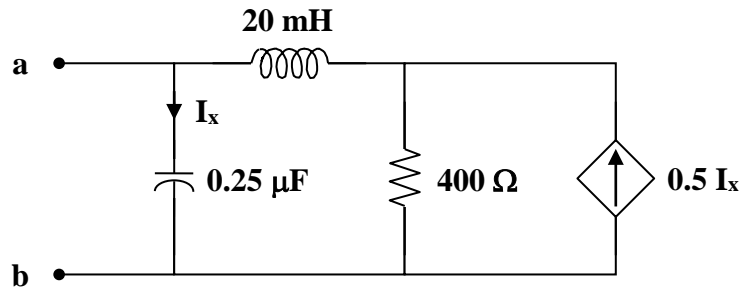

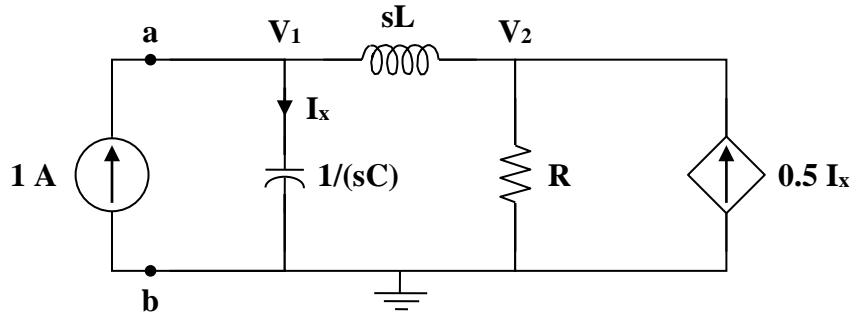(b) Insert a 1-A source at the terminals a-b.



At node 1,

$$1 = sC V_1 + \frac{V_1 - V_2}{sL} \quad (1)$$

At node 2,

$$\frac{V_1 - V_2}{sL} + 0.5 I_x = \frac{V_2}{R}$$

But, $I_x = sC V_1$.

$$\frac{V_1 - V_2}{sL} + 0.5 sC V_1 = \frac{V_2}{R} \quad (2)$$

Solving (1) and (2),

$$\mathbf{V}_1 = \frac{s\mathbf{L} + \mathbf{R}}{s^2\mathbf{LC} + 0.5s\mathbf{CR} + 1}$$

$$\mathbf{Z}_{\text{Th}} = \frac{\mathbf{V}_1}{1} = \frac{s\mathbf{L} + \mathbf{R}}{s^2\mathbf{LC} + 0.5s\mathbf{CR} + 1}$$

At $\omega = 10^4$,

$$\mathbf{Z}_{\text{Th}} = \frac{(j10^4)(20 \times 10^{-3}) + 400}{(j10^4)^2(20 \times 10^{-3})(0.25 \times 10^{-6}) + 0.5(j10^4)(0.25 \times 10^{-6})(400) + 1}$$

$$\mathbf{Z}_{\text{Th}} = \frac{400 + j200}{0.5 + j0.5} = 600 - j200$$

$$\mathbf{Z}_{\text{Th}} = \mathbf{632.5} \angle -18.435^\circ \text{ ohms}$$

Solution 14.81

(a)

$$\frac{1}{Z} = G + j\omega C + \frac{1}{R + j\omega L} = \frac{(G + j\omega C)(R + j\omega L) + 1}{R + j\omega L}$$

$$\text{which leads to } Z = \frac{j\omega L + R}{-\omega^2 LC + j\omega(RC + LG) + GR + 1}$$

$$Z(\omega) = \frac{j\frac{\omega}{C} + \frac{R}{LC}}{-\omega^2 + j\omega\left(\frac{R}{L} + \frac{G}{C}\right) + \frac{GR + 1}{LC}} \quad (1)$$

We compare this with the given impedance:

$$Z(\omega) = \frac{1000(j\omega + 1)}{-\omega^2 + 2j\omega + 1 + 2500} \quad (2)$$

Comparing (1) and (2) shows that

$$\frac{1}{C} = 1000 \quad \longrightarrow \quad C = 1 \text{ mF}, \quad R/L = 1 \quad \longrightarrow \quad R = L$$

$$\frac{R}{L} + \frac{G}{C} = 2 \quad \longrightarrow \quad G = C = 1 \text{ mS}$$

$$2501 = \frac{GR + 1}{LC} = \frac{10^{-3}R + 1}{10^{-3}R} \quad \longrightarrow \quad R = 0.4 = L$$

Thus,

$$R = \mathbf{0.4\Omega}, L = \mathbf{0.4 \text{ H}}, C = \mathbf{1 \text{ mF}}, G = \mathbf{1 \text{ mS}}$$

(b) By frequency-scaling, $K_f = 1000$.

$$R' = \mathbf{0.4 \Omega}, G' = \mathbf{1 \text{ mS}}$$

$$L' = \frac{L}{K_f} = \frac{0.4}{10^3} = \mathbf{0.4 \text{ mH}}, \quad C' = \frac{C}{K_f} = \frac{10^{-3}}{10^{-3}} = \mathbf{1 \mu F}$$

Solution 14.82

$$C' = \frac{C}{K_m K_f}$$

$$K_f = \frac{\omega'_c}{\omega} = \frac{200}{1} = 200$$

$$K_m = \frac{C}{C'} \cdot \frac{1}{K_f} = \frac{1}{10^{-6}} \cdot \frac{1}{200} = 5000$$

$$R' = K_m R = \mathbf{5 \text{ k}\Omega}, \quad \text{thus,} \quad R'_i = 2R_i = \mathbf{10 \text{ k}\Omega}$$

Solution 14.83

$$1\mu\text{F} \longrightarrow C' = \frac{1}{K_m K_f} C = \frac{10^{-6}}{100 \times 10^5} = \underline{0.1 \text{ pF}}$$



$$5\mu\text{F} \longrightarrow C' = \underline{0.5 \text{ pF}}$$


$$10 \text{ k}\Omega \longrightarrow R' = K_m R = 100 \times 10 \text{ k}\Omega = \underline{1 \text{ M}\Omega}$$

$$20 \text{ k}\Omega \longrightarrow R' = \underline{2 \text{ M}\Omega}$$

Solution 14.84



The schematic is shown below. A voltage marker is inserted to measure v_o . In the AC sweep box, we select Total Points = 50, Start Frequency = 1, and End Frequency = 1000. After saving and simulation, we obtain the magnitude and phase plots in the probe menu as shown below.

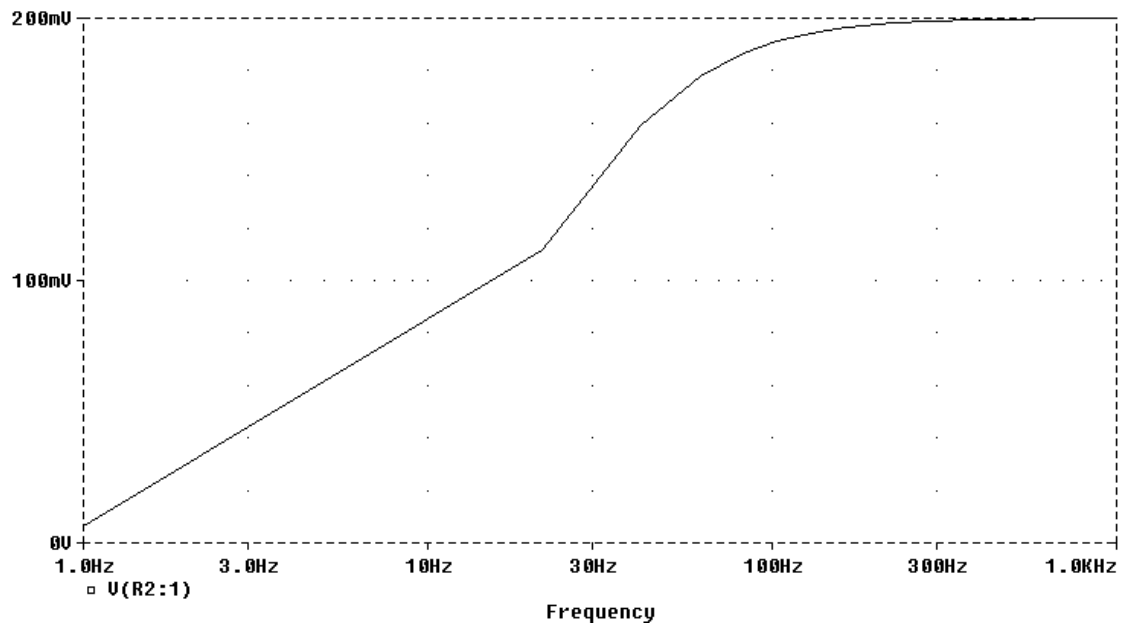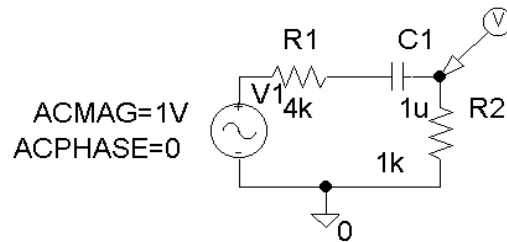


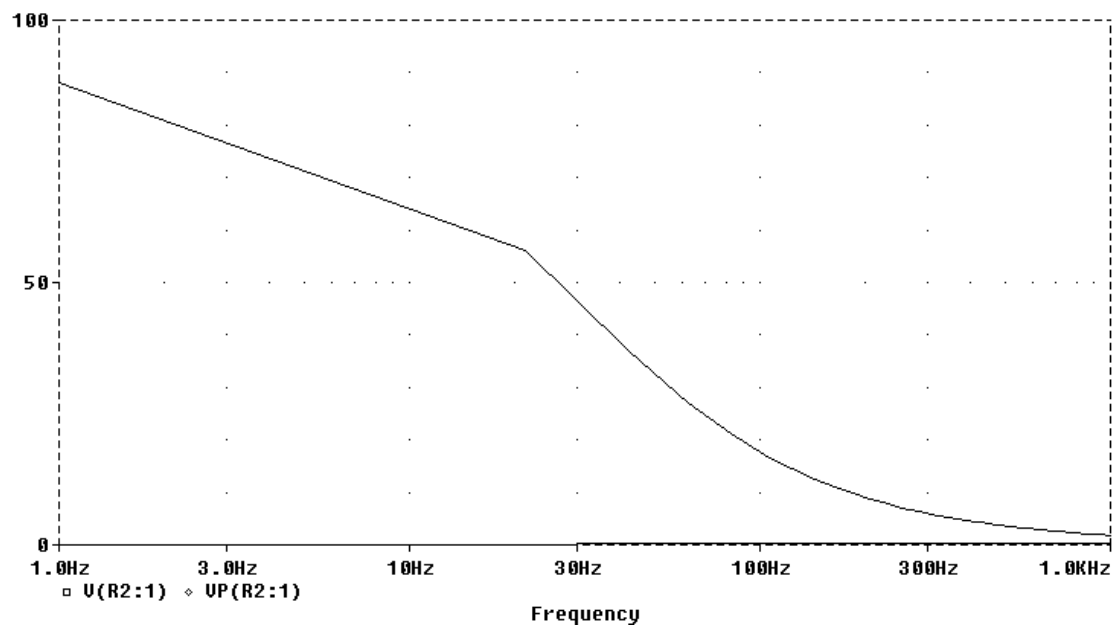

Solution 14.85

We let $I_s = 1\angle 0^\circ$ A so that $V_o / I_s = V_o$. The schematic is shown below. The circuit is simulated for $100 < f < 10$ kHz.

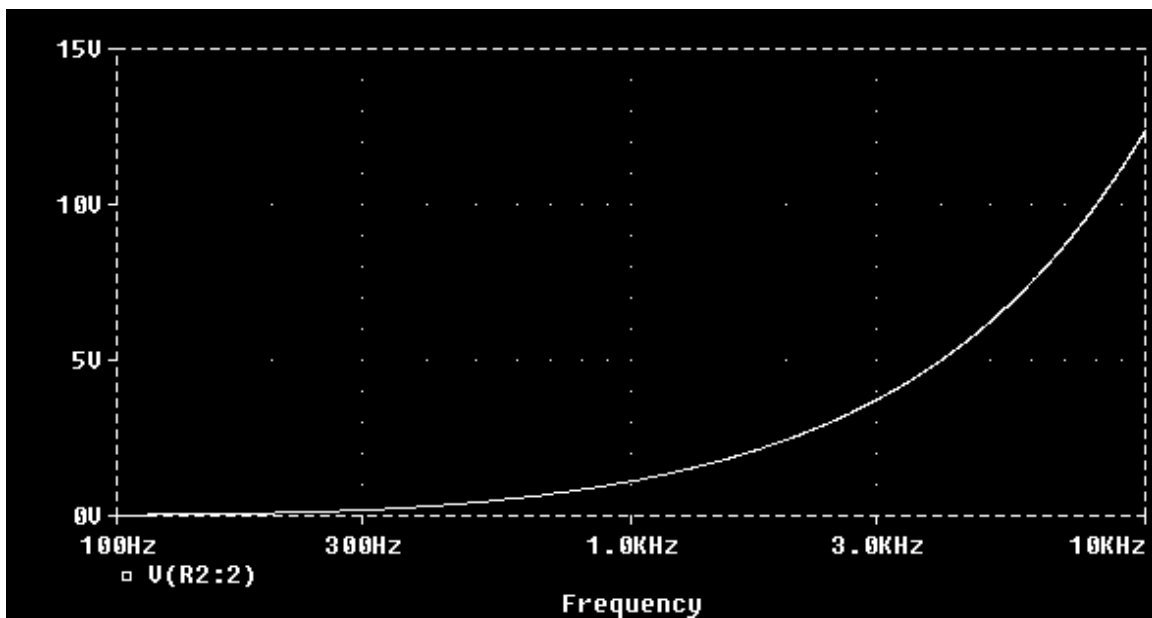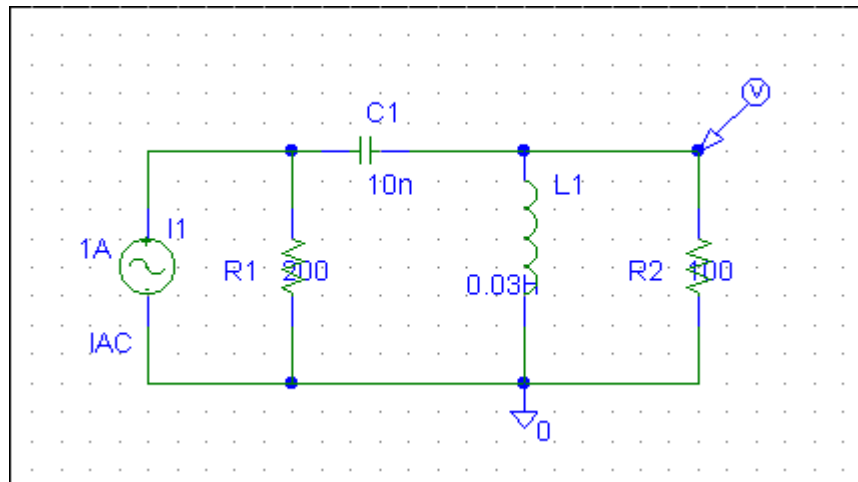

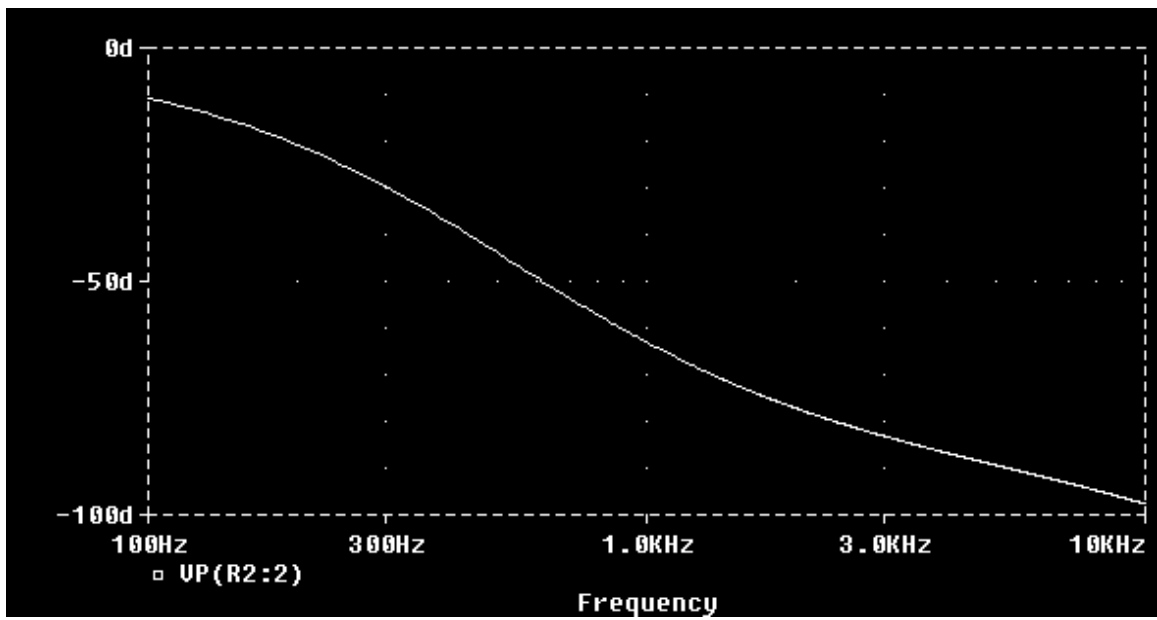

Solution 14.86

Using Fig. 14.103, design a problem to help other students to better understand how to use PSpice to obtain the frequency response (magnitude and phase of I) in electrical circuits.

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

Use *PSpice* to provide the frequency response (magnitude and phase of i) of the circuit in Fig. 14.103. Use linear frequency sweep from 1 to 10,000 Hz.



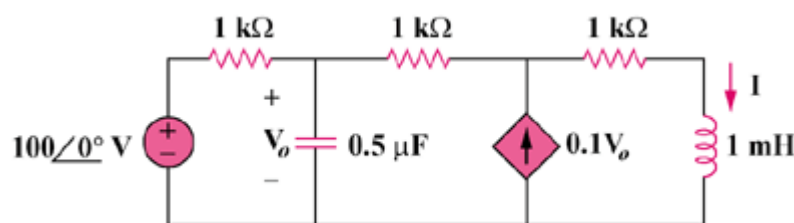
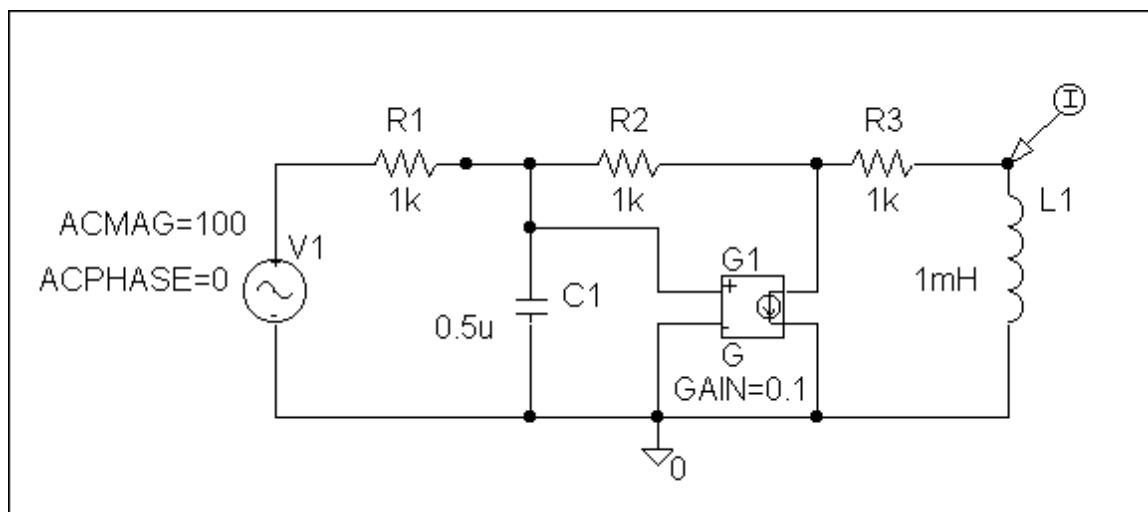


Figure 14.103

Solution



The schematic is shown below. A current marker is inserted to measure I . We set Total Points = 101, start Frequency = 1, and End Frequency = 10 kHz in the AC sweep box. After simulation, the magnitude and phase plots are obtained in the Probe menu as shown below.

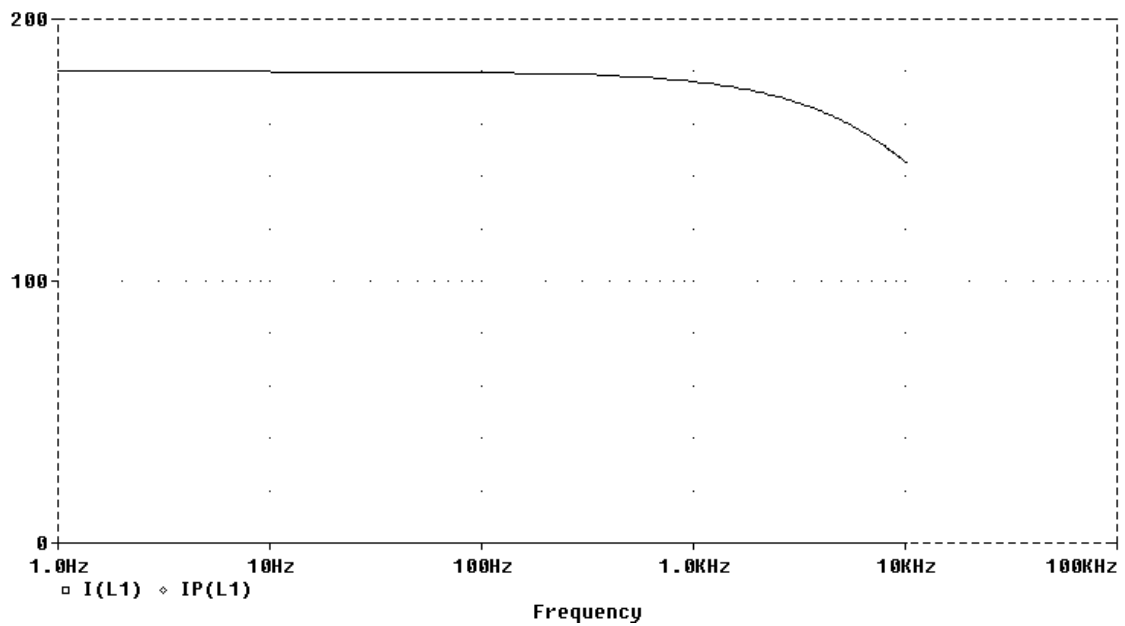

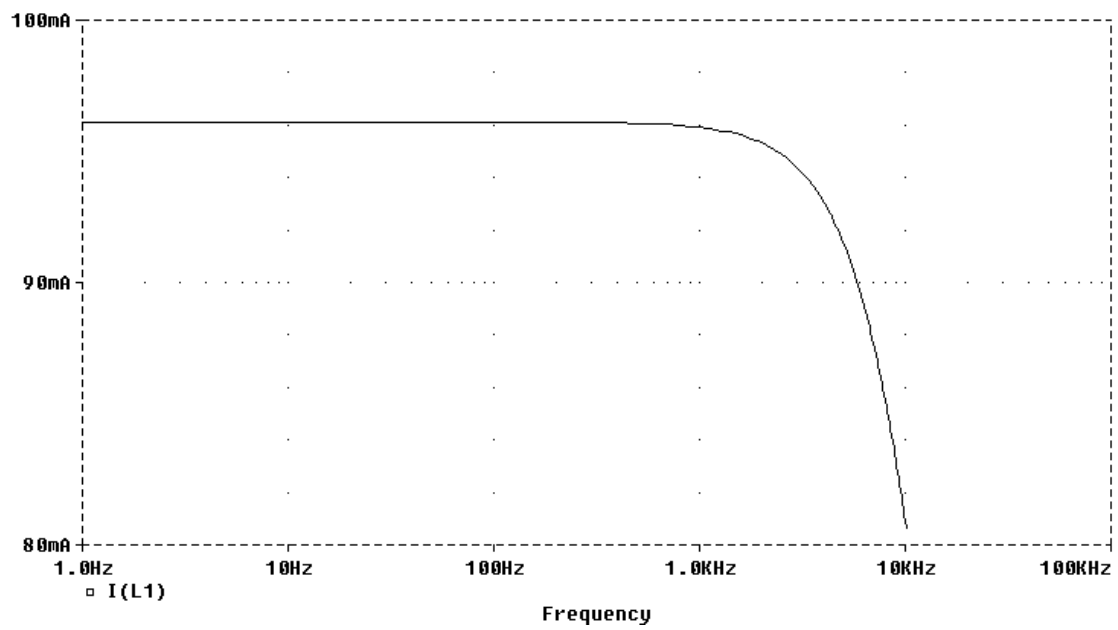



Solution 14.87


The schematic is shown below. In the AC Sweep box, we set Total Points = 50, Start Frequency = 1, and End Frequency = 100. After simulation, we obtain the magnitude response as shown below. It is evident from the response that the circuit represents a high-pass filter.

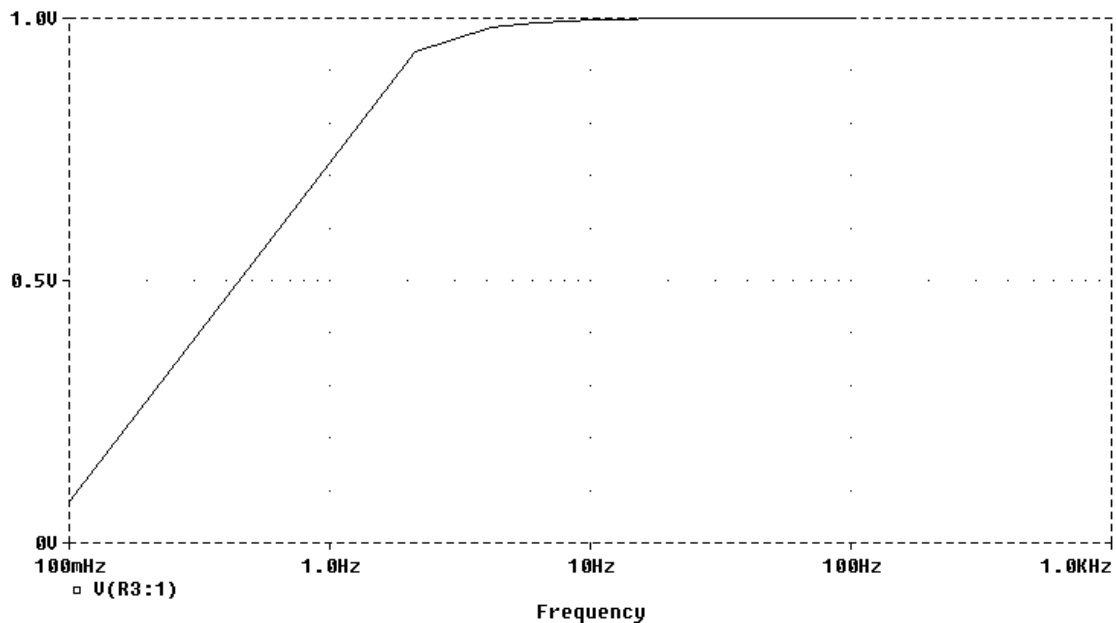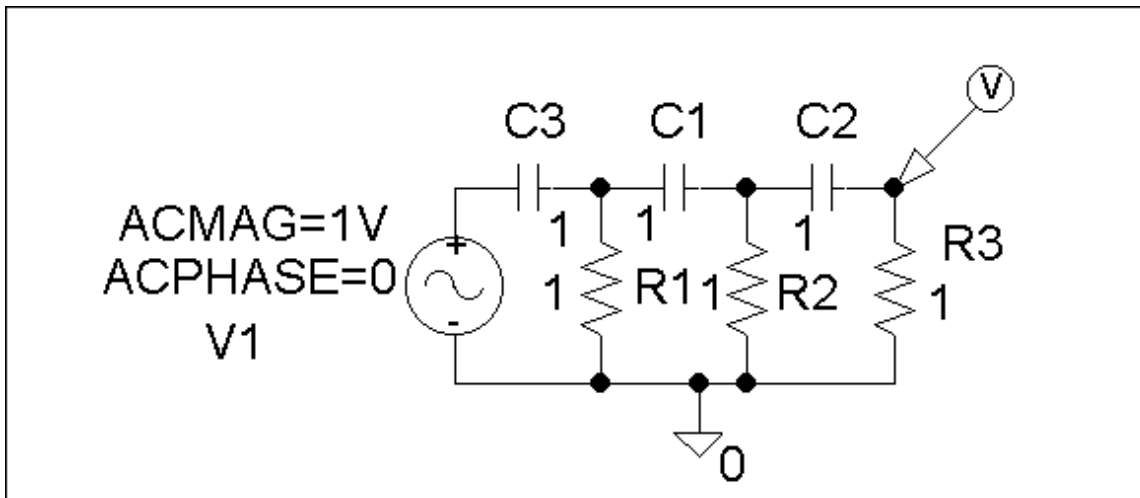

Solution 14.88



The schematic is shown below. We insert a voltage marker to measure V_o . In the AC Sweep box, we set Total Points = 101, Start Frequency = 1, and End Frequency = 100. After simulation, we obtain the magnitude and phase plots of V_o as shown below.

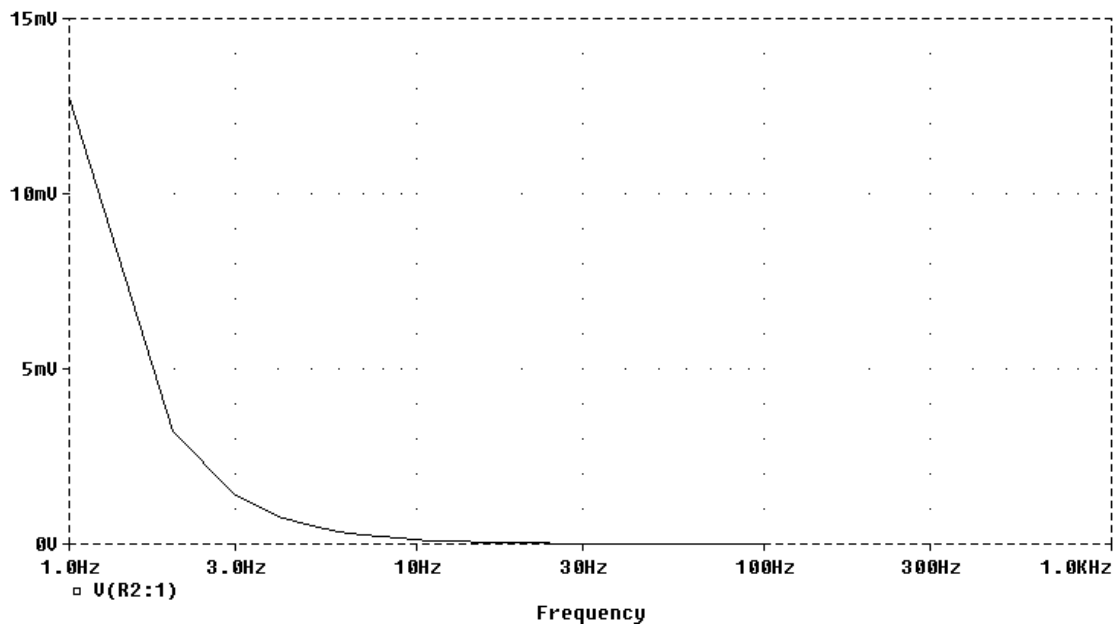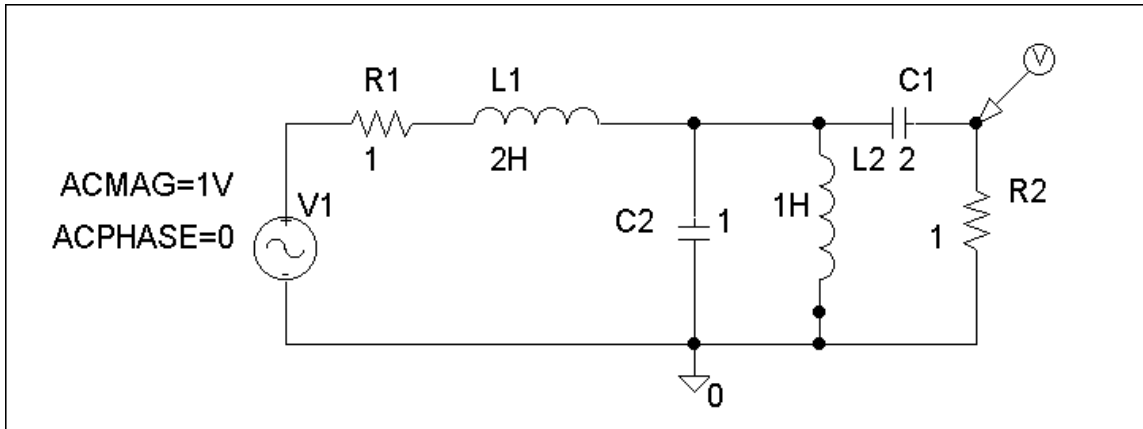

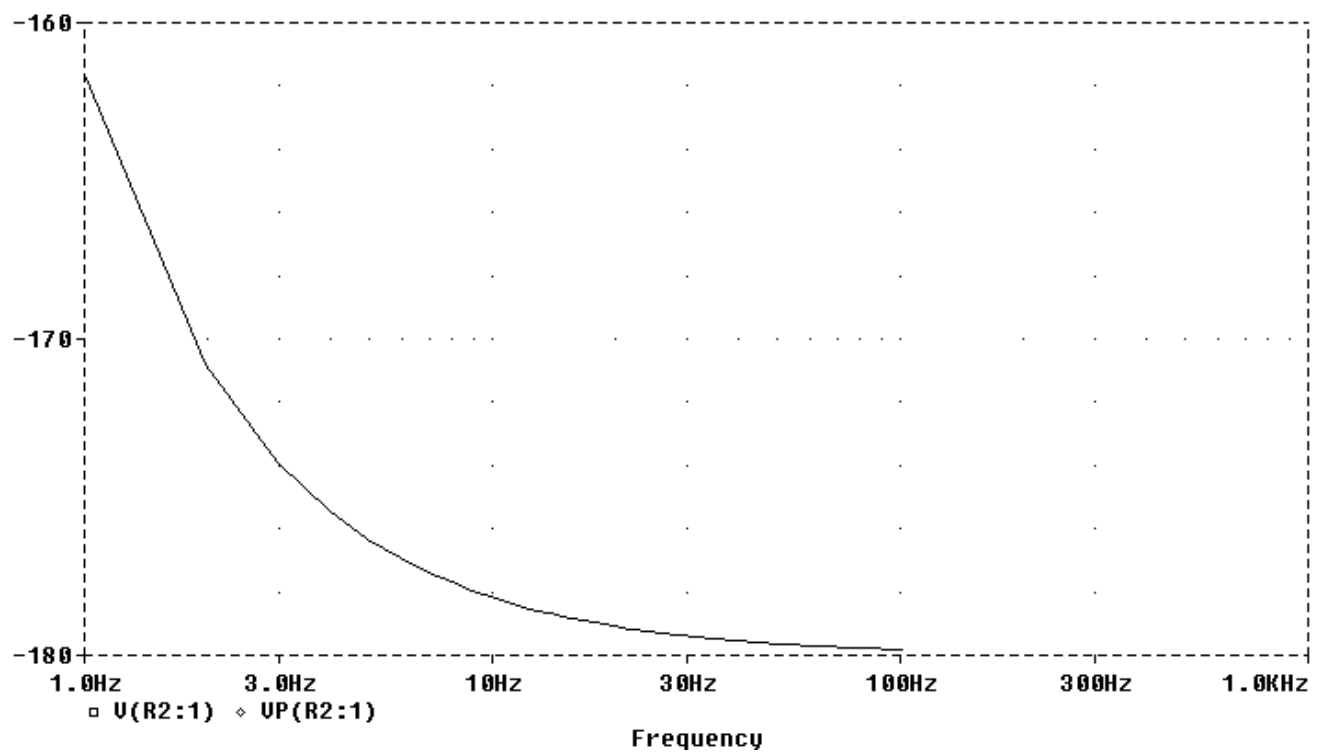



Solution 14.89

The schematic is shown below. In the AC Sweep box, we type Total Points = 101, Start Frequency = 100, and End Frequency = 1 k. After simulation, the magnitude plot of the response V_o is obtained as shown below.

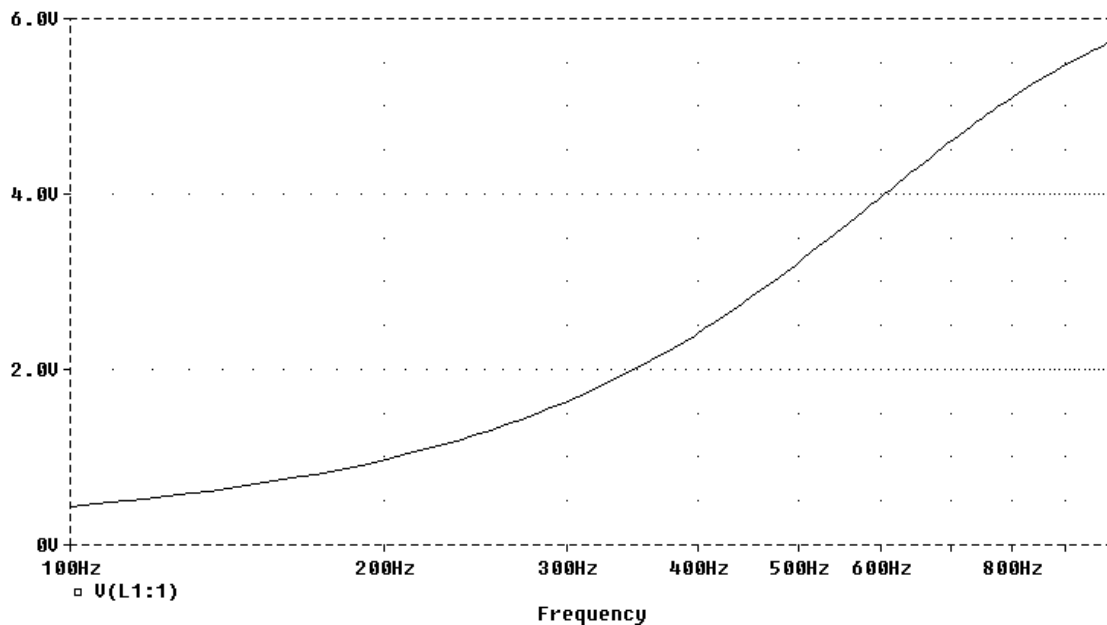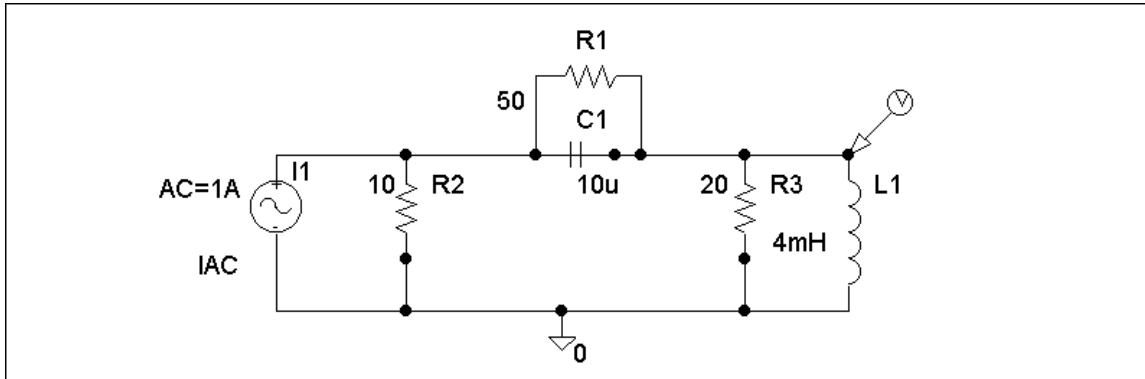



Solution 14.90

The schematic is shown below. In the AC Sweep box, we set Total Points = 1001, Start Frequency = 1, and End Frequency = 100k. After simulation, we obtain the magnitude plot of the response as shown below. The response shows that the circuit is a high-pass filter.

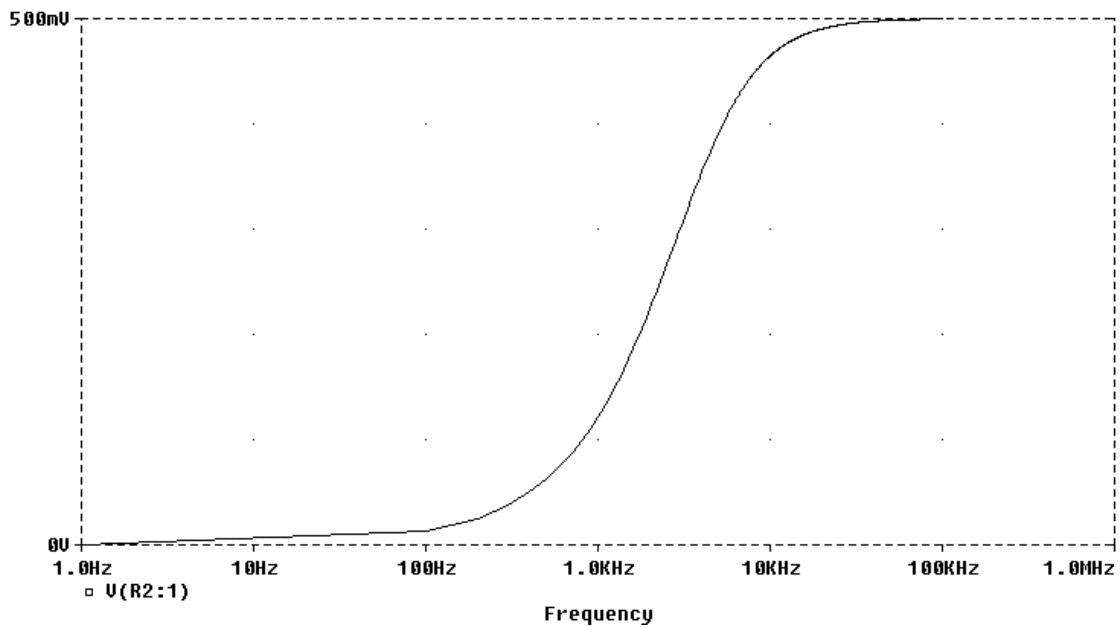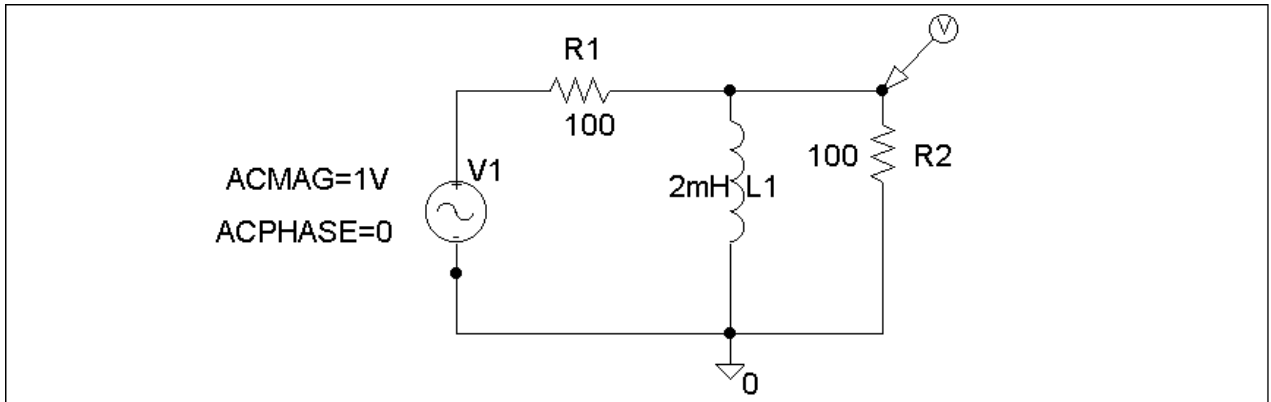



Solution 14.91

The schematic is shown below. In the AC Sweep box, we select Total Points = 101, Start Frequency = 10, and End Frequency = 10 k. After simulation, the magnitude plot of the frequency response is obtained. From the plot, we obtain the resonant frequency f_o is approximately equal to **800 Hz** so that $\omega_o = 2\pi f_o = 5026 \text{ rad/s}$.

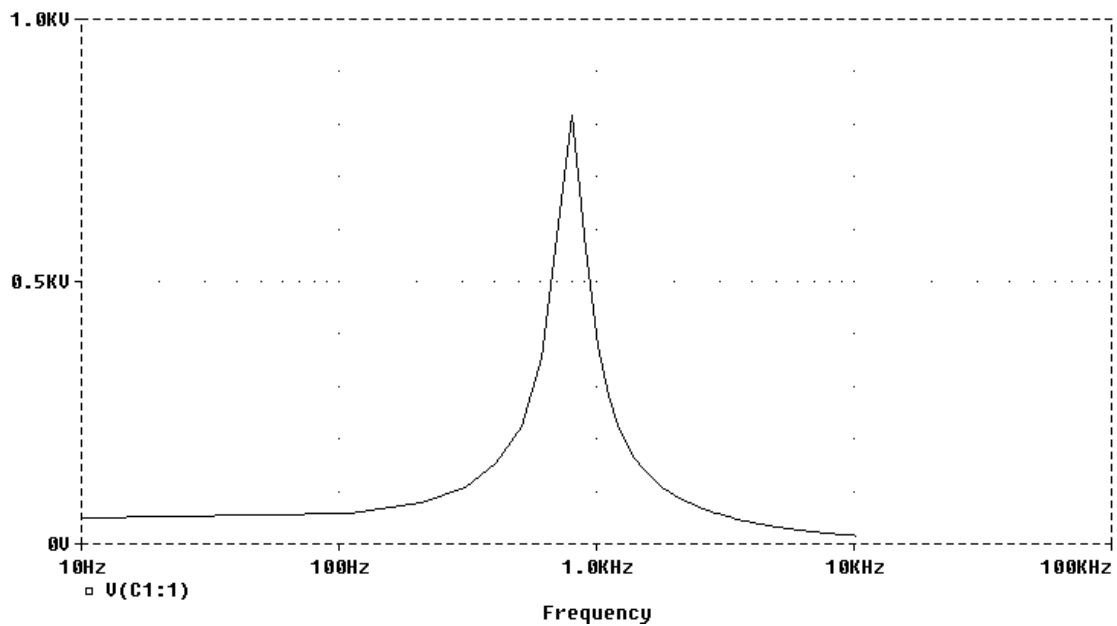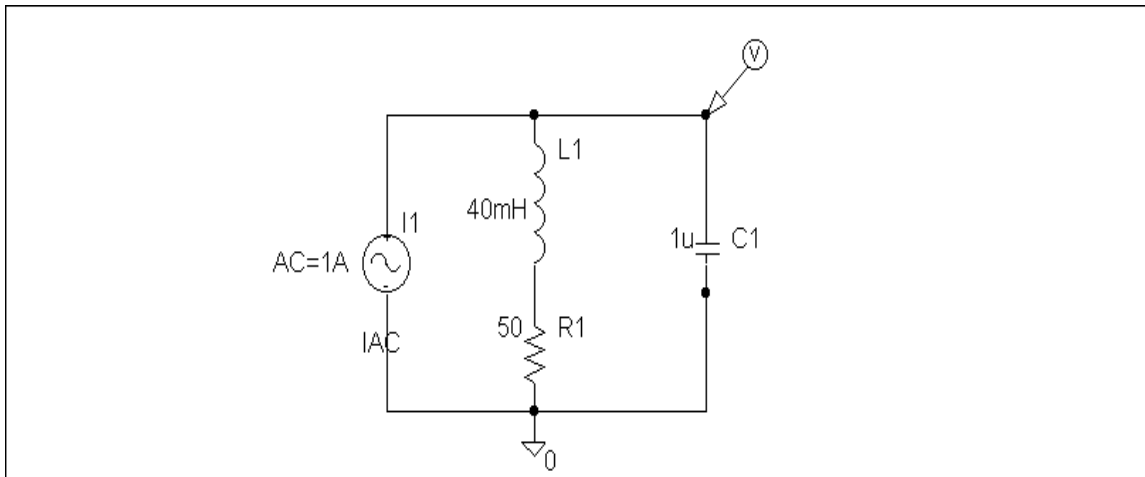


Solution 14.92

The schematic is shown below. We type Total Points = 101, Start Frequency = 1, and End Frequency = 100 in the AC Sweep box. After simulating the circuit, the magnitude plot of the frequency response is shown below.

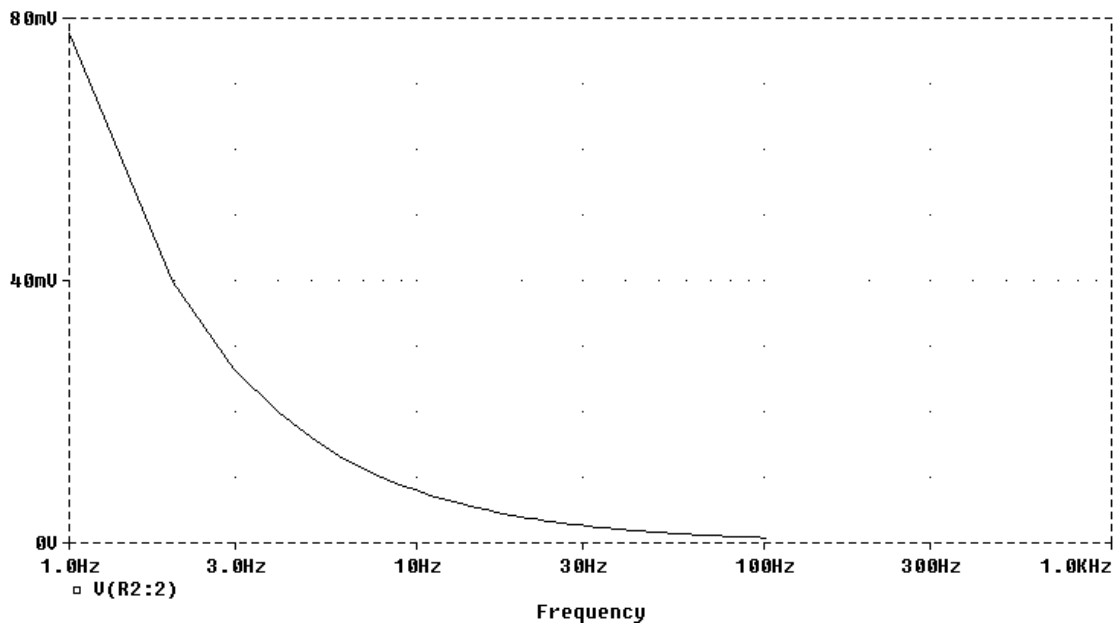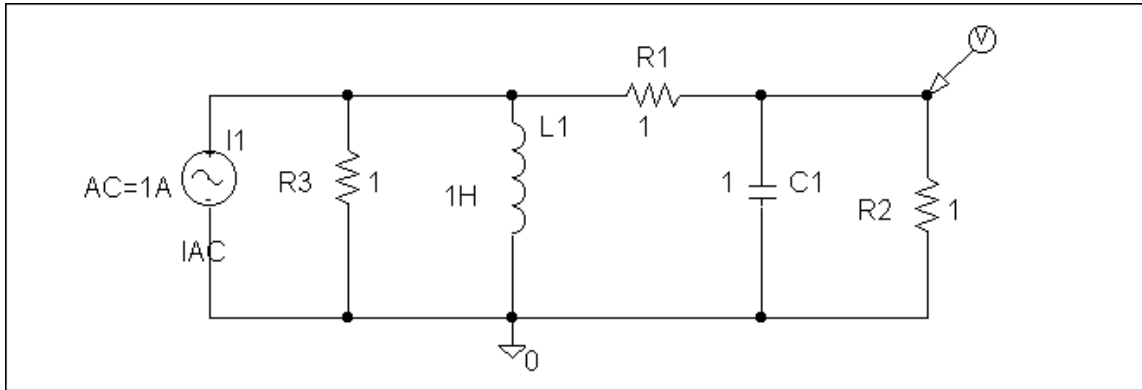

Solution 14.93

Consider the circuit as shown below.

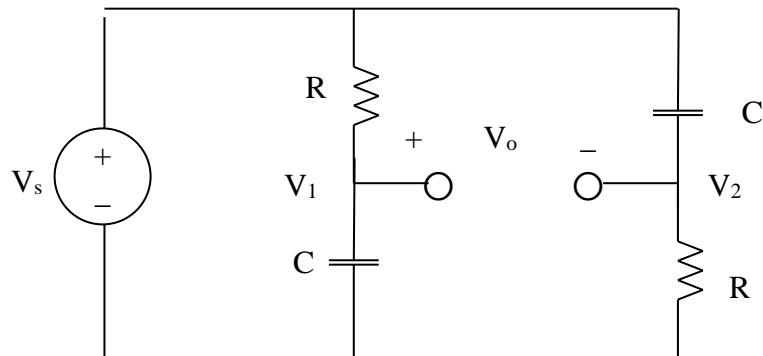

$$V_1 = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_s = \frac{V}{1 + sRC}$$

$$V_2 = \frac{R}{R + sC} V_s = \frac{sRC}{1 + sRC} V_s$$

$$V_o = V_1 - V_2 = \frac{1 - sRC}{1 + sRC} V_s$$

Hence,

$$H(s) = \frac{V_o}{V_s} = \frac{1 - sRC}{1 + sRC}$$

Solution 14.94

$$\omega_c = \frac{1}{RC}$$

We make R and C as small as possible. To achieve this, we connect 1.8 k Ω and 3.3 k Ω in parallel so that

$$R = \frac{1.8 \times 3.3}{1.8 + 3.3} = 1.164 \text{ k}\Omega$$

We place the 10-pF and 30-pF capacitors in series so that

$$C = (10 \times 30) / 40 = 7.5 \text{ pF}$$

Hence,

$$\omega_c = \frac{1}{RC} = \frac{1}{1.164 \times 10^3 \times 7.5 \times 10^{-12}} = \underline{114.55 \times 10^6 \text{ rad/s}}$$

Solution 14.95

$$(a) \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

When $C = 360 \text{ pF}$,

$$f_0 = \frac{1}{2\pi\sqrt{(240 \times 10^{-6})(360 \times 10^{-12})}} = 0.541 \text{ MHz}$$

When $C = 40 \text{ pF}$,

$$f_0 = \frac{1}{2\pi\sqrt{(240 \times 10^{-6})(40 \times 10^{-12})}} = 1.624 \text{ MHz}$$

Therefore, the frequency range is

$$\mathbf{0.541 \text{ MHz} < f_0 < 1.624 \text{ MHz}}$$

$$(b) \quad Q = \frac{2\pi fL}{R}$$


At $f_0 = 0.541 \text{ MHz}$,

$$Q = \frac{(2\pi)(0.541 \times 10^6)(240 \times 10^{-6})}{12} = \mathbf{67.98}$$

At $f_0 = 1.624 \text{ MHz}$,

$$Q = \frac{(2\pi)(1.624 \times 10^6)(240 \times 10^{-6})}{12} = \mathbf{204.1}$$

Solution 14.96

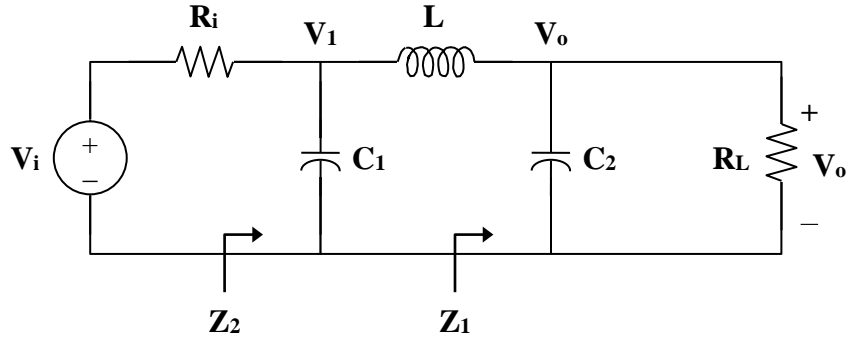

$$\mathbf{Z}_1 = \mathbf{R}_L \parallel \frac{1}{s\mathbf{C}_2} = \frac{\mathbf{R}_L}{1 + s\mathbf{R}_L\mathbf{C}_2}$$

$$\mathbf{Z}_2 = \frac{1}{s\mathbf{C}_1} \parallel (s\mathbf{L} + \mathbf{Z}_1) = \frac{1}{s\mathbf{C}_1} \parallel \left(\frac{s\mathbf{L} + \mathbf{R}_L + s^2\mathbf{R}_L\mathbf{C}_2\mathbf{L}}{1 + s\mathbf{R}_L\mathbf{C}_2} \right)$$

$$\mathbf{Z}_2 = \frac{\frac{1}{s\mathbf{C}_1} \cdot \frac{s\mathbf{L} + \mathbf{R}_L + s^2\mathbf{R}_L\mathbf{C}_2\mathbf{L}}{1 + s\mathbf{R}_L\mathbf{C}_2}}{\frac{1}{s\mathbf{C}_1} + \frac{s\mathbf{L} + \mathbf{R}_L + s^2\mathbf{R}_L\mathbf{C}_2\mathbf{L}}{1 + s\mathbf{R}_L\mathbf{C}_2}}$$

$$\mathbf{Z}_2 = \frac{s\mathbf{L} + \mathbf{R}_L + s^2\mathbf{R}_L\mathbf{C}_2\mathbf{L}}{1 + s\mathbf{R}_L\mathbf{C}_2 + s^2\mathbf{L}\mathbf{C}_1 + s\mathbf{R}_L\mathbf{C}_1 + s^3\mathbf{R}_L\mathbf{C}_1\mathbf{C}_2}$$

$$\mathbf{V}_1 = \frac{\mathbf{Z}_2}{\mathbf{Z}_2 + \mathbf{R}_i} \mathbf{V}_i$$

$$\mathbf{V}_o = \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + s\mathbf{L}} \mathbf{V}_1 = \frac{\mathbf{Z}_2}{\mathbf{Z}_2 + \mathbf{R}_i} \cdot \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + s\mathbf{L}} \mathbf{V}_i$$

$$\frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{\mathbf{Z}_2}{\mathbf{Z}_2 + \mathbf{R}_i} \cdot \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + s\mathbf{L}}$$

where

$$\frac{\mathbf{Z}_2}{\mathbf{Z}_2 + \mathbf{R}_i} =$$

$$\frac{s\mathbf{L} + \mathbf{R}_L + s^2\mathbf{R}_L\mathbf{C}_2\mathbf{L}}{s\mathbf{L} + \mathbf{R}_L + s^2\mathbf{R}_L\mathbf{C}_2\mathbf{L} + \mathbf{R}_i + s\mathbf{R}_i\mathbf{R}_L\mathbf{C}_2 + s^2\mathbf{R}_i\mathbf{L}\mathbf{C}_1 + s\mathbf{R}_i\mathbf{R}_L\mathbf{C}_1 + s^3\mathbf{R}_i\mathbf{R}_L\mathbf{C}_1\mathbf{C}_2}$$


and $\frac{\mathbf{Z}_1}{\mathbf{Z}_1 + s\mathbf{L}} = \frac{\mathbf{R}_L}{\mathbf{R}_L + s\mathbf{L} + s^2\mathbf{R}_L\mathbf{C}_2}$

Therefore,

$$\frac{V_o}{V_i} = \frac{R_L (sL + R_L + s^2 R_L L C_2)}{(sL + R_L + s^2 R_L L C_2 + R_i + s R_i R_L C_2 + s^2 R_i L C_1 + s R_i R_L C_1 + s^3 R_i R_L L C_1 C_2)(R_L + sL + s^2 R_L L C_2)}$$

where $s = j\omega$.

Solution 14.97

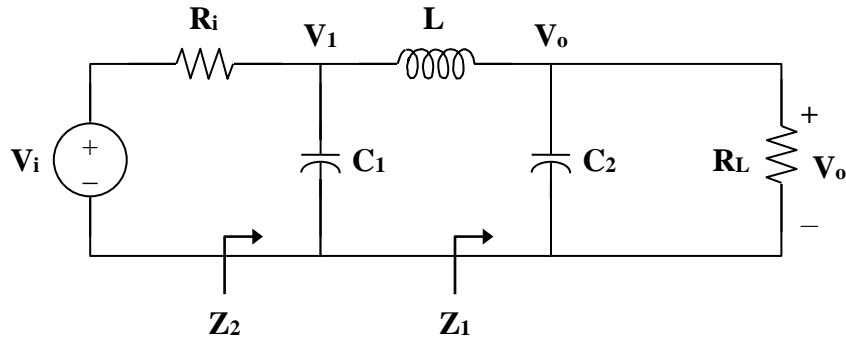

$$\mathbf{Z} = s\mathbf{L} \parallel \left(\mathbf{R}_L + \frac{1}{s\mathbf{C}_2} \right) = \frac{s\mathbf{L}(\mathbf{R}_L + 1/s\mathbf{C}_2)}{\mathbf{R}_L + s\mathbf{L} + 1/s\mathbf{C}_2}, \quad s = j\omega$$

$$\mathbf{V}_1 = \frac{\mathbf{Z}}{\mathbf{Z} + \mathbf{R}_i + 1/s\mathbf{C}_1} \mathbf{V}_i$$

$$\mathbf{V}_o = \frac{\mathbf{R}_L}{\mathbf{R}_L + 1/s\mathbf{C}_2} \mathbf{V}_1 = \frac{\mathbf{R}_L}{\mathbf{R}_L + 1/s\mathbf{C}_2} \cdot \frac{\mathbf{Z}}{\mathbf{Z} + \mathbf{R}_i + 1/s\mathbf{C}_1} \mathbf{V}_i$$

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{\mathbf{R}_L}{\mathbf{R}_L + 1/s\mathbf{C}_2} \cdot \frac{s\mathbf{L}(\mathbf{R}_L + 1/s\mathbf{C}_2)}{s\mathbf{L}(\mathbf{R}_L + 1/s\mathbf{C}_2) + (\mathbf{R}_i + 1/s\mathbf{C}_1)(\mathbf{R}_L + s\mathbf{L} + 1/s\mathbf{C}_2)}$$

$$\mathbf{H}(\omega) = \frac{s^3 \mathbf{L} \mathbf{R}_L \mathbf{C}_1 \mathbf{C}_2}{(s\mathbf{R}_i \mathbf{C}_1 + 1)(s^2 \mathbf{L} \mathbf{C}_2 + s\mathbf{R}_L \mathbf{C}_2 + 1) + s^2 \mathbf{L} \mathbf{C}_1 (s\mathbf{R}_L \mathbf{C}_2 + 1)}$$

where $s = j\omega$.

Solution 14.98

$$B = \omega_2 - \omega_1 = 2\pi (f_2 - f_1) = 2\pi (454 - 432) = 44\pi$$

$$\omega_0 = 2\pi f_0 = QB = (20)(44\pi)$$

$$f_0 = \frac{(20)(44\pi)}{2\pi} = (20)(22) = \mathbf{440 \text{ Hz}}$$

Solution 14.99

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi f X_c} = \frac{1}{(2\pi)(2 \times 10^6)(5 \times 10^3)} = \frac{10^{-9}}{20\pi}$$

$$X_L = \omega L = 2\pi f L$$

$$L = \frac{X_L}{2\pi f} = \frac{300}{(2\pi)(2 \times 10^6)} = \frac{3 \times 10^{-4}}{4\pi}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{\frac{3 \times 10^{-4}}{4\pi} \cdot \frac{10^{-9}}{20\pi}}} = \mathbf{8.165 \text{ MHz}}$$

$$B = \frac{R}{L} = (100) \left(\frac{4\pi}{3 \times 10^{-4}} \right) = \mathbf{4.188 \times 10^6 \text{ rad/s}}$$

Solution 14.100

$$\omega_c = 2\pi f_c = \frac{1}{RC}$$

$$R = \frac{1}{2\pi f_c C} = \frac{1}{(2\pi)(20 \times 10^3)(0.5 \times 10^{-6})} = \mathbf{15.91 \, \Omega}$$

Solution 14.101

$$\omega_c = 2\pi f_c = \frac{1}{RC}$$

$$R = \frac{1}{2\pi f_c C} = \frac{1}{(2\pi)(15)(10 \times 10^{-6})} = \mathbf{1.061 \text{ k}\Omega}$$

Solution 14.102

- (a) When $R_s = 0$ and $R_L = \infty$, we have a low-pass filter.

$$\omega_c = 2\pi f_c = \frac{1}{RC}$$

$$f_c = \frac{1}{2\pi RC} = \frac{1}{(2\pi)(4 \times 10^3)(40 \times 10^{-9})} = \mathbf{994.7 \text{ Hz}}$$

- (b) We obtain R_{Th} across the capacitor.

$$R_{Th} = R_L \parallel (R + R_s)$$

$$R_{Th} = 5 \parallel (4 + 1) = 2.5 \text{ k}\Omega$$

$$f_c = \frac{1}{2\pi R_{Th} C} = \frac{1}{(2\pi)(2.5 \times 10^3)(40 \times 10^{-9})}$$

$$f_c = \mathbf{1.59 \text{ kHz}}$$

Solution 14.103

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{\mathbf{R}_2}{\mathbf{R}_2 + \mathbf{R}_1 \parallel 1/j\omega\mathbf{C}}, \quad s = j\omega$$

$$\mathbf{H}(s) = \frac{\mathbf{R}_2}{\mathbf{R}_2 + \frac{\mathbf{R}_1(1/s\mathbf{C})}{\mathbf{R}_1 + 1/s\mathbf{C}}} = \frac{\mathbf{R}_2(\mathbf{R}_1 + 1/s\mathbf{C})}{\mathbf{R}_1\mathbf{R}_2 + (\mathbf{R}_1 + \mathbf{R}_2)(1/s\mathbf{C})}$$

$$\mathbf{H}(s) = \frac{\mathbf{R}_2(1 + s\mathbf{C}\mathbf{R}_1)}{\mathbf{R}_1 + \mathbf{R}_2 + s\mathbf{C}\mathbf{R}_1\mathbf{R}_2}$$

Solution 14.104

The schematic is shown below. We click Analysis/Setup/AC Sweep and enter Total Points = 1001, Start Frequency = 100, and End Frequency = 100 k. After simulation, we obtain the magnitude plot of the response as shown.

