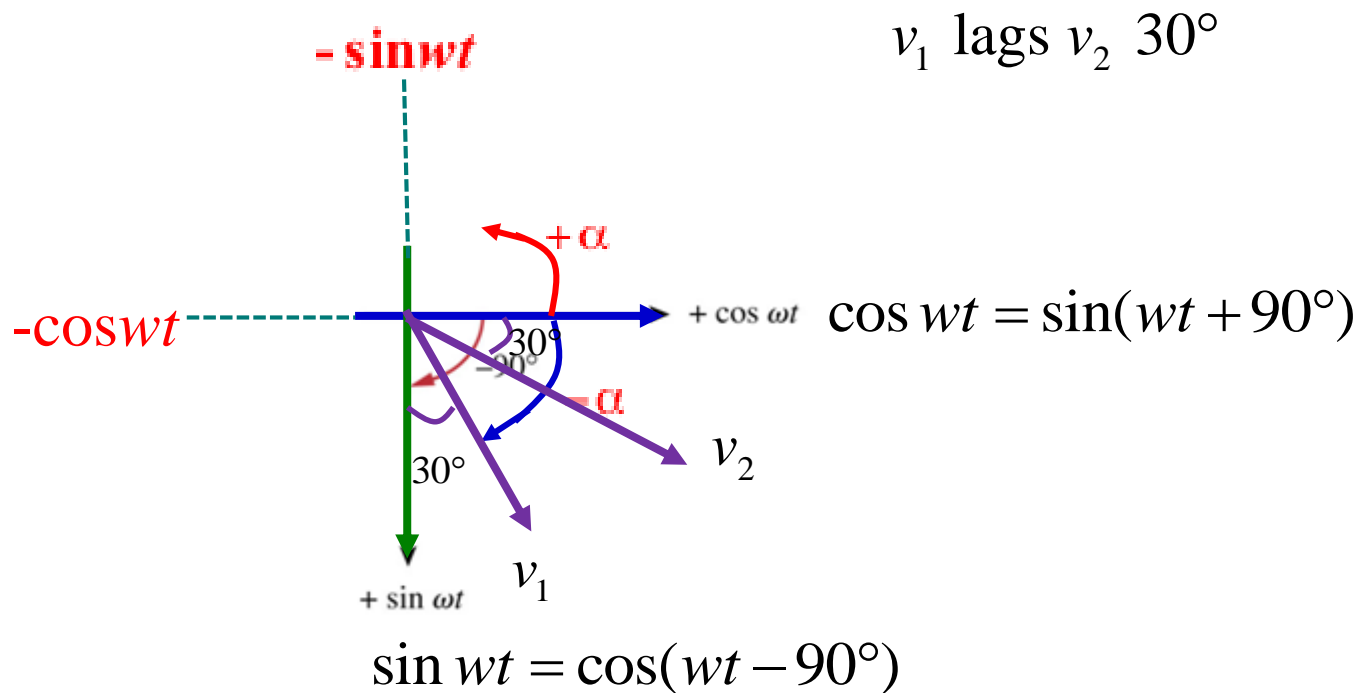


- 9.5 Given $v_1 = 45 \sin(\omega t + 30^\circ)$ V and $v_2 = 50 \cos(\omega t - 30^\circ)$ V, determine the phase angle between the two sinusoids and which one lags the other.




9.16 Transform the following sinusoids to phasors:

(c) $20 \cos(2t) + 15 \sin(2t)$


$$20 \cos(2t) + 15 \sin(2t) = 25 \cos(2t - 37^\circ)$$

So: The phasor = $25 \angle -37^\circ$

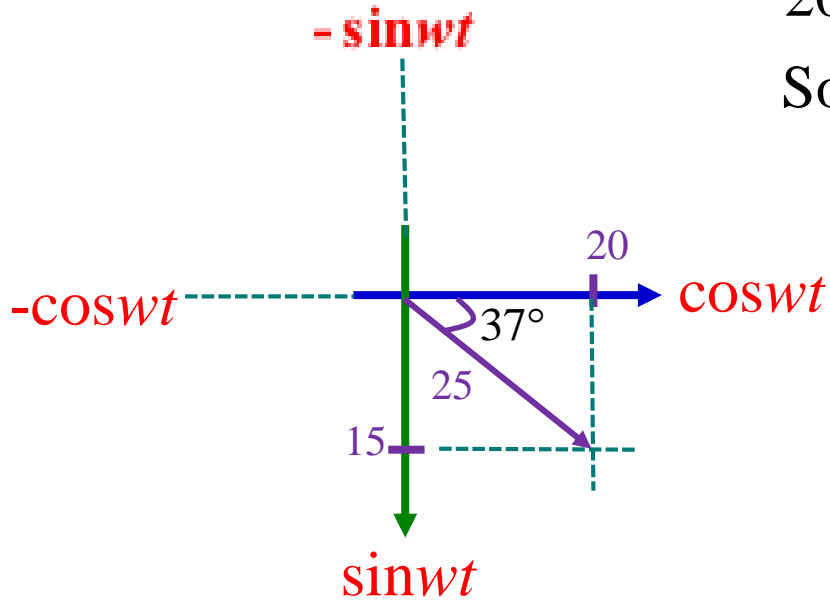

9.18 Obtain the sinusoids corresponding to each of the following phasors:

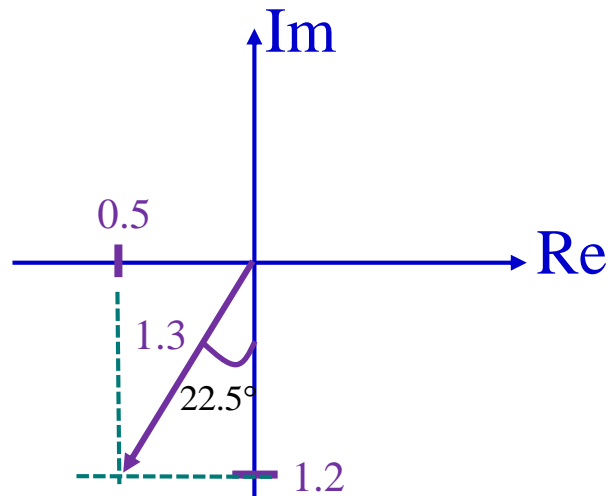(d) $\mathbf{I}_2 = -0.5 - j1.2 \text{ A}, \omega = 10^3$



$$\mathbf{I}_2 = 1.3 \angle -112.5^\circ$$

So: The sinusoid = $1.3 \cos(10^3 t - 112.5^\circ)$

9.27 A parallel *RLC* circuit has the node equation

$$\frac{dv}{dt} + 50v + 100 \int v dt = 110 \cos(377t - 10^\circ) \text{ V}$$

Determine $v(t)$ using the phasor method. You may assume that the value of the integral at $t = -\infty$ is zero.

Solution:

$$\begin{aligned} j\omega V + 50V + \frac{100V}{j\omega} &= 110\angle -10^\circ \\ \Rightarrow V &= \frac{110\angle -10^\circ}{j\omega + 50 + \frac{100}{j\omega}} \\ &= \frac{110\angle -10^\circ}{j377 + 50 + \frac{100}{j377}} \\ &= 0.289\angle -92.5^\circ \end{aligned}$$

So: $v(t) = 0.289 \cos(377t - 92.5^\circ)$

9.30 A voltage $v(t) = 100 \cos(60t + 20^\circ)$ V is applied to a parallel combination of a 40-k Ω resistor and a 50- μ F capacitor. Find the steady-state currents through the resistor and the capacitor.

Solution:

$$V = 100 \angle 20^\circ$$

$$Z_C = \frac{1}{j60 \times 50 \times 10^{-6}} = -\frac{j}{3} \text{ k}\Omega$$

$$I_R = \frac{V}{R} = \frac{100 \angle 20^\circ}{40} = 2.5 \angle 20^\circ \text{ mA}$$


$$I_C = \frac{V}{Z_C} = \frac{100 \angle 20^\circ}{-\frac{j}{3}} = 300 \angle 110^\circ \text{ mA}$$

$$\text{So: } i_R = 2.5 \cos(60t + 20^\circ) \text{ mA}$$

$$i_C = 300 \cos(60t + 110^\circ) \text{ mA}$$

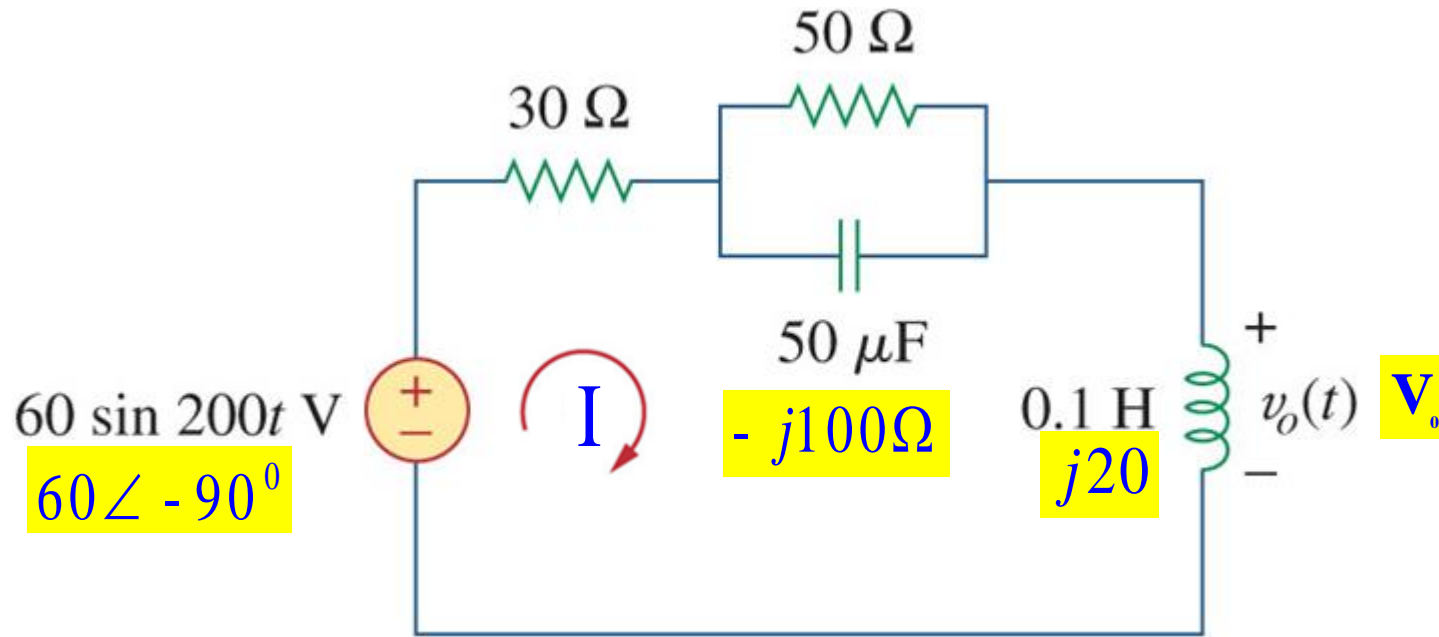Problem 9.42 P406

Calculate $v_o(t)$ in the circuit of Fig. 9.49.



Solution:

$$V_o = I \times j20$$


$$= \frac{60 \angle -90^\circ}{30 + 50 \parallel (-j100) + j20} \times j20$$

$$= 17.14 \angle 0^\circ$$

$$\text{So: } v_o(t) = 17.14 \cos(200t) \text{ V}$$

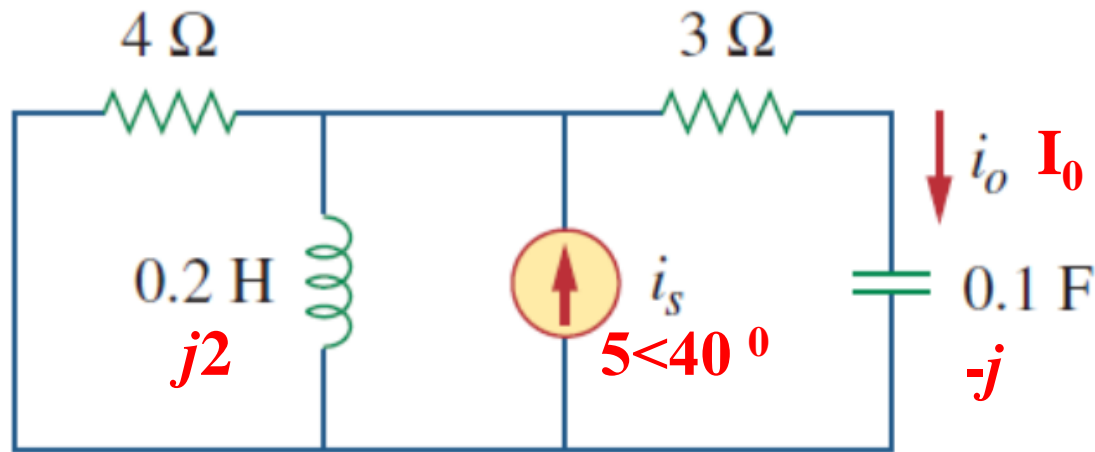Problem 9.46 P407

If $i_s = 5 \cos(10t + 40^\circ)$ A in the circuit of Fig. 9.53, find i_o .




Solution:

$$I_0 = \frac{4 \parallel j2}{4 \parallel j2 + 3 - j} \times 5 \angle 40^\circ$$
$$= 2.325 \angle 94.5^\circ$$

So: $i_o = 2.325 \cos(10t + 94.5^\circ)$ A

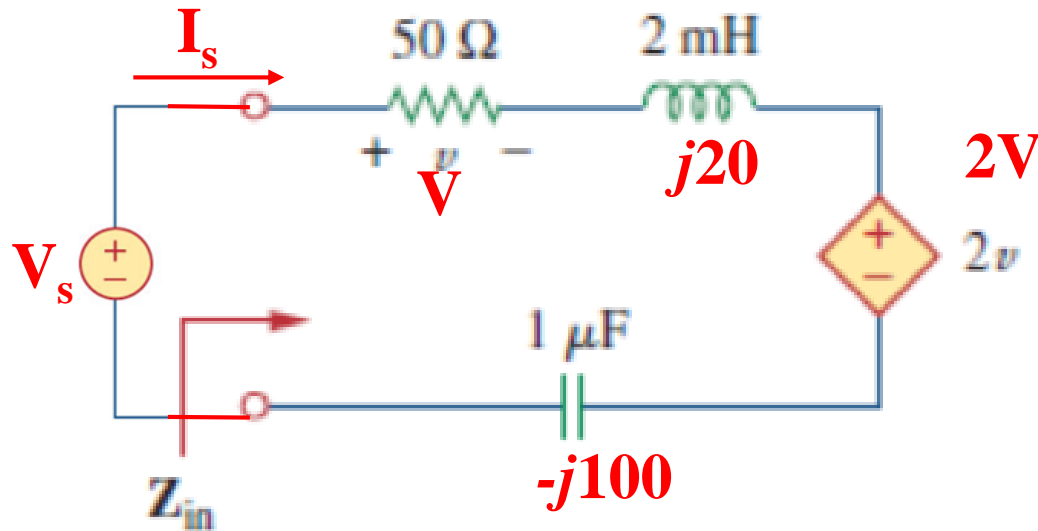Problem 9.62 P408

For the circuit in Fig. 9.69, find the input impedance Z_{in} at 10 krad/s.



Solution:


$$V_s = I_s (50 + j20 - j100) + 2V$$

$$\text{Since } V = 50I_s$$

$$\text{So: } Z_{in} = \frac{V_s}{I_s} = 150 - j80$$

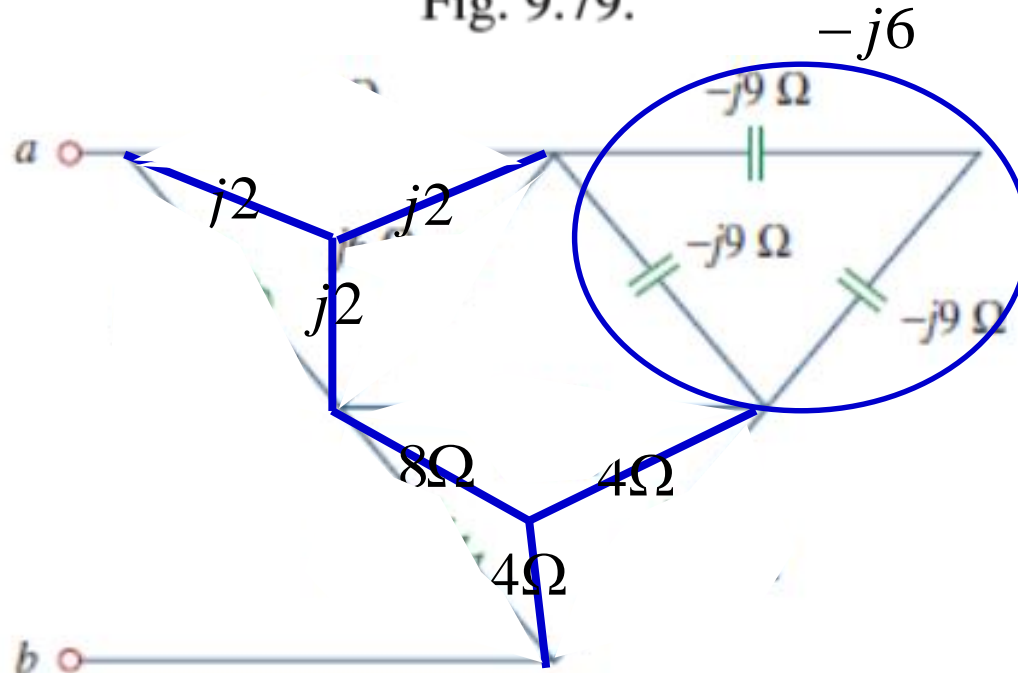Problem 9.72 P410

Calculate the value of Z_{ab} in the network of Fig. 9.79.



$$Z_{ab} = 7.567 + j0.5946$$