

Examples – Circuits and Electronics

Decoders and Multiplexers – Week 2

Example 1

A combinational circuit is defined by the following three output functions:

$$F_1 = \overline{X}\overline{Y} + XY\overline{Z}$$

$$F_2 = \overline{X} + Y$$

$$F_3 = XY + \overline{X}\overline{Y}$$

- a) Use two 4-to-1 multiplexers, an OR gate and an inverter in the implementation
- b) Design the circuit using a 3-to-8 line decoder and external NAND gates.

Example 2

Implement a full adder circuit which will add two bits, A and B, using two 4-to-1 multiplexers. Use input variables B and Carry-in (C_i) connected to select lines S_1 and S_0 , respectively.

Example 3

Consider the function $F(A,B,C,D) = \Sigma m(2,3,8,10,13,14)$ that is $F(A,B,C,D)=1$ for $ABCD=0010, 0011, \text{etc...}$

Implement the above function using **ONLY the 4-to-1 multiplexer shown below, inverters or any number of 2-input NOR gates.** Note that in the 4:1 multiplexer shown below, **input variables A, B have been connected to select lines S_1, S_0 , respectively..** Assume variables A, B, C and D are **NOT available in their complemented form.** Show your working using the truth table drawn below.

A	B	C	D	F	
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

