

Tutorial 7 -MOS transistors

Problem 1:

Figure 1 shows the NMOS and PMOS devices with drain, source and gate ports annotated.

Determine the mode of operation (Saturation, Triode, Cut-off) as well as the drain current I_D for each of the biasing configurations given below. Use the following transistor data:

NMOS: $K_n' = 60 \mu\text{A}/\text{V}^2$, $V_{T0} = 0.7\text{V}$, $\lambda = 0.1 \text{ V}^{-1}$

PMOS: $K_p' = 20 \mu\text{A}/\text{V}^2$, $V_{T0} = -0.8\text{V}$, $\lambda = -0.1 \text{ V}^{-1}$

Assume that $W/L = 1$ for both transistors.

Biasing configurations:

(a). NMOS: $V_{GS} = 3.3\text{V}$; $V_{DS} = 3.3\text{V}$. PMOS: $V_{GS} = -0.5\text{V}$; $V_{DS} = -1.5\text{V}$

(b). NMOS: $V_{GS} = 3.3\text{V}$; $V_{DS} = 2.2\text{V}$. PMOS: $V_{GS} = -3.3\text{V}$; $V_{DS} = -2.6\text{V}$

(c). NMOS: $V_{GS} = 0.6\text{V}$; $V_{DS} = 0.1\text{V}$. PMOS: $V_{GS} = -3.3\text{V}$; $V_{DS} = -0.5\text{V}$



Fig.1 NMOS (left) and PMOS (right) transistors notations.

Problem 2:

Assume no body effect or channel length modulation

Various NMOS and PMOS transistors are measured in operation, as shown in the table below. For each transistor, find the value of $\mu C_{ox} W/L$ and V_t that apply and complete the table with V in Volts, I in μA , and $\mu C_{ox} W/L$ in $\mu\text{A}/\text{V}^2$.

Case	Transistor	V_S	V_G	V_D	I_D	Type	Mode	$\mu C_{ox} W/L$	V_t
a	1	0	2	5	100				
	1	0	3	5	400				
b	2	5	3	-4.5	50				
	2	5	2	-0.5	450				
c	3	5	3	4	200				
	3	5	2	0	800				
d	4	-2	0	0	72				
	4	-4	0	-3	270				

Problem 3:

- What is the operating mode of the two transistors represented in Fig.a and b if we assume that the voltage V_x varies from 0 to V_{DD} ?
- For $V_x=(V_{DD}/2)=2.5V$, what will be the value of the current I_{DS} for both transistors?

Use the following transistor data:

NMOS: $K_n'=60\mu A/V^2$, $V_{TO}=0.7V$, $\lambda=0.1 V^{-1}$;

PMOS: $K_p'=20\mu A/V^2$, $V_{TO}=-0.8V$, $\lambda=-0.1 V^{-1}$

Assume that $W/L = 1$ for both transistors.

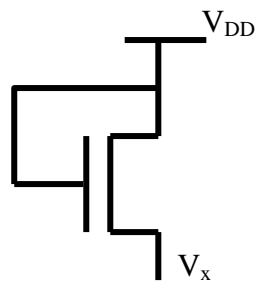


Fig.a

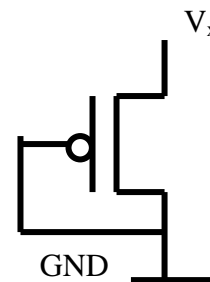


Fig.b

Problem 4:

Consider the circuit configuration of Figure 2. $K_p'=5.4 \mu A/V^2$ and $V_{thp}=-0.739V$

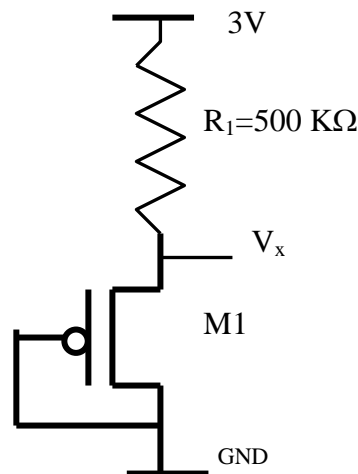


Fig2.

- Assuming $V_x > -V_{thp}$; find out the operating mode of the transistor and deduce the expression of the current I_{DS} .
- Deduce the expression of the voltage V_x (Assume that the channel length modulation coefficient λ is zero. $\lambda=0$).
- Determine the required width of the transistor (for $L=1.2\mu m$) such that $V_x=1.5V$.