
Lecture 8



The Bipolar Junction Transistor

A bit of History

❑ BJT was **invented in 1948** at Bell Telephone Laboratories.

Ushered in a new era of **solid-state circuits**.

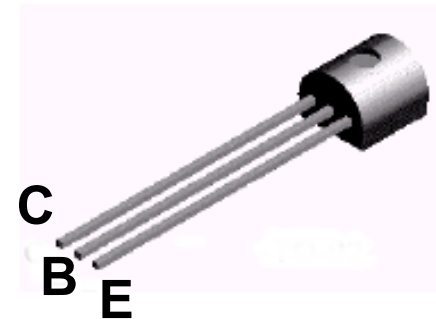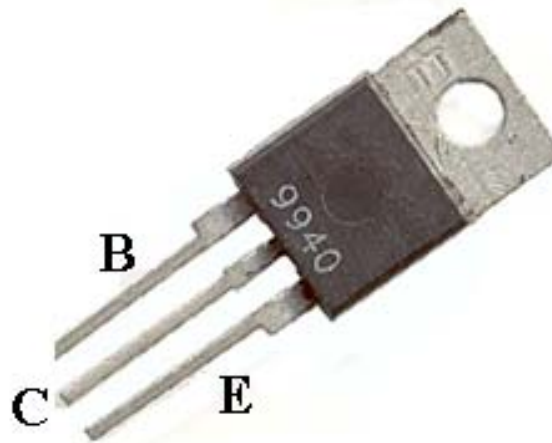It was **replaced by MOSFET** as predominant transistor used in modern electronics.



The BJT structure and symbols

❑ Two types of BJT:

npn. (most common, focus on it)

pnp.


❑ Three adjacent regions of doped Si (each connected to a lead):

Base. (thin layer, less doped).


Collector.

Emitter.

npn BJT

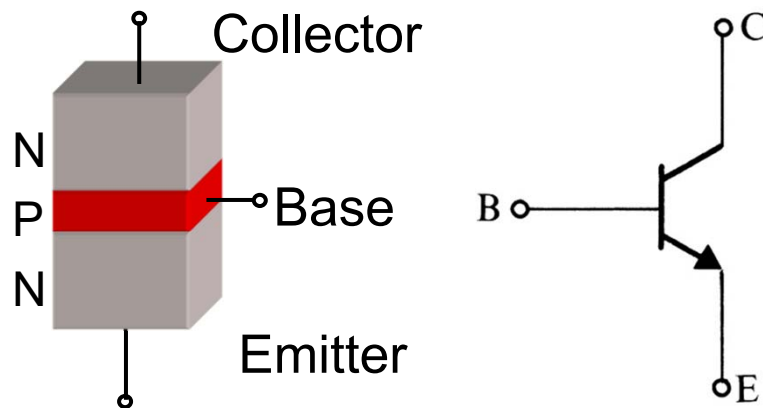

pnp BJT

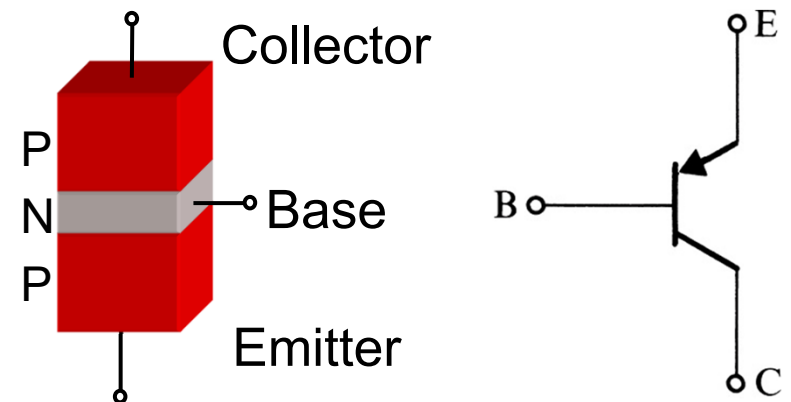

nnp BJT transistor

❑ N-type of emitter: more heavily doped than collector.

❑ With $V_C > V_B > V_E$:

Base-Emitter junction forward biased, Base-Collector reverse biased.


Electrons diffuse from Emitter to Base (from n to p).

There's a depletion layer on the Base-Collector junction → no flow of e^- allowed.

BUT the Base is thin and Emitter region is n^+ (heavily doped) → electrons have enough momentum to cross the Base into the Collector.

The small base current I_B controls a large current I_C
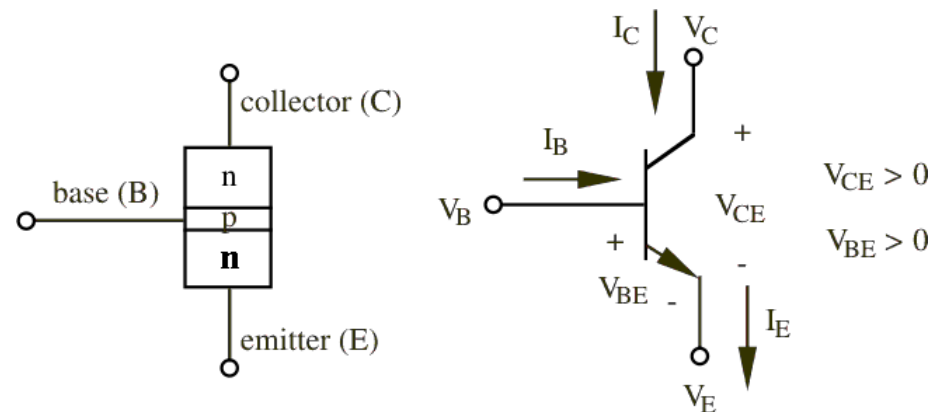
$$\begin{aligned}
 V_C > V_B > V_E \quad & I_E = I_C + I_B \\
 & V_{BE} = V_B - V_E \\
 & V_{CE} = V_C - V_E \\
 & I_C = \beta I_B
 \end{aligned}$$



BJT characteristics

5

❑ All current which enters transistor must leave: $i_E = i_C + i_B$

❑ Current Gain:

α is the fraction of electrons that diffuse across the narrow Base region

$1 - \alpha$ is the fraction of electrons that recombine with holes in the Base region to create base current

❑ The current Gain is expressed in terms of the β (beta) of the transistor (often called h_{fe} by manufacturers).

❑ β (beta) is Temperature and Voltage dependent.

❑ It can vary a lot among transistors (common values for signal BJT: 20 - 200).

$$I_C = \alpha I_E$$

$$I_B = (1 - \alpha) I_E$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$

BJT characteristics (cont'd)

6

- **common-emitter current gain (β)** – is influenced by **two factors**:
 - width of base region (W)
 - relative doping of base emitter regions (N_A/N_D)
- **High Value of β**
 - **thin base** (small W in nano-meters)
 - **lightly doped base / heavily doped emitter** (small N_A/N_D)

$$i_C = I_s e^{V_{BE}/V_T} \qquad i_E = \frac{\beta + 1}{\beta} i_C = \frac{\beta + 1}{\beta} \left(I_s e^{V_{BE}/V_T} \right)$$

- **common-base current gain (α)**

$$i_C = \alpha I_E \quad \Rightarrow \quad \alpha = \frac{\beta}{\beta + 1} \qquad \beta = \frac{\alpha}{1 - \alpha}$$

Modes of Operation

- ❑ Transistor consists of **two *pn*-junctions**:
 - emitter-base** junction (EBJ)
 - collector-base** junction (CBJ)
- ❑ Operating **mode** depends on biasing.
 - active** mode – used for amplification
 - cutoff** and **saturation** modes – used for switching.

<i>Operation Region</i>	<i>I_B or V_{CE} Char.</i>	<i>BC and BE Junctions</i>	<i>Mode</i>
Cutoff	I_B = Very small	Reverse & Reverse	Open Switch
Saturation	V_{CE} = Small	Forward & Forward	Closed Switch
Active Linear	V_{CE} = Moderate	Reverse & Forward	Linear Amplifier
Break-down	V_{CE} = Large	Beyond Limits	Overload

Summary of BJT C-V relationship in active mode ⁸

Summary of the BJT Current-Voltage Relationships in the Active Mode

$$i_C = I_S e^{v_{BE}/V_T}$$

$$i_B = \frac{i_C}{\beta} = \left(\frac{I_S}{\beta}\right) e^{v_{BE}/V_T}$$

$$i_E = \frac{i_C}{\alpha} = \left(\frac{I_S}{\alpha}\right) e^{v_{BE}/V_T}$$

Note: For the *pnp* transistor, replace v_{BE} with v_{EB} .

$$i_C = \alpha i_E \qquad i_B = (1 - \alpha) i_E = \frac{i_E}{\beta + 1}$$



$$i_C = \beta i_B \qquad i_E = (\beta + 1) i_B$$

$$\beta = \frac{\alpha}{1 - \alpha} \qquad \alpha = \frac{\beta}{\beta + 1}$$

$$V_T = \text{thermal voltage} = \frac{kT}{q} \simeq 25 \text{ mV at room temperature}$$


npn common emitter BJT circuits

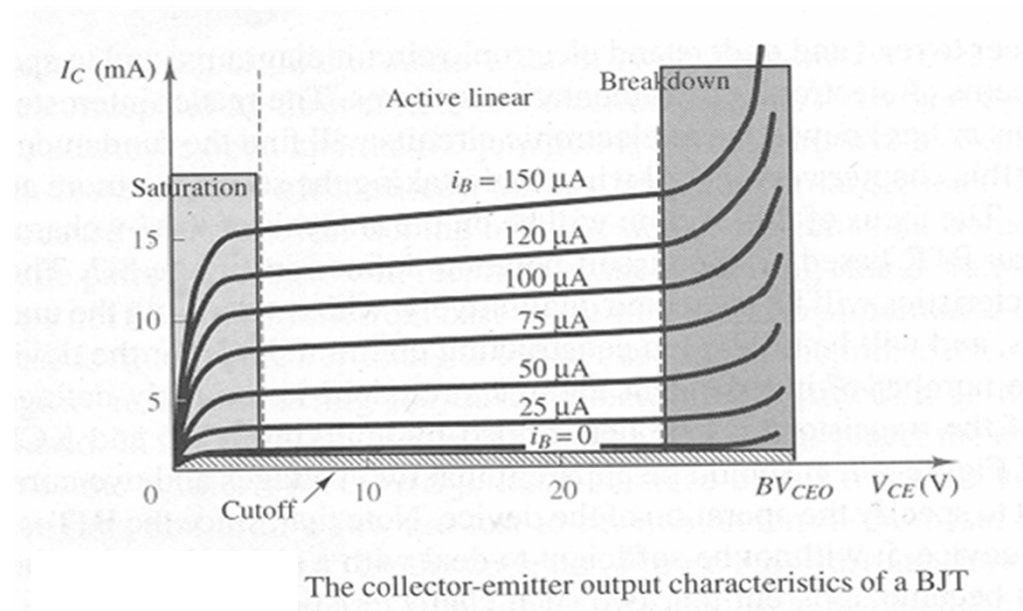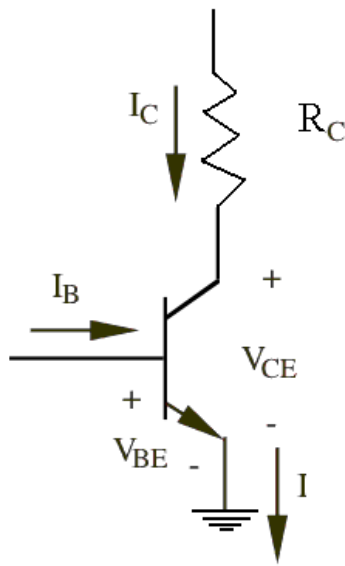- Emitter is grounded.
- Base-Emitter starts to conduct with $V_{BE}=0.6V$ (for example), I_C flows and it's $I_C=b \cdot I_B$.
- Increasing I_B , V_{BE} slowly increases to $0.7V$ (for example) but I_C rises exponentially.
- As I_C rises, voltage drop across R_C increases and V_{CE} drops toward ground. (transistor in saturation, no more linear relation between I_C and I_B)




The collector-emitter output characteristics of a BJT

Common Emitter characteristics (input)

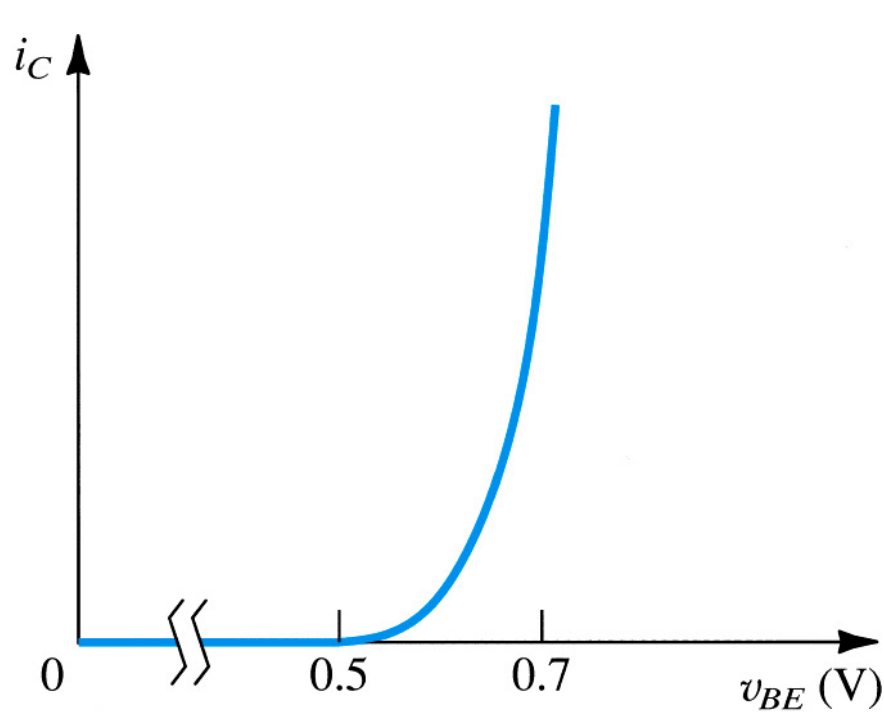

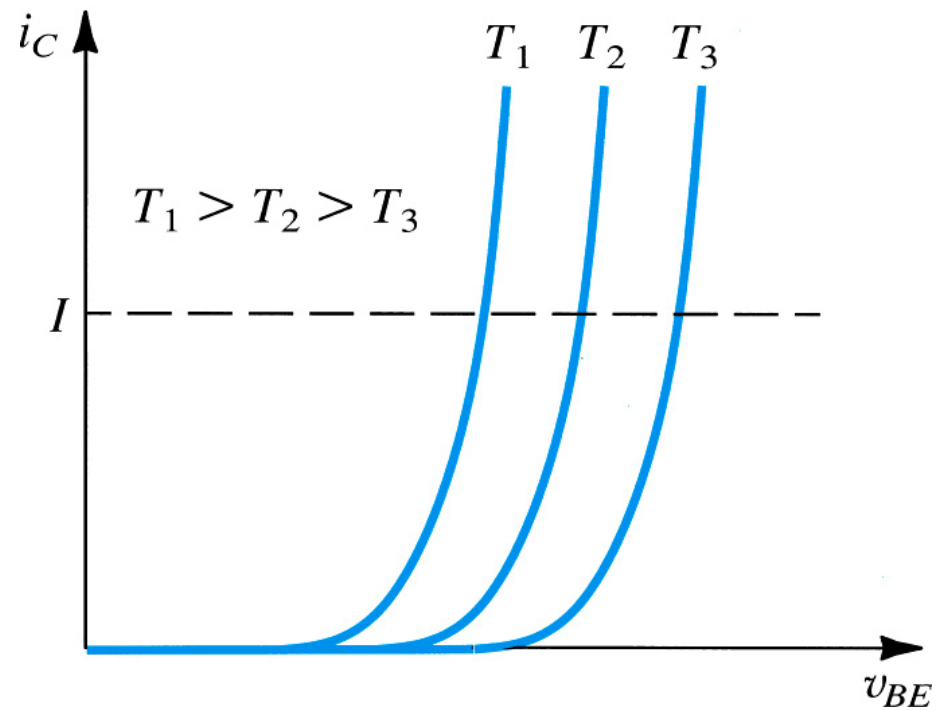The i_C - v_{BE} characteristic for an npn transistor.



Effect of temperature on the i_C - v_{BE} characteristic.

Common Emitter characteristics (output)


11

Collector current controlled by the collector circuit.
([Switch behavior](#))

In full saturation
 $V_{CE} = 0.2V$.

Collector current proportional to Base current

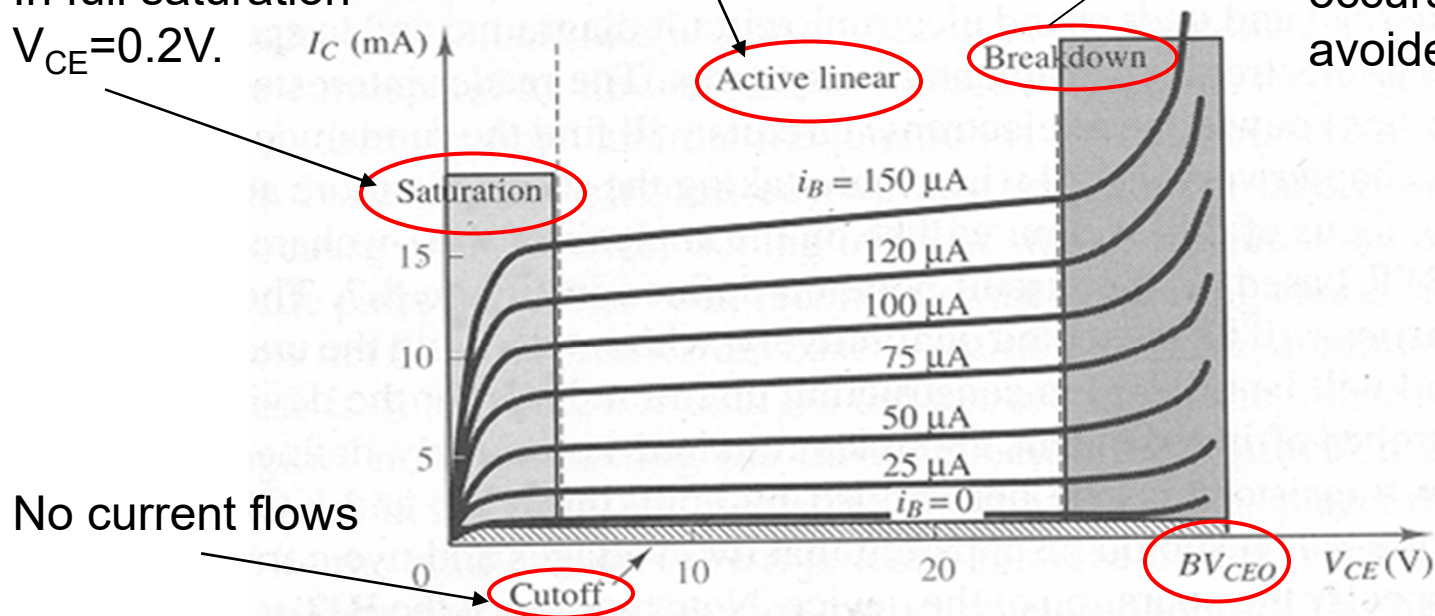
The avalanche multiplication of current through collector junction occurs: to be avoided



The collector-emitter output characteristics of a BJT

Common Emitter characteristics – cont'd


12

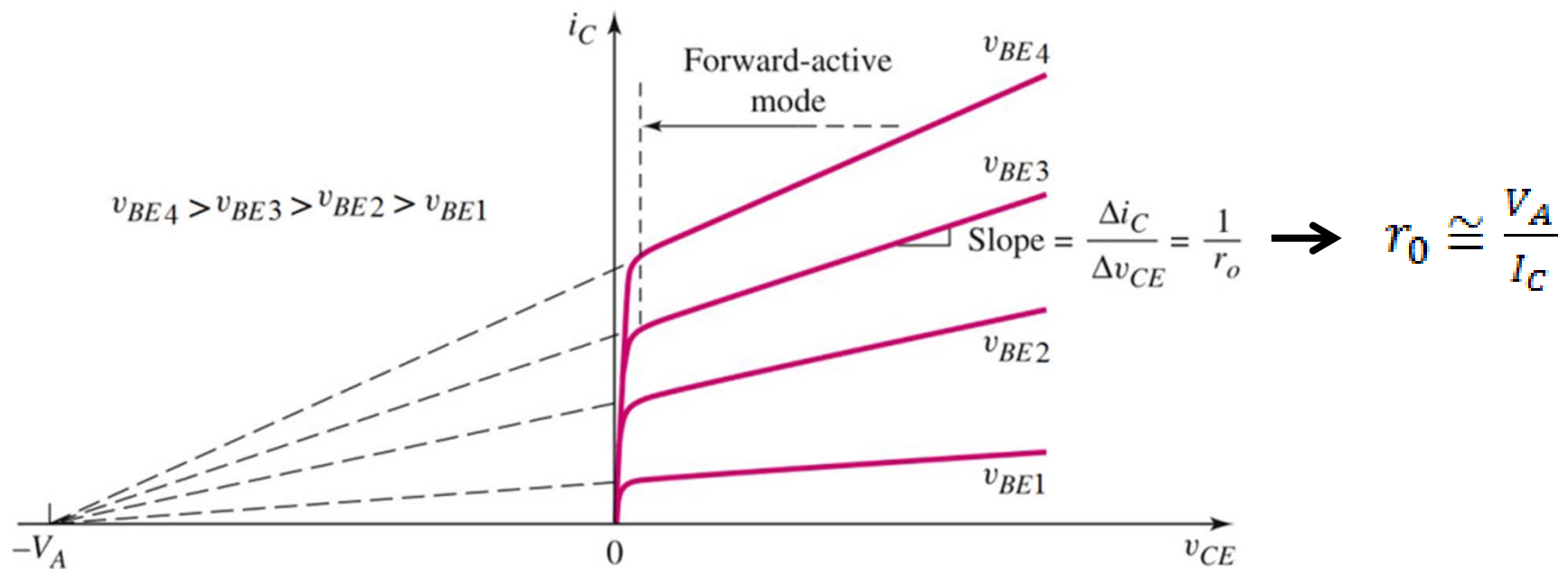

I - V characteristic of common-emitter BJT circuit, showing Early voltage and the finite output resistance, of the transistor

BJT as switch (digital circuit)- example

13

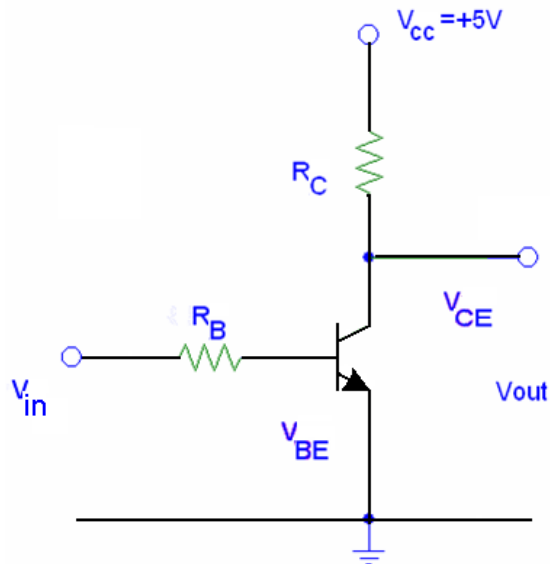

■ $V_{in}(\text{Low}) < 0.7 \text{ V}$


- BE junction not forward biased
- Cutoff region
- No current flows
- $V_{out} = V_{CE} = V_{CC}$

■ $V_{out} = \text{High}$

■ $V_{in}(\text{High})$


- BE junction forward biased ($V_{BE} = 0.7V$)
- Saturation region
- V_{CE} small ($\sim 0.2 \text{ V}$ for saturated BJT)
- $V_{out} = \text{small}$
- $I_B = (V_{in} - V_B) / R_B$

■ $V_{out} = \text{Low}$

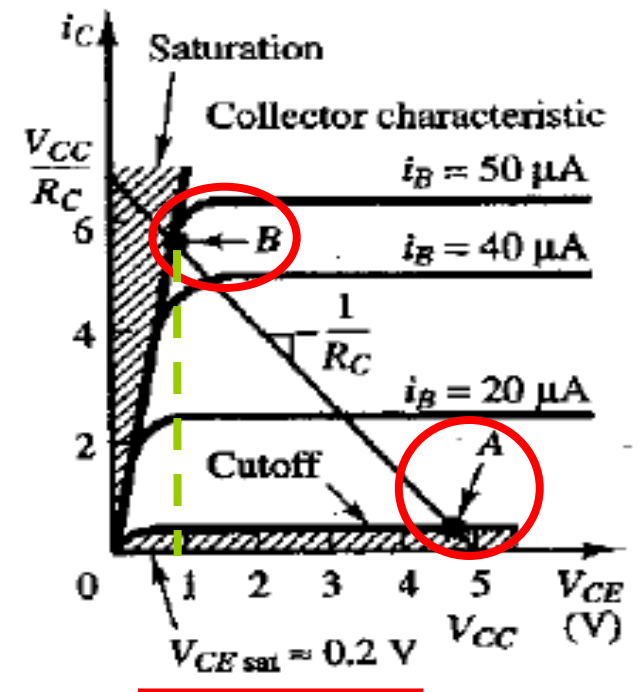

BJT as amplifier (analogue circuit) - example

14

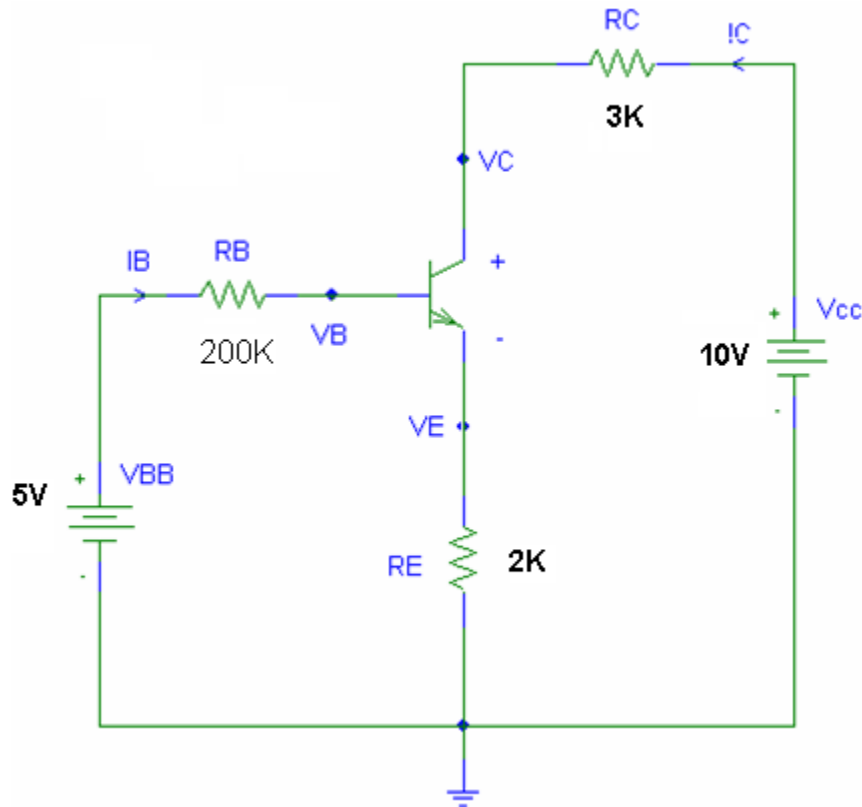


- Common emitter mode
- Linear Active Region
- Significant current Gain

Example:

- Let Gain, $\beta = 100$
- Assume to be in active region
→ $V_{BE} = 0.7V$
- Find if it's in active region?

BJT as amplifier – example (cont'd)

15

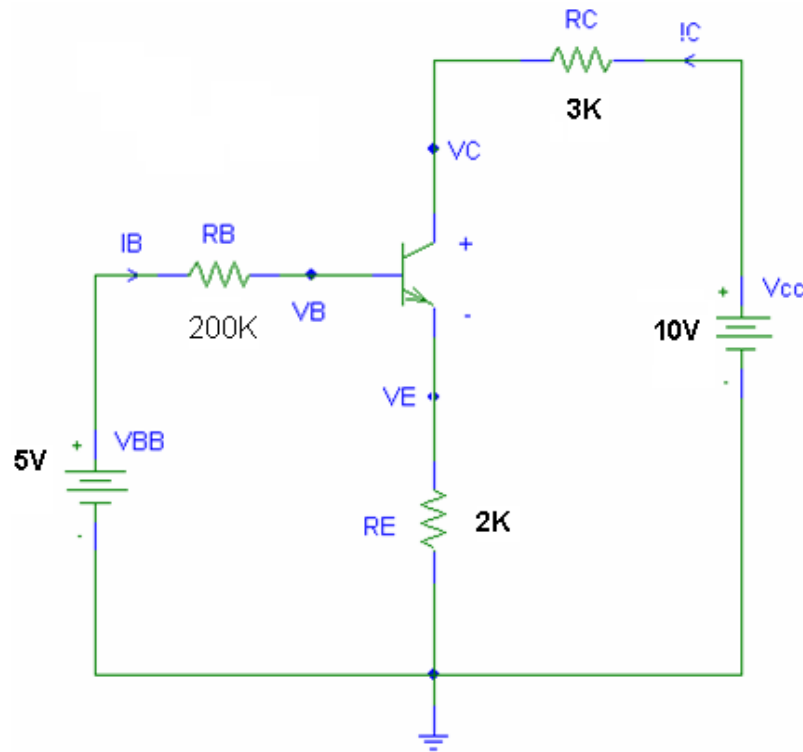

$$\underline{V_{BE}} = 0.7V$$

$$\underline{I_E} = I_B + I_C = (\beta + 1)I_B$$

$$\underline{I_B} = \frac{V_{BB} - V_{BE}}{R_B + R_E * 101} = \frac{5 - 0.7}{402} = 0.0107mA$$

$$\underline{I_C} = \beta * I_B = 100 * 0.0107 = 1.07mA$$

$$\begin{aligned}\underline{V_{CB}} &= V_{CC} - I_C * R_C - I_E * R_E - V_{BE} = \\ &= 10 - (3)(1.07) - (2)(101 * 0.0107) - 0.7 = \\ &= 3.93V\end{aligned}$$

$V_{CB} > 0$ so the BJT is in active region

BJT as amplifier – example 2

Calculate the collector and emitter currents, given the base current and current gain. Assume a common-base current gain $\alpha = 0.97$ and a base current of $i_B = 25 \mu\text{A}$. Also assume that the transistor is biased forward in the forward active mode.

Solution: The common-emitter current gain is $\beta = \frac{\alpha}{1-\alpha} = \frac{0.97}{1-0.97} = 32.33$

The collector current is $i_C = \beta i_B = 32.33 \times 25 = 808.25 \mu\text{A}$

And the emitter current is $i_E = i_B + i_C = 25 + 808.25 = 833.25 \mu\text{A}$

Acknowledgments

- ❑ Lecture slides are based on lecture materials from various sources, including book “Microelectronic Circuits” by Sedra and Smith (Oxford Publishing), Kirk Glazer (Gatech) and Nor Farahidah Za'bah (IIUM).
- ❑ Credit is acknowledged where credit is due. Please refer to the full list of references.