
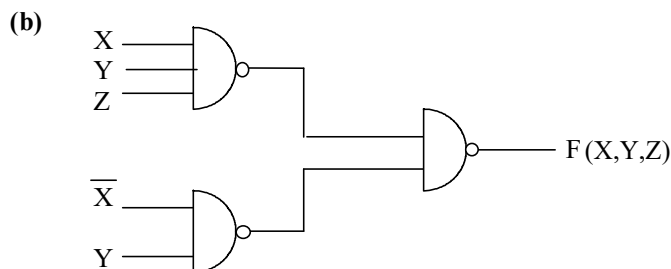


Homework Questions
Circuits and Electronics
Week 1

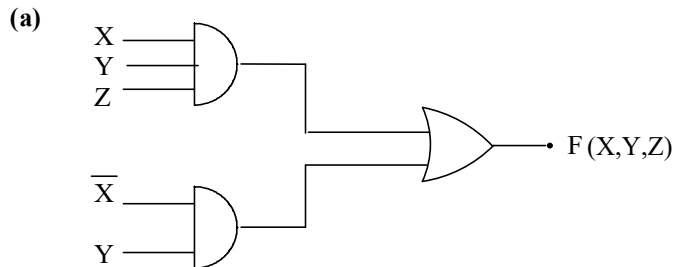Q.1 Determine the truth table for the following logic circuits



(c) What can you say about the above two circuits?

Q.2 Consider the following Boolean function:

$$\overline{F} = \overline{B}D + \overline{A}B\overline{C} + ACD + \overline{A}BC$$

- Find the complement of the Boolean function and reduce it to seven literals in sum-of-products form.
- Using a truth table show that the reduced Boolean function for is equivalent to the original expression.
- Implement the simplified expression using AND, OR and NOT logic gates in a 2-level gate circuit.

Q.3 Use Karnaugh maps to obtain the simplified expressions in sum-of-products form for the following Boolean functions:

- $ABD + \overline{A}\overline{C}\overline{D} + \overline{A}B + \overline{A}C\overline{D} + A\overline{B}\overline{D}$
- $\overline{X}Z + \overline{W}X\overline{Y} + W(\overline{X}Y + X\overline{Y})$

Q.4 Using Karnaugh maps, simplify the following expressions, using sum-of-products form:

$$(a) \quad ABC + \overline{A}\overline{B}C + \overbrace{\overline{A}BC + A\overline{B}C + ABC}^{\text{don't cares}}$$

$$(b) \quad ABCD + \overline{A}\overline{B}CD + \overbrace{\overline{A}BCD + A\overline{B}CD + \overline{A}\overline{B}\overline{C}D}^{\text{don't cares}}$$

$$(c) \quad \overline{A}\overline{B}C\overline{D} + A\overline{B}C\overline{D} + \overbrace{\overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D}}^{\text{don't cares}}$$