

---

# **Lecture 13**

## **Implementation technologies**

# Learning outcomes

---

- ❑ Identify the appropriate modern realization technologies and synthesis techniques for the implementation of a given digital system
- ❑ Discuss the different types of programmable logic
- ❑ Describe the basic architecture and operation of programmable logic


# IMPLEMENTATION TECHNOLOGIES

---


- ❑ Discrete parts (e.g. 7400 devices)
- ❑ Full Custom design
  - Mostly manual design, long design cycle
  - High performance, high volume
  - Microprocessors, analog, IP ...
- ❑ Standard cell
  - Pre-designed cells, CAD, short design cycle
  - Medium performance, ASIC
- ❑ Programmable logic devices
  - Pre-fabricated, fast automated design, low cost
  - Prototyping, reconfigurable computing
 
# Using Discrete Parts

- ❑ Discrete parts (e.g. 7400 devices)
- ❑ Theoretically, we only need 2-input NAND or NOR gates to build anything
- ❑ Bulky, slow, expensive, and tedious.




Dual-inline package

 

Structure of 7404 chip

# Using Discrete Parts

5

 

Implementation of  $f = \bar{x}_2x_3 + x_1x_2$

# Full Custom ASIC – Intel Core i7

---

- ❑ A full-custom ASIC design defines all photolithographic layers required for manufacturing. Each transistor/wire is drawn and connected in a full-custom manner by hand!


- ❑ Benefits

- reduced area and power
- higher performance

- ❑ Drawbacks

- increased design time
- higher designer skills required
- increased manufacturing time and cost
- Not viable unless the market is very large
- Highly risky: once designed, it cannot be changed easily.

## Intel Core i7

 


over  $\frac{3}{4}$  billion transistors



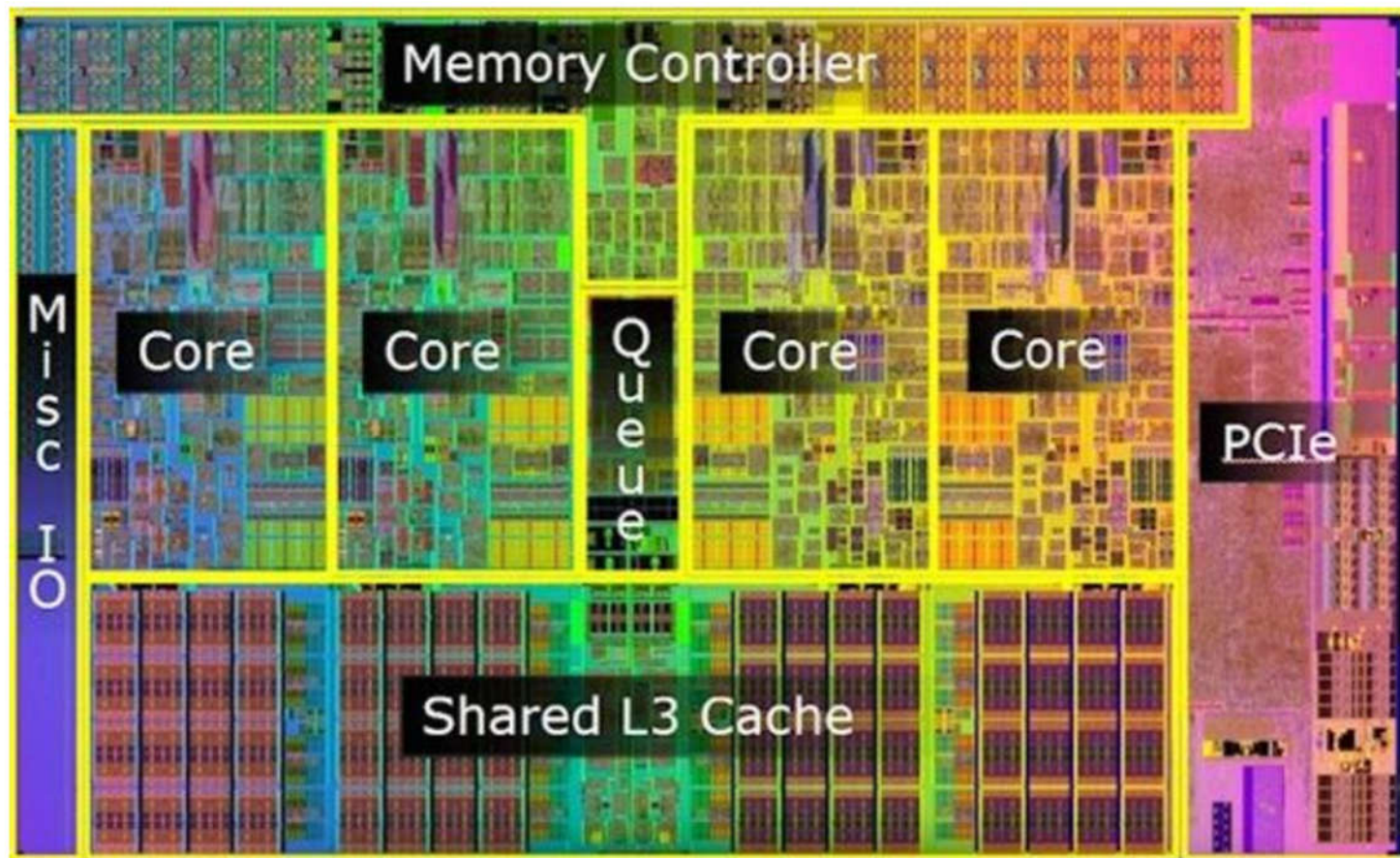
# Standard cell ASIC

- ❑ A basic cell library (gates, flip-flops, memory cells) is available with different views of the cells provided: schematic symbol, device-level structure, layout.
- ❑ CAD tools are used to determine the floorplan that minimizes chip-level global routing.


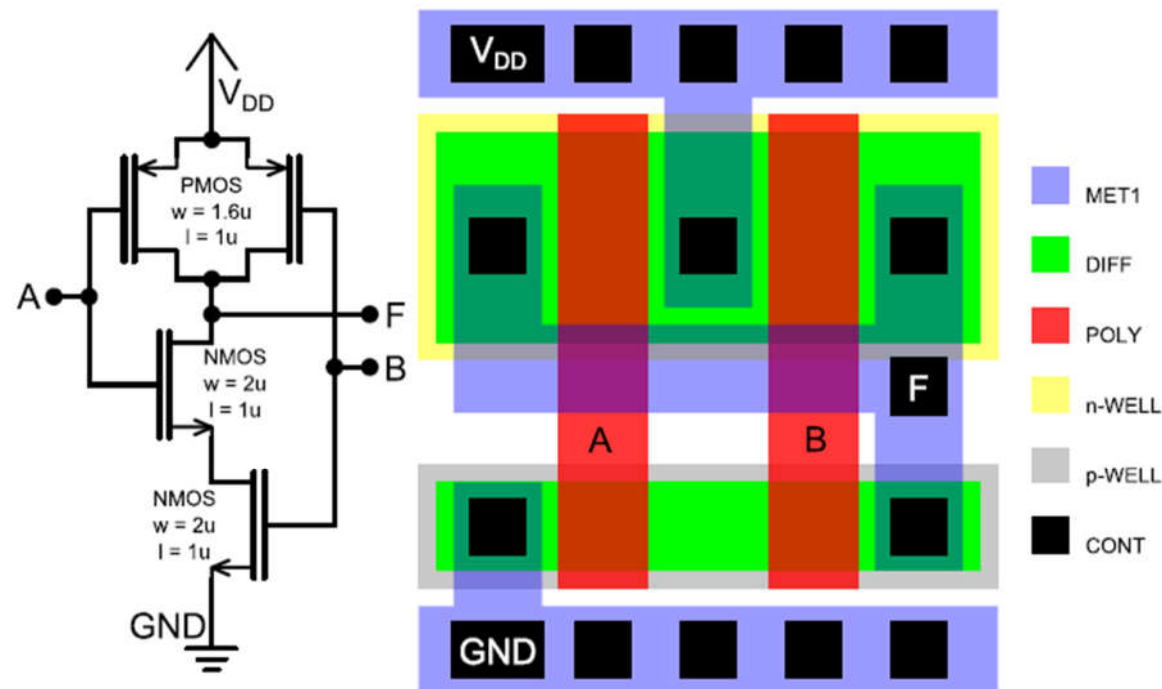
# Standard cell ASIC


- ❑ Highly optimized design units
- ❑ The function and the timing are verified
- ❑ Geometric restrictions of the standard cells
  - common height (arbitrary width)
  - position of the supply rails ( $V_{DD}$ , GND)
  - inputs and outputs on grid





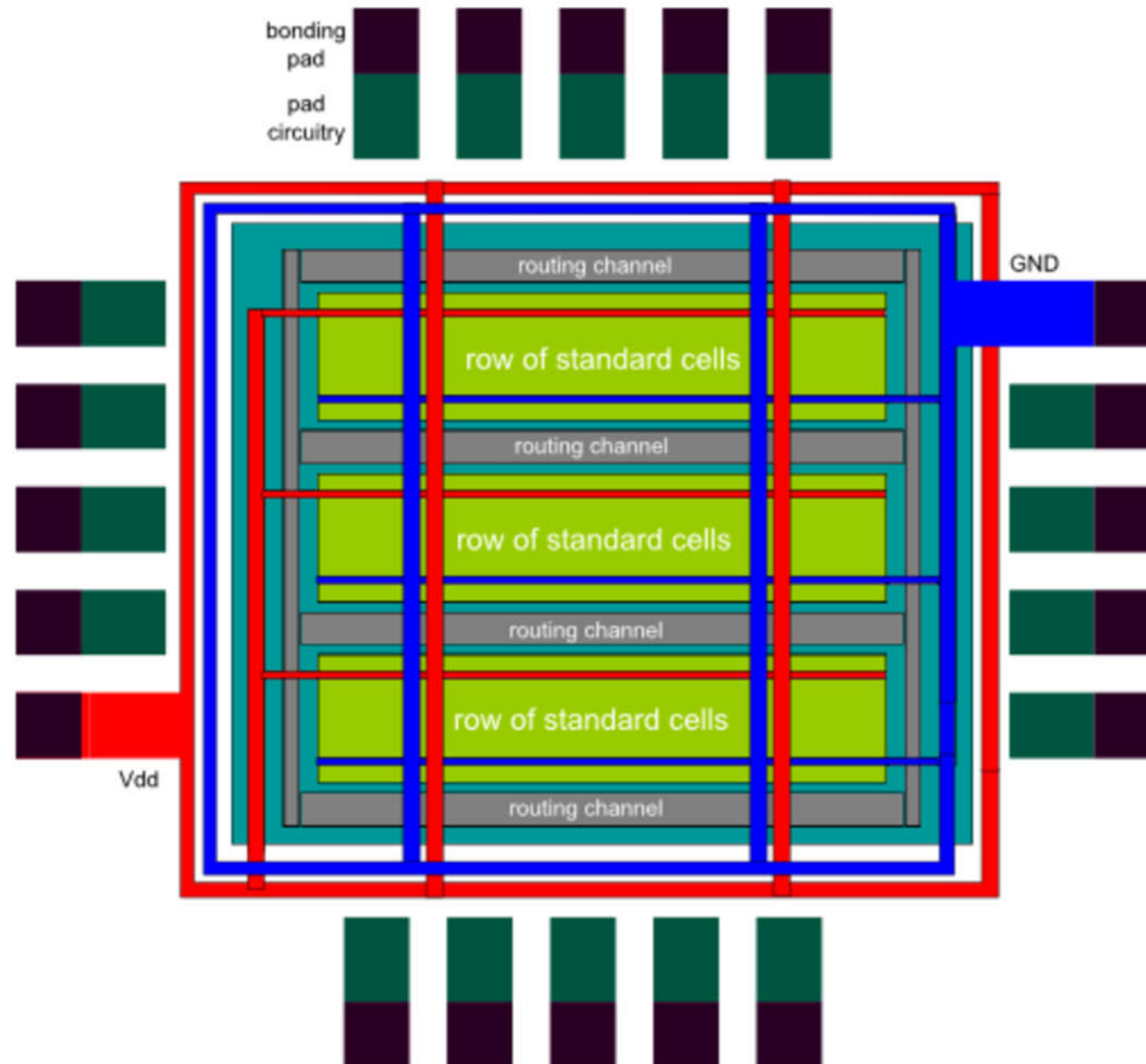
# Standard cell ASIC

- ❑ The basic standard-cell floorplan consists of cell-rows and routing


 
# Programmable Logic Device (PLD)

- ❑ A PLD is a general purpose chip for implementing logic circuitry
- ❑ Can be viewed as a black box containing logic gates and programmable switches that allow for different connections between the logic elements
- ❑ Can implement whatever logic circuit is needed – subject to resources of the device




## Classification — Programmable Logic Devices (PLDs)

- ❑ **PLA** — a Programmable Logic Array (PLA) is a relatively small PLD that contains two levels of logic, an AND-plane and an OR-plane, where both levels are programmable
- ❑ **PAL** — a Programmable Array Logic (PAL) is a relatively small PLD that has a programmable AND-plane followed by a fixed OR-plane
- ❑ **SPLD** — refers to any type of Simple PLD, usually either a PLA or PAL
- ❑ **CPLD** — a more Complex PLD that consists of an arrangement of multiple SPLD-like blocks on a single chip.
- ❑ **FPGA** — a Field-Programmable Gate Array is a PLD featuring a general structure that allows very high logic capacity.

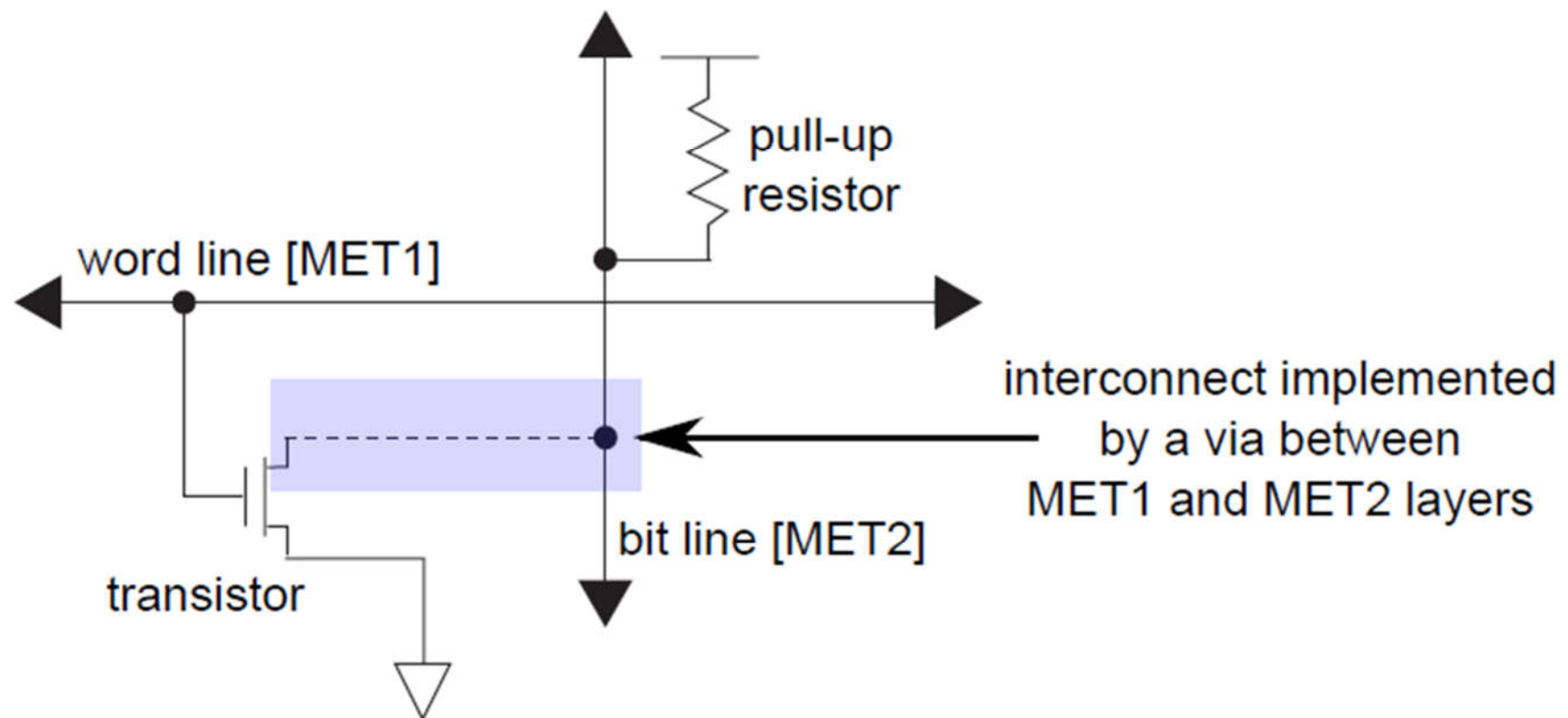
# Implementing programmable interconnections

12

- ❑ **Mask-programming**: The interconnection between two wires is implemented by a **metal or contact window layer**. The interconnect configuration or the content of the ROM **cannot be changed after the manufacturing**.



 - ❑ **Anti-fuse**: An "anti-fuse" physically consists of three sandwiched layers: the top and bottom layers are conductors and the middle layer is an insulator. With a **high voltage pulse** the insulator turns into a low-resistance connection (**One-time programmable device**)




- ❑ **Anti-fuse**: normally disconnected, make wanted connections
- ❑ **Fuse** also exist: normally connected, break unwanted ones


# Implementing programmable interconnections

14

Unprogrammed Antifuse

 

Programmed Antifuse

 



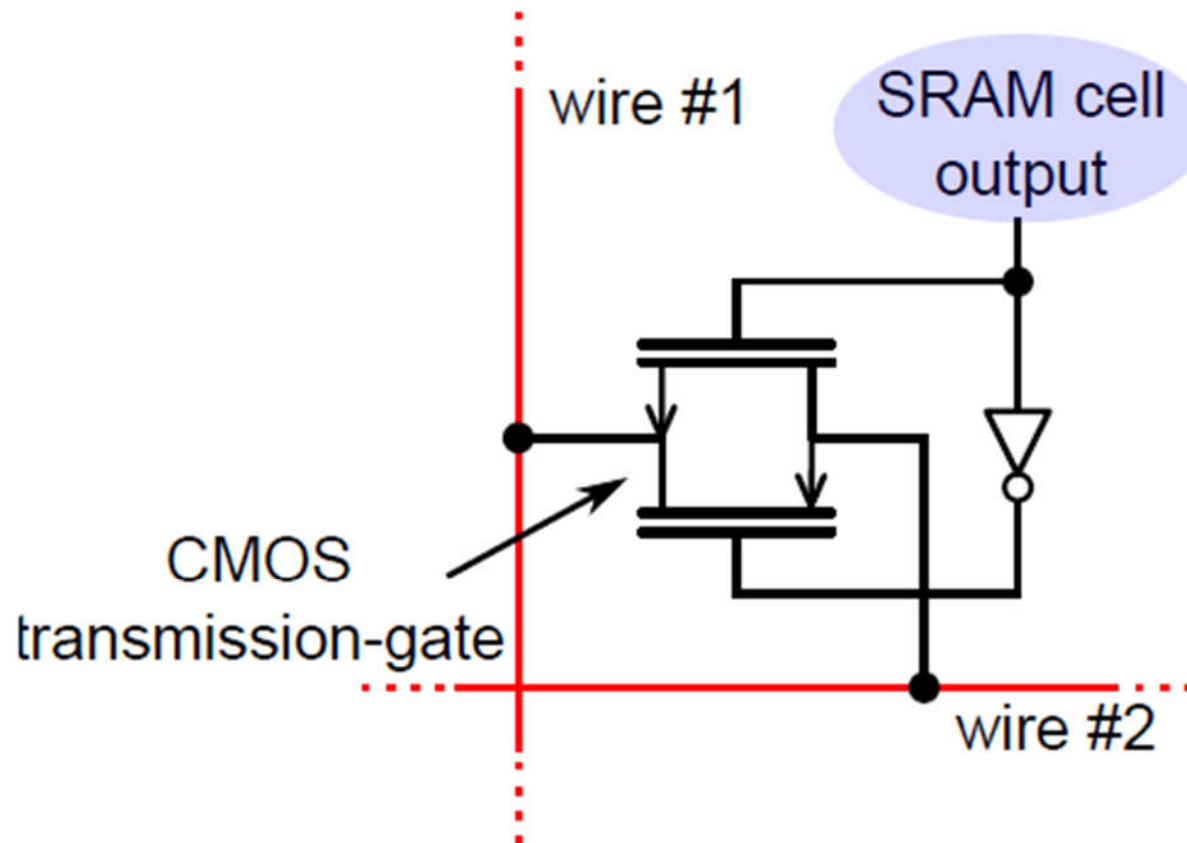
# Implementing programmable interconnections

15

- ❑ **SRAM + transmission-gate**: A **transmission-gate** is placed between the wires, whose gate is connected to a specific SRAM configuration bit. The configuration can be changed **by the user**.





## ❑ Static – SRAM

- data is stored as long as voltage supply is enabled
- large cells (6 FETs/cell) → fewer bits/chip
- fast → used where speed is important (e.g., caches)

  
## ❑ Dynamic – DRAM

- periodic refresh required (every 1 to 4 ms)
- small cells (1 FET/cell) → more bits/chip
- slower → used for main memories


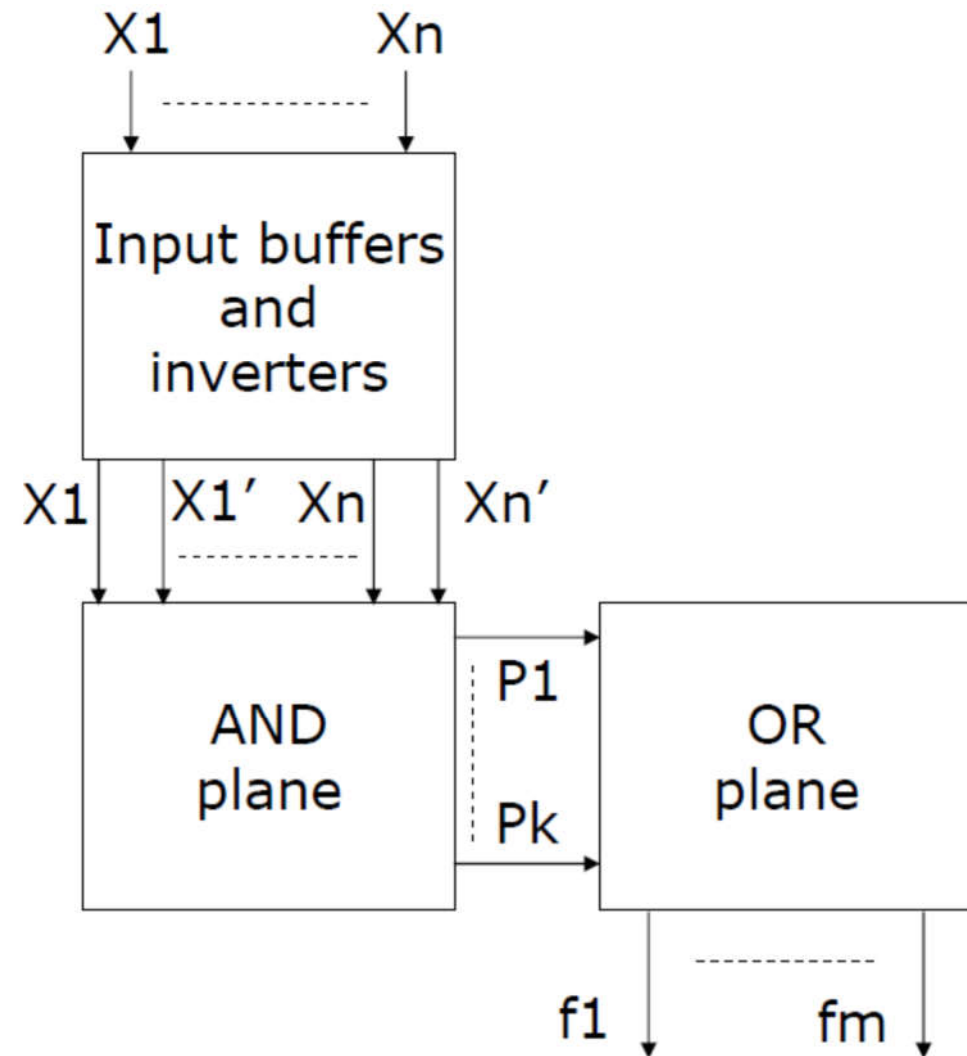
# Programmable Logic Array (PLA)

- ❑ The first PLD developed was the ***programmable logic array*** (PLA)
- ❑ Based on the premise that any function can be written in SOP form, a PLA consists of:
  - Input buffers and inverters that provide the true and complement form for each input variable
  - A collection of AND gates, with inputs that are selectable (programmable)
  - A collection of OR gates, with inputs that are selectable programmable)




# Gate-level diagram of a PLA

Pre-fabricated building block of many AND/OR gates

“Personalized” by making/breaking connections among the gates

 Programmable array block diagram for sum of products form



## ❑ Shared product terms among outputs

example:

$$F0 = A + B' C'$$

$$F1 = A C' + A B$$

$$F2 = B' C' + A B$$

$$F3 = B' C + A$$

personality matrix

product term	inputs			outputs			
	A	B	C	F0	F1	F2	F3
AB	1	1	–	0	1	1	0
B'C	–	0	1	0	0	0	1
AC'	1	–	0	0	1	0	0
B'C'	–	0	0	1	0	1	0
A	1	–	–	1	0	0	1

input side:

1 = uncomplemented in term

0 = complemented in term

– = does not participate


output side:

1 = term connected to output

0 = no connection to output

reuse of terms

 - ❑ Assume that all possible connections are available before "programming"






# After programming

21


- ❑ Unwanted connections are "blown"

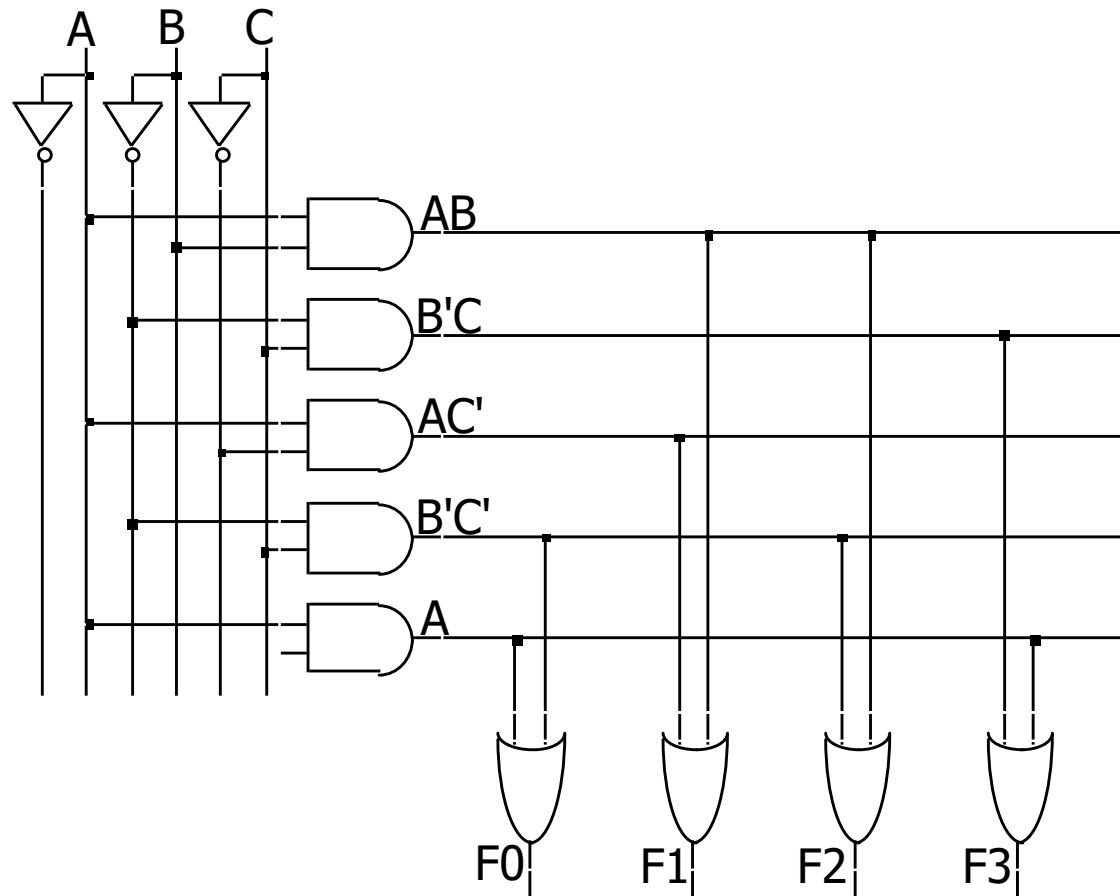

$$\begin{aligned} F0 &= A + B' C' \\ F1 &= A C' + A B \\ F2 &= B' C' + A B \\ F3 &= B' C + A \end{aligned}$$
 
# Alternate representation for high fan-in structures


- ❑ Short-hand notation so we don't have to draw all the wires
  - × signifies a connection is present and perpendicular signal is an input to gate



notation for implementing

$$F0 = A B + A' B'$$

$$F1 = C D' + C' D$$

 


# Programmable logic array example

## Multiple functions of A, B, C


- $F1 = A B C$
- $F2 = A + B + C$
- $F3 = A' B' C'$
- $F4 = A' + B' + C'$
- $F5 = A \text{ xor } B \text{ xor } C$
- $F6 = A \text{ xnor } B \text{ xnor } C$

A	B	C	F1	F2	F3	F4	F5	F6
0	0	0	0	0	1	1	0	0
0	0	1	0	1	0	1	1	1
0	1	0	0	1	0	1	1	1
0	1	1	0	1	0	1	0	0
1	0	0	0	1	0	1	1	1
1	0	1	0	1	0	1	0	0
1	1	0	0	1	0	1	0	0
1	1	1	1	1	0	0	1	1

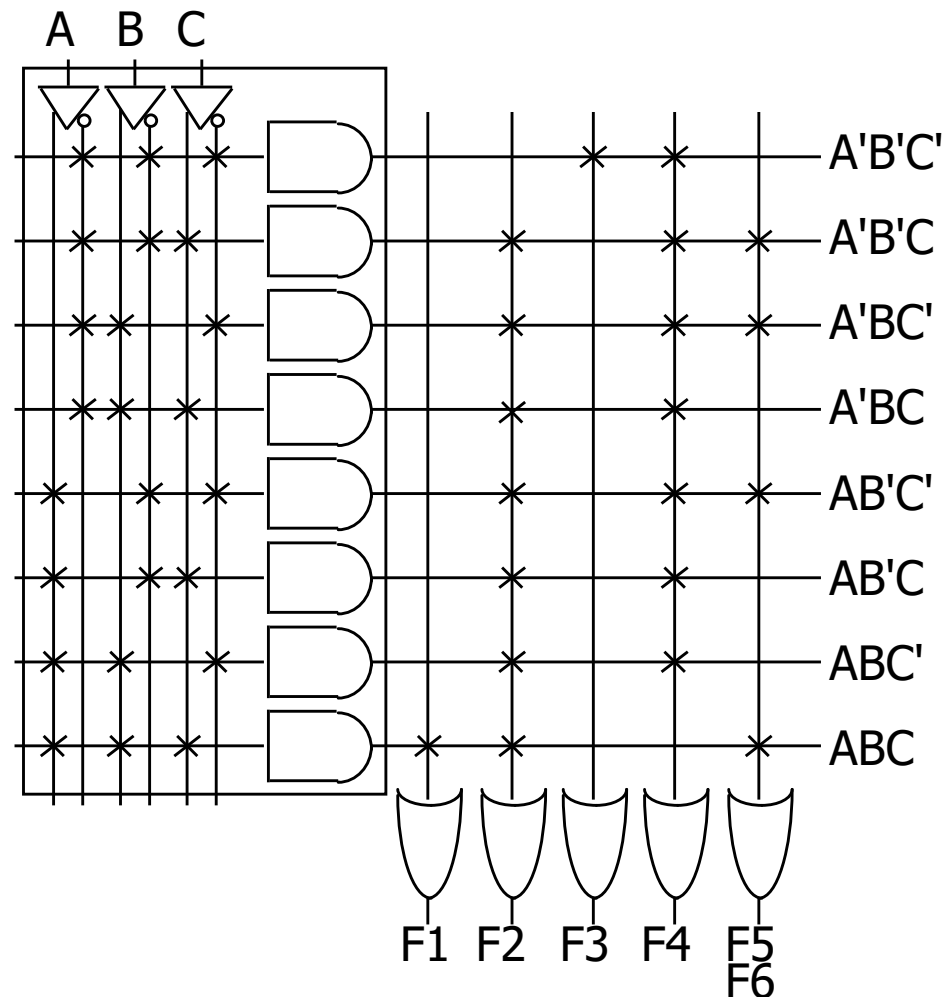

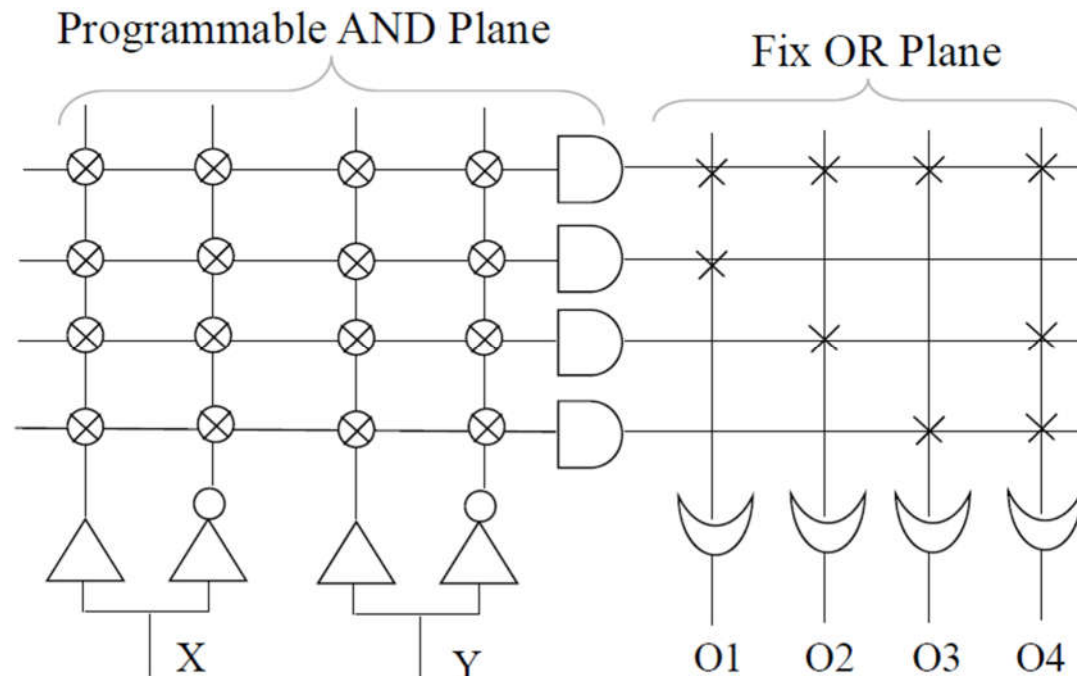
# Programmable Array Logic (PAL)

- ❑ The PAL (programmable array logic) is a special case of the programmable logic array in which the AND array is programmable and the OR array is fixed.
- ❑ The basic structure of the PAL is the same as the PLA.
- ❑ Because only the AND array is programmable, the PAL is less expensive than the more general PLA, and the PAL is easier to program.


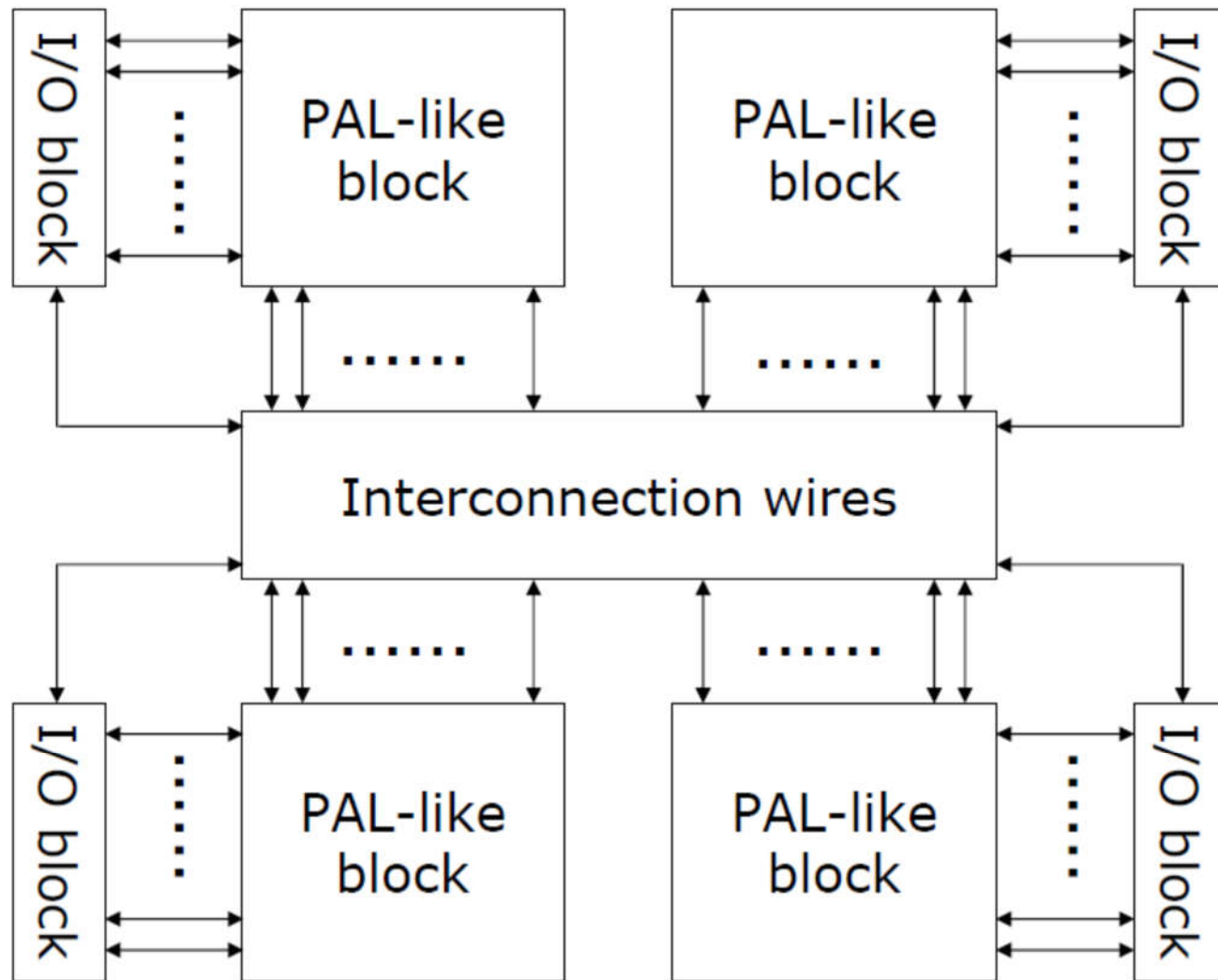
# Complex Programmable Logic Device (CPLD)

- ❑ For larger designs that single PLAs or PALs cannot accommodate, a **complex programmable logic device** (CPLD) can be utilized



# Complex Programmable Logic Devices (CPLD)

26


- ❑ A CPLD consists of multiple circuit blocks with internal wiring to connect the blocks together and to the pins on the chip
- ❑ Each circuit block is similar to a PAL
  - PAL-like blocks
- ❑ Commercial CPLDs have from 2 to more than 100 PAL-like blocks, with 16 macrocells in each block
  - Each macrocell is the equivalent of approximately 20 gates
  - About 20,000 equivalent gates in a CPLD of 1000 macrocells
- ❑ Can construct moderately large logic circuits in a single chip


 
# Field Programmable Gate Arrays

---

- ❑ To implement even larger circuits, need to use a different chip that has an even larger logic capacity:
  - **An Field Programmable Gate Array (FPGA)** introduced by *Xilinx Inc.* in 1985.
  - Misleading name - there is no array of gates.
  - Does not contain AND and OR planes.
  - Consists of general purpose and application specific logic elements, connection resources, and I/O resources.
  - Capable of implementing logic functions of millions of equivalent gates.
  - FPGAs can be programmed by the user "in the field".



# What FPGA can do?

---

- ❑ Can you use your Intel processor as an AMD processor tomorrow and again as an Intel processor the day after tomorrow?
- ❑ You receive software updates frequently, did you ever received a hardware update? Can you upgrade your core i5 to core i7?
- ❑ Can you fix a bug in your chip after you have already received it?



# How Do FPGAs Work?


---

- ❑ FPGAs offer **device-wide reprogrammability**, which is achieved by:
  - ❑ Programmable **logic blocks**
    - Performs computation
  - ❑ Programmable **routing**
    - Connects computation (logic blocks) inside the chip fabric
  - ❑ Programmable **interface (I/O)**
    - Connects to the outside world
    - Various I/O standards and speeds supported

# Basic FPGA Architecture

---

30

 

## Other Components in Modern FPGAs


---

- ❑ Modern FPGAs are not limited to only LUTs, routing, and I/Os.
- ❑ **Memory blocks** (e.g., 16384 bits per block) are available in basically all modern FPGAs.
- ❑ **Hardwired multipliers** (often called DSP blocks, e.g.,  $18 \times 18$ -bit multiplier) can be used to speed up multiplication
- ❑ Many FPGAs have **hardwired processor cores** (ARM Cortex-A9, Cortex-A53) embedded into the chip
- ❑ PLLs, Ethernet MACs, PCI Express, ADCs, . . .
- ❑ More on this later.



# Modern FPGA Architecture


32

 


 
# How can we implement any circuit in an FPGA?

- ❑ First, focus on combinational logic
- ❑ Combinational logic represented by truth table
- ❑ What kind of hardware can implement a truth table?
- ❑ Example: Half adder




Input		Out
A	B	S
0	0	0
0	1	1
1	0	1
1	1	0


Input		Out
A	B	C
0	0	0
0	1	0
1	0	0
1	1	1
 
# Look-up-tables (LUTs)

- ❑ Implement truth table in small memories



 $n$  words  $\rightarrow n$  select signals




Decoder reduces # of inputs

$$k = \log_2 n$$

# Look-up-tables (LUTs)



- ❑ Implement truth table in small memories

Usually SRAM

 

**Logic inputs connect to address inputs, logic output is memory output**


A	B	S
0	0	0
0	1	1
1	0	1
1	1	0

  

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1




2-input,  
1-output  
LUTs

 

 
# Look-up-tables (LUTs)

- ❑ Alternatively, could have used a 2-input, 2-output LUT
  - Outputs commonly use same inputs


 
# Look-up-tables (LUTs)

- ❑ The great thing about an **n-input LUT** is that it **can implement any possible n-input combinatorial logic function**.
- ❑ Full adder example → 3-input, 2-output LUT



*Truth Table*

Inputs			Outputs	
A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

*3-input, 2-output LUT*

	0	0
A	1	0
B	1	0
Cin	0	1
	1	0
	0	1
	0	1
	1	1
	S	Cout


# Look-up-tables (LUTs)

---

- ❑ Why aren't FPGAs just a big LUT?
  - Size of truth table grows exponentially based on # of inputs
    - 3 inputs = 8 rows, 4 inputs = 16 rows, 5 inputs = 32 rows, etc.
  - Same number of rows in truth table and LUT
  - LUTs grow exponentially based on # of inputs
- ❑ Number of SRAM bits in a LUT =  $2^i * o$ 
  - $i$  = # of inputs,  $o$  = # of outputs
  - Example: 64 input combinational logic with 1 output would require  $2^{64}$  SRAM bits
    - $1.84 \times 10^{19}$
- ❑ Clearly, not feasible to use large LUTs
  - So, how do FPGAs implement logic with many inputs?

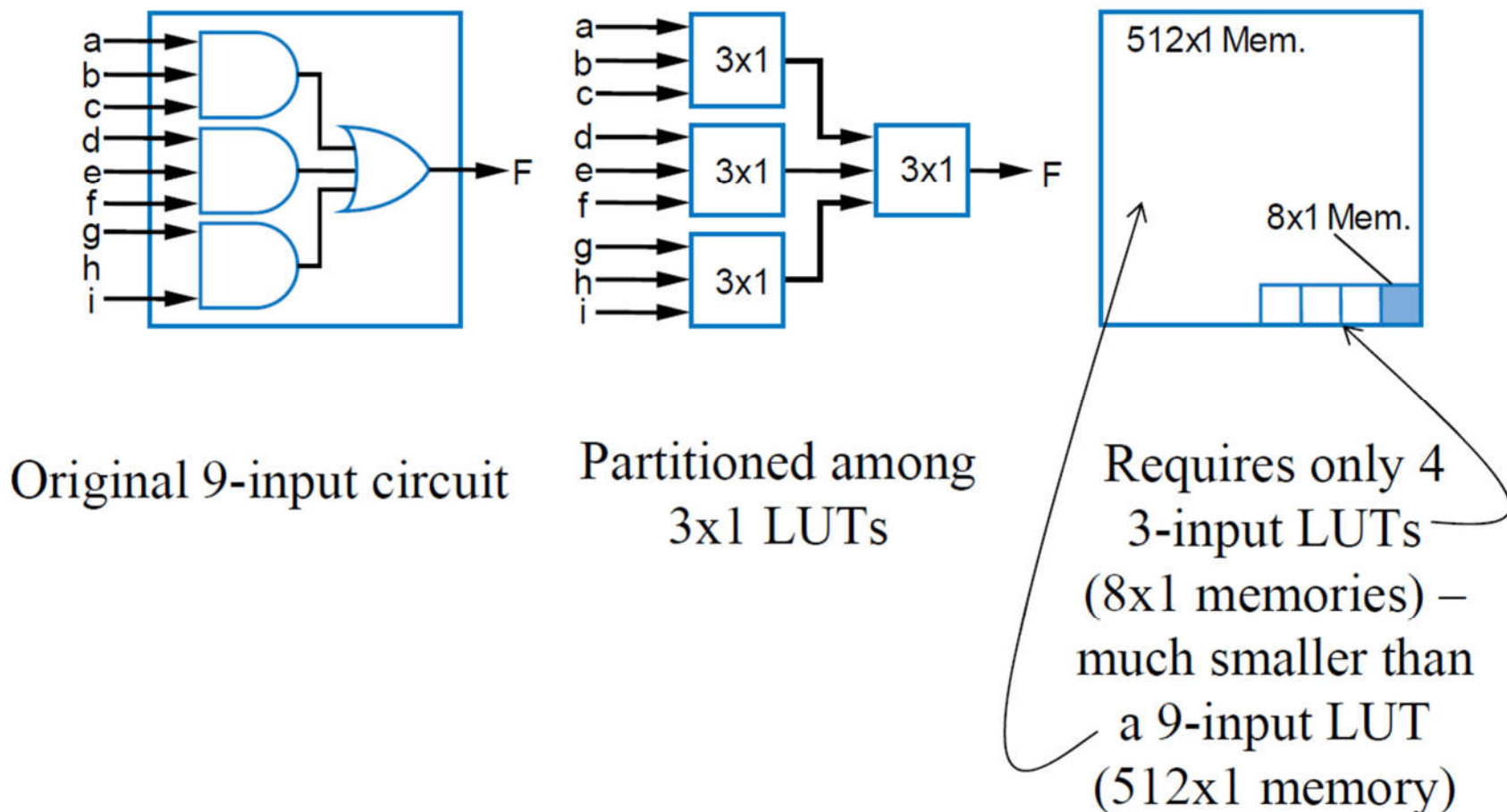
# Look-up-tables – Partitioning

- ❑ Fortunately, we can map circuits onto multiple LUTs
  - Divide circuit into smaller circuits that fit in LUTs (same # of inputs and outputs)
  - Example: 9-input circuit
  - Partitioning among smaller LUTs is more size efficient


 
## Partitioning LUTs – Example 2


- ❑ FPGAs thus have numerous small (3, 4, 5, or even 6-input) LUTs
- ❑ If circuit has more inputs, must partition circuit among LUTs




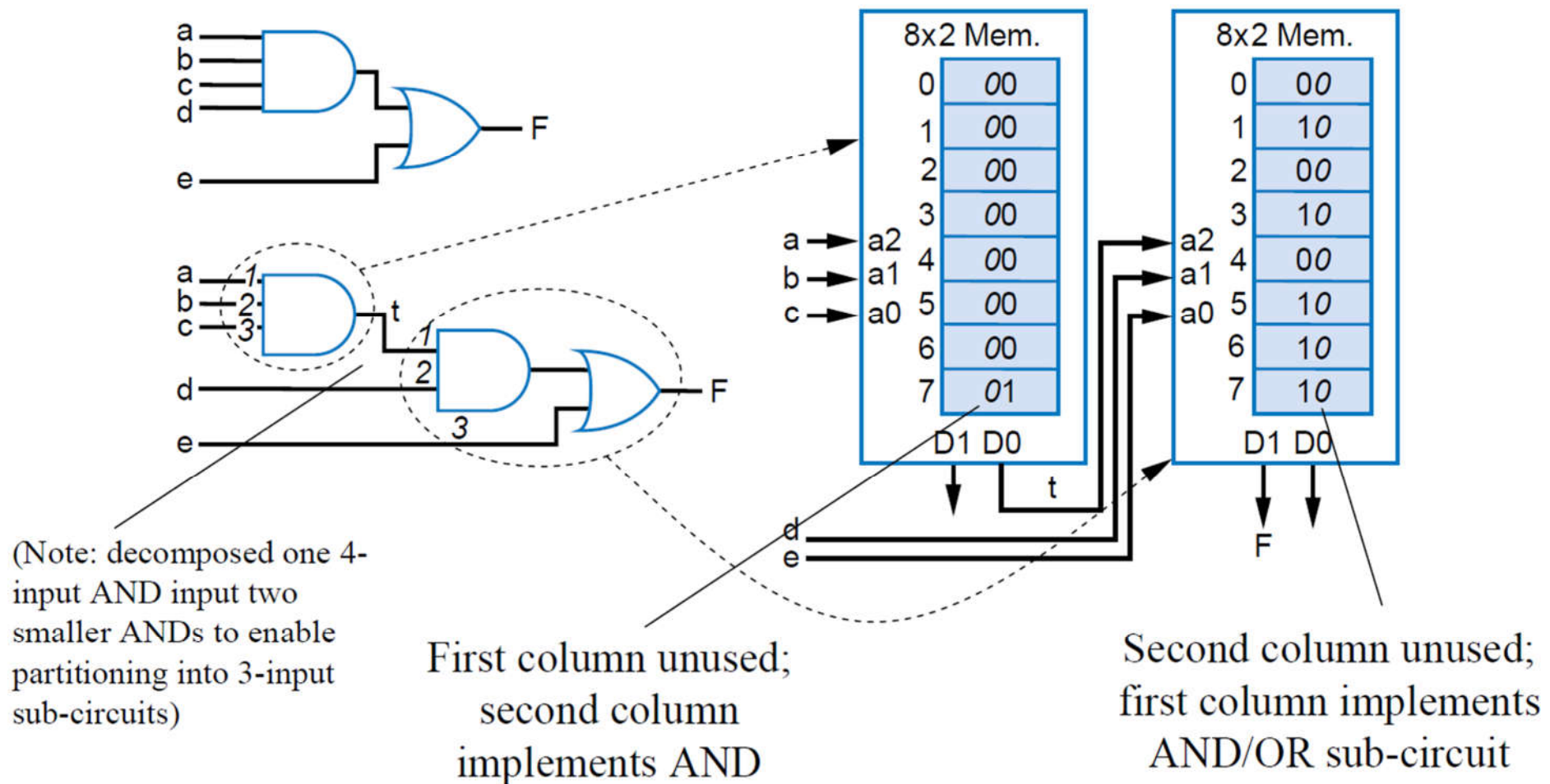
# Partitioning LUTs – Example 3

- ❑ LUT typically has 2 (or more) outputs, not just one
- ❑ Partitioning a circuit among 3-input 2-output lookup tables





# Look-up-tables (LUTs)

---
  
## ❑ Important Point

The number of gates in a circuit has no effect on the mapping into a LUT

- All that matters is the number of inputs and outputs
- Unfortunately, it isn't common to see large circuits with a few inputs



***Both of these circuits can be implemented in a single 3-input, 1-output LUT***

# Look-up-tables

---

## ❑ What if circuit doesn't map perfectly?

More inputs in LUT than in circuit

- Truth table handles this problem
- Unused inputs are ignored

More outputs in LUT than in circuit

- Extra outputs simply not used
  - Space is wasted, so should use multiple outputs whenever possible

## ❑ Many successful FPGA architectures are based on 4-input LUT.

## ❑ Mixture of different LUT sizes is possible but uniformity and regularity are preferred by synthesis tools.

## ❑ Very fast moving sector so things may change in the near future.

# Typical Applications for FPGAs

---

- ❑ Communications, both wired and wireless
- ❑ Industrial control systems
- ❑ Robotics, motor control
- ❑ Defence and Military
- ❑ Healthcare, especially imaging
- ❑ “Big Data” applications (genetics, financial)
- ❑ Artificial Intelligence and Machine Learning
- ❑ ASIC prototyping

# Advantages of FPGAs

---

- ❑ Off-the-shelf
- ❑ Flexibility
- ❑ Upgradability
- ❑ Low cost for small projects
- ❑ Short Time to the market
- ❑ Prototyping
- ❑ High performance DSP algorithms


## Disadvantages of FPGAs

---

- ❑ Wastage of on-chip resources in programmable routing
- ❑ High power consumption compared to the same implementation on full custom design
- ❑ Low operating speed compared to the same implementation on full custom design

# COMPARISON OF TECHNOLOGIES

47

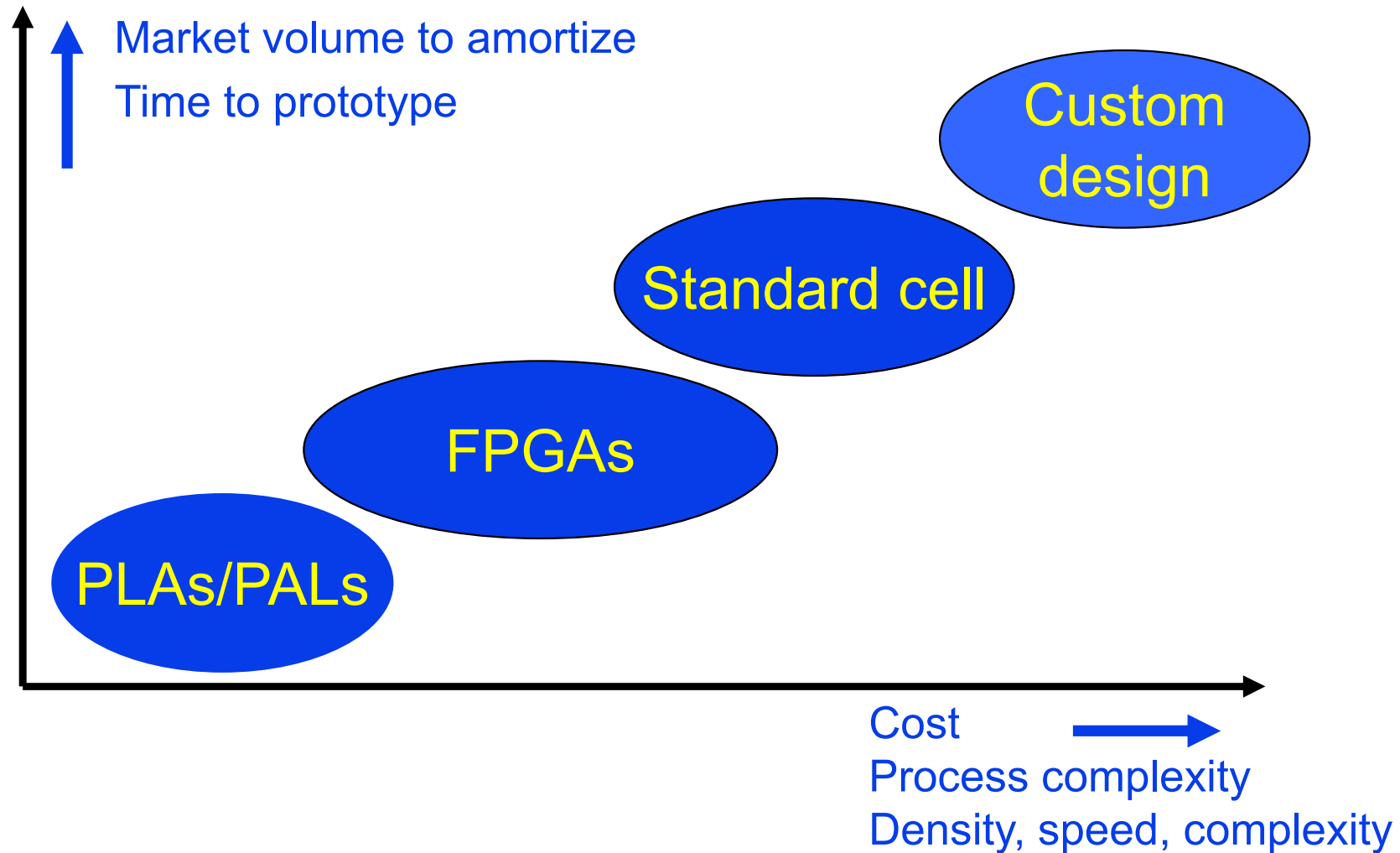

# Acknowledgments

---

- ❑ Credit is acknowledged where credit is due.  
Please refer to the full list of references.