

**12.5** For a Y-connected load, the time-domain expressions for three line-to-neutral voltages at the terminals are:

$$v_{AN} = 120 \cos(\omega t + 32^\circ) \text{ V}$$

$$v_{BN} = 120 \cos(\omega t - 88^\circ) \text{ V}$$

$$v_{CN} = 120 \cos(\omega t + 152^\circ) \text{ V}$$

Write the time-domain expressions for the line-to-line voltages  $v_{AB}$ ,  $v_{BC}$ , and  $v_{CA}$ .

**Solution:**


$$v_{AB} = 120\sqrt{3} \cos(\omega t + 32^\circ + 30^\circ) = 207.8 \cos(\omega t + 62^\circ)$$

$$v_{BC} = 207.8 \cos(\omega t - 58^\circ)$$

$$v_{CA} = 207.8 \cos(\omega t + 182^\circ) = 207.8 \cos(\omega t - 178^\circ)$$
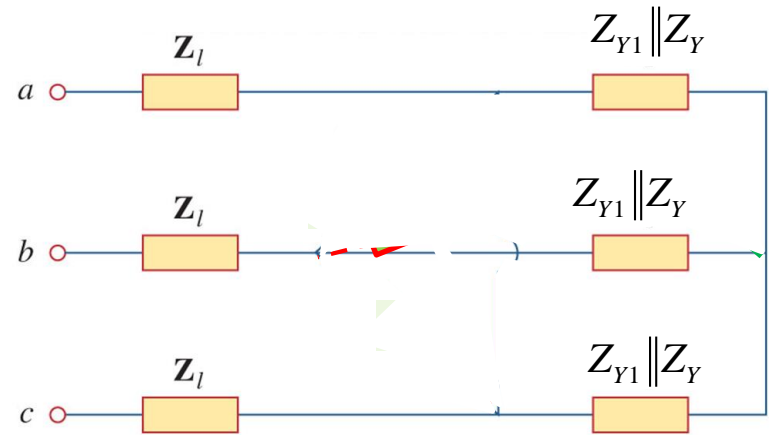
## Problem 12.15 P546

The circuit in Fig. 12.48 is excited by a balanced three-phase source with a line voltage of 210 V. If  $Z_l = 1 + j1 \Omega$ ,  $Z_\Delta = 24 - j30 \Omega$ , and  $Z_Y = 12 + j5 \Omega$ , determine the magnitude of the line current of the combined loads.



**Solution:**  $Z_\Delta \Rightarrow Z_{Y1}$


$$Z_{Y1} = \frac{1}{3} Z_\Delta = 8 - j10 \Omega$$

$$\begin{aligned} \text{So : } Z_{Ytotal} &= Z_l + Z_{Y1} \parallel Z_Y = 1 + j1 + (8 - j10) \parallel (12 + j15) \\ &= 8.874 \angle -7^\circ \end{aligned}$$

$$\text{Then : } I_l = \frac{210 / \sqrt{3}}{|Z_{Ytotal}|} = 13.66 \text{ A}$$
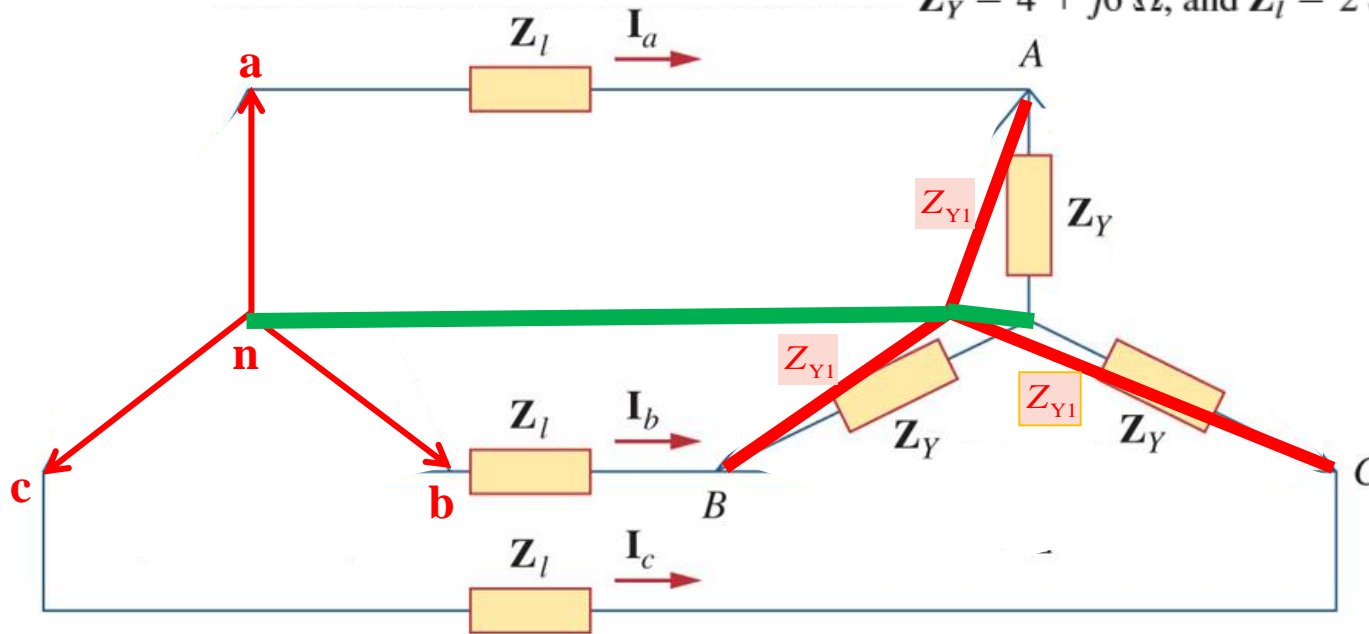
## Problem 12.22 P547

Find the line currents  $I_a$ ,  $I_b$ , and  $I_c$  in the three-phase network of Fig. 12.53 below. Take  $Z_\Delta = 12 - j15 \Omega$ ,  $Z_Y = 4 + j6 \Omega$ , and  $Z_l = 2 \Omega$ .



**Solution:**  $Z_\Delta \Rightarrow Z_{Y1}: Z_{Y1} = \frac{1}{3} Z_\Delta = 4 - j5 \Omega$

$$Z_{Ytotal} = Z_l + Z_{Y1} \parallel Z_Y = 2 + (4 - j5) \parallel (4 + j6) = 7.723 - j0.215$$

$$V_{an} = \frac{440 \angle 0^\circ}{\sqrt{3} \angle 30^\circ} = 254 \angle -30^\circ$$

$$I_a = \frac{V_{an}}{Z_{Ytotal}} = 32.88 \angle -28^\circ$$

$$I_b = I_a \angle -120^\circ = 32.88 \angle -148^\circ$$

$$I_c = I_a \angle 120^\circ = 32.88 \angle 92^\circ$$

**12.47** The following three parallel-connected three-phase loads are fed by a balanced three-phase source:

Load 1: 250 kVA, 0.8 pf lagging

Load 2: 300 kVA, 0.95 pf leading

Load 3: 450 kVA, unity pf

If the line voltage is 13.8 kV, calculate the line current and the power factor of the source. Assume that the line impedance is zero.

### Solution:

$$S_1 = 250 \text{ kVA}$$

$$\text{pf}_1 = 0.8 \text{ lagging}$$

$$\text{So: } \theta_1 = \cos^{-1} 0.8 = 37^\circ$$

$$P_1 = S_1 \times \cos \theta_1 = 200 \text{ kW}$$

$$Q_1 = S_1 \times \sin \theta_1 = 150 \text{ kVAR}$$

$$S_2 = 300 \text{ kVA}$$

$$\text{pf}_2 = 0.95 \text{ leading}$$

$$\text{So: } \theta_2 = -\cos^{-1} 0.95 = -18^\circ$$

$$P_2 = S_2 \times \cos \theta_2 = 285 \text{ kW}$$

$$Q_2 = S_2 \times \sin \theta_2 = -93 \text{ kVAR}$$

$$S_3 = 450 \text{ kVA}$$

$$\text{pf}_3 = 1$$

$$\text{So: } P_3 = 450 \text{ kW}$$

$$Q_3 = 0 \text{ kVAR}$$

$$\begin{aligned} \text{So: } S &= P_1 + P_2 + P_3 + j(Q_1 + Q_2 + Q_3) \\ &= 935 + j57 = 936.7 \angle 3.5^\circ \text{ kVA} \end{aligned}$$

$$\text{As: } |S| = \sqrt{3} V_l I_l$$

$$\Rightarrow I_l = \frac{936.7 \times 10^3}{\sqrt{3} \times 13.8 \times 10^3} = 39.2 \text{ A rms}$$

$$\text{pf} = \cos 3.5^\circ = 0.998 \text{ lagging}$$

$$\text{or: } \text{pf} = \frac{P}{S} = \frac{935}{936.7} = 0.998 \text{ lagging}$$

**12.50** A balanced three-phase source with  $V_L = 240$  V rms is supplying 8 kVA at 0.6 power factor lagging to two wye-connected parallel loads. If one load draws 3 kW at unity power factor, calculate the impedance per phase of the second load.

**Solution:**

$$S = 8 \text{ kVA. pf} = 0.6 \text{ lagging}$$

$$\text{So: } P = S \times \text{pf} = 4.8 \text{ kW}$$

$$Q = \sqrt{S^2 - P^2} = 6.4 \text{ kVAR}$$

$$P_1 = 3 \text{ kW. pf}_1 = 1$$

$$\text{So: } Q_1 = 0 \text{ kVAR}$$

$$\text{So: } P_2 = P - P_1 = 1.8 \text{ kW}$$

$$Q_2 = Q - Q_1 = 6.4 \text{ kVAR}$$

$$\text{So: } S_2 = \sqrt{P_2^2 + Q_2^2} = 6.65 \text{ kVA}$$

$$\text{As: } V_p = \frac{V_L}{\sqrt{3}} = \frac{240}{\sqrt{3}} \text{ V rms}$$

$$S_2 = \frac{3V_p^2}{|Z_2|}$$

$$\text{So: } |Z_2| = \frac{240^2}{6.65 \times 10^3} = 8.66 \Omega$$

$$\theta_{Z_2} = \tan^{-1} \left( \frac{Q_2}{P_2} \right) = \tan^{-1} \left( \frac{6.4}{1.8} \right) = 74^\circ$$

$$\begin{aligned} \text{So: } Z_2 &= |Z_2| \angle \theta_{Z_2} = 8.66 \angle 74^\circ \\ &= 2.39 + j8.32 \Omega \end{aligned}$$