
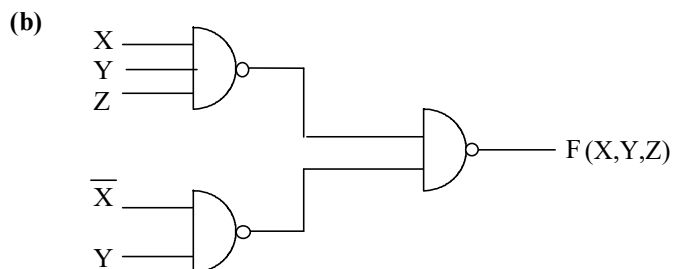


Homework Questions
Circuits and Electronics
Week 1

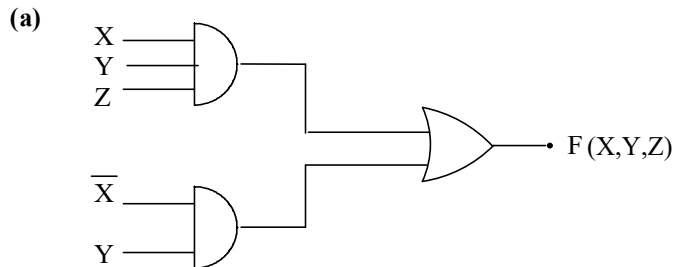Q.1 Determine the truth table for the following logic circuits



(c) What can you say about the above two circuits?

Q.2 Consider the following Boolean function:

$$\overline{F} = \overline{B}D + \overline{A}B\overline{C} + ACD + \overline{A}BC$$

- Find the complement of the Boolean function and reduce it to seven literals in sum-of-products form.
- Using a truth table show that the reduced Boolean function for is equivalent to the original expression.
- Implement the simplified expression using AND, OR and NOT logic gates in a 2-level gate circuit.

Q.3 Use Karnaugh maps to obtain the simplified expressions in sum-of-products form for the following Boolean functions:

- $ABD + \overline{A}\overline{C}\overline{D} + \overline{A}B + \overline{A}C\overline{D} + A\overline{B}\overline{D}$
- $\overline{X}Z + \overline{W}X\overline{Y} + W(\overline{X}Y + X\overline{Y})$

Q.4 Using Karnaugh maps, simplify the following expressions, using sum-of-products form:

$$(a) \quad ABC + \overline{A}\overline{B}C + \overbrace{\overline{A}BC + A\overline{B}C + ABC}^{\text{don't cares}}$$

$$(b) \quad ABCD + \overline{A}\overline{B}CD + \overbrace{\overline{A}BCD + A\overline{B}CD + \overline{A}\overline{B}\overline{C}D}^{\text{don't cares}}$$

$$(c) \quad \overline{A}\overline{B}C\overline{D} + A\overline{B}C\overline{D} + \overbrace{\overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D}}^{\text{don't cares}}$$

Solutions

Q1.

(a) $F = XYZ + \bar{X}Y$

X	Y	Z	XYZ	$\bar{X}Y$	F
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	1	1
0	1	1	0	1	1
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	1	0	1

(b) $F = \overline{(XYZ)} \overline{(\bar{X}Y)}$

X	Y	Z	\overline{XYZ}	$\overline{\bar{X}Y}$	F
0	0	0	1	1	0
0	0	1	1	1	0
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	1	1	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	0	1	1

(c) The two circuits are equivalent

Q2.

(a)

$$\bar{F} = \bar{B}D + \bar{A}B\bar{C} + ACD + \bar{A}BC$$

$$F = (\bar{B}D + \bar{A}B\bar{C} + ACD + \bar{A}BC)$$

$$= (\bar{B}D + \bar{A}B(\bar{C} + C) + ACD)$$

$$= (\bar{B}D + \bar{A}B + ACD)$$

$$= (B + \bar{D})(A + \bar{B})(\bar{A} + \bar{C} + \bar{D})$$

$$= (AB + A\bar{D} + \cancel{B\bar{B}} + \bar{B}\bar{D})(\bar{A} + \bar{C} + \bar{D})$$

$$= \bar{A}\bar{B}\bar{D} + AB\bar{C} + A\bar{C}\bar{D} + \bar{B}\bar{C}\bar{D}$$

$$+ AB\bar{D} + A\bar{D} + \bar{B}\bar{D}$$


$$= \bar{B}\bar{D} [1 + \cancel{\bar{A} + \bar{C}}] + A\bar{D} [1 + \cancel{\bar{C} + B}] + AB\bar{C}$$

$$F = \bar{B}\bar{D} + A\bar{D} + AB\bar{C}$$

(b)


A	B	C	D	$\bar{B}D$	$\bar{A}B\bar{C}$	ACD	$\bar{A}B\bar{C}$	\bar{F}	F
0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	0	0	0	1	0
0	0	1	0	0	0	0	0	0	1
0	0	1	1	0	0	0	0	1	0
0	1	0	0	0	1	0	0	1	0
0	1	0	1	0	0	0	0	1	0
0	1	1	0	0	0	0	1	1	0
0	1	1	1	0	0	0	1	0	1
1	0	0	0	0	0	0	0	1	0
1	0	0	1	1	0	0	0	0	1
1	0	1	0	0	0	1	0	0	0
1	0	1	1	0	0	1	0	0	0
1	1	0	0	0	0	0	0	0	1
1	1	0	1	0	0	0	0	0	1
1	1	1	0	0	0	0	0	0	1
1	1	1	1	0	0	1	0	1	0
A	B	C	D	$\bar{B}D$	$A\bar{D}$	$AB\bar{C}$			F
0	0	0	0	1	0	0			1
0	0	0	1	0	0	0			0
0	0	1	0	0	0	0			1
0	0	1	1	0	0	0			0
0	1	0	0	0	0	0			0
0	1	0	1	0	0	0			0
0	1	1	0	0	0	0			0
0	1	1	1	0	0	0			0
1	0	0	0	1	1	0			1
1	0	0	1	0	1	0			0
1	0	1	0	0	1	0			1
1	0	1	1	0	1	0			0
1	1	0	0	0	0	1			1
1	1	0	1	0	0	1			0
1	1	1	0	0	0	1			1
1	1	1	1	0	0	0			0

(c)

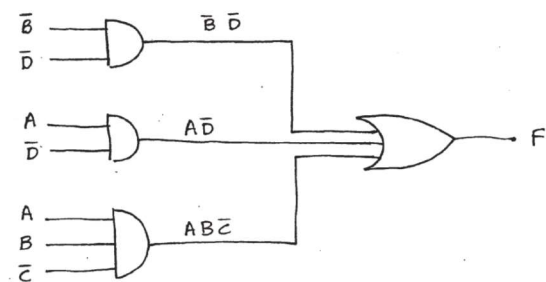

Q3.

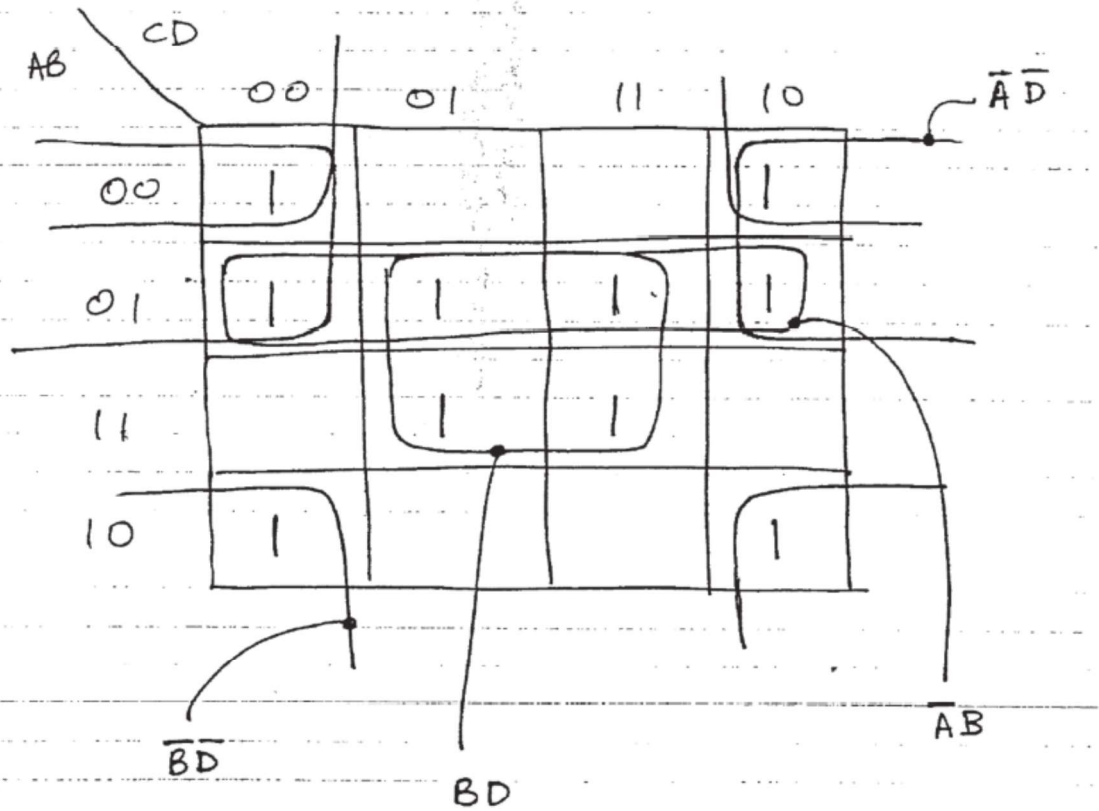(a) $F = ABD + \bar{A}\bar{C}\bar{D} + \bar{A}B + \bar{A}C\bar{D} + \bar{A}\bar{B}\bar{D}$



$$F = \bar{A}\bar{B} + \bar{B}\bar{D} + BD$$

OR $F = \bar{A}\bar{D} + \bar{B}\bar{D} + BD$

(b) $F = \bar{X}Z + \bar{W}X\bar{Y} + W(\bar{X}Y + X\bar{Y})$

$WX \backslash YZ$		00	01	11	10
00			1	1	
01		1	1		
11		1	1		
10			1	1	1

$X\bar{Y}$ (points to cell 11, 01)
 $\bar{X}Z$ (points to cell 11, 11)
 $W\bar{X}Y$ (points to cell 10, 11)

$F = X\bar{Y} + \bar{X}Z + W\bar{X}Y$

Q4.

a)

AB \ C	0	1
00		1
01		X
11	X	1
10		X

$$f = C$$

b)

AB \ CD	00	01	11	10
00	X		1	
01			X	
11			1	
10			X	

$$f = CD$$

c)

AB \ CD	00	01	11	10
00				
01	X	X		
11				
10			1	1

$$f = A\bar{B}C$$