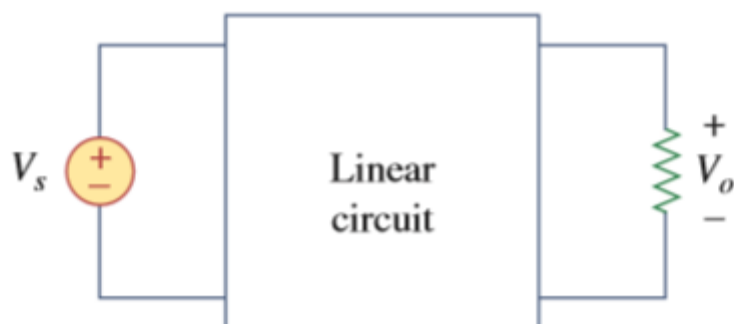


4.6 For the linear circuit shown in Fig. 4.74, use linearity to complete the following table.

Experiment	V_s	V_o
1	12 V	4 V
2		16 V
3	1 V	
4		-2 V





4.6

	V_s	V_o
1	12 V	4 V
2	$4 \times 12 \text{ V} = 48 \text{ V}$	$16 \text{ V} = 4 \times 4 \text{ V}$
3	$1 \text{ V} = \frac{1}{12} \times 12 \text{ V}$	$\frac{1}{12} \times 4 \text{ V} = \frac{1}{3} \text{ V}$
4	$-\frac{1}{2} \times 12 \text{ V} = -6 \text{ V}$	$-2 \text{ V} = -\frac{1}{2} \times 4 \text{ V}$


4.16 Given the circuit in Fig. 4.84, use superposition to obtain i_0 .

第5版

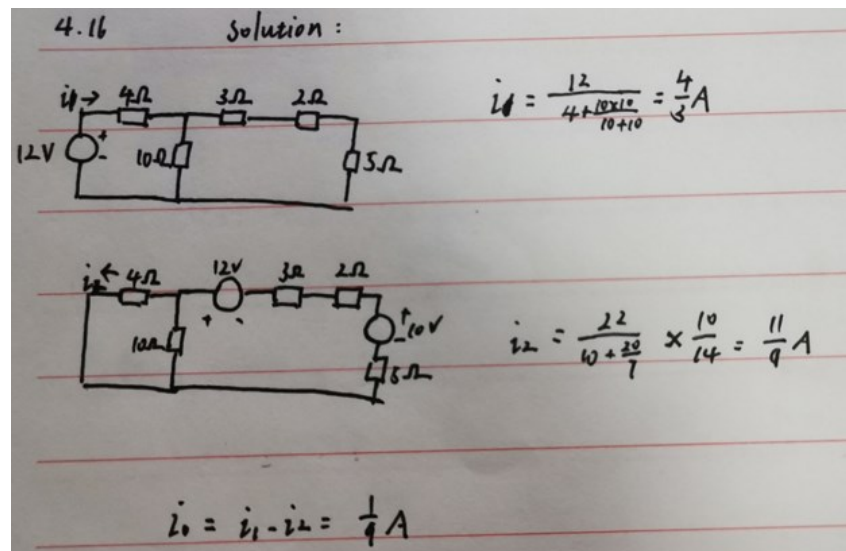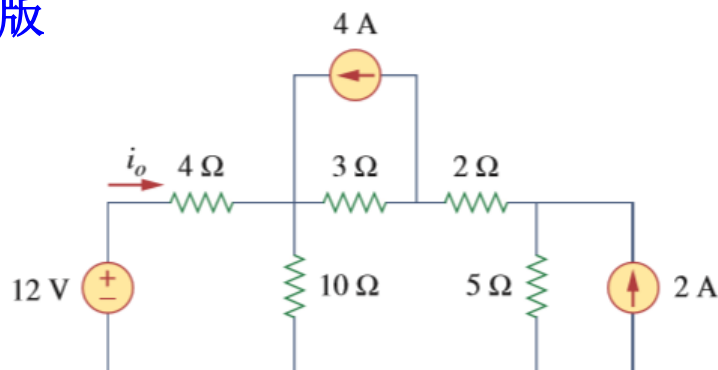


4.16

12-V source only:

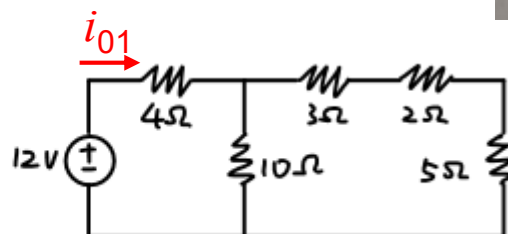

$$i_{01} = \frac{12}{4 + 10 \parallel (3 + 2 + 5)} = \frac{4}{3}$$

Current source only:

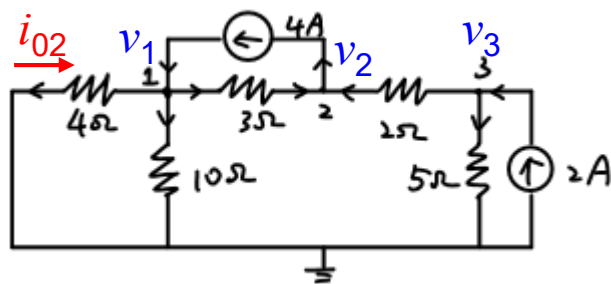


$$\begin{cases} \text{node 1: } \frac{V_1}{4} + \frac{V_1}{10} + \frac{V_1 - V_2}{3} = 4 \text{ A} \\ \text{node 2: } \frac{V_1 - V_2}{3} + \frac{V_2 - V_3}{2} = 4 \text{ A} \\ \text{node 3: } \frac{V_2 - V_3}{2} + \frac{V_3}{5} = 2 \text{ A} \end{cases} \Rightarrow v_1 = \frac{44}{9}$$

$$\text{Then: } i_{02} = -\frac{44}{9 \times 4} = -\frac{11}{9}$$

$$\text{So: } i_0 = i_{01} + i_{02} = \frac{1}{9}$$


第6版 $i_0 = 12 - 11 = 1\text{A}$

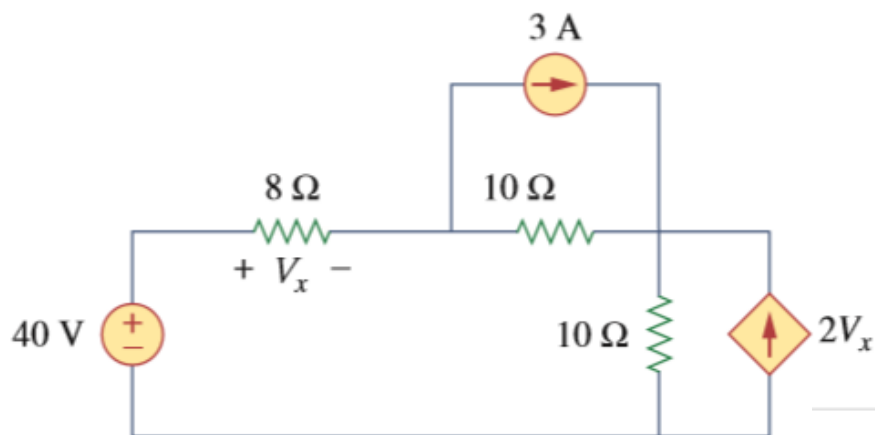4.24 Use source transformation to find the voltage V_x in the circuit of Fig. 4.92.



Solution =

change the circuit =

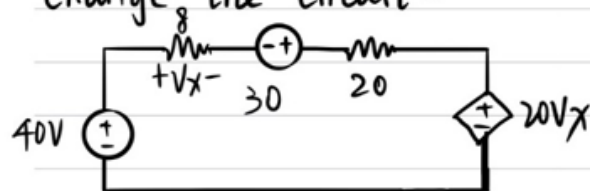

Use KVL =


$$\textcircled{1} \quad i = \frac{V_x}{8}$$

$$\textcircled{2} \quad -40 + V_x - 30 + 20 \times \frac{V_x}{8} + 20V_x = 0$$

$$\text{Result} = V_x = \frac{140}{47} \text{ V}$$

4.36 Solve for the current i in the circuit of Fig. 4.103 using Thevenin's theorem. (*Hint:* Find the Thevenin equivalent seen by the $12\text{-}\Omega$ resistor.)

第5版

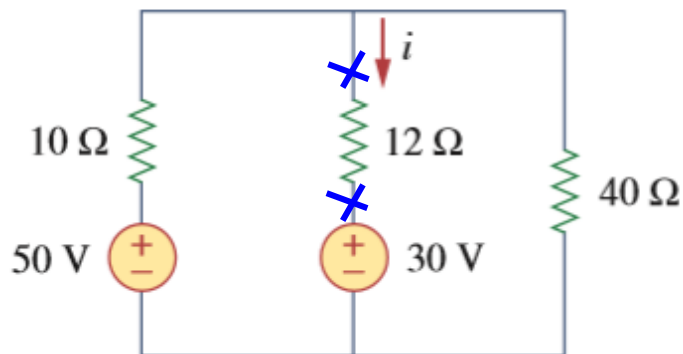


4.36

$$R_{Th} = \frac{1}{\frac{1}{10} + \frac{1}{40}} = 8\Omega$$

$$V_{Th} = \frac{40}{10+40} \times 50V = 40V$$


$$v_{TH} = \frac{40}{10+40} \times 50 - 30 = 10V$$

$$i = \frac{10}{8+12} = 0.5A$$

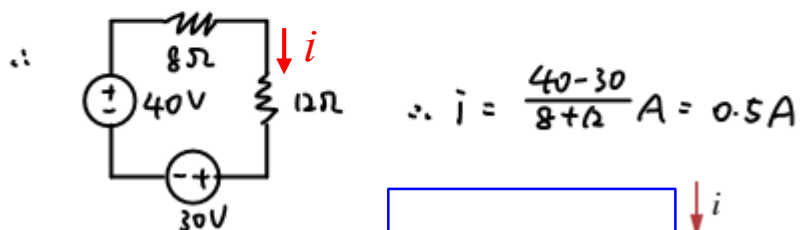


第6版 $i = 3A$


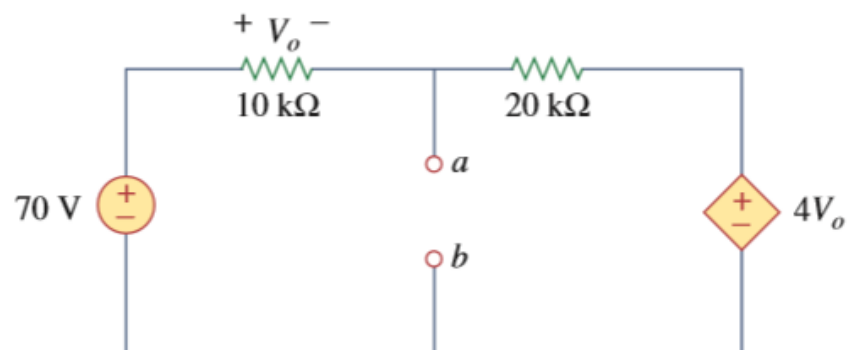
4.40 Find the Thevenin equivalent at terminals a - b of the circuit in Fig. 4.107.



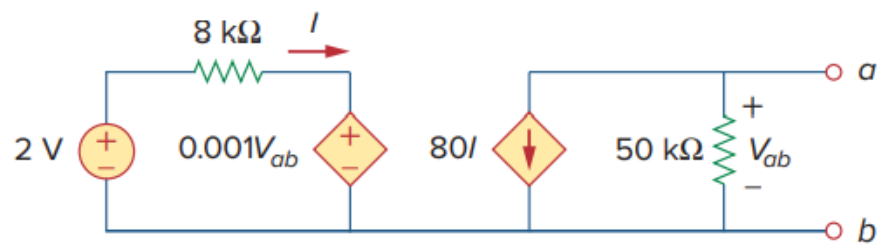***4.55** Obtain the Norton equivalent at terminals a - b of the circuit in Fig. 4.121.



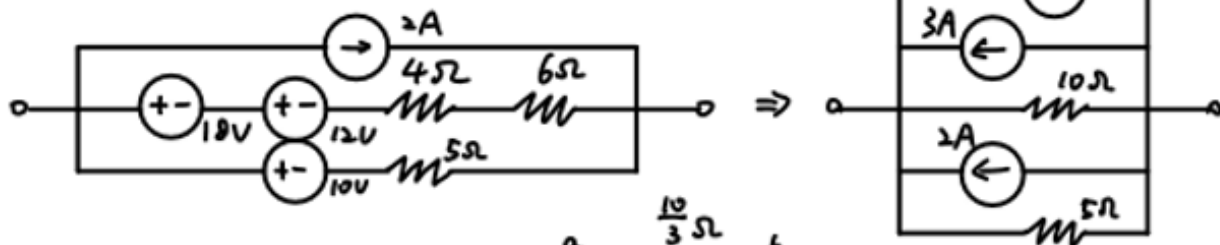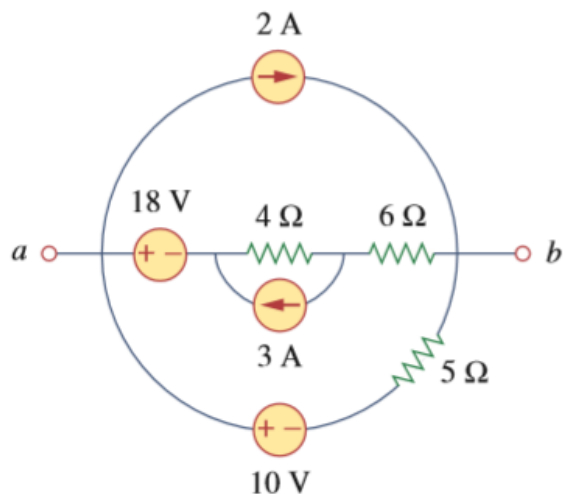
*4.60 For the circuit in Fig. 4.126, find the Thevenin and Norton equivalent circuits at terminals a - b .



$$\therefore I_N = 3 + 2 - 2 = 3A$$

$$R_N = R_{Th} = 10 \parallel 5 = \frac{10}{3}$$

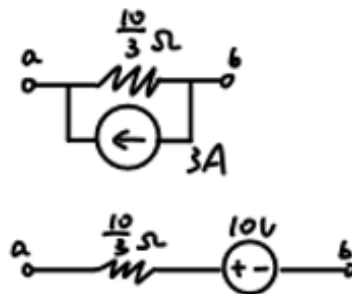
$$\therefore V_{Th} = 3 \times \frac{10}{3} = 10V$$



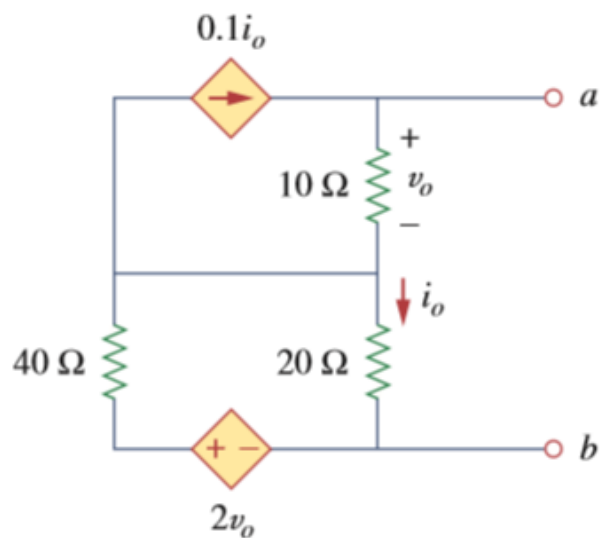*4.62 Find the Thevenin equivalent of the circuit in

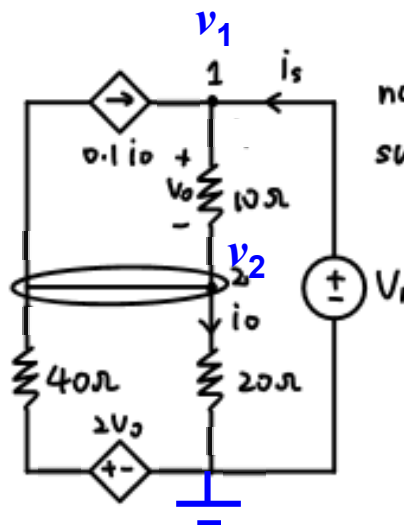


Fig. 4.128.



4.62

R_{Th} :



$$\text{node 1: } i_s + 0.1 i_o = \frac{V_1 - V_2}{10}$$

$$\text{supernode 2: } \frac{V_1 - V_2}{10} + \frac{2V_0 - V_2}{40} = 0.1 i_o + \frac{V_2}{20}$$


$$i_o = \frac{V_2}{20}$$

$$V_0 = V_1 - V_2$$

$$\therefore V_2 = \frac{15}{23} V_1 \quad i_o = \frac{3}{92} V_1$$

$$\therefore i_s = \frac{29}{920} V_1$$
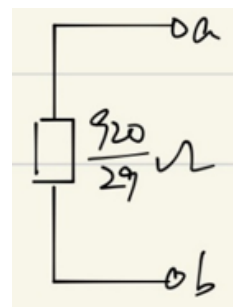
$$R_{Th} = \frac{V_1}{i_s} = \frac{920}{29} \Omega \approx 31.72 \Omega$$



$$V_{Th} = 0V$$

4.67 The variable resistor R in Fig. 4.133 is adjusted until it absorbs the maximum power from the circuit.


(a) Calculate the value of R for maximum power.

(b) Determine the maximum power absorbed by R .

第6版

$$R = 25\text{k}\Omega$$


$$p_{\max} = 49\text{mW}$$

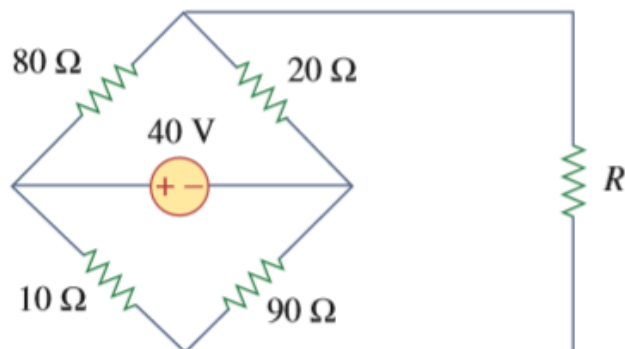

第5版


4.67

(a.) :

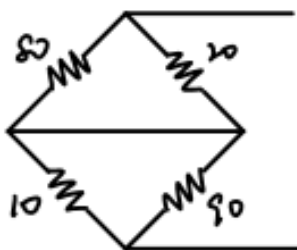

$$R_{Th} = (80 // 20) + (10 // 90) = 25 \Omega = R$$

(b.) :

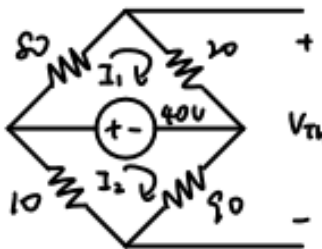


$$(80 + 20)I_1 = 40 \quad \therefore I_1 = 0.4\text{A}$$

$$(10 + 90)I_2 = -40 \quad \therefore I_2 = -0.4\text{A}$$


$$\therefore V_{Th} = 20I_1 + 90I_2 = 8 - 36 = -28\text{V}$$


$$P = \frac{V_{Th}^2}{4R_{Th}} = \frac{(-28)^2}{4 \times 25} = 7.84\text{W}$$

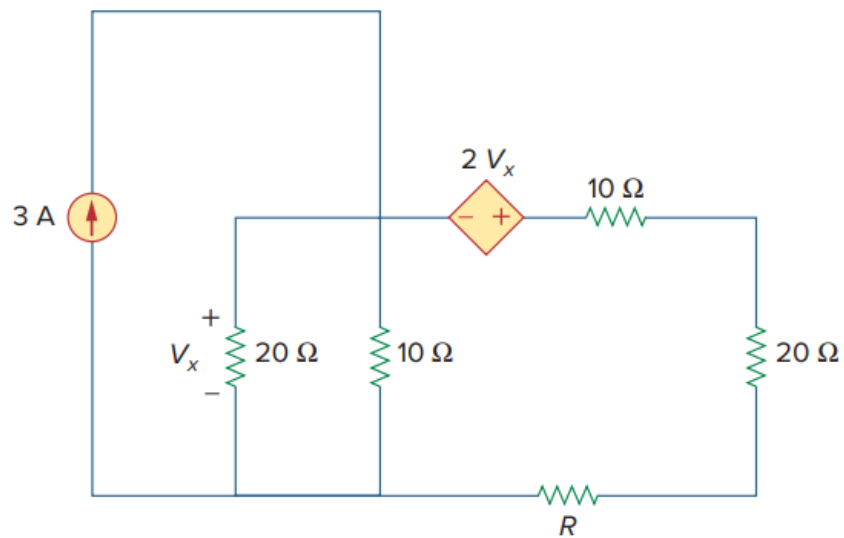
4.70 Determine the maximum power delivered to the variable resistor R shown in the circuit of Fig. 4.136.



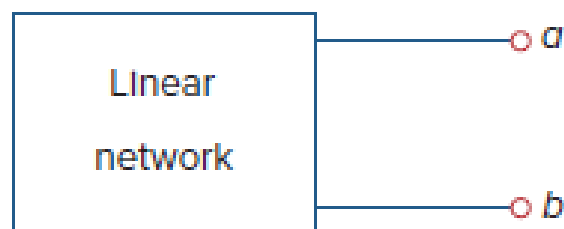- 4.85 The Thevenin equivalent at terminals a - b of the linear network shown in Fig. 4.142 is to be determined by measurement. When a $10\text{-k}\Omega$ resistor is connected to terminals a - b , the voltage V_{ab} is measured as 20 V. When a $30\text{-k}\Omega$ resistor is connected to the terminals, V_{ab} is measured as 40 V. Determine: (a) the Thevenin equivalent at terminals a - b , (b) V_{ab} when a $20\text{-k}\Omega$ resistor is connected to terminals a - b .



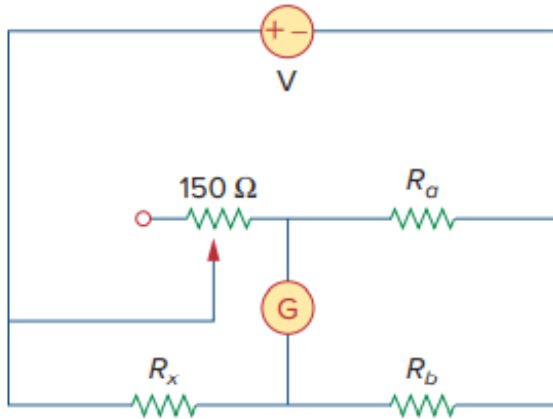- 4.91** (a) In the Wheatstone bridge circuit of Fig. 4.147
 select the values of R_a and R_b such that the bridge can measure R_x in the range of 0–25 Ω .
 (b) Repeat for the range of 0–250 Ω .



Solution:

The condition of The bridge is balanced is :

$$R_a R_x = R_b R_{0-150}$$

(a) When $R_{0-150} = 150\Omega$

$$R_x = 25\Omega$$

We get: $R_a = 6 R_b$

Such,we select : $R_b = 10\Omega$, $R_a = 60\Omega$

(b) When $R_{0-150} = 150\Omega$

$$R_x = 250\Omega$$

We get: $R_a = 3/5 R_b$

Such,we select : $R_b = 10\Omega$, $R_a = 6\Omega$