

Problem 14.30 P665

14.30 A circuit consisting of a coil with inductance 10 mH and resistance 20 Ω is connected in series with a capacitor and a generator with an rms voltage of 120 V. Find:

- (a) the value of the capacitance that will cause the circuit to be in resonance at 15 kHz
- (b) the current through the coil at resonance
- (c) the Q of the circuit

Solution:

$$(a) \omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow C = \frac{1}{\omega_0^2 L} = \frac{1}{(2\pi \times 15 \times 10^3)^2 \times 10 \times 10^{-3}} = 11.27 \text{ pF}$$

$$(b) I = \frac{V}{R} = \frac{120}{20} = 6 \text{ A rms}$$

$$(c) Q = \frac{\omega_0 L}{R} = \frac{2\pi \times 15 \times 10^3 \times 10 \times 10^{-3}}{20} = 47$$

$$(d) P(\omega_0) = I^2 R = 6^2 \times 20 = 720 \text{ W}$$

$$P(\omega_1) = P(\omega_2) = \frac{1}{2} P(\omega_0) = 360 \text{ W}$$

Problem 14.40 P665 14.40

A parallel resonance circuit has a resistance of $2\text{ k}\Omega$ and half-power frequencies of 86 kHz and 90 kHz . Determine:

- (a) the capacitance
- (b) the inductance
- (c) the resonant frequency
- (d) the bandwidth
- (e) the quality factor

Solution:

$$\omega_0 = \frac{1}{2}(2\pi f_1 + 2\pi f_2) = 3.14 \times 10^3(86 + 90) = 552.6 \text{ krad/s}$$

$$B = 2\pi f_2 - 2\pi f_1 = 2 \times 3.14 \times 10^3(90 - 86) = 25.12 \text{ krad/s}$$


$$Q = \frac{\omega_0}{B} = \frac{552.6}{25.12} = 22$$

$$B = \frac{1}{RC} \Rightarrow C = \frac{1}{BR} = \frac{1}{25.12 \times 10^3 \times 2 \times 10^3} = 19.9 \text{ pF}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega_0^2 C} = \frac{1}{(552.6 \times 10^3)^2 \times 19.9 \times 10^{-9}} = 164.5 \text{ uH}$$

Problem 14.48 P666

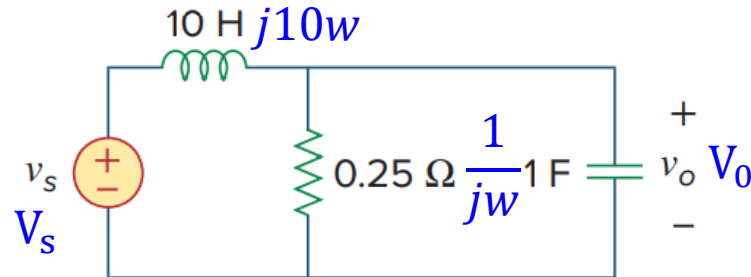14.48 Find the transfer function V_o/V_s of the circuit in Fig. 14.86. Show that the circuit is a lowpass filter.



Solution:


$$H(\omega) = \frac{V_o}{V_s} = \frac{0.25 \parallel \frac{1}{j\omega}}{j10\omega + 0.25 \parallel \frac{1}{j\omega}} = \frac{1}{j40\omega - 10\omega^2 + 1}$$

$$H(0) = 1, \quad H(\infty) = 0$$

So it is a lowpass filter.

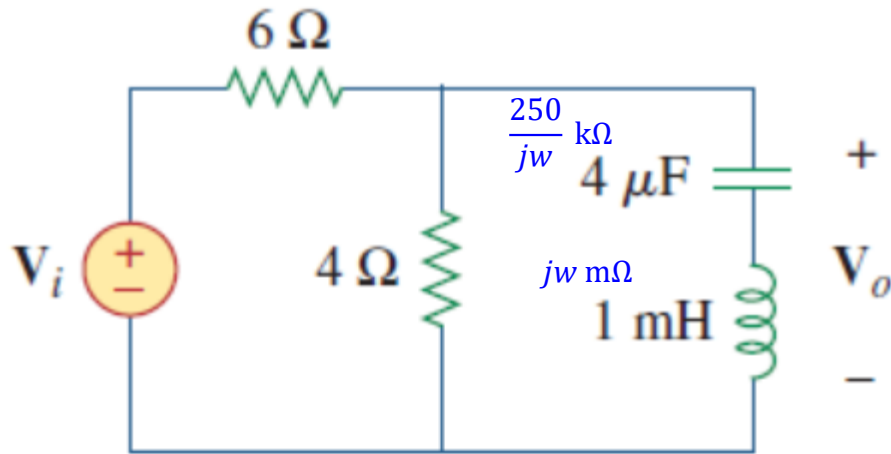Problem 14.59 P667

Find the bandwidth and center frequency of the bandstop filter of Fig. 14.89.



Solution:

$$H(\omega) = \frac{V_o}{V_s} = \frac{4 \left\| \left(\frac{2.5 \times 10^5}{j\omega} + j\omega \times 10^{-3} \right) \right\|}{6 + 4 \left\| \left(\frac{2.5 \times 10^5}{j\omega} + j\omega \times 10^{-3} \right) \right\|}$$

$$= \frac{10^6 - 4 \times 10^{-3} \omega^2}{j24\omega + 2.5 \times 10^6 - 10^{-2} \omega^2}$$

$$H(0) = H(\infty) = 0.4 \quad (=H_{\max})$$

$$H(\omega_c) = 0 \Rightarrow \omega_c = 15.8 \text{ krad/s}$$

$$|H(\omega)| = \frac{1}{\sqrt{2}} H_{\max} \Rightarrow \omega_1 = 14.6 \text{ krad/s}, \omega_2 = 17 \text{ krad/s}$$

$$B = \omega_2 - \omega_1 = 2.4 \text{ krad/s}$$