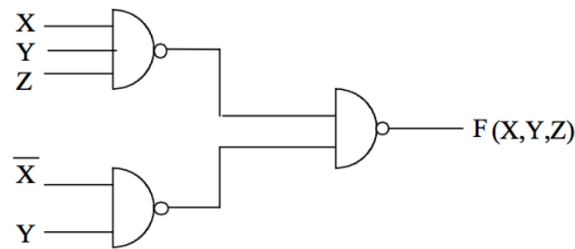


Homework 1 -- Combinatorial Logic & CPU

1. Determine the truth table for the following Boolean functions.

$$F(X, Y, Z) = \overline{XZ} + XYZ$$

2. Determine the truth table for the following logic circuit.



3. (a) Find the **complement** of the following Boolean function and reduce it to seven literals in sum-of-products form.

$$\bar{F} = \bar{B}D + \bar{A}B\bar{C} + ACD + \bar{A}BC$$

- (b) Implement the simplified expression F from Q.3(a) using AND, OR and NOT logic gates in a 2-level gate circuit.

4. Design an ALU with 3-bit commands and operations:

0: NOP
1: $\text{Accu} = -\text{Accu}$
2: $\text{Accu} = \text{Accu} + \text{data}$
3: $\text{Accu} = \text{Accu} - \text{data}$
4: $\text{Accu} = \text{Accu} * \text{data}$
5: $\text{Accu} = \text{data}$
6: don't care
7: don't care

5. Build a CU which advances the program counter by 2 in every step.

6. Review Functionality of CPU4 where its diagram and opcodes were showing below. Write a machine program to multiply two numbers by repeated addition by using the opcodes of CPU4. Your code must satisfy: (a). The two operands are in memory cells **0xA1** and **0xA2**; (b). Store the result in memory cell **0xFF**.

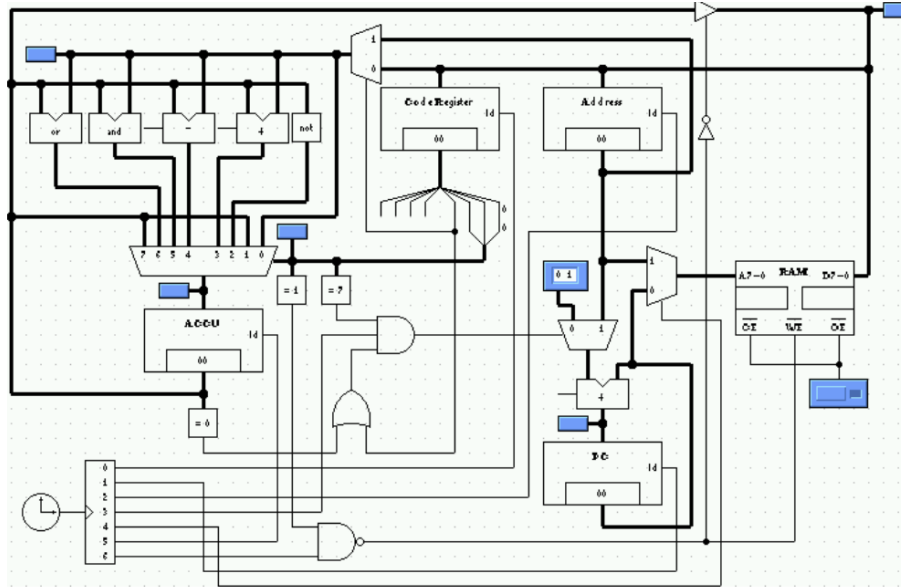


Fig.1 CPU4

Table 1 Opcodes

Opcode	Description	Abbreviation
0	$acc \leftarrow memory$ $pc \leftarrow pc + 2$	LOAD memory
1	$memory \leftarrow acc$ $pc \leftarrow pc + 2$	STORE memory
2	$acc \leftarrow NOT\ acc$ $pc \leftarrow pc + 2$	NOT
3	$acc \leftarrow acc + memory$ $pc \leftarrow pc + 2$	ADD memory
4	$acc \leftarrow acc - memory$ $pc \leftarrow pc + 2$	SUB memory
5	$acc \leftarrow acc\ AND\ memory$ $pc \leftarrow pc + 2$	AND memory
6	$acc \leftarrow acc\ OR\ memory$ $pc \leftarrow pc + 2$	OR memory
7	(* acc unchanged *) if $acc = 0$ then $pc \leftarrow pc + address$ else $pc \leftarrow pc + 2$	BEQ address
8	$acc \leftarrow constant$ $pc \leftarrow pc + 2$	LOAD constant
9		
10		
11	$acc \leftarrow acc + constant$ $pc \leftarrow pc + 2$	ADD constant
12	$acc \leftarrow acc - constant$ $pc \leftarrow pc + 2$	SUB constant
13	$acc \leftarrow acc\ AND\ constant$ $pc \leftarrow pc + 2$	AND constant
14	$acc \leftarrow acc\ OR\ constant$ $pc \leftarrow pc + 2$	OR constant
15	(* acc unchanged *) $pc \leftarrow pc + address$	BRA address