

---

## **Lecture 5**

# **Hazards**

# Learning outcomes


---

- ❑ Describe how the timing of a circuit can produce erroneous glitches.
- ❑ Define static and dynamic hazards.
- ❑ Identify and eliminate static hazards using a k-map.
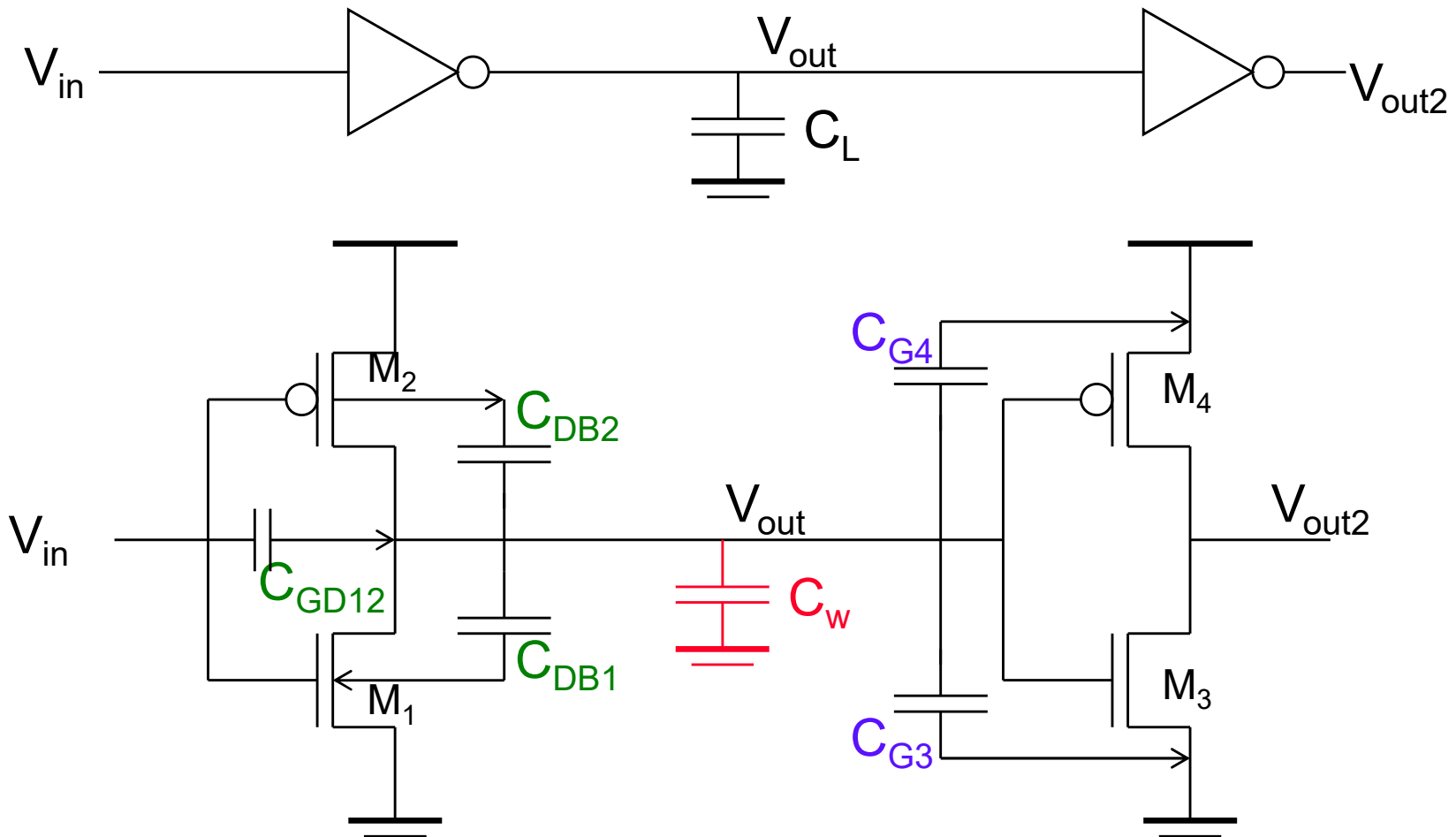
# Introduction


- ❑ Speed of operation of digital systems is limited by the *propagation delay* of logic gates from which circuit is constructed. In MOS circuits, capacitive loading is the main cause of delay due to:

- Device capacitance, Interconnect capacitance and Fan-out gates


 
# Propagation Delay $t_p$ Definitions


- ❑ Defines how quickly it responds to a change at its input(s).
- ❑ Expresses *the delay experienced by a signal when passing through a gate.*
- ❑ Measured between the 50% transition points of the input and output waveforms, as shown for an inverting gate.
- ❑ Because a gate displays different response times for rising or falling input waveforms, two definitions of the propagation delay are necessary.



# Propagation Delay Definitions

- $t_{pLH}$  defines the response time of the gate for a *low to high* (or positive) output transition.
- $t_{pHL}$  refers to a *high to low* (or negative) transition.
- The propagation delay  $t_p$  is defined as the average of the two:

$$t_p = \frac{t_{pLH} + t_{pHL}}{2}$$

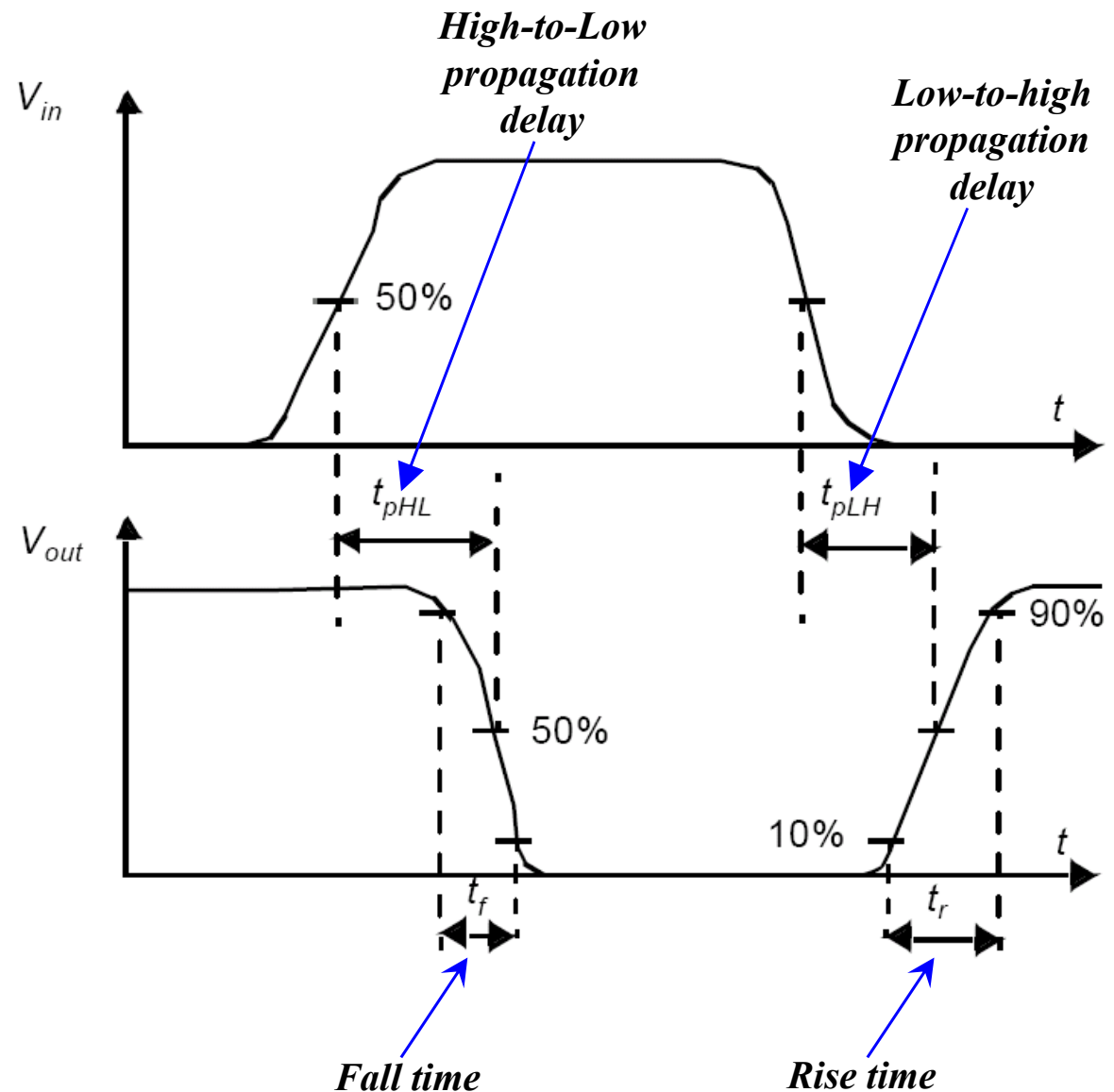

# Propagation Delay: A Quality metric

---

- ❑ In contrast to  $t_{pLH}$  and  $t_{pHL}$ , the propagation delay  $t_p$  is an artificial gate quality metric, and has no physical meaning per se. It is mostly used to compare different semiconductor technologies, or logic design styles.
- ❑ The propagation delay is not only a function of the circuit technology and topology, but depends upon other factors as well. Most importantly, the delay is a function of the *slopes* of the input and output signals of the gate.
- ❑ To quantify these properties, we introduce the *rise and fall times*  $t_r$  and  $t_f$ , which are metrics that apply to individual signal waveforms rather than gates and express how fast a signal transits between the different levels. The uncertainty over when a transition actually starts or ends is avoided by defining the rise and fall times between the 10% and 90% points of the waveform.

# Circuit's Behavior


---

- ❑ The **steady-state behavior** of a circuit is the value of the output after the inputs have been stable for a long time.
- ❑ The **transient behavior** of a circuit is the value of the output while (or soon after) the inputs change
- ❑ The **glitch** is a (often undesirable) short pulse produced in the output during a transient phase.
- ❑ If a circuit has **the possibility** of producing a glitch, the circuit has a **hazard**.

# Types of Hazards

 
## ❑ Static 1-hazard

- Occurs when output should remain static at 1 but temporarily switches to a 0 due to a change in an input.




 
## ❑ Static 0-hazard

- Occurs when output should remain static at 0 but temporarily switches to a 1 due to a change in an input.


  
## ❑ Dynamic hazards



- Occurs when an input changes, and a circuit output should change 0 -> 1 or 1 -> 0, but temporarily flips multiple times between values.




  
# Example


Assume all gates have the same propagation delay



Static 1 Hazard
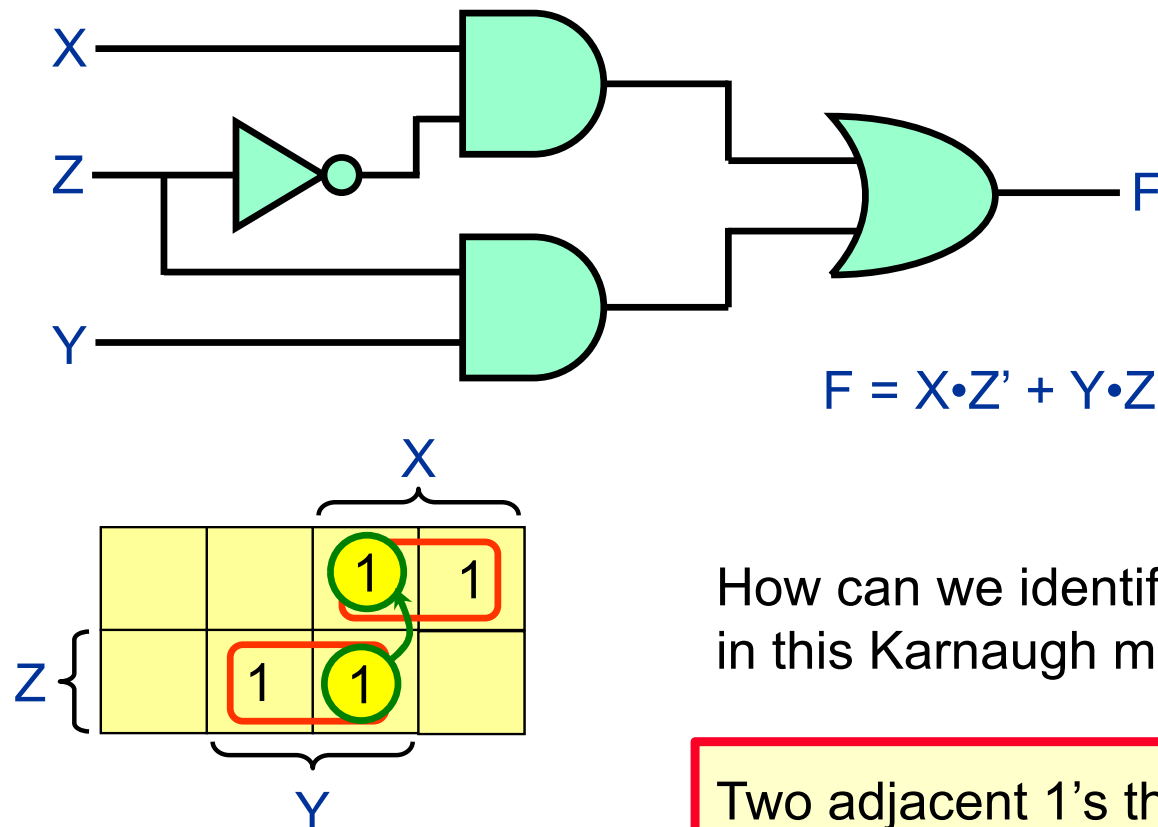
# Static 1 Hazards in Karnaugh Maps

- When circuits are implemented as 2-level SOP, we can detect and remove static-1 hazards by inspecting the k-map and adding redundant product terms.




How can we identify a static-1 hazard in this Karnaugh map?

Two adjacent 1's that are not covered in the same term cause a static-1 hazard.


Note that the occurrence of a static hazard can depend on the direction of a signal change. Here no hazard for  $Z:0 \rightarrow 1$  but hazard for  $Z:1 \rightarrow 0$ , with  $XY=11$ .

# Static 1 Hazards in Karnaugh Maps

11

 

$$F = X \cdot Z' + Y \cdot Z$$

 

How can we eliminate the hazard?



We can add one extra term to F.

$$F = X \cdot Z' + Y \cdot Z + \textcircled{X \cdot Y}$$

Additional  
Prime implicant

# Static 1 Hazards in Karnaugh Maps

12

 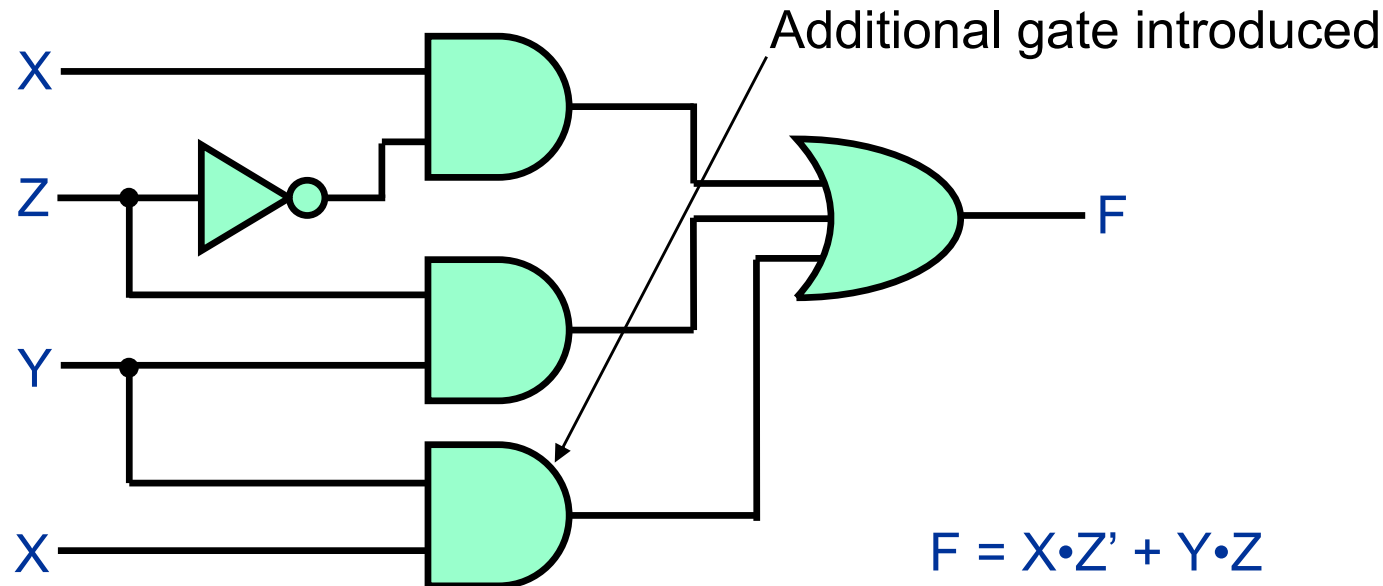


How can we eliminate the hazard?

We can add one extra term to F.

$$F = X \cdot Z' + Y \cdot Z + X \cdot Y$$

Additional prime implicant



- ❑ In our study of hazards, we'll assume that input variable changes are spaced such that the effects of a change in one variable is permitted to propagate throughout the circuit before another variable is allowed to change.
- ❑ This is the single-input change case, since input signal patterns can change in only one variable at a time. For example, 00 can be followed by 01 or 10, but not 11.
- ❑ A *static hazard* is here a momentary change in an output that occurs as the result of the change of a single input variable when the value of the output variable is to remain fixed.

 

- ❑ The cause of hazards is the timing delay of different components in the circuit.
- ❑ When certain paths through the circuit allow a variable change to propagate faster than other paths, this may cause glitches.
- ❑ The resulting glitches in the circuit may or may not induce additional problems - other than increased issues due to switching noise. It is good design practice to design circuits to minimize these hazards.
- ❑ **Static-1 hazards** occur in **sum-of-products** implementations, but do not occur in product-of-sums implementations.
- ❑ **Static-0 hazards** occur in **product-of-sums** implementations, but do not occur in sum-of-products implementations.

# Static-0 Hazards

15

  

# Static-0 Hazards in Karnaugh Maps

---


- ❑ We have seen that a logic circuit has a **static-1 hazard** if there are two adjacent 1's not covered by a common product term in a sum of products implementation.
- ❑ Similarly, a logic circuit has a **static-0 hazard** if there are two adjacent 0's not covered by a common sum term in a product of sums implementation.



# Static 0 Hazards in Karnaugh Maps


17

Minimal implementation

 

$$F = (a'+c)(b+c')$$

 Static-0 Hazard-free  
Minimal implementation




$$F = (a'+c)(b+c')(a'+b)$$

 
# Dynamic Hazards: Multiple Glitches

---

- ❑ A circuit has a dynamic hazard if an input transition is supposed to cause a single transition in an output, but causes two or more transitions before reached its expected value.
- ❑ Dynamic hazards are a consequence of multiple static hazards in a multi-level circuit.
- ❑ In general, very difficult to eliminate all dynamic hazards.
- ❑ Design critical circuits to be two-level circuits and eliminate all of the static hazards.
- ❑ Wait until signals are stable.




# Dynamic Hazard Example

 


# Dynamic Hazard Example

20

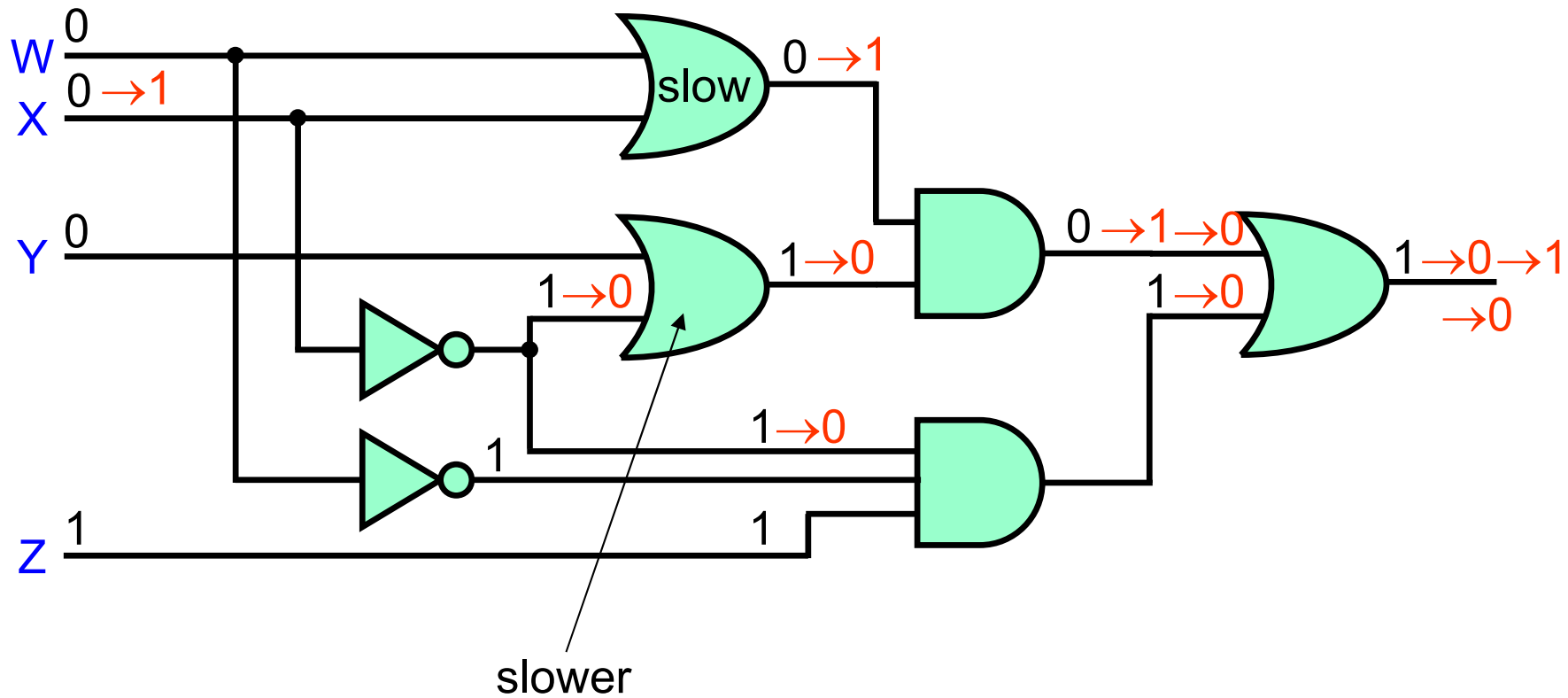


				W		
				{		
				1	1	1
Y {	1	1		1	Z {	
	1	1		1		
		1	1	1		
				X		

 1. Write minimal form for F
2. Identify static-1 hazards
3. Eliminate static-1 hazards



 
$$F = W' \cdot Z + X \cdot Z' + X' \cdot W$$




$$F = W' \cdot Z + X \cdot Z' + X' \cdot W$$

 
1. Write minimal form for F
2. Identify static-1 hazards
3. Eliminate static-1 hazards



 
$$F = W' \cdot Z + X \cdot Z' + X' \cdot W$$


 
$$F = W' \cdot Z + X \cdot Z' + X' \cdot W + X \cdot W'$$



 
$$F = W' \cdot Z + X \cdot Z' + X' \cdot W$$




$$F = W' \cdot Z + X \cdot Z' + X' \cdot W + X \cdot W'$$

 1. Write minimal form for F
2. Identify static-1 hazards
3. Eliminate static-1 hazards





 
$$F = W' \cdot Z + X \cdot Z' + X' \cdot W$$




$$F = W' \cdot Z + X \cdot Z' + X' \cdot W + X \cdot W' + W \cdot Z'$$

 1. Write minimal form for F
2. Identify static-1 hazards
3. Eliminate static-1 hazards


 
$$F = W' \cdot Z + X \cdot Z' + X' \cdot W$$



$$F = W' \cdot Z + X \cdot Z' + X' \cdot W + X \cdot W' + W \cdot Z' + X' \cdot Z$$

1. Write minimal form for F
2. Identify static-1 hazards
3. Eliminate static-1 hazards

- ❑ Glitching is due to a mismatch in the path lengths in the logic network; if all input signals of a gate change simultaneously, no glitching occurs.
- ❑ Equalizing the lengths of timing paths through logic is not easy.
- ❑ Glitches increase power dissipation and noise.
- ❑ Glitches can cause circuit failure if value is read while output is still unstable.
- ❑ A Karnaugh map can be used to eliminate static hazards but it usually results in more devices (a non-minimal circuit).
- ❑ Another method to eliminate timing hazards uses a clock to wait long enough for the output to become stable before reading it.
- ❑ Clocking the signal does not eliminate the glitch but stops it from causing circuit failure.

# Acknowledgments

---

- ❑ Credit is acknowledged where credit is due.  
Please refer to the full list of references.