

ENSC3021 Tutorial Problems 5A

Martin T. Hill, 30th March 2019

Question 1.

Find the z-parameters for the two port network of figure 1.

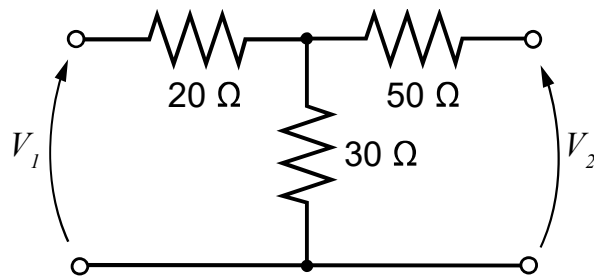


Figure 1.

Question 2.

Find the z-parameters for the two port network of figure 2

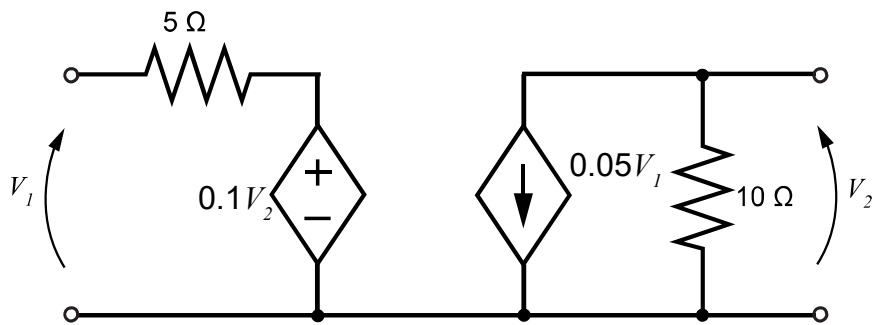


Figure 2.

Question 3.

A two port with the z parameters given below is connected as shown in figure 3.

$$[z] = \begin{bmatrix} 10^3 & 10 \\ -10^6 & 10^4 \end{bmatrix}$$

- Find the voltage gain of the two port, i.e. V_2/V_1 .
- Find the input impedance to the two port, i.e. $Z_{in} = V_1/I_1$

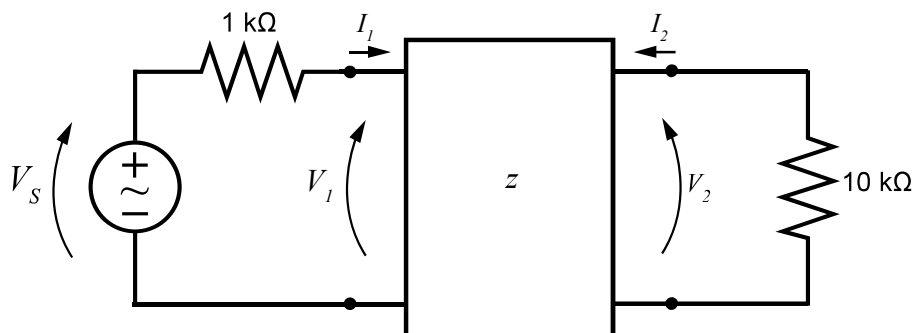


Figure 3.

Question 4.

- a) Find the ABCD (transmission) parameters for the network of figure 4.

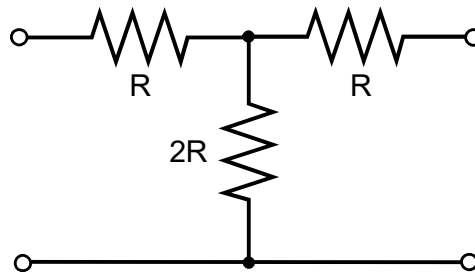


Figure 4.

- b) Using this general result find the ABCD (transmission) parameters for the network of figure 5.

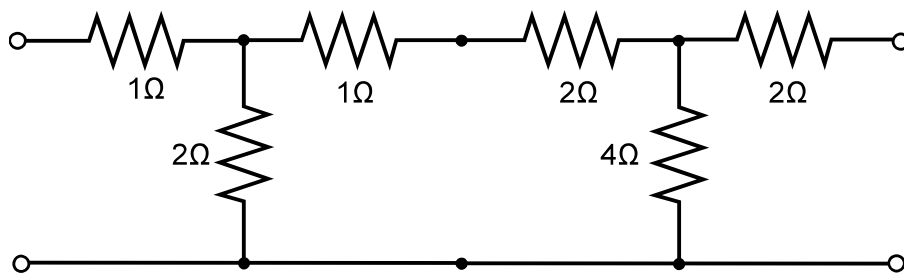


Figure 5.