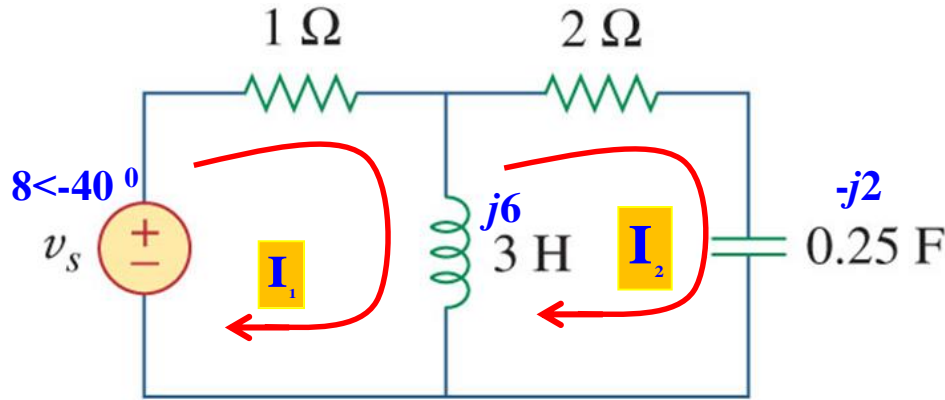


## Problem 11.5 P491

Assuming that  $v_s = 8 \cos(2t - 40^\circ)$  V in the circuit of Fig. 11.37, find the average power delivered to each of the passive elements.



### Solution:

$$I_1 : (1 + j6)I_1 - j6I_2 = 8\angle -40^\circ$$

$$I_2 : -j6I_1 + (2 - j2 + j6)I_2 = 0$$

$$\Rightarrow I_1 = 1.68\angle -25^\circ$$

$$I_2 = 2.26\angle 1^\circ$$

$$\text{So: } P_{1\Omega} = \frac{|I_1|^2}{2} \times 1 = \frac{1.68^2}{2} = 1.41 \text{ W}$$

$$P_{2\Omega} = \frac{|I_2|^2}{2} \times 2 = \frac{2.26^2}{2} \times 2 = 5.11 \text{ W}$$

$$P_{3H} = P_{0.25F} = 0 \text{ W}$$

# Problem 11.15 P492

## Solution:

As shown in Fig.(b), for find  $Z_{Th}$ ,  
Adding a current source  $I_s$ , Applying  
KCL at node A and node B:

$$\left( \frac{1}{1} + \frac{1}{-j1} + \frac{1}{j1} \right) V_0 - \frac{1}{-j1} V_s = 0$$

$$-\frac{1}{-j1} V_0 + \frac{1}{-j1} V_s = 2V_0 + I_s$$

$$\text{So we get } Z_{Th} = \frac{V_s}{I_s} = 0.5 + j0.5$$



$$\text{So } Z_L = 0.5 - j0.5$$

For the  $V_{Th}$ . As shown in Fig.(a) Applying  
KCL at node C and node D:

$$\left( \frac{1}{1} + \frac{1}{-j1} + \frac{1}{j1} \right) V_0 - \frac{1}{-j1} V_{Th} - \frac{1}{1} \times 12 = 0$$

$$-\frac{1}{-j1} V_0 + \frac{1}{-j1} V_{Th} = 2V_0$$

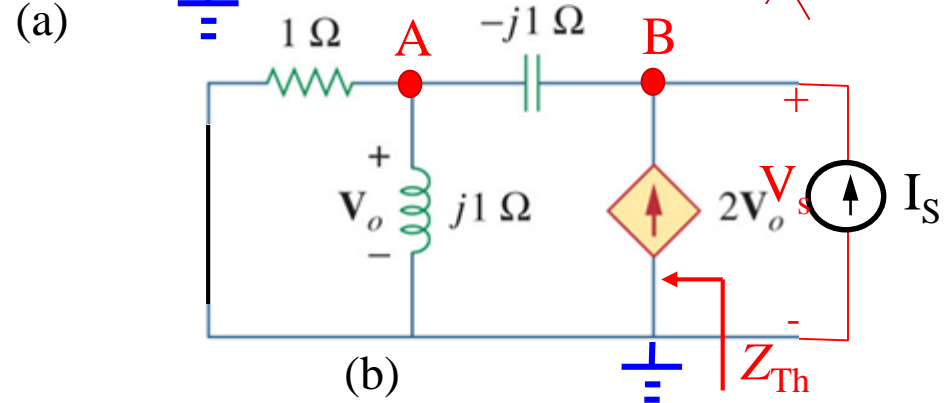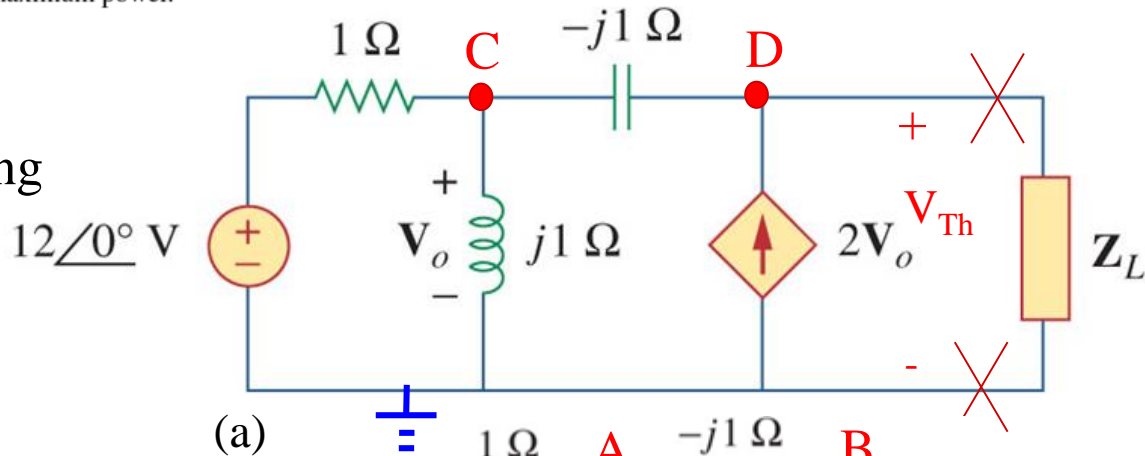In the circuit of Fig. 11.46, find the value of  $Z_L$  that will absorb the maximum power and the value of the maximum power.



$$\text{So we get } V_{Th} = 6(-3 + j)$$


$$|V_{Th}| = 6\sqrt{10}$$

$$\text{So we find } P_{\max} = \frac{|V_{Th}|^2}{8R_{Th}} = \frac{(6\sqrt{10})^2}{8 \times 0.5} = 90 \text{ W}$$

## Problem 11.20 P492

The load resistance  $R_L$  in Fig. 11.51 is adjusted until it absorbs the maximum average power. Calculate the value of  $R_L$  and the maximum average power.

**Solution:** For  $V_{Th}$ :

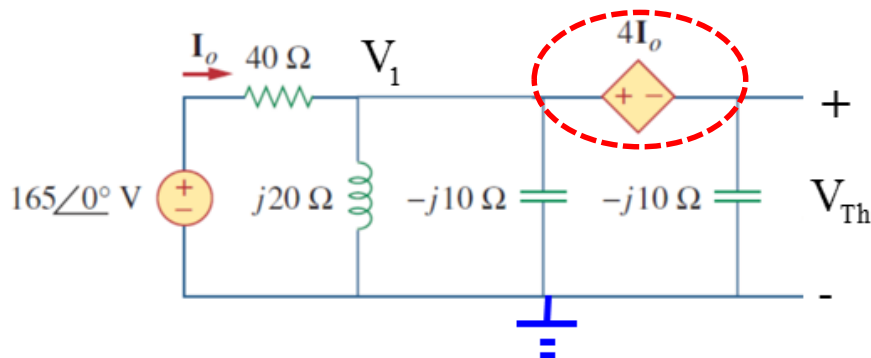

$$V_1 + V_{Th}: \left( \frac{1}{40} + \frac{1}{j20} + \frac{1}{-j10} \right) V_1 + \frac{1}{-j10} V_{Th} - \frac{1}{40} \times 165 \angle 0^\circ = 0$$


$$V_1 - V_{Th} = 4I_0$$

$$I_0 = \frac{165 \angle 0^\circ - V_1}{40}$$


$$\Rightarrow V_{Th} = 26 \angle -92^\circ$$

$$\text{So: } R_L = |Z_{Th}| = 6.79 \Omega$$
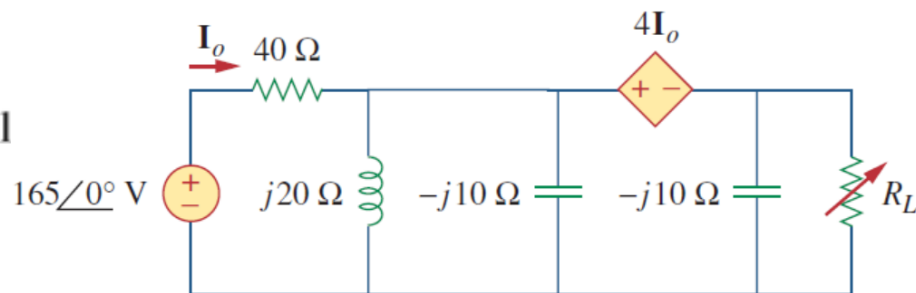
$$I = \frac{V_{Th}}{Z_{Th} + R} = \frac{26 \angle -92^\circ}{1.05 - j6.71 + 6.79}$$



For  $Z_{Th}$ :

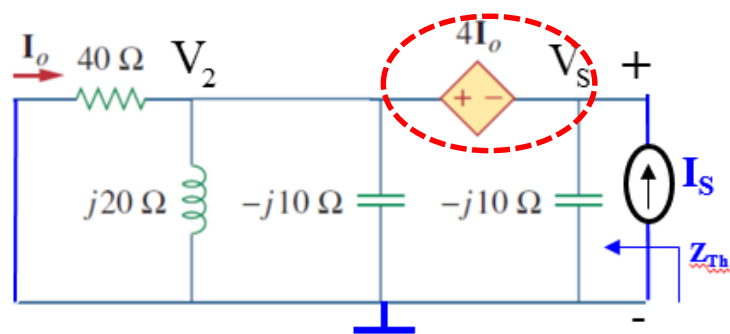

$$V_2 + V_s: \left( \frac{1}{40} + \frac{1}{j20} + \frac{1}{-j10} \right) V_2 + \frac{1}{-j10} V_s = I_s$$

$$V_2 - V_s = 4I_0$$

$$I_0 = \frac{-V_2}{40}$$


$$\Rightarrow Z_{Th} = \frac{V_s}{I_s} = 1.05 - j6.71$$

$$P_{\max} = \frac{1}{2} |I|^2 R_L$$

$$= \frac{1}{2} \times \frac{26^2}{(1.06 + 6.79)^2 + 6.71^2} \times 6.79 = 21.55 \text{ W}$$
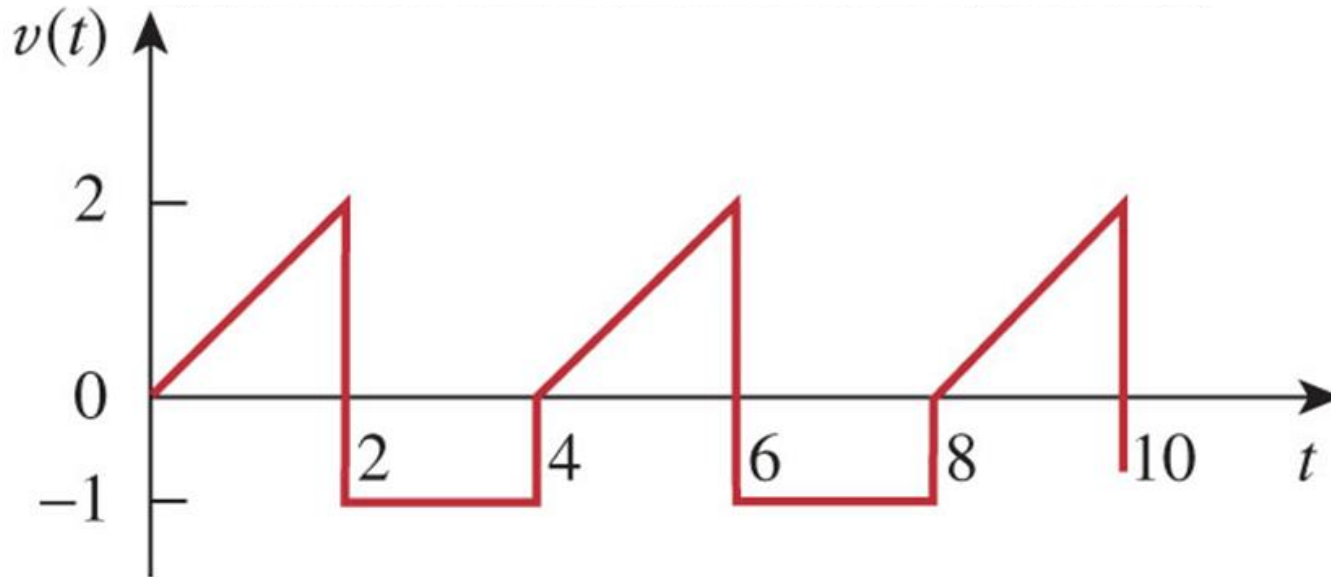
## Problem 11.30 P494

Compute the rms value of the waveform depicted in Fig. 11.61.




**Solution:**

$$V_{\text{rms}} = \sqrt{\frac{1}{4} \int_0^4 v^2 dt} = \frac{1}{2} \sqrt{\int_0^2 t^2 dt + \int_2^4 (-1)^2 dt} = 1.08 \text{ V}$$
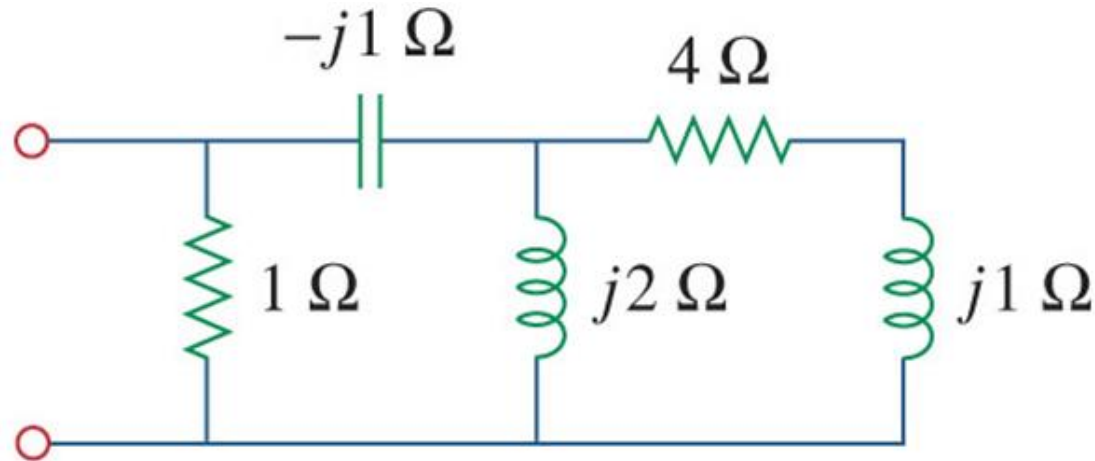
## Problem 11.41 P495

Obtain the power factor for each of the circuits in Fig. 11.68. Specify each power factor as leading or lagging.




**Solution:**  $Z = [(4 + j1) \parallel j2 - j1] \parallel 1 = 0.48 \angle 21.5^\circ$

$$\text{pf} = \cos 21.5^\circ = 0.93 \text{ lagging}$$
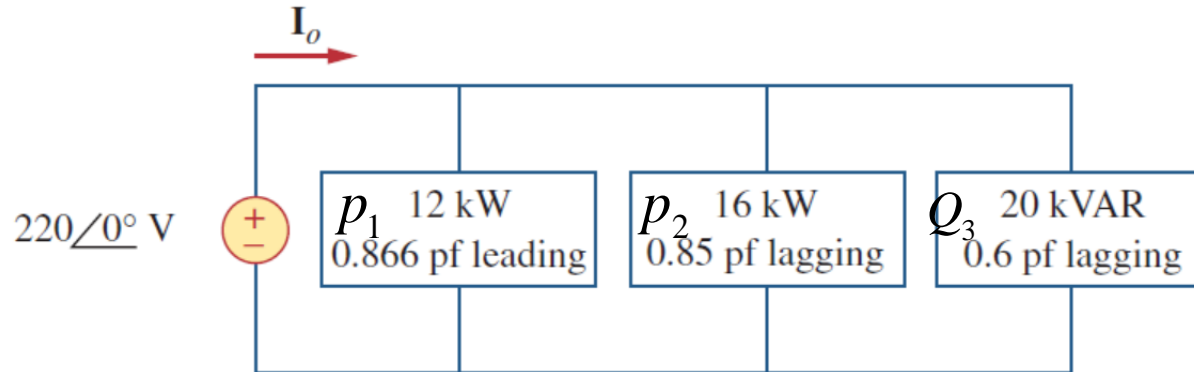
## Problem 11.63 P497

Find  $I_o$  in the circuit of Fig. 11.82.



### Solution:

$$P_1 = 12 \text{ kW}. \quad \theta_1 = -\cos^{-1} 0.866 = -30^\circ. \quad Q_1 = P_1 \times \tan(-30^\circ) = -6.924 \text{ kVAR}$$

$$P_2 = 16 \text{ kW}. \quad \theta_2 = \cos^{-1} 0.85 = 32^\circ. \quad Q_2 = P_2 \times \tan(32^\circ) = 10 \text{ kVAR}$$

$$Q_3 = 20 \text{ kVAR}. \quad \theta_3 = \cos^{-1} 0.6 = 53^\circ. \quad P_3 = Q_3 \times \cot \theta_3 = 15.08 \text{ kW}$$

$$\text{So: } P = P_1 + P_2 + P_3 = 43.08 \text{ kW}$$

$$Q = Q_1 + Q_2 + Q_3 = 23.08 \text{ kVAR}$$


$$\theta = \tan^{-1} \left( \frac{Q}{P} \right) = 28^\circ$$

$$\text{As: } P = V_{\text{rms}} I_{\text{rms}} \cos \theta \Rightarrow I_{\text{rms}} = \frac{43.08 \times 10^3}{220 \times \cos 28^\circ} = 221.7 \text{ A}$$

$$\text{So: } I = 221.7 \angle -28^\circ \text{ A}$$
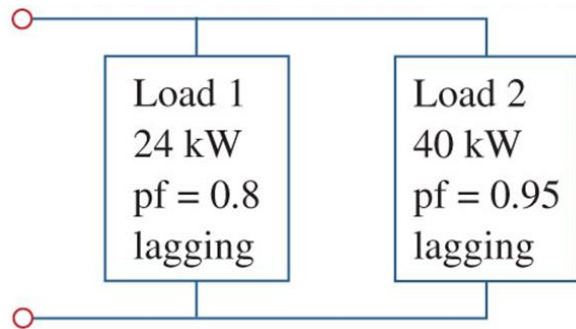
## Problem 11.74 P499

A 120-V rms 60-Hz source supplies two loads connected in parallel, as shown in Fig. 11.89.



- (a) Find the power factor of the parallel combination.
- (b) Calculate the value of the capacitance connected in parallel that will raise the power factor to unity.

### Solution:

$$P_1 = 24 \text{ kW}. \quad \theta_1 = \cos^{-1} 0.8 = 37^\circ. \quad Q_1 = P_1 \times \tan(37^\circ) = 18 \text{ kVAR}$$

$$P_2 = 40 \text{ kW}. \quad \theta_2 = \cos^{-1} 0.95 = 18^\circ. \quad Q_2 = P_2 \times \tan(18^\circ) = 13 \text{ kVAR}$$

$$\text{So : } P = P_1 + P_2 = 64 \text{ kW}$$

$$Q = Q_1 + Q_2 = 31 \text{ kVAR} \quad \text{pf} = \cos \left[ \tan^{-1} \left( \frac{Q}{P} \right) \right] = 0.9 \text{ lagging}$$

$$\text{As : } Q = \omega C \times V_{\text{rms}}^2 \Rightarrow C = \frac{31 \times 10^3}{2\pi \times 60 \times 120^2} = 5.71 \text{ mF}$$