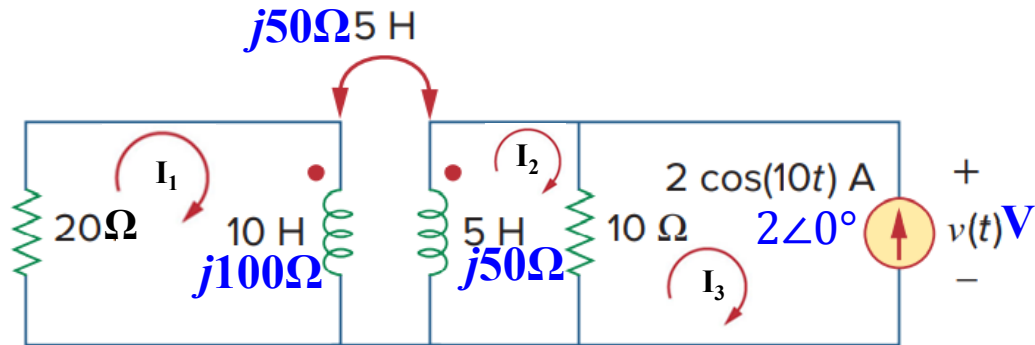


Problem 13.8 P597

Find $v(t)$ for the circuit in Fig. 13.77.



Solution:

$$(20 + j100)\mathbf{I}_1 - j50\mathbf{I}_2 = 0$$

$$-j50\mathbf{I}_1 + (10 + j50)\mathbf{I}_2 - 10\mathbf{I}_3 = 0 \quad \Rightarrow \quad \mathbf{I}_2 = 0.67\angle 120^\circ$$

$$\mathbf{I}_3 = -2\angle 0^\circ$$

$$\text{So: } V = 10 (I_2 - I_3) = 17.6 \angle 19^\circ \text{ V}$$


Then: $v(t) = 17.6\cos(10t + 19^\circ)$ V

Problem 13.36 P601


As done in Fig. 13.32, obtain the relationships between terminal voltages and currents for each of the ideal transformers in Fig. 13.105.

$$\frac{V_2}{V_1} = -n$$

$$\frac{I_2}{I_1} = \frac{1}{n}$$

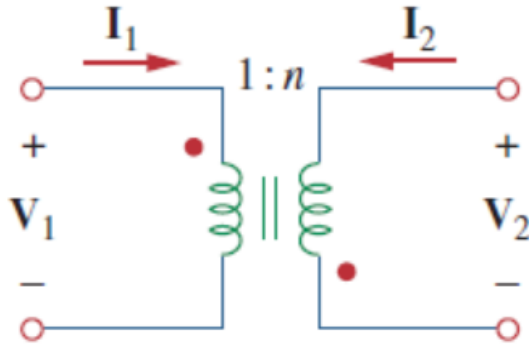

(a)

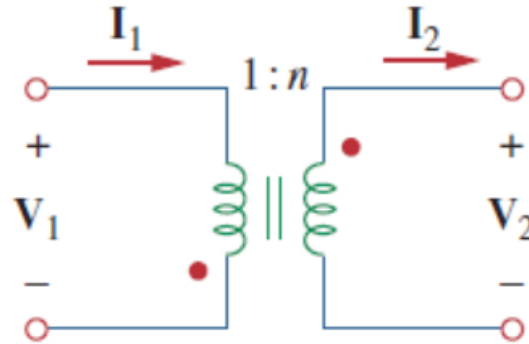


(b)

$$\frac{V_2}{V_1} = -n$$


$$\frac{I_2}{I_1} = -\frac{1}{n}$$

$$\frac{V_2}{V_1} = n$$

$$\frac{I_2}{I_1} = \frac{1}{n}$$

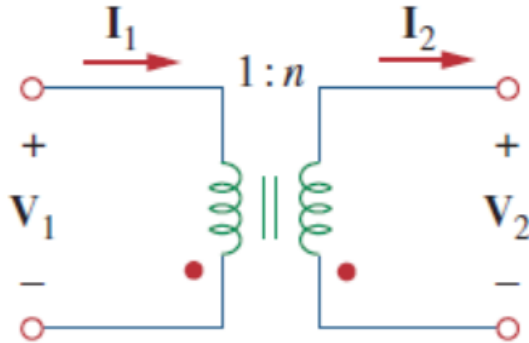

(c)

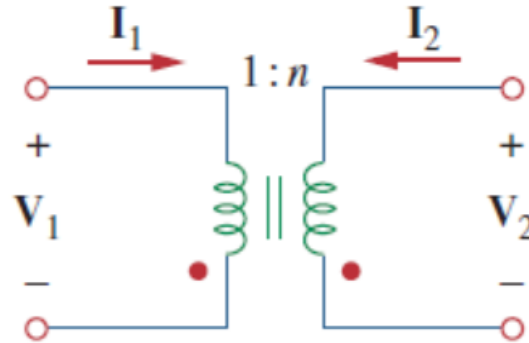


(d)

$$\frac{V_2}{V_1} = n$$


$$\frac{I_2}{I_1} = -\frac{1}{n}$$

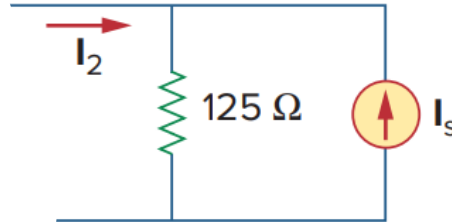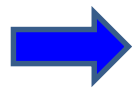Problem 13.41 P602

Given $I_2 = 2$ A, determine the value of I_s in Fig. 13.106.




Solution: $-10 \times 5^2 I_2 = 125(I_2 + I_s)$

 $I_s = -3I_2 = -6$ A

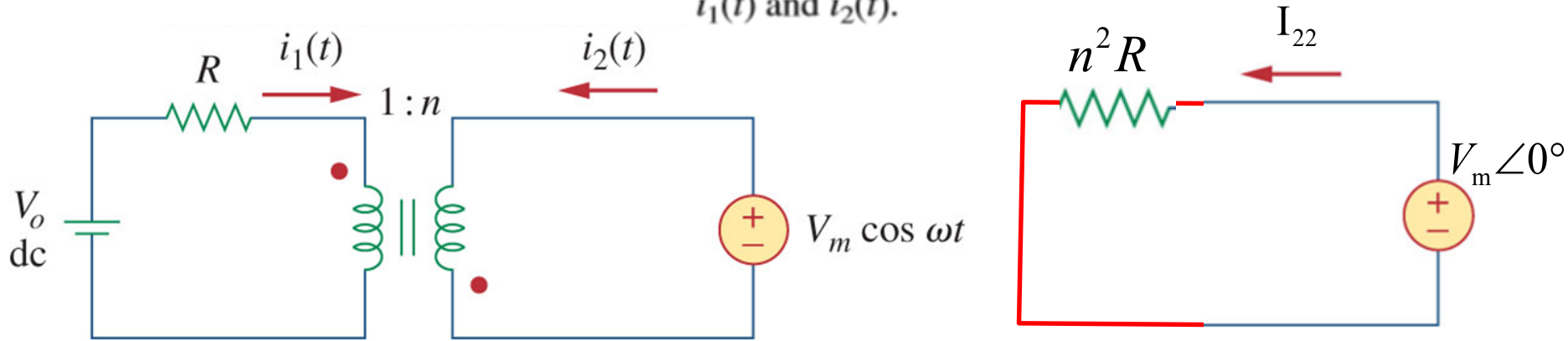Problem 13.44 P602

In the ideal transformer circuit of Fig. 13.109, find $i_1(t)$ and $i_2(t)$.



Solution: When V_0 acts alone: $i_{11}(t) = \frac{V_0}{R}$, $i_{21}(t) = 0$

When $V_m \cos \omega t$ acts alone:

$$I_{22} = \frac{V_m \angle 0^\circ}{n^2 R} \quad \frac{I_{22}}{I_{12}} = \frac{1}{n} \Rightarrow I_{12} = n I_{22} = \frac{V_m \angle 0^\circ}{n R}$$


$$\text{So: } i_{12}(t) = \frac{V_m}{n R} \cos \omega t, \quad i_{22}(t) = \frac{V_m}{n^2 R} \cos \omega t$$

$$\text{Then: } i_1(t) = i_{11}(t) + i_{12}(t) = \frac{V_0}{R} + \frac{V_m}{n R} \cos \omega t, \quad i_2(t) = i_{21}(t) + i_{22}(t) = \frac{V_m}{n^2 R} \cos \omega t$$

Problem 13.53 P603

Refer to the network in Fig. 13.118.

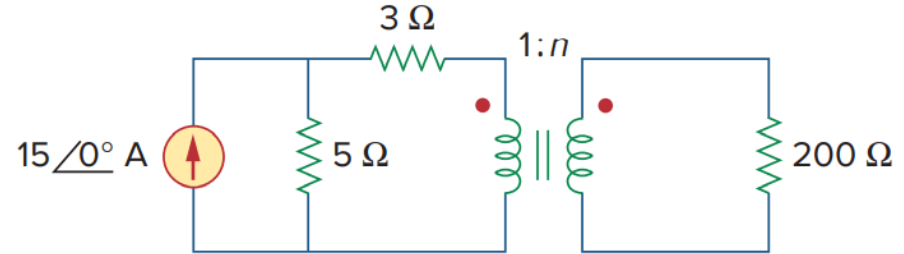
- (a) Find n for maximum power supplied to the $200\text{-}\Omega$ load.
- (b) Determine the power in the $200\text{-}\Omega$ load if $n = 10$.



Solution:

$$(a) \quad 8n^2 = 200 \quad \Rightarrow n = 5$$
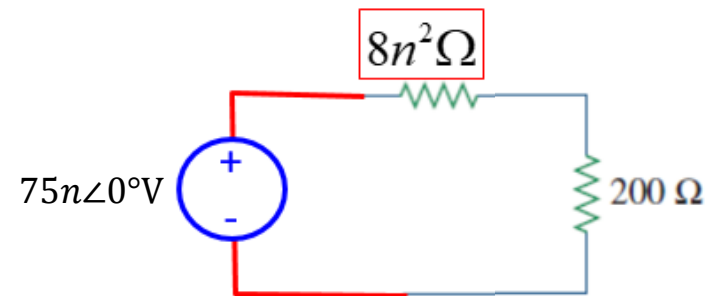
$$\begin{aligned} (b) \quad P &= \left(\frac{75n}{8n^2 + 200} \right)^2 \times 200 \\ &= \left(\frac{75 \times 10}{8 \times 10^2 + 200} \right)^2 \times 200 \\ &= 112.5 \text{ W} \end{aligned}$$



$$P_{max} = \frac{(75 \times 5)^2}{4 \times 200} = 176 \text{ W}$$