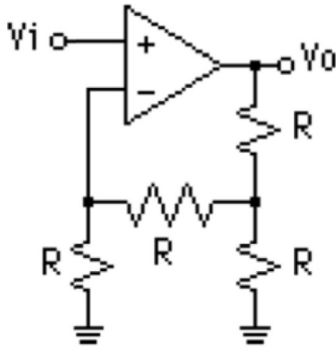



Tutorial 9 - Operational Amplifier Abstraction

Q1. We have the following Op-amp circuit. Determine the circuit gain $A_v = v_o/v_i$.




Q2. The circuit shown below is intended to supply a voltage to floating loads (those for which both terminals are ungrounded) while making greatest possible use of the available power supply.

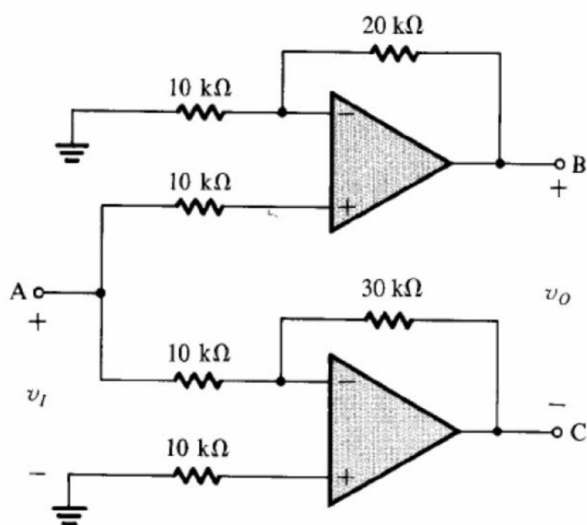- a) Assuming ideal op amps, sketch the voltage waveforms at nodes B and C for a 1-V peak-to-peak sine wave applied at A. Also sketch v_o .
- b) What is the voltage gain v_o/v_i ?
- c) Assuming the op amps operate from ± 15 -V power supplies and their output saturates at ± 14 V, what is the largest sine wave output wave output that can be accommodated? Specify its peak-to-peak value.



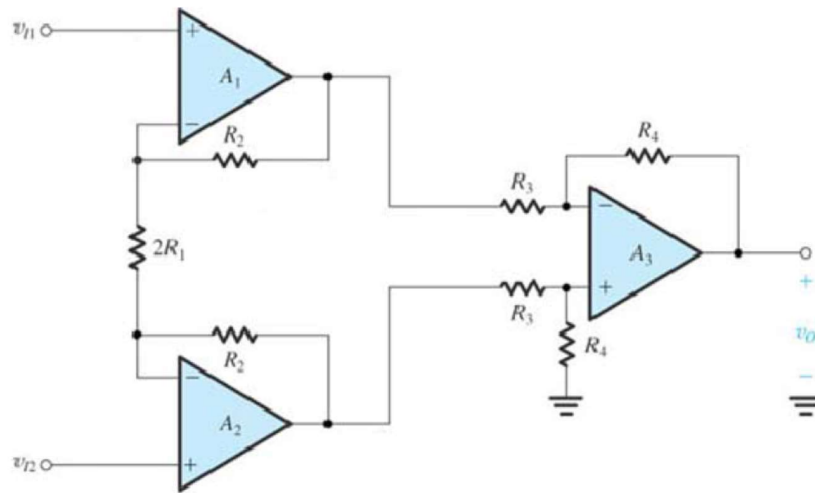Q3. Determine the expression of the output v_o as a function of inputs v_{i1} and v_{i2}



Q4. Consider the difference amplifier shown below. Calculate the differential gain $A_d = v_o/v_{id}$. Assume that R_5 and R_6 are much smaller than R so that the current through R is much lower than the current in the voltage divider, with the result that $\beta = R_6/(R_5 + R_6)$.

