

Solution 6.1

$$i = C \frac{dv}{dt} = 7.5(2e^{-3t} - 6te^{-3t}) = \mathbf{15(1 - 3t)e^{-3t} \text{ A}}$$

$$p = vi = 15(1-3t)e^{-3t} \cdot 2t e^{-3t} = \mathbf{30t(1 - 3t)e^{-6t} \text{ W.}}$$

$$\mathbf{15(1 - 3t)e^{-3t} \text{ A}, 30t(1 - 3t)e^{-6t} \text{ W}}$$

Solution 6.2

$$w(t) = (1/2)C(v(t))^2 \text{ or } (v(t))^2 = 2w(t)/C = (20\cos^2(377t))/(50 \times 10^{-6}) = 0.4 \times 10^6 \cos^2(377t)$$

or

$$v(t) = \pm 632.5 \cos(377t) \text{ V.}$$

Let us assume that $v(t) = 632.5 \cos(377t)$ V, which leads to
 $i(t) = C(dv/dt) = 50 \times 10^{-6}(632.5)(-377 \sin(377t))$

$$= -11.923 \sin(377t) \text{ A.}$$

Please note that if we had chosen the negative value for v , then $i(t)$ would have been positive.

Solution 6.3

Design a problem to help other students to better understand how capacitors work.

Although there are many ways to work this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

In 5 s, the voltage across a 40-mF capacitor changes from 160 V to 220 V. Calculate the average current through the capacitor.

Solution

$$i = C \frac{dv}{dt} = 40 \times 10^{-3} \frac{220 - 160}{5} = \mathbf{480 \text{ mA}}$$

Solution 6.4

A voltage across a capacitor is equal to $[2-2 \cos(4t)]$ V and the current flowing through it is equal to $2\sin(4t)$ μ A, determine the value of the capacitance. Calculate the power being stored by the capacitor.

Solution


Starting with $i_C = Cdv_C/dt$ and $v_C = [2-2 \cos(4t)]$ V and that $i_C = 2\sin(4t)$ μ A,

we get $c = 2\sin(4t) \times 10^{-6} / 8\sin(4t) = \mathbf{0.25 \mu F}$.

$P_C = v_C i_C = [2-2 \cos(4t)][2\sin(4t) \times 10^{-6}] = \mathbf{[4\sin(4t)-4\cos(4t)\sin(4t)] \mu W}$.


Solution 6.5

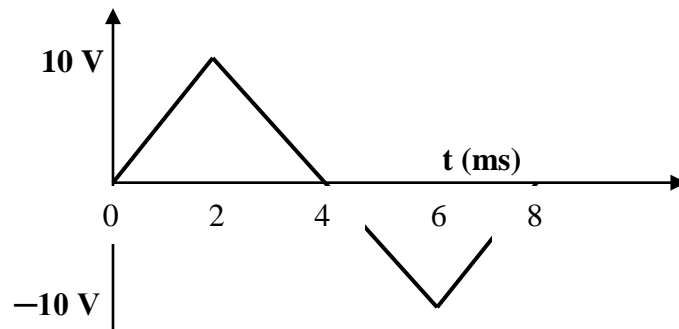The voltage across a 4- μF capacitor is shown below. Find the current waveform.



Step 1.
$$v = \begin{cases} 5000t, & 0 < t < 2\text{ms} \\ 20 - 5000t, & 2 < t < 6\text{ms} \\ -40 + 5000t, & 6 < t < 8\text{ms} \end{cases} \text{ and } i_C(t) = Cdv_C(t)/dt.$$

Step 2. For $0 < t < 2\text{ms}$, $i_C(t) = 4 \times 10^{-6} d(5000t)/dt = 20 \text{ mA}$;
for $2\text{ms} < t < 6\text{ms}$, $i_C(t) = 4 \times 10^{-6} d(20 - 5000t)/dt = -20 \text{ mA}$;
and for $6\text{ms} < t < 8\text{ms}$, $i_C(t) = 4 \times 10^{-6} d(-40 + 5000t)/dt = 20 \text{ mA}$.

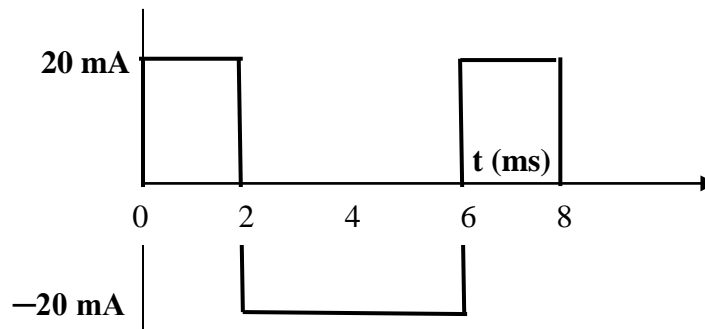

Solution 6.6


$i = C \frac{dv}{dt} = 55 \times 10^{-6}$ times the slope of the waveform.

For example, for $0 < t < 2$,

$$\frac{dv}{dt} = \frac{10}{2 \times 10^{-3}}$$

$$i = C \frac{dv}{dt} = (55 \times 10^{-6}) \frac{10}{2 \times 10^{-3}} = 275 \text{ mA}$$

Thus the current $i(t)$ is sketched below.

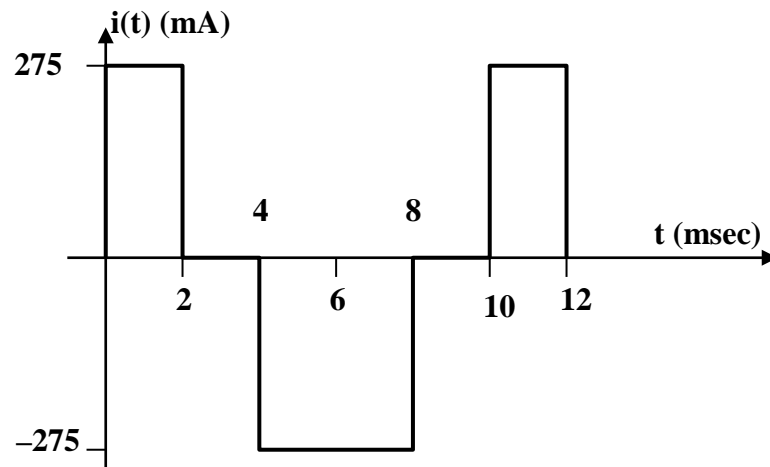

Solution 6.7

$$\begin{aligned}v &= \frac{1}{C} \int i dt + v(t_o) = \frac{1}{25 \times 10^{-3}} \int_o^t 5tx10^{-3} dt + 10 \\&= \frac{2.5t^2}{25} + 10 = \mathbf{[0.1t^2 + 10] \text{ V.}}\end{aligned}$$

Solution 6.8

$$(a) \quad i = C \frac{dv}{dt} = -100ACe^{-100t} - 600BCe^{-600t} \quad (1)$$

$$i(0) = 2 = -100AC - 600BC \quad \longrightarrow \quad 5 = -A - 6B \quad (2)$$

$$v(0^+) = v(0^-) \quad \longrightarrow \quad 50 = A + B \quad (3)$$

Solving (2) and (3) leads to

$$\underline{A=61, \quad B=-11}$$

$$(b) \quad \text{Energy} = \frac{1}{2} C v^2(0) = \frac{1}{2} \times 4 \times 10^{-3} \times 2500 = \underline{5 \text{ J}}$$

(c) From (1),

$$i = -100 \times 61 \times 4 \times 10^{-3} e^{-100t} - 600 \times 11 \times 4 \times 10^{-3} e^{-600t} = \underline{-24.4e^{-100t} - 26.4e^{-600t} \text{ A}}$$

Solution 6.9

$$v(t) = \frac{1}{1/2} \int_0^t 6(1 - e^{-t}) dt + 0 = 12 \left(t + e^{-t} \right) \Big|_0^t \text{ V} = 12(t + e^{-t}) - 12$$

$$v(2) = 12(2 + e^{-2}) - 12 = \mathbf{13.624 \text{ V}}$$

$$p = iv = [12(t + e^{-t}) - 12]6(1 - e^{-t})$$

$$p(2) = [12(2 + e^{-2}) - 12]6(1 - e^{-2}) = \mathbf{70.66 \text{ W}}$$

Solution 6.10

$$i = C \frac{dv}{dt} = 5 \times 10^{-3} \frac{dv}{dt}$$

$$v = \begin{cases} 16t, & 0 < t < 1\mu s \\ 16, & 1 < t < 3\mu s \\ 64 - 16t, & 3 < t < 4\mu s \end{cases}$$

$$\frac{dv}{dt} = \begin{cases} 16 \times 10^6, & 0 < t < 1\mu s \\ 0, & 1 < t < 3\mu s \\ -16 \times 10^6, & 3 < t < 4\mu s \end{cases}$$

$$i(t) = \begin{cases} 80 \text{ kA}, & 0 < t < 1\mu s \\ 0, & 1 < t < 3\mu s \\ -80 \text{ kA}, & 3 < t < 4\mu s \end{cases}$$

Solution 6.11

$$v = \frac{1}{C} \int_0^t i dt + v(0) = 10 + \frac{1}{4 \times 10^{-3}} \int_0^t i(t) dt$$

$$\text{For } 0 < t < 2, i(t) = 15 \text{ mA}, V(t) = 10 + \frac{10^3}{4 \times 10^{-3}} \int_0^t 15 dt = 10 + 3.75t$$

$$v(2) = 10 + 7.5 = 17.5$$

For $2 < t < 4$, $i(t) = -10 \text{ mA}$

$$v(t) = \frac{1}{4 \times 10^{-3}} \int_2^t i(t) dt + v(2) = -\frac{10 \times 10^{-3}}{4 \times 10^{-3}} \int_2^t dt + 17.5 = 22.5 - 2.5t$$

$$v(4) = 22.5 - 2.5 \times 4 = 12.5$$

$$\text{For } 4 < t < 6, i(t) = 0, \quad v(t) = \frac{1}{4 \times 10^{-3}} \int_4^t 0 dt + v(4) = 12.5$$


For $6 < t < 8$, $i(t) = 10 \text{ mA}$

$$v(t) = \frac{10 \times 10^{-3}}{4 \times 10^{-3}} \int_6^t dt + v(6) = 2.5(t - 6) + 12.5 = 2.5t - 2.5$$

Hence,

$$v(t) = \begin{cases} 10 + 3.75t \text{ V}, & 0 < t < 2 \text{ s} \\ 22.5 - 2.5t \text{ V}, & 2 < t < 4 \text{ s} \\ 12.5 \text{ V}, & 4 < t < 6 \text{ s} \\ 2.5t - 2.5 \text{ V}, & 6 < t < 8 \text{ s} \end{cases}$$

which is sketched below.

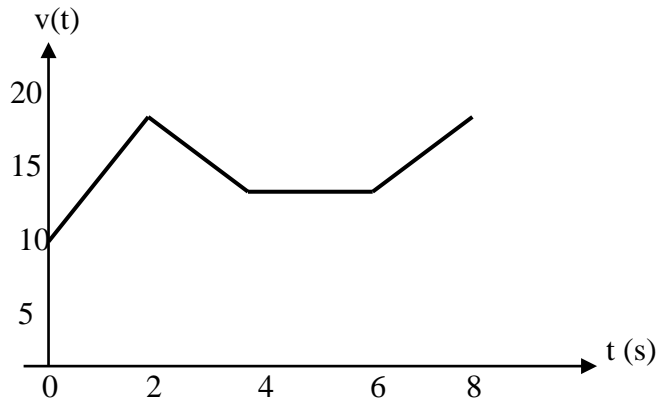

Solution 6.12

A voltage of $45e^{-2000t}$ V appears across a parallel combination of a 100-mF capacitor and a 12- Ω resistor. Calculate the power absorbed by the parallel combination.


Solution

$$i_R = V/R = (45/12)e^{-2000t} = 3.75 e^{-2000t} \text{ and}$$
$$i_C = C(dv/dt) = 0.1 \times 45(-2000) e^{-2000t} = -9000 e^{-2000t} \text{ A.}$$

Thus, $i = i_R + i_C = -8,996.25e^{-2000t}$. The power is equal to:
 $p_i = -40.48 \text{ 179.925 } e^{-4000t} \text{ kW.}$

Solution 6.13

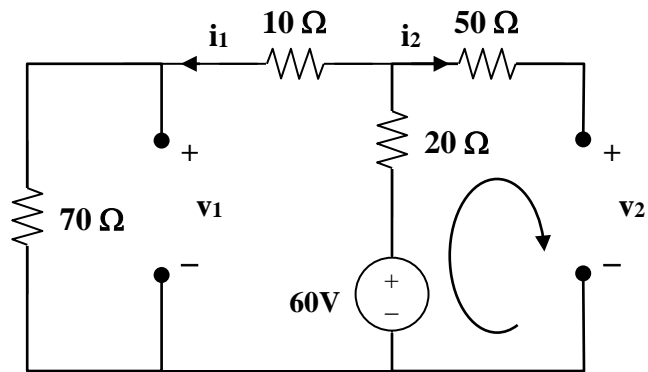Under dc conditions, the circuit becomes that shown below:



$$i_2 = 0, i_1 = 60/(70+10+20) = 0.6 \text{ A}$$

$$v_1 = 70i_1 = 42 \text{ V}, v_2 = 60 - 20i_1 = 48 \text{ V}$$

Thus, $v_1 = 42 \text{ V}, v_2 = 48 \text{ V}.$

Solution 6.14

20 pF is in series with 60pF = $20 \times 60 / 80 = 15$ pF


30-pF is in series with 70pF = $30 \times 70 / 100 = 21$ pF

15pF is in parallel with 21pF = $15 + 21 = \mathbf{36 \text{ pF}}$

Solution 6.15

Arranging the capacitors in parallel results in circuit shown in Fig. (1) (It should be noted that the resistors are in the circuits only to limit the current surge as the capacitors charge. Once the capacitors are charged the current through the resistors are obviously equal to zero.):

$$v_1 = v_2 = 100$$

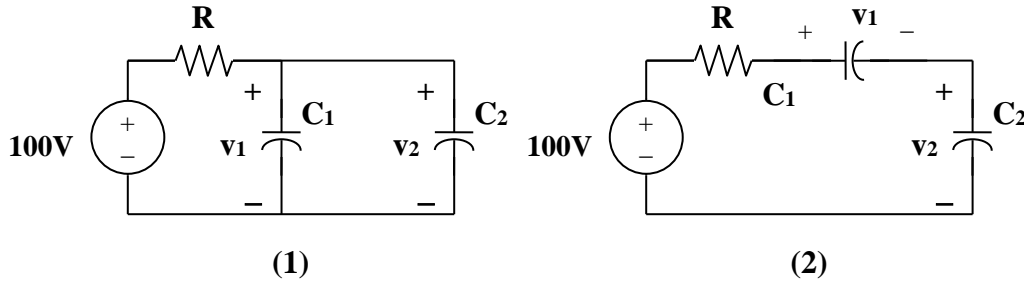

$$w_{20} = \frac{1}{2} C v^2 = \frac{1}{2} \times 25 \times 10^{-6} \times 100^2 = \mathbf{125 \text{ mJ}}$$

$$w_{30} = \frac{1}{2} \times 75 \times 10^{-6} \times 100^2 = \mathbf{375 \text{ mJ}}$$

(b) Arranging the capacitors in series results in the circuit shown in Fig. (2):

$$v_1 = \frac{C_2}{C_1 + C_2} V = \frac{75}{100} \times 100 = 75 \text{ V}, v_2 = 25 \text{ V}$$

$$w_{25} = \frac{1}{2} \times 25 \times 10^{-6} \times 75^2 = \mathbf{70.31 \text{ mJ}}$$

$$w_{75} = \frac{1}{2} \times 75 \times 10^{-6} \times 25^2 = \mathbf{23.44 \text{ mJ.}}$$

(a) **125 mJ, 375 mJ** (b) **70.31 mJ, 23.44 mJ**

Solution 6.16

The equivalent capacitance at terminals a - b in the circuit in Fig. 6.50 is $20\ \mu\text{F}$. Calculate the value of C .

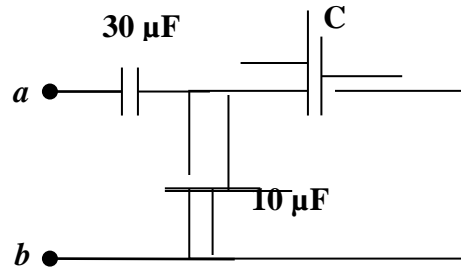


Figure 6.50
For Prob. 6.16.

Solution

The capacitance looking into terminals a and b is equal to,

$$C_{\text{eq}} = 20 \times 10^{-6} = 30 \times 10^{-6} (10 \times 10^{-6} + C) / (30 \times 10^{-6} + 10 \times 10^{-6} + C).$$

$$30 \times 10^{-6} + 10 \times 10^{-6} + C = (30/20)(10 \times 10^{-6} + C) \text{ or} \\ (1.5 - 1)C = 30 \times 10^{-6} + 10 \times 10^{-6} - 15 \times 10^{-6} = 25 \times 10^{-6} \text{ or}$$

$$C = 25 \times 10^{-6} / 0.5 = \mathbf{50\ \mu\text{F}}.$$

Solution 6.17

- (a) $4F$ in series with $12F = 4 \times 12/(16) = 3F$
 $3F$ in parallel with $6F$ and $3F = 3+6+3 = 12F$
 $4F$ in series with $12F = 3F$
i.e. $C_{eq} = \mathbf{3F}$
- (b) $C_{eq} = 5 + [6 \times (4 + 2)/(6+4+2)] = 5 + (36/12) = 5 + 3 = \mathbf{8F}$
- (c)
- (d) $3F$ in series with $6F = (3 \times 6)/9 = 2F$

$$\frac{1}{C_{eq}} = \frac{1}{2} + \frac{1}{6} + \frac{1}{3} = 1$$

$$C_{eq} = \mathbf{1F}$$


Solution 6.18

$4\ \mu\text{F}$ in parallel with $4\ \mu\text{F} = 8\ \mu\text{F}$

$4\ \mu\text{F}$ in series with $4\ \mu\text{F} = 2\ \mu\text{F}$

$2\ \mu\text{F}$ in parallel with $4\ \mu\text{F} = 6\ \mu\text{F}$

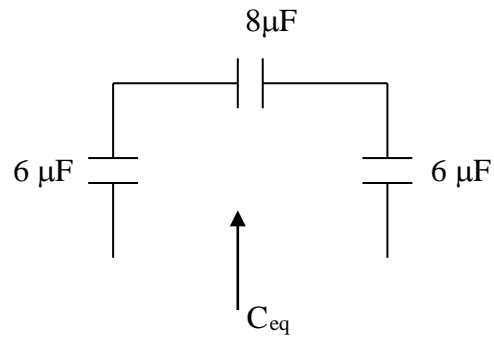Hence, the circuit is reduced to that shown below.




$$\frac{1}{C_{eq}} = \frac{1}{6} + \frac{1}{6} + \frac{1}{8} = 0.4583 \quad \longrightarrow \quad C_{eq} = \underline{2.1818\ \mu\text{F}}$$

Solution 6.19

We combine 10-, 20-, and 30- μF capacitors in parallel to get 60 μF . The 60 - μF capacitor in series with another 60- μF capacitor gives 30 μF .

$$30 + 50 = 80 \mu\text{F}, \quad 80 + 40 = 120 \mu\text{F}$$

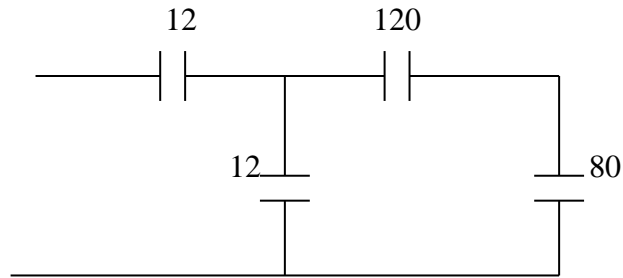The circuit is reduced to that shown below.




120- μF capacitor in series with 80 μF gives $(80 \times 120) / 200 = 48$

$$48 + 12 = 60$$

60- μF capacitor in series with 12 μF gives $(60 \times 12) / 72 = \mathbf{10 \mu\text{F}}$

Solution 6.20

Consider the circuit shown below.

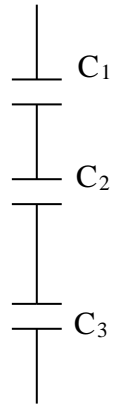

$$C_1 = 1 + 1 = 2\mu F$$

$$C_2 = 2 + 2 + 2 = 6\mu F$$

$$C_3 = 4 \times 3 = 12\mu F$$

$$1/C_{eq} = (1/C_1) + (1/C_2) + (1/C_3) = 0.5 + 0.16667 + 0.08333 = 0.75 \times 10^{-6}$$

$$C_{eq} = \mathbf{1.3333\ \mu F}.$$

Solution 6.21

$4\mu\text{F}$ in series with $12\mu\text{F} = (4 \times 12)/16 = 3\mu\text{F}$

$3\mu\text{F}$ in parallel with $3\mu\text{F} = 6\mu\text{F}$

$6\mu\text{F}$ in series with $6\mu\text{F} = 3\mu\text{F}$


$3\mu\text{F}$ in parallel with $2\mu\text{F} = 5\mu\text{F}$

$5\mu\text{F}$ in series with $5\mu\text{F} = 2.5\mu\text{F}$

Hence $C_{\text{eq}} = \mathbf{2.5\mu\text{F}}$

Solution 6.22

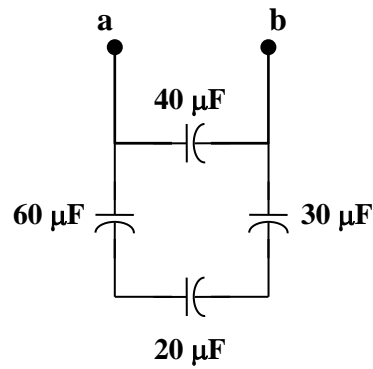Combining the capacitors in parallel, we obtain the equivalent circuit shown below:



Combining the capacitors in series gives C_{eq}^1 , where

$$\frac{1}{C_{\text{eq}}^1} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30} = \frac{1}{10} \longrightarrow C_{\text{eq}}^1 = 10\ \mu\text{F}$$

Thus

$$C_{\text{eq}} = 10 + 40 = \mathbf{50\ \mu\text{F}}$$

Solution 6.23

Using Fig. 6.57, design a problem to help other students better understand how capacitors work together when connected in series and parallel.

Although there are many ways to work this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

For the circuit in Fig. 6.57, determine:

- (a) the voltage across each capacitor,
- (b) the energy stored in each capacitor.

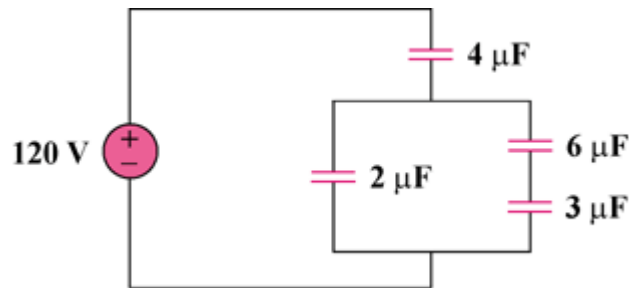


Figure 6.57

Solution

- (a) $3\mu\text{F}$ is in series with $6\mu\text{F}$ $3 \times 6 / (9) = 2\mu\text{F}$

$$V_{4\mu\text{F}} = 1/2 \times 120 = \mathbf{60V}$$

$$V_{2\mu\text{F}} = \mathbf{60V}$$

$$V_{6\mu\text{F}} = \frac{3}{6+3}(60) = \mathbf{20V}$$

$$V_{3\mu\text{F}} = 60 - 20 = \mathbf{40V}$$

- (b) Hence $w = 1/2 C v^2$

$$W_{4\mu\text{F}} = 1/2 \times 4 \times 10^{-6} \times 3600 = \mathbf{7.2mJ}$$

$$W_{2\mu\text{F}} = 1/2 \times 2 \times 10^{-6} \times 3600 = \mathbf{3.6mJ}$$

$$W_{6\mu\text{F}} = 1/2 \times 6 \times 10^{-6} \times 400 = \mathbf{1.2mJ}$$

$$W_{3\mu\text{F}} = 1/2 \times 3 \times 10^{-6} \times 1600 = \mathbf{2.4mJ}$$

Solution 6.24

In the circuit shown in Fig. 6.58 assume that the capacitors were initially uncharged and that the current source has been connected to the circuit long enough for all the capacitors to reach steady-state (no current flowing through the capacitors), determine the voltage across each capacitor and the energy stored in each.

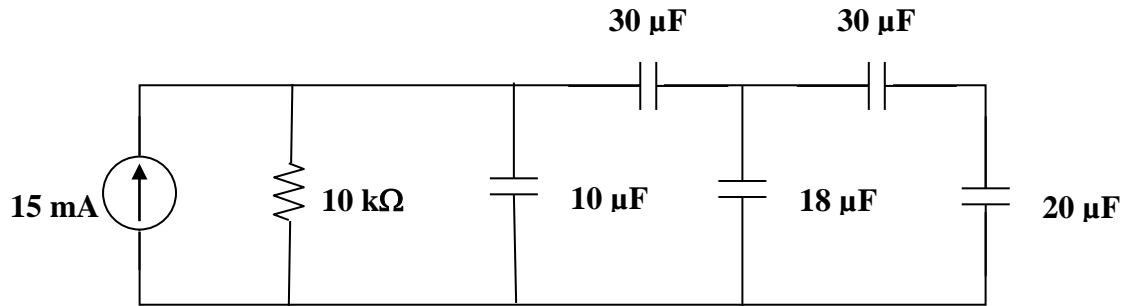


Figure 6.58
For Prob. 6.24.

Solution

Reducing the capacitance starting from right to left. $30\mu\text{F}$ in series with $20\mu\text{F}$ we get, $30 \times 20\mu\text{F} / (30 + 20) = 12\mu\text{F}$ in parallel with $18\mu\text{F}$ we get $(12 + 18)\mu\text{F} = 30\mu\text{F}$.

Now

$$v_{10} = 15 \times 10 = \mathbf{150 \text{ V}} \text{ and } w_{10} = 0.5 \times 10 \times 150^2 \times 10^{-6} = \mathbf{112.5 \text{ mJ}}$$

$$v_{30} = \mathbf{75 \text{ V}} \text{ and } w_{30} = 0.5 \times 30 \times 75^2 \times 10^{-6} = \mathbf{84.38 \text{ mJ}}$$

$$v_{18} = \mathbf{75 \text{ V}} \text{ and } w_{18} = 0.5 \times 18 \times 75^2 \times 10^{-6} = \mathbf{50.62 \text{ mJ}}$$

$$v_{30} = [20 / (30 + 20)] 75 = \mathbf{30 \text{ V}} \text{ and } w_{30} = 0.5 \times 30 \times 30^2 \times 10^{-6} = \mathbf{13.5 \text{ mJ}}$$

$$v_{20} = [30 / (30 + 20)] 75 = \mathbf{45 \text{ V}} \text{ and } w_{20} = 0.5 \times 20 \times 45^2 \times 10^{-6} = \mathbf{20.25 \text{ mJ}}$$

Solution 6.25

(a) For the capacitors in series,

$$Q_1 = Q_2 \longrightarrow C_1 v_1 = C_2 v_2 \longrightarrow \frac{v_1}{v_2} = \frac{C_2}{C_1}$$

$$v_s = v_1 + v_2 = \frac{C_2}{C_1} v_2 + v_2 = \frac{C_1 + C_2}{C_1} v_2 \longrightarrow v_2 = \frac{C_1}{C_1 + C_2} v_s$$

Similarly, $v_1 = \frac{C_2}{C_1 + C_2} v_s$

(b) For capacitors in parallel

$$v_1 = v_2 = \frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

$$Q_s = Q_1 + Q_2 = \frac{C_1}{C_2} Q_2 + Q_2 = \frac{C_1 + C_2}{C_2} Q_2$$

or

$$Q_2 = \frac{C_2}{C_1 + C_2} Q_s$$

$$Q_1 = \frac{C_1}{C_1 + C_2} Q_s$$

$$i = \frac{dQ}{dt} \longrightarrow i_1 = \frac{C_1}{C_1 + C_2} i_s, \quad i_2 = \frac{C_2}{C_1 + C_2} i_s$$

Solution 6.26

Three capacitors, $C_1 = 5 \mu\text{F}$, $C_2 = 10 \mu\text{F}$, and $C_3 = 20 \mu\text{F}$, are connected in parallel across a 200-V source. Determine:

- (a) the total capacitance,
- (b) the charge on each capacitor,
- (c) the total energy stored in the parallel combination.

Solution

(a) $C_{eq} = C_1 + C_2 + C_3 = \mathbf{35\mu F}$

(b) $Q_1 = C_1 v = 5 \times 200 \mu\text{C} = \mathbf{1 \text{ mC}}$
 $Q_2 = C_2 v = 10 \times 200 \mu\text{C} = \mathbf{2 \text{ mC}}$
 $Q_3 = C_3 v = 20 \times 200 \mu\text{C} = \mathbf{4 \text{ mC}}$

(c) $w = \frac{1}{2} C_{eq} v^2 = \frac{1}{2} \times 35 \times 200^2 \mu\text{J} = \mathbf{700 \text{ mJ}}$

Solution 6.27

Given that four 10- μF capacitors can be connected in series and in parallel, find the minimum and maximum values that can be obtained by such series/parallel combinations.

Solution

If they are all connected in parallel, we get $C_{\text{total}} = 4 \times 10 \mu\text{F} = 40 \mu\text{F}$.


If they are all connected in series, we get $C_{\text{total}} = 1/(4/10 \mu\text{F}) = 2.5 \mu\text{F}$.

Since all other combinations fall within these two extreme cases. Thus,

$C_{\text{min}} = 2.5 \mu\text{F}$, $C_{\text{max}} = 40 \mu\text{F}$.

Solution 6.28

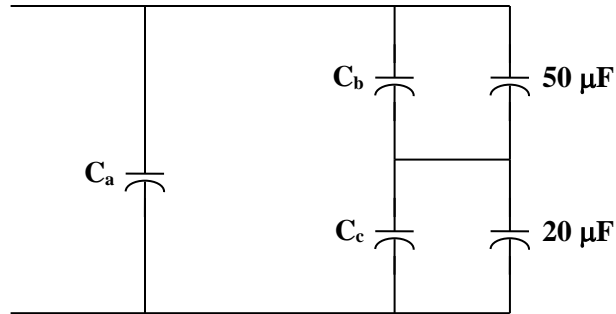We may treat this like a resistive circuit and apply delta-wye transformation, except that R is replaced by $1/C$.



$$\frac{1}{C_a} = \frac{\left(\frac{1}{10}\right)\left(\frac{1}{40}\right) + \left(\frac{1}{10}\right)\left(\frac{1}{30}\right) + \left(\frac{1}{30}\right)\left(\frac{1}{40}\right)}{\frac{1}{30}}$$

$$= \frac{3}{40} + \frac{1}{10} + \frac{1}{40} = \frac{2}{10}$$

$$C_a = 5\mu\text{F}$$

$$\frac{1}{C_b} = \frac{\frac{1}{400} + \frac{1}{300} + \frac{1}{1200}}{\frac{1}{10}} = \frac{2}{30}$$

$$C_b = 15\mu\text{F}$$

$$\frac{1}{C_c} = \frac{\frac{1}{400} + \frac{1}{300} + \frac{1}{1200}}{\frac{1}{40}} = \frac{4}{15}$$

$$C_c = 3.75\mu\text{F}$$

$$C_b \text{ in parallel with } 50\mu\text{F} = 50 + 15 = 65\mu\text{F}$$

$$C_c \text{ in series with } 20\mu\text{F} = 23.75\mu\text{F}$$

$$65\mu\text{F} \text{ in series with } 23.75\mu\text{F} = \frac{65 \times 23.75}{88.75} = 17.39\mu\text{F}$$

$$17.39\mu\text{F} \text{ in parallel with } C_a = 17.39 + 5 = 22.39\mu\text{F}$$

$$\text{Hence } C_{eq} = \mathbf{22.39\mu\text{F}}$$

Solution 6.29


(a) C in series with $C = C/(2)$

$C/2$ in parallel with $C = 3C/2$

$$\frac{3C}{2} \text{ in series with } C = \frac{Cx \frac{3C}{2}}{5 \frac{C}{2}} = \frac{3C}{5}$$

$$3 \frac{C}{5} \text{ in parallel with } C = C + 3 \frac{C}{5} = \mathbf{1.6 C}$$

(b)

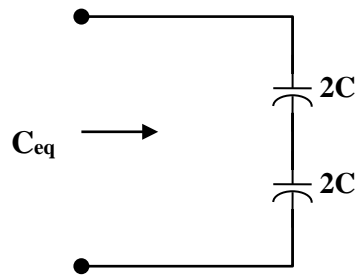

$$\frac{1}{C_{eq}} = \frac{1}{2C} + \frac{1}{2C} = \frac{1}{C}$$

$$C_{eq} = \mathbf{1 C}$$

Solution 6.30

$$v_o = \frac{1}{C} \int_0^t i dt + i(0)$$

For $0 < t < 1$, $i = 90t$ mA,

$$v_o = \frac{10^{-3}}{3 \times 10^{-6}} \int_0^t 90t dt + 0 = 15t^2 \text{ kV}$$
$$v_o(1) = 15 \text{ kV}$$

For $1 < t < 2$, $i = (180 - 90t)$ mA,

$$v_o = \frac{10^{-3}}{3 \times 10^{-6}} \int_1^t (180 - 90t) dt + v_o(1)$$
$$= [60t - 15t^2]_1^t + 15 \text{ kV}$$
$$= [60t - 15t^2 - (60 - 15) + 15] \text{ kV} = [60t - 15t^2 - 30] \text{ kV}$$

$$v_o(t) = \begin{cases} 15t^2 \text{ kV}, & 0 < t < 1 \\ [60t - 15t^2 - 30] \text{ kV}, & 1 < t < 2 \end{cases}$$

Solution 6.31

$$i_s(t) = \begin{cases} 30tmA, & 0 < t < 1 \\ 30mA, & 1 < t < 3 \\ -75 + 15t, & 3 < t < 5 \end{cases}$$

$$C_{eq} = 4 + 6 = 10\mu F$$

$$v = \frac{1}{C_{eq}} \int_0^t i dt + v(0)$$

For $0 < t < 1$,

$$v = \frac{10^{-3}}{10 \times 10^{-6}} \int_0^t 30t dt + 0 = 1.5t^2 \text{ kV}$$

For $1 < t < 3$,

$$\begin{aligned} v &= \frac{10^3}{10} \int_1^t 20dt + v(1) = [3(t-1) + 1.5]kV \\ &= [3t - 1.5]kV \end{aligned}$$

For $3 < t < 5$,

$$\begin{aligned} v &= \frac{10^3}{10} \int_3^t 15(t-5)dt + v(3) \\ &= \left[1.5 \frac{t^2}{2} - 7.5t \right] \Big|_3^t + 7.5kV = [0.75t^2 - 7.5t + 23.25]kV \end{aligned}$$

$$v(t) = \begin{cases} 1.5t^2kV, & 0 < t < 1s \\ [3t - 1.5]kV, & 1 < t < 3s \\ [0.75t^2 - 7.5t + 23.25]kV, & 3 < t < 5s \end{cases}$$

$$i_1 = C_1 \frac{dv}{dt} = 6 \times 10^{-6} \frac{dv}{dt}$$

$$i_1 = \begin{cases} 18tmA, & 0 < t < 1s \\ 18mA, & 1 < t < 3s \\ [9t - 45]mA, & 3 < t < 5s \end{cases}$$

$$i_2 = C_2 \frac{dv}{dt} = 4 \times 10^{-6} \frac{dv}{dt}$$

$$i_2 = \begin{cases} 12t \text{mA}, & 0 < t < 1\text{s} \\ 12 \text{mA}, & 1 < t < 3\text{s} \\ [6t - 30] \text{mA}, & 3 < t < 5\text{s} \end{cases}$$

Solution 6.32

In the circuit in Fig. 6.64, let $i_s = 4.5e^{-2t}$ mA and the voltage across each capacitor is equal to zero at $t = 0$. Determine v_1 and v_2 and the energy stored in each capacitor for all $t > 0$.

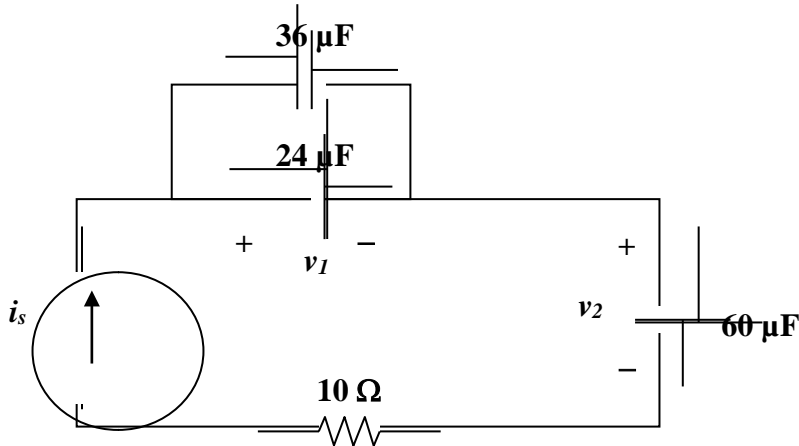


Figure 6.64
For Prob. 6.32.

Solution

Combining the $36\ \mu\text{F}$ with the $24\ \mu\text{F}$ we get $60\ \mu\text{F}$ which leads to $v_1 = \frac{1}{60\mu} \int_0^t 4.5e^{-2\tau} m d\tau$
 $= [37.5 - 37.5e^{-2t}] \text{ V} = v_2$.

$$(v_1)^2 = [(37.5)^2 - 2(37.5)^2e^{-2t} + (37.5)^2e^{-4t}] = 1406.25[1 - 2e^{-2t} + e^{-4t}] = (v_2)^2$$

$$w_{24} = 0.5 \times 24 \times 10^{-6} (v_1)^2 = \mathbf{16.875[1 - 2e^{-2t} + e^{-4t}] \text{ mJ}}$$

$$w_{36} = 0.5 \times 36 \times 10^{-6} (v_1)^2 = \mathbf{25.31[1 - 2e^{-2t} + e^{-4t}] \text{ mJ}}$$

$$w_{60} = 0.5 \times 60 \times 10^{-6} (v_2)^2 = \mathbf{42.19[1 - 2e^{-2t} + e^{-4t}] \text{ mJ}}$$

Solution 6.33

Because this is a totally capacitive circuit, we can combine all the capacitors using the property that capacitors in parallel can be combined by just adding their values and we combine capacitors in series by adding their reciprocals. However, for this circuit we only have the three capacitors in parallel.

$$3 \text{ F} + 2 \text{ F} = 5 \text{ F} \text{ (we need this to be able to calculate the voltage)}$$

$$C_{\text{Th}} = C_{\text{eq}} = 5 + 3 + 2 = 10 \text{ F}$$

The voltage will divide equally across the two 5 F capacitors. Therefore, we get:

$$V_{\text{Th}} = \mathbf{15 \text{ V}}, \quad C_{\text{Th}} = \mathbf{10 \text{ F}}.$$

15 V, 10 F

Solution 6.34

The current through a 25-mH inductor is $10e^{-t/2}$ A. Find the voltage and the power at $t = 3$ s.

Solution

$$i = 10e^{-t/2}$$

$$\begin{aligned} v &= L \frac{di}{dt} = 25 \times 10^{-3} (10) \left(\frac{-1}{2} \right) e^{-t/2} \\ &= -125e^{-t/2} \text{ mV} \end{aligned}$$

$$v(3) = -125e^{-3/2} \text{ mV} = \mathbf{-27.89 \text{ mV}}$$

$$p = vi = -1.25e^{-t} \text{ W}$$

$$p(3) = -1.25e^{-3} \text{ W} = \mathbf{-62.23 \text{ mW}}.$$

Solution 6.35

An inductor has a linear change in current from 100 mA to 200 mA in 2 ms and induces a voltage of 160 mV. Calculate the value of the inductor.

Solution

$$v = L(di/dt) \text{ or } L = v/(di/dt)$$

Clearly $di/dt = (0.2-0.1)/0.002 = 50$ amp/sec. Thus,

$$L = 0.16/50 = \mathbf{3.2 \text{ mH}}.$$

Solution 6.36

Design a problem to help other students to better understand how inductors work.

Although there are many ways to work this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

The current through a 12-mH inductor is $i(t) = 30te^{-2t}$ A, $t \geq 0$. Determine: (a) the voltage across the inductor, (b) the power being delivered to the inductor at $t = 1$ s, (c) the energy stored in the inductor at $t = 1$ s.

Solution

$$(a) \ v = L \frac{di}{dt} = 12 \times 10^{-3} (30e^{-2t} - 60te^{-2t}) = \underline{(0.36 - 0.72t)e^{-2t} \text{ V}}$$

$$(b) \ p = vi = (0.36 - 0.72 \times 1)e^{-2} \times 30 \times 1e^{-2} = 0.36 \times 30e^{-4} = \underline{-0.1978 \text{ W}}$$

$$(c) \ w = \frac{1}{2} Li^2 = 0.5 \times 12 \times 10^{-3} (30 \times 1e^{-2})^2 = \underline{\underline{98.9 \text{ mJ}}}.$$

Solution 6.37

$$v = L \frac{di}{dt} = 12 \times 10^{-3} \times 4(100) \cos 100t$$
$$= \mathbf{4.8 \cos (100t) \text{ V}}$$

$$p = vi = 4.8 \times 4 \sin 100t \cos 100t = 9.6 \sin 200t$$

$$w = \int_0^t p dt = \int_0^{11/200} 9.6 \sin 200t$$
$$= -\frac{9.6}{200} \cos 200t \Big|_0^{11/200} \text{ J}$$
$$= -48(\cos \pi - 1) \text{ mJ} = \mathbf{96 \text{ mJ}}$$

Please note that this problem could have also been done by using $(1/2)Li^2$.

Chapter 6.38

$$\begin{aligned} v &= L \frac{di}{dt} = 40 \times 10^{-3} (e^{-2t} - 2te^{-2t}) dt \\ &= 40(1 - 2t)e^{-2t} \text{ mV}, t > 0 \end{aligned}$$

Solution 6.39

The voltage across a 50-mH inductor is given by

$$v(t) = [5e^{-2t} + 2t + 4] \text{ V for } t > 0.$$

Determine the current $i(t)$ through the inductor. Assume that $i(0) = 0$ A.

Solution

$$v = L \frac{di}{dt} \longrightarrow i = \frac{1}{L} \int_0^t i d\tau + i(0)$$

$$i = \frac{1}{50 \times 10^{-3}} \int_0^t (5e^{-2\tau} + 2\tau + 4) d\tau + 0$$

$$= 20(-2.5e^{-2\tau} + \tau^2 + 4\tau) \Big|_0^t$$

$$i(t) = [-50e^{-2t} + 50 + 20t^2 + 80t] \text{ A.}$$

Solution 6.40

$$i = \begin{cases} 5t, & 0 < t < 2\text{ms} \\ 10, & 2 < t < 4\text{ms} \\ 30 - 5t, & 4 < t < 6\text{ms} \end{cases}$$

$$v = L \frac{di}{dt} = \frac{5 \times 10^{-3}}{10^{-3}} \begin{cases} 5, & 0 < t < 2\text{ms} \\ 0, & 2 < t < 4\text{ms} \\ -5, & 4 < t < 6\text{ms} \end{cases} = \begin{cases} 25, & 0 < t < 2\text{ms} \\ 0, & 2 < t < 4\text{ms} \\ -25, & 4 < t < 6\text{ms} \end{cases}$$

At $t = 1\text{ms}$, $v = \mathbf{25\text{ V}}$

At $t = 3\text{ms}$, $v = \mathbf{0\text{ V}}$

At $t = 5\text{ms}$, $v = \mathbf{-25\text{ V}}$

Solution 6.41

$$\begin{aligned}
 i &= \frac{1}{L} \int_0^t v dt + C = \left(\frac{1}{2} \right) \int_0^t 20(1 - e^{-2t}) dt + C \\
 &= 10 \left(t + \frac{1}{2} e^{-2t} \right) \Big|_0^t + C = 10t + 5e^{-2t} - 4.7 \text{ A}
 \end{aligned}$$

Note, we get $C = -4.7$ from the initial condition for i needing to be 0.3 A.

We can check our results by solving for $v = L di/dt$.

$$v = 2(10 - 10e^{-2t}) \text{ V which is what we started with.}$$

$$\text{At } t = 1 \text{ s, } i = 10 + 5e^{-2} - 4.7 = 10 + 0.6767 - 4.7 = \mathbf{5.977 \text{ A}}$$

$$w = \frac{1}{2} L i^2 = \mathbf{35.72 \text{ J}}$$

Solution 6.42

$$i = \frac{1}{L} \int_0^t v dt + i(0) = \frac{1}{5} \int_0^t v(t) dt - 1$$

$$\text{For } 0 < t < 1, \quad i = \frac{10}{5} \int_0^t dt - 1 = 2t - 1 \text{ A}$$

$$\text{For } 1 < t < 2, \quad i = 0 + i(1) = 1 \text{ A}$$

$$\begin{aligned} \text{For } 2 < t < 3, \quad i &= \frac{1}{5} \int 10 dt + i(2) = 2t \Big|_2^t + 1 \\ &= 2t - 3 \text{ A} \end{aligned}$$

$$\text{For } 3 < t < 4, \quad i = 0 + i(3) = 3 \text{ A}$$

$$\begin{aligned} \text{For } 4 < t < 5, \quad i &= \frac{1}{5} \int_4^t 10 dt + i(4) = 2t \Big|_4^t + 3 \\ &= 2t - 5 \text{ A} \end{aligned}$$

Thus,

$$i(t) = \begin{cases} 2t - 1 \text{ A}, & 0 < t < 1 \\ 1 \text{ A}, & 1 < t < 2 \\ 2t - 3 \text{ A}, & 2 < t < 3 \\ 3 \text{ A}, & 3 < t < 4 \\ 2t - 5, & 4 < t < 5 \end{cases}$$

Solution 6.43

The current in a 150-mH inductor increases from 0 to 60 mA (steady-state). How much energy is stored in the inductor?

Solution

$$w = (1/2)L(i(t))^2 = 0.5 \times 0.15 \times 0.06^2 = \mathbf{270 \mu J}.$$

Solution 6.44

A 100-mH inductor is connected in parallel with a 2-k Ω resistor. The current through the inductor is $i(t) = 35e^{-400t}$ mA.

(a) Find the voltage $v_L(t)$ across the inductor. (b) Find the voltage $v_R(t)$ across the resistor. (c) Is $v_R(t) + v_L(t) = 0$? (d) Calculate the energy stored in the inductor at $t=0$.

Solution

(a) $v_L(t) = L di/dt = 0.1(-400)0.035e^{-400t} = \mathbf{1.4e^{-400t} \text{ V}}$.

(b) Since R and L are in parallel, $v_R(t) = v_L(t) = \mathbf{1.4e^{-400t} \text{ V}}$.

(c) Again, since the two elements are in parallel, $v_R(t) = v_L(t) = 1.4e^{-400t}$ V thus, $v_R(t) + v_L(t) = 2.8e^{-400t}$ and **not equal to zero!**

(d) $w = 0.5Li^2 = 0.5(0.1)(0.035)^2 = \mathbf{61.25 \text{ }\mu\text{J}}$.

Solution 6.45

If the voltage waveform in Fig. 6.68 is applied to a 25-mH inductor, find the inductor current $i(t)$ for $0 < t < 2$ seconds. Assume $i(0) = 0$.

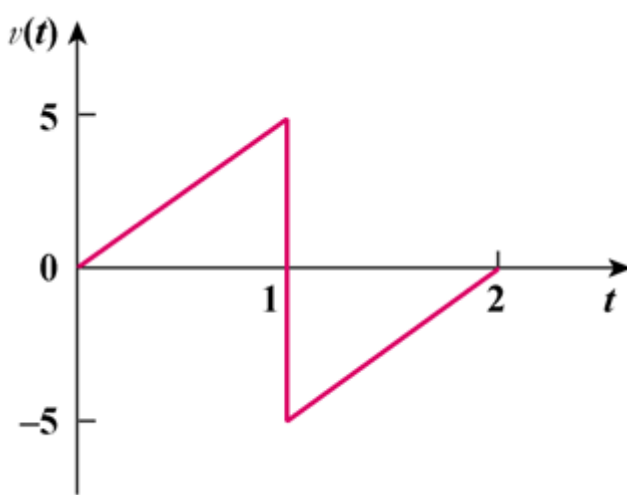


Figure 6.68
For Prob. 6.45.

Solution

$$i(t) = \frac{1}{L} \int_0^t v(t) dt + i(0)$$

For $0 < t < 1$, $v = 5t$


$$\begin{aligned} i &= \frac{1}{25 \times 10^{-3}} \int_0^t 5t dt + 0 \\ &= \mathbf{100t^2 \text{ A.}} \end{aligned}$$

For $1 < t < 2$, $v = -10 + 5t$

$$\begin{aligned} i &= \frac{1}{25 \times 10^{-3}} \int_1^t (-10 + 5t) dt + i(1) \\ &= \left(\int_1^t (0.2\tau - 0.4) d\tau + 0.1 \right) \text{ kA} = \{ [0.1\tau^2 - 0.4\tau]_1^t + 0.1 \} \text{ kA} \\ &= \mathbf{[400 - 400t + 100t^2] \text{ A.}} \end{aligned}$$

Solution 6.46

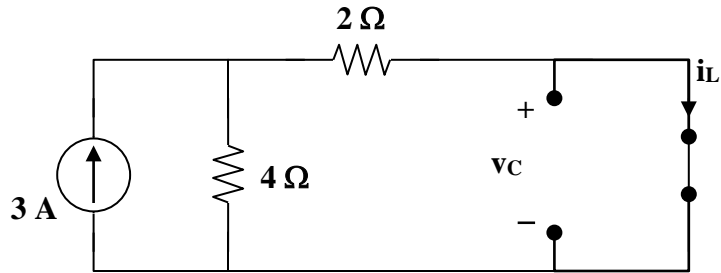Under dc conditions, the circuit is as shown below:



By current division,


$$i_L = \frac{4}{4+2}(3) = \mathbf{2A}, \quad v_C = \mathbf{0V}$$

$$w_L = \frac{1}{2}L i_L^2 = \frac{1}{2}\left(\frac{1}{2}\right)(2)^2 = \mathbf{1J}$$

$$w_C = \frac{1}{2}C v_C^2 = \frac{1}{2}(2)(0) = \mathbf{0J}$$

Solution 6.47

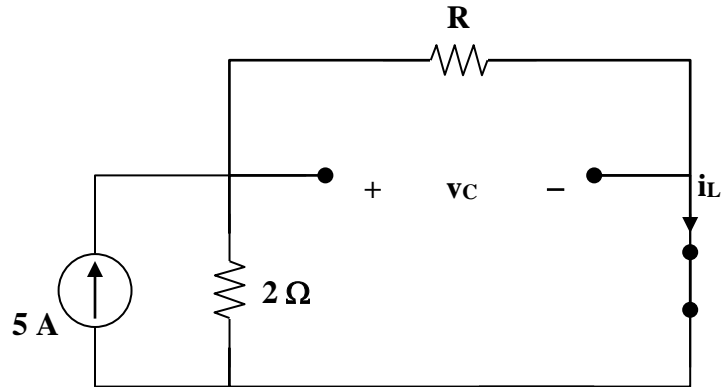Under dc conditions, the circuit is equivalent to that shown below:



$$i_L = \frac{2}{R+2}(5) = \frac{10}{R+2}, \quad v_c = Ri_L = \frac{10R}{R+2}$$

$$w_c = \frac{1}{2}Cv_c^2 = 80 \times 10^{-6} \times \frac{100R^2}{(R+2)^2}$$

$$w_L = \frac{1}{2}Li_L^2 = 2 \times 10^{-3} \times \frac{100}{(R+2)^2}$$

If $w_c = w_L$,

$$80 \times 10^{-6} \times \frac{100R^2}{(R+2)^2} = \frac{2 \times 10^{-3} \times 100}{(R+2)^2} \rightarrow 80 \times 10^{-3} R^2 = 2$$

$$R = 5\Omega$$

Solution 6.48

Under steady-state dc conditions, find i and v in the circuit in Fig. 6.71.

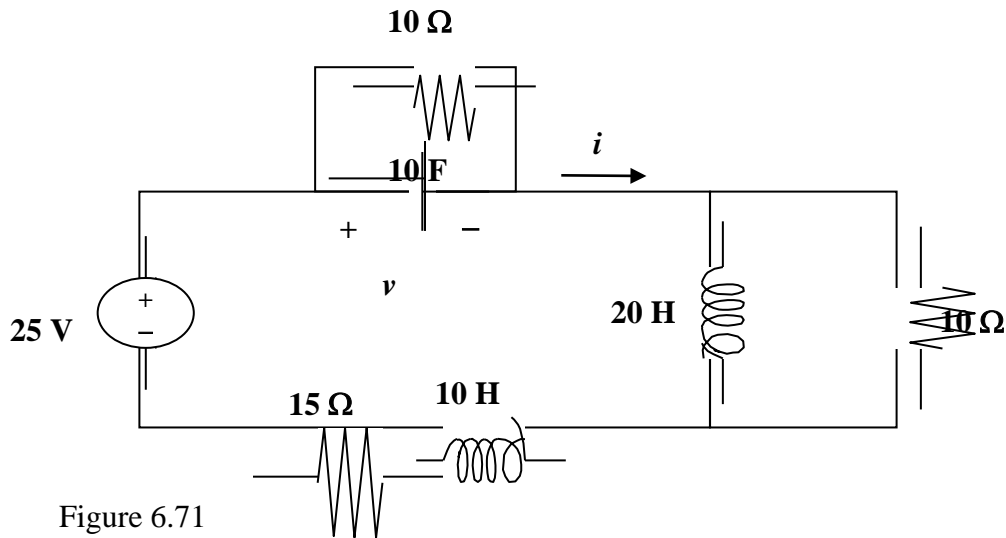


Figure 6.71
For Prob. 6.48.

Solution

Under steady-state, the inductor acts like a short-circuit, while the capacitor acts like an open circuit. Thus the resistor on the right is shorted out and the voltage source only sees the top 10 Ω resistor in series with the 15 Ω resistor for a total of 25 Ω.

Thus $i = 25/25 = 1 \text{ A}$ and $v = 10 \times 1 = 10 \text{ V}$.

Solution 6.49

Find the equivalent inductance of the circuit in Fig. 6.72. Assume all inductors are 40 mH.


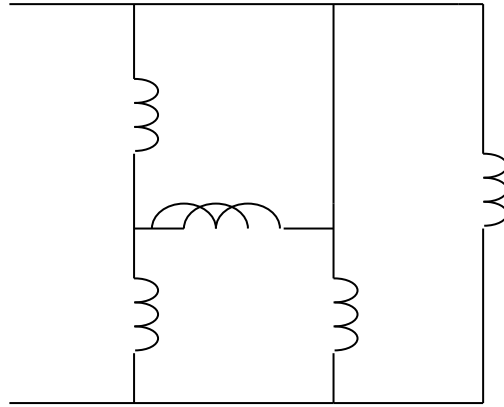


Figure 6.72
For Prob. 6.49.

Solution

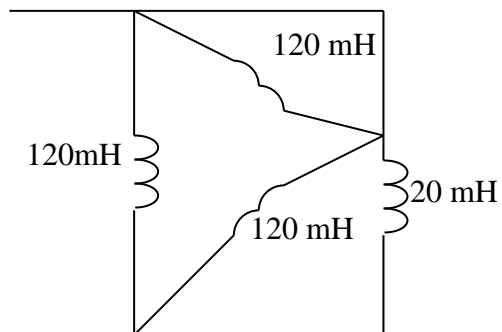Converting the wye-subnetwork to its equivalent delta gives the circuit below.



$$120 \parallel 0 = 0, \quad 120 \parallel 20 = 120 \times 20 / 140 = 17.14286 \text{ mH.}$$

Finally,

$$L_{eq} = 0.12 \times 0.01714286 / (0.12 + 0.01714286) = \mathbf{15 \text{ mH.}}$$

Solution 6.50

16mH in series with 14 mH = $16+14=30$ mH

24 mH in series with 36 mH = $24+36=60$ mH

30mH in parallel with 60 mH = $30 \times 60 / 90 = \mathbf{20\ mH}$

Solution 6.51

$$\frac{1}{L} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30} = \frac{1}{10} \quad L = 10 \text{ mH}$$

$$L_{\text{eq}} = 10 \parallel (25 + 10) = \frac{10 \times 35}{45}$$

$$= \mathbf{7.778 \text{ mH}}$$

Solution 6.52

Using Fig. 6.74, design a problem to help other students better understand how inductors behave when connected in series and when connected in parallel.

Although there are many ways to work this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

Find L_{eq} in the circuit of Fig. 6.74.

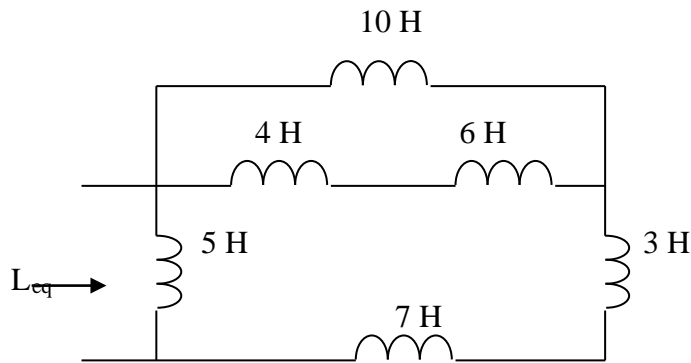


Figure 6.74 For Prob. 6.52.

Solution

$$L_{eq} = 5 // (7 + 3 + 10 // (4 + 6)) = 5 // (7 + 3 + 5) = \frac{5 \times 15}{20} = \underline{3.75 \text{ H}}$$

Solution 6.53

$$L_{\text{eq}} = 6 + 10 + 8 \parallel [5 \parallel (8 + 12) + 6 \parallel (8 + 4)]$$

$$= 16 + 8 \parallel (4 + 4) = 16 + 4$$

$$L_{\text{eq}} = \mathbf{20 \text{ mH}}$$

Solution 6.54

Find the equivalent inductance looking into the terminals of the circuit in Fig. 6.76.

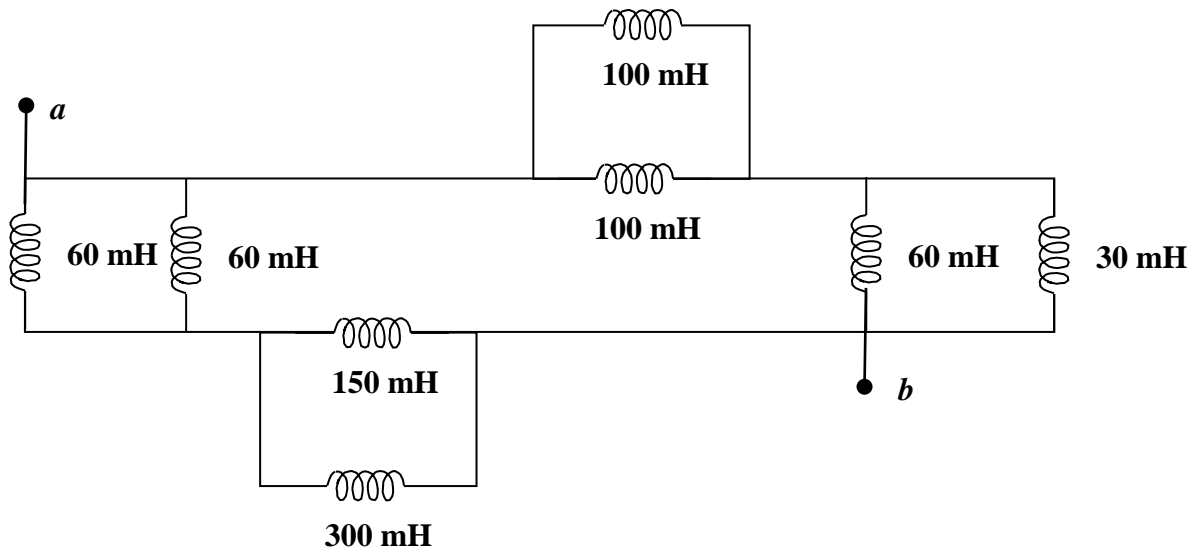


Figure 6.76
For Prob. 6.54.

Solution

The parallel combinations gives us $L_{6060} = [60 \times 60 / (60 + 60)] \text{ mH} = 30 \text{ mH}$;
 $L_{150300} = [150 \times 300 / (150 + 300)] \text{ mH} = 100 \text{ mH}$; $L_{6030} = [60 \times 30 / (60 + 30)] \text{ mH} = 20 \text{ mH}$; and $L_{100100} = [100 \times 100 / (100 + 100)] \text{ mH} = 50 \text{ mH}$.

We now have inductors in series and then in parallel or $L_{30100} = 130 \text{ mH}$ and $L_{2050} = 70 \text{ mH}$ and finally we get $L_{ab} = [130 \times 70 / (130 + 70)] \text{ mH} = \mathbf{45.5 \text{ mH}}$.

Solution 6.55

(a) $L//L = 0.5L$, $L + L = 2L$

$$L_{eq} = L + 2L // 0.5L = L + \frac{2L \times 0.5L}{2L + 0.5L} = \underline{1.4L} = \mathbf{1.4 L}.$$


(b) $L//L = 0.5L$, $L//L + L//L = L$

$$L_{eq} = L//L = \mathbf{500 \text{ mL}}$$

Solution 6.56

$$L \parallel L \parallel L = \frac{1}{\frac{1}{L} + \frac{1}{L} + \frac{1}{L}} = \frac{L}{3}$$

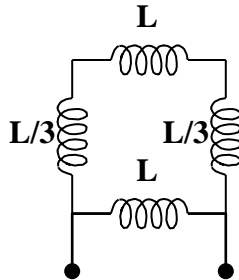Hence the given circuit is equivalent to that shown below:



$$L_{eq} = L \parallel \left(L + \frac{2}{3}L \right) = \frac{L \times \frac{5}{3}L}{L + \frac{5}{3}L} = \frac{5}{8}L$$

Solution 6.57

$$\text{Let } v = L_{\text{eq}} \frac{di}{dt} \quad (1)$$

$$v = v_1 + v_2 = 4 \frac{di}{dt} + v_2 \quad (2)$$

$$i = i_1 + i_2 \longrightarrow i_2 = i - i_1 \quad (3)$$

$$v_2 = 3 \frac{di_1}{dt} \text{ or } \frac{di_1}{dt} = \frac{v_2}{3} \quad (4)$$

and

$$\begin{aligned} -v_2 + 2 \frac{di}{dt} + 5 \frac{di_2}{dt} &= 0 \\ v_2 &= 2 \frac{di}{dt} + 5 \frac{di_2}{dt} \end{aligned} \quad (5)$$

Incorporating (3) and (4) into (5),

$$v_2 = 2 \frac{di}{dt} + 5 \frac{di}{dt} - 5 \frac{di_1}{dt} = 7 \frac{di}{dt} - 5 \frac{v_2}{3}$$

$$v_2 \left(1 + \frac{5}{3} \right) = 7 \frac{di}{dt}$$

$$v_2 = \frac{21}{8} \frac{di}{dt}$$

Substituting this into (2) gives

$$v = 4 \frac{di}{dt} + \frac{21}{8} \frac{di}{dt}$$

$$= \frac{53}{8} \frac{di}{dt}$$


Comparing this with (1),

$$L_{\text{eq}} = \frac{53}{8} = \mathbf{6.625 \text{ H}}$$

Solution 6.58

$$v = L \frac{di}{dt} = 3 \frac{di}{dt} = 3 \times \text{slope of } i(t).$$

Thus v is sketched below:

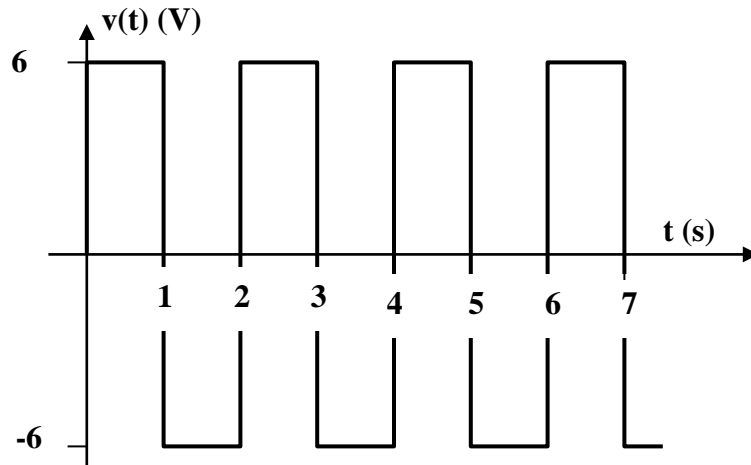

Solution 6.59

$$(a) \quad v_s = (L_1 + L_2) \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{v_s}{L_1 + L_2}$$

$$v_1 = L_1 \frac{di}{dt}, \quad v_2 = L_2 \frac{di}{dt}$$

$$v_1 = \frac{L_1}{L_1 + L_2} v_s, \quad v_2 = \frac{L_2}{L_1 + L_2} v_s$$

$$(b) \quad v_1 = v_2 = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt}$$

$$i_s = i_1 + i_2$$

$$\frac{di_s}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} = \frac{v}{L_1} + \frac{v}{L_2} = v \frac{(L_1 + L_2)}{L_1 L_2}$$

$$i_1 = \frac{1}{L_1} \int v dt = \frac{1}{L_1} \int \frac{L_1 L_2}{L_1 + L_2} \frac{di_s}{dt} dt = \frac{L_2}{L_1 + L_2} i_s$$

$$i_2 = \frac{1}{L_2} \int v dt = \frac{1}{L_2} \int \frac{L_1 L_2}{L_1 + L_2} \frac{di_s}{dt} dt = \frac{L_1}{L_1 + L_2} i_s$$

Solution 6.60

$$L_{eq} = 3 // 5 = \frac{15}{8}$$

$$v_o = L_{eq} \frac{di}{dt} = \frac{15}{8} \frac{d}{dt} (4e^{-2t}) = \underline{-15e^{-2t}}$$

$$i_o = \frac{1}{L} \int_0^t v_o(t) dt + i_o(0) = 2 + \frac{1}{5} \int_0^t (-15)e^{-2t} dt = 2 + 1.5e^{-2t} \Big|_0^t$$

$$i_o = \mathbf{(0.5 + 1.5e^{-2t}) \text{ A}}$$

Solution 6.61

$$(a) \quad L_{eq} = 20 // (4 + 6) = 20 \times 10 / 30 = \underline{6.667 \text{ mH}}$$

Using current division,

$$i_1(t) = \frac{10}{10 + 20} i_s = \underline{e^{-t} \text{ mA}}$$

$$i_2(t) = \underline{2e^{-t} \text{ mA}}$$

$$(b) \quad v_o = L_{eq} \frac{di_s}{dt} = \frac{20}{3} \times 10^{-3} (-3e^{-t} \times 10^{-3}) = \underline{-20e^{-t} \mu\text{V}}$$

$$(c) \quad w = \frac{1}{2} L i_1^2 = \frac{1}{2} \times 20 \times 10^{-3} \times e^{-2} \times 10^{-6} = \underline{1.3534 \text{ nJ}}$$

Solution 6.62

Consider the circuit in Fig. 6.84. Given that $v(t) = 12e^{-3t}$ mV for $t > 0$ and $i_1(0) = -30$ mA, find: (a) $i_2(0)$, (b) $i_1(t)$ and $i_2(t)$.

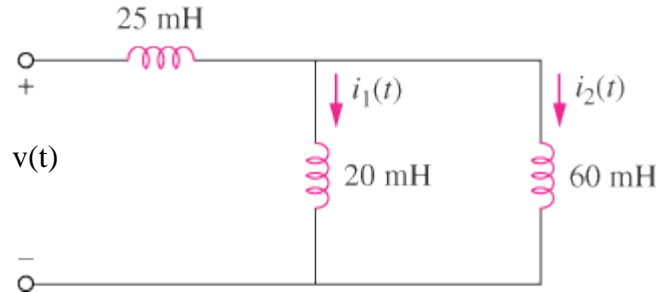


Figure 6.84
For Prob. 6.62.

Solution

$$(a) \quad L_{eq} = 25 + 20 \parallel 60 = 25 + \frac{20 \times 60}{80} = 40 \text{ mH}$$

$$v = L_{eq} \frac{di}{dt} \quad \longrightarrow \quad i = \frac{1}{L_{eq}} \int v(t) dt + i(0) = \frac{10^{-3}}{40 \times 10^{-3}} \int_0^t 12e^{-3t} dt + i(0) = -0.1(e^{-3t} - 1) + i(0)$$

Using current division and the fact that all the currents were zero when the circuit was put together, we get,

$$i_1 = \frac{60}{80}i = \frac{3}{4}i, \quad i_2 = \frac{1}{4}i$$

$$i_1(0) = \frac{3}{4}i(0) \quad \longrightarrow \quad 0.75i(0) = -0.03 \quad \longrightarrow \quad i(0) = -0.04$$

$$i_2 = \frac{1}{4}(-0.1e^{-3t} + 0.06) \text{ A} = (-25e^{-3t} + 15) \text{ mA}$$

$$i_2(0) = -25 + 15 = \mathbf{-10 \text{ mA.}}$$

$$(b) \quad i_1(t) = 0.75(-0.1e^{-3t} + 0.06) = \mathbf{(-75e^{-3t} + 45) \text{ mA}} \text{ and } i_2(t) = \mathbf{(-25e^{-3t} + 15) \text{ mA.}}$$


Solution 6.63

We apply superposition principle and let


$$v_o = v_1 + v_2$$

where v_1 and v_2 are due to i_1 and i_2 respectively.
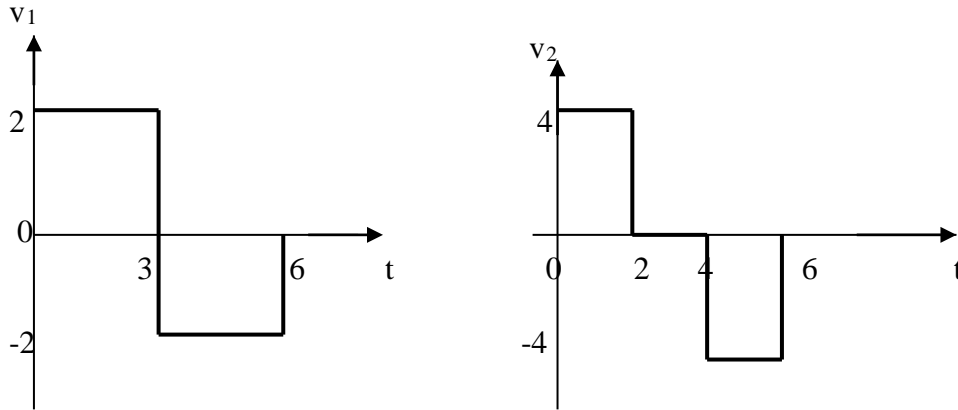
$$v_1 = L \frac{di_1}{dt} = 2 \frac{di_1}{dt} = \begin{cases} 2, & 0 < t < 3 \\ -2, & 3 < t < 6 \end{cases}$$
$$v_2 = L \frac{di_2}{dt} = 2 \frac{di_2}{dt} = \begin{cases} 4, & 0 < t < 2 \\ 0, & 2 < t < 4 \\ -4, & 4 < t < 6 \end{cases}$$



Adding v_1 and v_2 gives v_o , which is shown below.

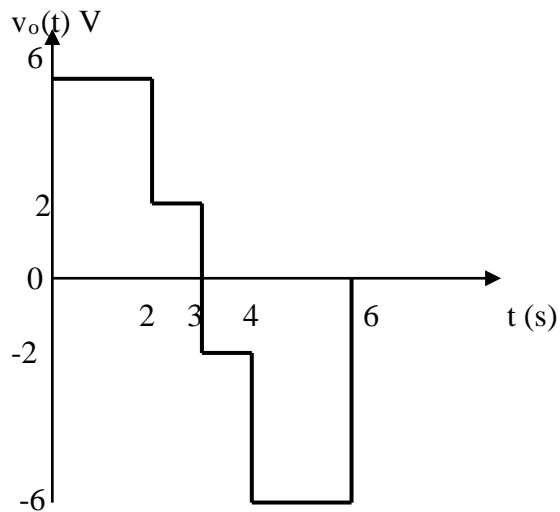

Solution 6.64

(a) When the switch is in position A, $i = -6 = i(0)$

When the switch is in position B, $i(\infty) = 12 / 4 = 3$, $\tau = L / R = 1 / 8$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$i(t) = (3 - 9e^{-8t}) \text{ A}$$

(b) $-12 + 4i(0) + v = 0$, i.e. $v = 12 - 4i(0) = 36 \text{ V}$

(c) At steady state, the inductor becomes a short circuit so that $v = 0 \text{ V}$.

Solution 6.65

$$(a) \quad w_5 = \frac{1}{2} L_1 i_1^2 = \frac{1}{2} \times 5 \times (4)^2 = \mathbf{40 \text{ J}}$$

$$w_{20} = \frac{1}{2} (20)(-2)^2 = \mathbf{40 \text{ J}}$$

$$(b) \quad w = w_5 + w_{20} = \mathbf{80 \text{ J}}$$

$$(c) \quad i_1 = \frac{1}{L_1} \int_0^t -50e^{-200t} dt + i_1(0) = \frac{1}{5} \left(\frac{1}{200} \right) \left(50e^{-200t} \times 10^{-3} \right) \Big|_0^t + 4 \\ = \mathbf{[5 \times 10^{-5} (e^{-200t} - 1) + 4] \text{ A}}$$

$$i_2 = \frac{1}{L_2} \int_0^t -50e^{-200t} dt + i_2(0) = \frac{1}{20} \left(\frac{1}{200} \right) \left(50e^{-200t} \times 10^{-3} \right) \Big|_0^t - 2 \\ = \mathbf{[1.25 \times 10^{-5} (e^{-200t} - 1) - 2] \text{ A}}$$

$$(d) \quad i = i_1 + i_2 = \mathbf{[6.25 \times 10^{-5} (e^{-200t} - 1) + 2] \text{ A}}$$

Solution 6.66

If $v=i$, then

$$i = L \frac{di}{dt} \longrightarrow \frac{dt}{L} = \frac{di}{i}$$

Integrating this gives

$$\frac{t}{L} = \ln(i) - \ln(C_o) = \ln\left(\frac{i}{C_o}\right) \rightarrow i = C_o e^{t/L}$$

$$i(0) = 2 = C_o$$

$$i(t) = 2e^{t/0.02} = 2e^{50t} \text{ A.}$$

Solution 6.67

$$v_o = -\frac{1}{RC} \int v_i dt, RC = 50 \times 10^3 \times 0.04 \times 10^{-6} = 2 \times 10^{-3}$$

$$v_o = \frac{-10^3}{2} \int 10 \sin 50t dt$$

$$v_o = \mathbf{100 \cos(50t) \text{ mV}}$$

Solution 6.68

A 6-V dc voltage is applied to an integrator with $R = 50 \text{ k}\Omega$, $C = 100 \text{ }\mu\text{F}$ at $t = 0$. How long will it take for the op amp to saturate if the saturation voltages are +12 V and -12 V? Assume that the initial capacitor voltage was zero.

Solution

$$v_o = -\frac{1}{RC} \int v_i dt + v_o(0), \quad RC = 50 \times 10^3 \times 100 \times 10^{-6} = 5$$

$$v_o = -\frac{1}{5} \int_0^t 6 d\tau + 0 = -\frac{6t}{5} = -1.2t .$$

The op amp will saturate at $v_o = \pm 12$

$$-12 = -1.2t \longrightarrow t = \mathbf{10 \text{ s}} .$$

Solution 6.69

$$RC = 4 \times 10^6 \times 1 \times 10^{-6} = 4$$

$$v_o = -\frac{1}{RC} \int v_i dt = -\frac{1}{4} \int v_i dt$$

$$\text{For } 0 < t < 1, v_i = 20, v_o = -\frac{1}{4} \int_0^t 20 dt = -5t \text{ mV}$$


$$\begin{aligned} \text{For } 1 < t < 2, v_i = 10, v_o &= -\frac{1}{4} \int_1^t 10 dt + v(1) = -2.5(t-1) - 5 \\ &= -2.5t - 2.5 \text{ mV} \end{aligned}$$

$$\begin{aligned} \text{For } 2 < t < 4, v_i = -20, v_o &= +\frac{1}{4} \int_2^t 20 dt + v(2) = 5(t-2) - 7.5 \\ &= 5t - 17.5 \text{ mV} \end{aligned}$$

$$\begin{aligned} \text{For } 4 < t < 5, v_i = -10, v_o &= \frac{1}{4} \int_4^t 10 dt + v(4) = 2.5(t-4) + 2.5 \\ &= 2.5t - 7.5 \text{ mV} \end{aligned}$$

$$\begin{aligned} \text{For } 5 < t < 6, v_i = 20, v_o &= -\frac{1}{4} \int_5^t 20 dt + v(5) = -5(t-5) + 5 \\ &= -5t + 30 \text{ mV} \end{aligned}$$

Thus $v_o(t)$ is as shown below:

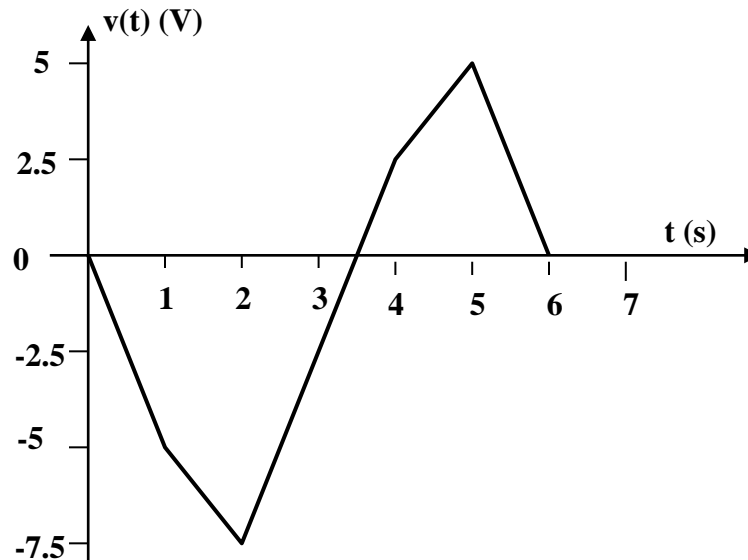

Solution 6.70

Using a single op amp, a capacitor, and resistors of 100 k Ω or less, design a circuit to implement

$$v_o = -2 \int_0^t v_i(\tau) d\tau$$

Assume $v_o = 0$ at $t = 0$.

Solution

One possibility is as follows:

Let $RC = 0.5$ (which produces $(1/RC) = 2$).

Next we need to either pick R or C. Let us choose $R = 100 \text{ k}\Omega$ a practical value. This means that $C = 0.5/10^5 = 5 \text{ }\mu\text{F}$.

Solution 6.71


Show how you would use a single op amp to generate

$$v_o = -\int (v_1 + 4v_2 + 10v_3) dt$$

If the integrating capacitor is $C = 5 \mu\text{F}$, obtain other component values.

Solution

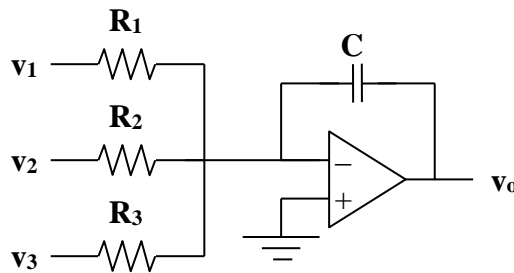By combining a summer with an integrator, we have the circuit below:



$$v_o = -\frac{1}{R_1 C} \int v_1 dt - \frac{1}{R_2 C} \int v_2 dt - \frac{1}{R_3 C} \int v_2 dt$$

For the given problem, $C = 5 \mu\text{F}$,

$$R_1 C = 1 \text{ gives us } R_1 = 1/C = 10^6/5 = \mathbf{200 \text{ k}\Omega}$$

$$R_2 C = 1/4 \text{ gives us } R_2 = 0.25/(C) = 0.25 \times 200 \text{ k}\Omega = \mathbf{50 \text{ k}\Omega}$$

$$R_3 C = 1/10 \text{ gives us } R_3 = 0.1 \times 200 \text{ k}\Omega = \mathbf{20 \text{ k}\Omega}$$

Solution 6.72

The output of the first op amp is

$$v_i = -\frac{1}{RC} \int v_i dt = -\frac{1}{10 \times 10^3 \times 2 \times 10^{-6}} \int_0^t v_i dt = -\frac{100t}{2}$$
$$= -50t$$

$$v_o = -\frac{1}{RC} \int v_i dt = -\frac{1}{20 \times 10^3 \times 0.5 \times 10^{-6}} \int_0^t (-50t) dt$$
$$= 2500t^2$$

At $t = 1.5\text{ms}$,


$$v_o = 2500(1.5)^2 \times 10^{-6} = \mathbf{5.625\text{ mV}}$$

Solution 6.73

Consider the op amp as shown below:

Let $v_a = v_b = v$
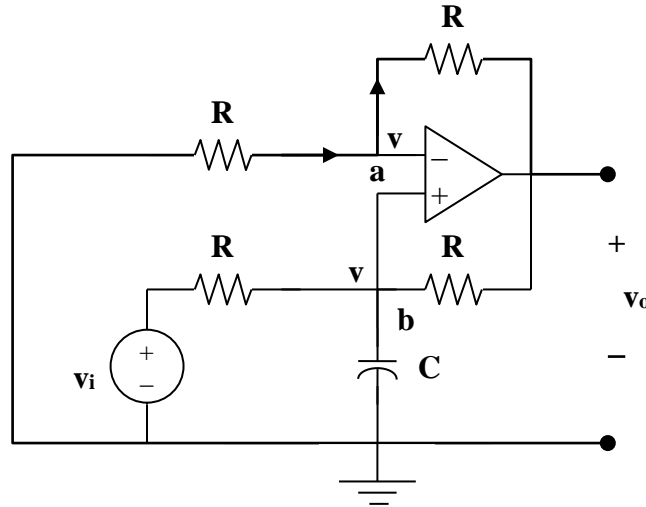
$$\text{At node a, } \frac{0 - v}{R} = \frac{v - v_o}{R} \longrightarrow 2v - v_o = 0 \quad (1)$$



$$\begin{aligned} \text{At node b, } \frac{v_i - v}{R} &= \frac{v - v_o}{R} + C \frac{dv}{dt} \\ v_i &= 2v - v_o + RC \frac{dv}{dt} \end{aligned} \quad (2)$$

Combining (1) and (2),

$$v_i = v_o - v_o + \frac{RC}{2} \frac{dv_o}{dt}$$

or

$$v_o = \frac{2}{RC} \int v_i dt$$

showing that the circuit is a noninverting integrator.


Solution 6.74

$$RC = 0.01 \times 20 \times 10^{-3} \text{ sec}$$

$$v_o = -RC \frac{dv_i}{dt} = -0.2 \frac{dv}{dt} \text{ msec}$$

$$v_o = \begin{cases} -2V, & 0 < t < 1 \\ 2V, & 1 < t < 3 \\ -2V, & 3 < t < 4 \end{cases}$$

Thus $v_o(t)$ is as sketched below:

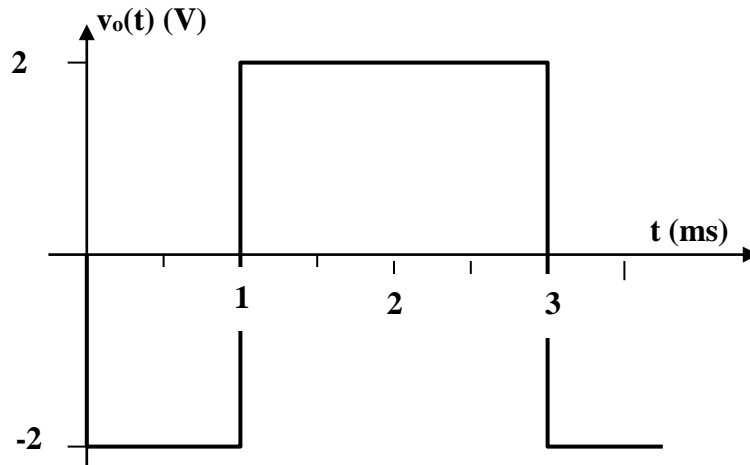

Solution 6.75

An op amp differentiator has $R = 250 \text{ k}\Omega$ and $C = 10 \text{ }\mu\text{F}$. The input voltage is a ramp $r(t) = 7t \text{ mV}$. Find the output voltage.

Solution

$$v_o = -RC \frac{dv_i}{dt}, \quad RC = 250 \times 10^3 \times 10 \times 10^{-6} = 2.5$$


$$v_o = -2.5 \frac{d}{dt}(7t) = \mathbf{-17.5 \text{ mV}}.$$

Solution 6.76


$$v_o = -RC \frac{dv_i}{dt}, \quad RC = 50 \times 10^3 \times 10 \times 10^{-6} = 0.5$$

$$v_o = -0.5 \frac{dv_i}{dt} = \begin{cases} -10, & 0 < t < 5 \\ 5, & 5 < t < 15 \end{cases}$$

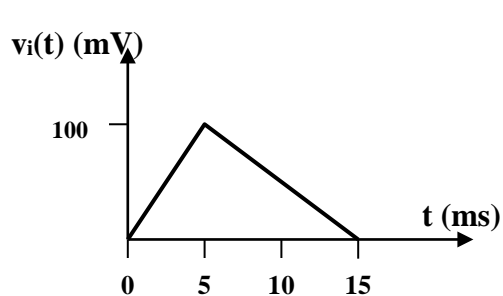The input is sketched in Fig. (a), while the output is sketched in Fig. (b).



(a)

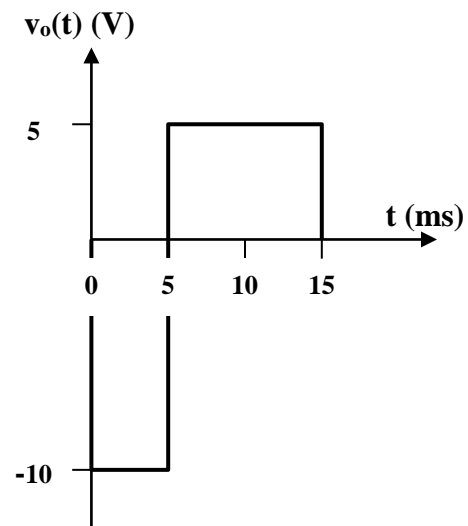

(b)

Solution 6.77




$$i = i_R + i_C$$

$$\frac{v_i - 0}{R} = \frac{0 - v_o}{R_F} + C \frac{d}{dt}(0 - v_o)$$

$$R_F C = 10^6 \times 10^{-6} = 1$$

$$\text{Hence } v_i = -\left(v_o + \frac{dv_o}{dt}\right)$$

Thus v_i is obtained from v_o as shown below:

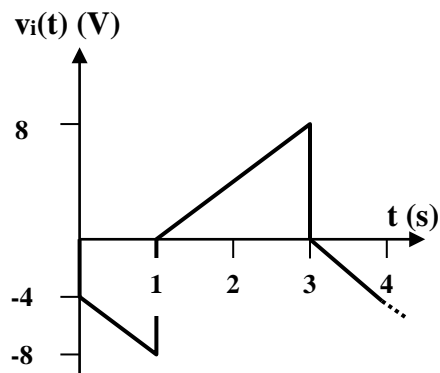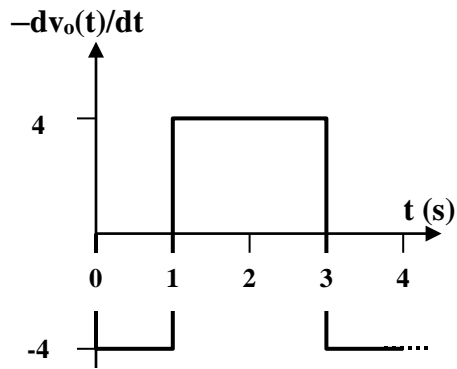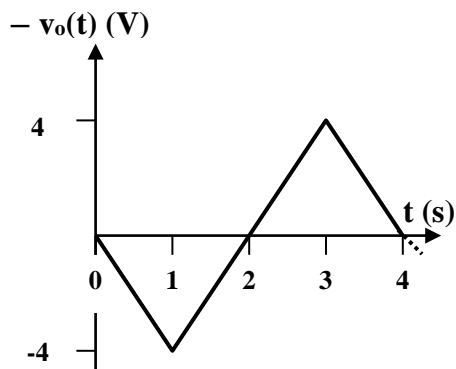

Solution 6.78

Design an analog computer to simulate


$$\frac{d^2 v_o}{dt^2} + 2 \frac{dv_o}{dt} + v_o = 10 \sin 2t$$

where $v_o(0) = -6$ V and $v_o'(0) = 0$.

Solution

$$\frac{d^2 v_o}{dt^2} = 10 \sin 2t - \frac{2dv_o}{dt} - v_o$$

Thus, by combining integrators with a summer, we obtain the appropriate analog computer as shown below, where $v_o(0) = -6$ V:

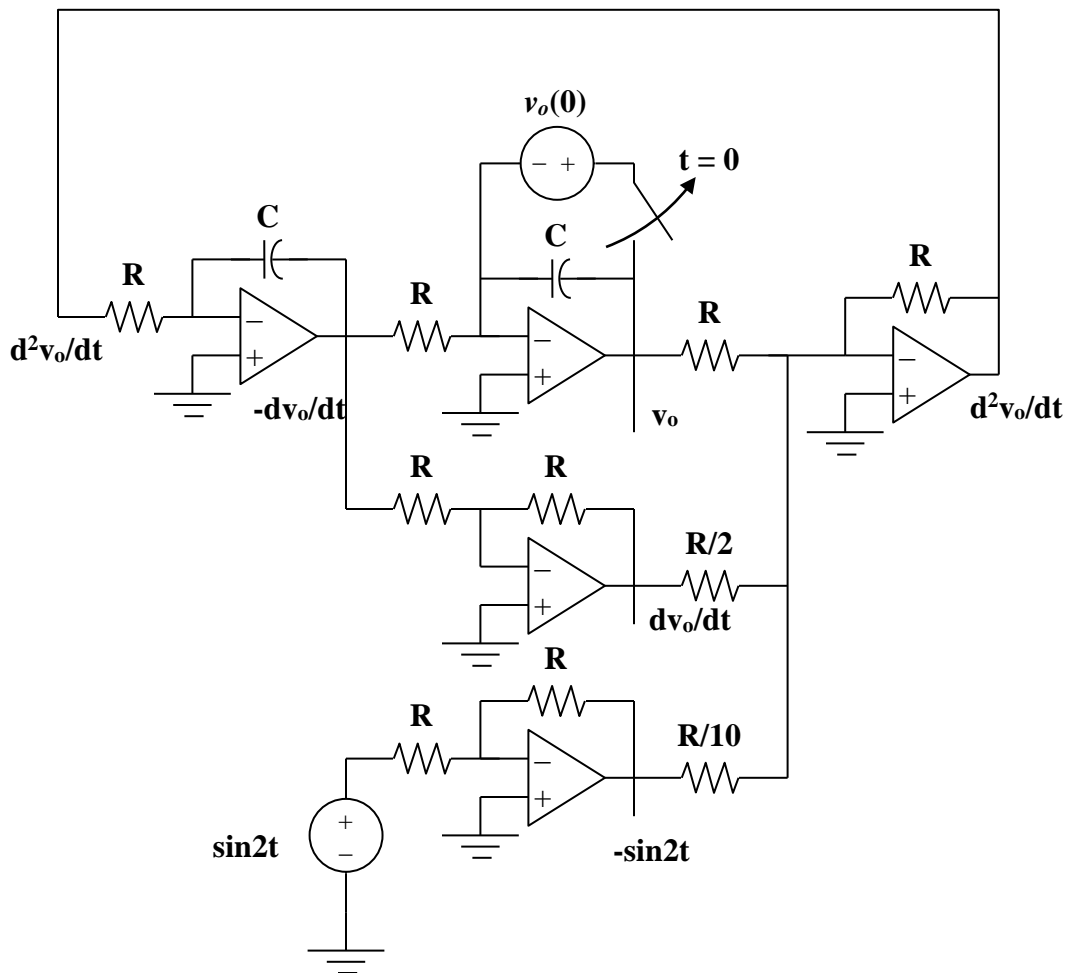


Solution 6.79

Design an analog computer circuit to solve for $v(t)$ given the following equation and a value for $f(t)$ and that $v(0) = 0$ V.

$$\frac{dv(t)}{dt} + 3v(t) = \int f(t) dt$$

Solution

We can write the equation as $\frac{dv(t)}{dt} = \int f(t) dt - 3v(t)$. As with any design problem, there are many acceptable solutions, this is just one of them.

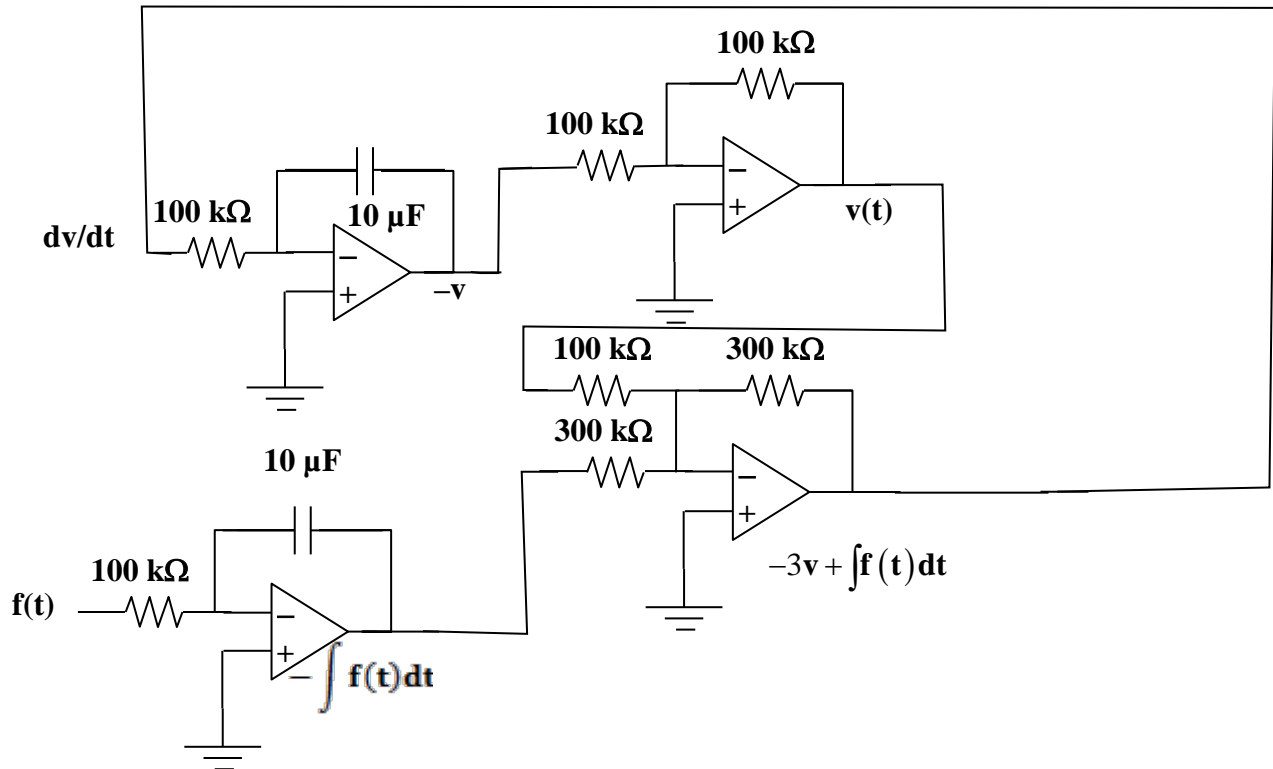

Solution 6.80

From the given circuit,

$$\frac{d^2 v_o}{dt^2} = f(t) - \frac{1000k\Omega}{5000k\Omega} v_o - \frac{1000k\Omega}{200k\Omega} \frac{dv_o}{dt}$$

or

$$\frac{d^2 v_o}{dt^2} + 5 \frac{dv_o}{dt} + 2v_o = f(t)$$

Solution 6.81


Design an analog computer to simulate the following equation to solve for $v(t)$ (assume the initial conditions are zero):

$$\frac{d^3 v(t)}{dt^3} + 3 \frac{dv(t)}{dt} = 4f(t).$$

Solution


If we integrate both sides we can end up with $\frac{d^2 v(t)}{dt^2} = -3v(t) + 4 \int f(t) dt$.

As with any design problem there are many acceptable solutions, this is one of them. Note, the above can also be solved without the integration step and would also be an accurate solution.

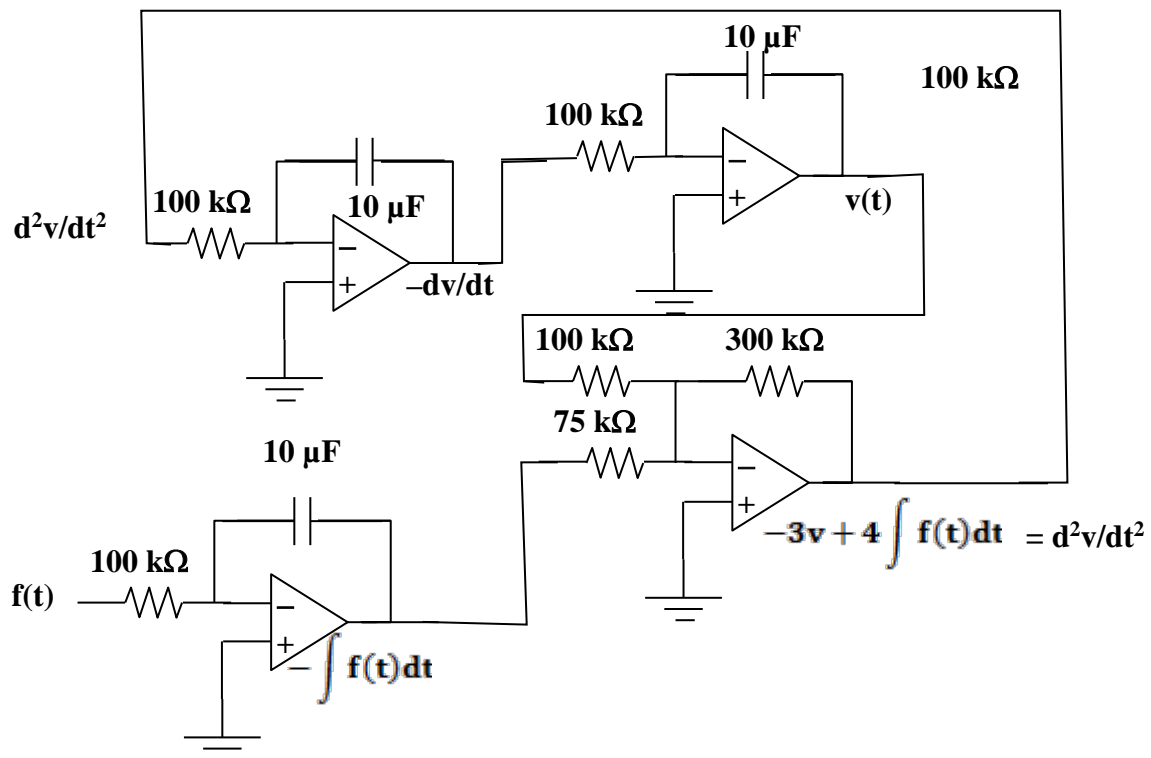

Solution 6.82

The circuit consists of a summer, an inverter, and an integrator. Such circuit is shown below.

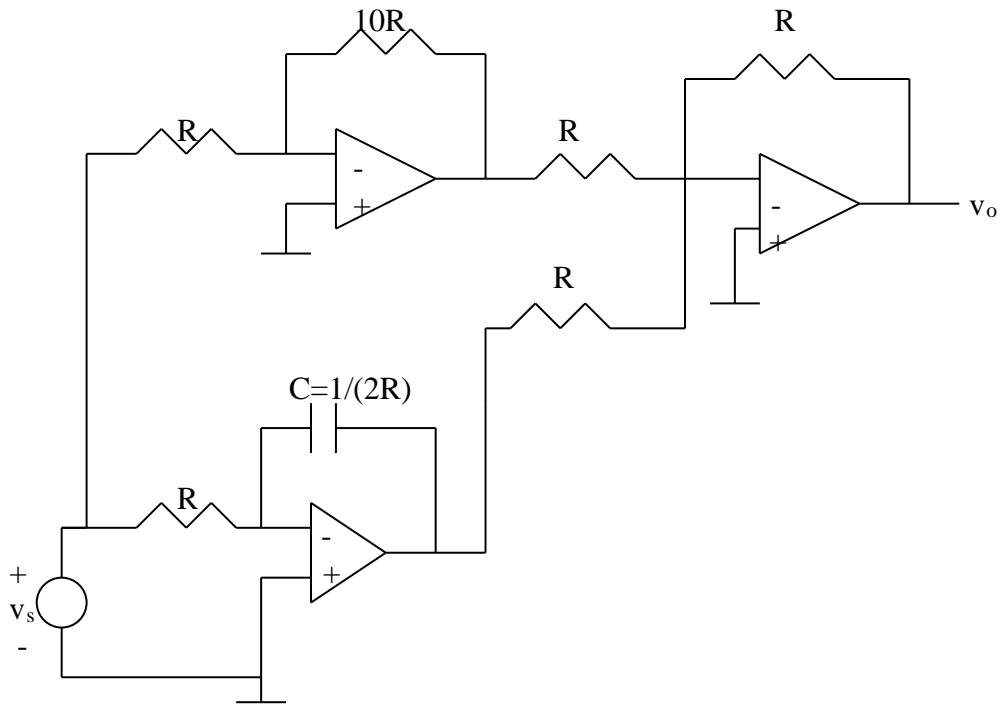


Solution 6.83

Your laboratory has available a large number of $5\text{-}\mu\text{F}$ capacitors rated at 150 V . To design a capacitor bank of $10\text{-}\mu\text{F}$ rated at 600 V , how many $5\text{-}\mu\text{F}$ capacitors are needed and how would you connect them?

Solution

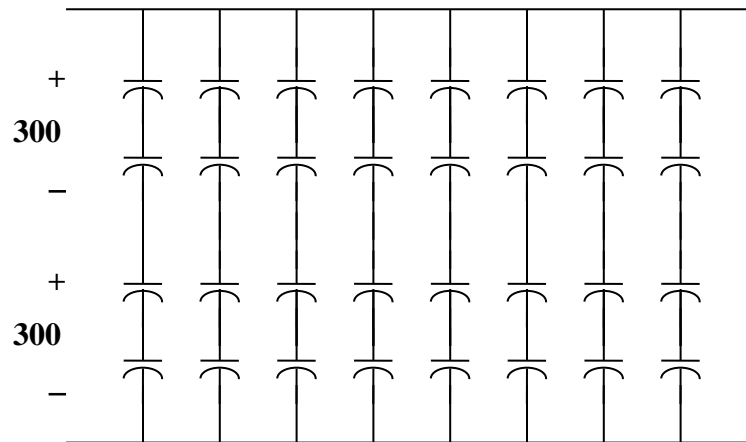Since four $5\text{ }\mu\text{F}$ capacitors in series gives $1.25\text{ }\mu\text{F}$, rated at 600V , it requires 8 groups in parallel with each group consisting of four capacitors in series, as shown below:



Answer: **Eight groups in parallel with each group made up of four capacitors in series.**

Solution 6.84

An 8-mH inductor is used in a fusion power experiment. If the current through the inductor is $i(t) = 10\cos^2(\pi t)$ mA, for all $t > 0$ sec, find the power being delivered to the inductor and the energy stored in it at $t=0.5$ s.

Solution

$$v = L(di/dt) = 8 \times 10^{-3} \times 10 \times (-2\pi) \cos(\pi t) \sin(\pi t) 10^{-3} = -80\pi \sin(2\pi t) \mu\text{V}.$$

$$p = vi = -80\pi \sin(2\pi t) 10 \cos^2(\pi t) 10^{-9} \text{ W. At } t = 0.5 \text{ s, } p(0.5) = 0 \text{ W.}$$

$$\text{At } t = 0.5 \text{ s, } w(0.5) = (1/2)Li(0.5)^2 = 0.5 \times 8 \times 10^{-3} (10 \times 10^{-3} \times 0)^2 = 0 \text{ J.}$$

Solution 6.85

It is evident that differentiating i will give a waveform similar to v . Hence,

$$v = L \frac{di}{dt}$$

$$i = \begin{cases} 4t, & 0 < t < 1\text{ms} \\ 8 - 4t, & 1 < t < 2\text{ms} \end{cases}$$

$$v = L \left[\frac{di}{dt} = \begin{cases} 4000L, & 0 < t < 1\text{ms} \\ -4000L, & 1 < t < 2\text{ms} \end{cases} \right]$$

But,

$$v = \begin{cases} 5\text{V}, & 0 < t < 1\text{ms} \\ -5\text{V}, & 1 < t < 2\text{ms} \end{cases}$$

Thus, $4000L = 5 \longrightarrow L = 1.25 \text{ mH}$ in a **1.25 mH inductor**

Solution 6.86

$$v = v_R + v_L = Ri + L \frac{di}{dt} = 12 \times 2te^{-10t} + 200 \times 10^{-3} \times (-20te^{-10t} + 2e^{-10t}) = \underline{(0.4 - 20t)e^{-10t} \text{ V}}$$