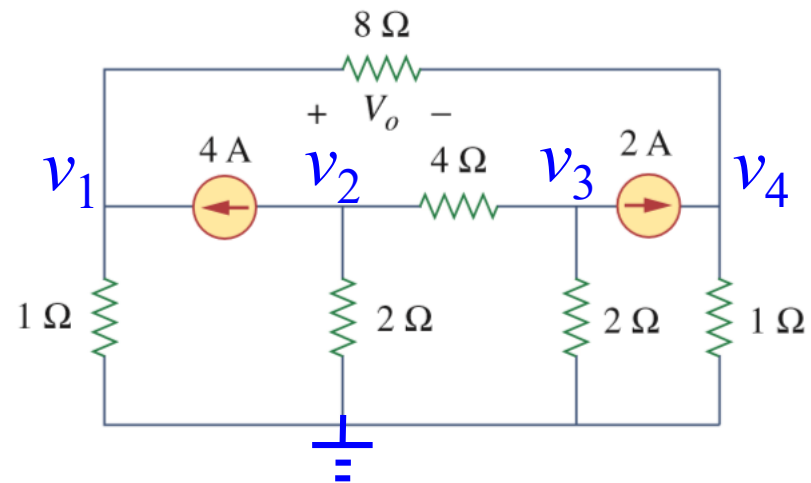


Current flowing into node A:

$$\frac{v_b - v_a}{R}$$

Current flowing out of node A:


$$\frac{v_a - v_b}{R}$$



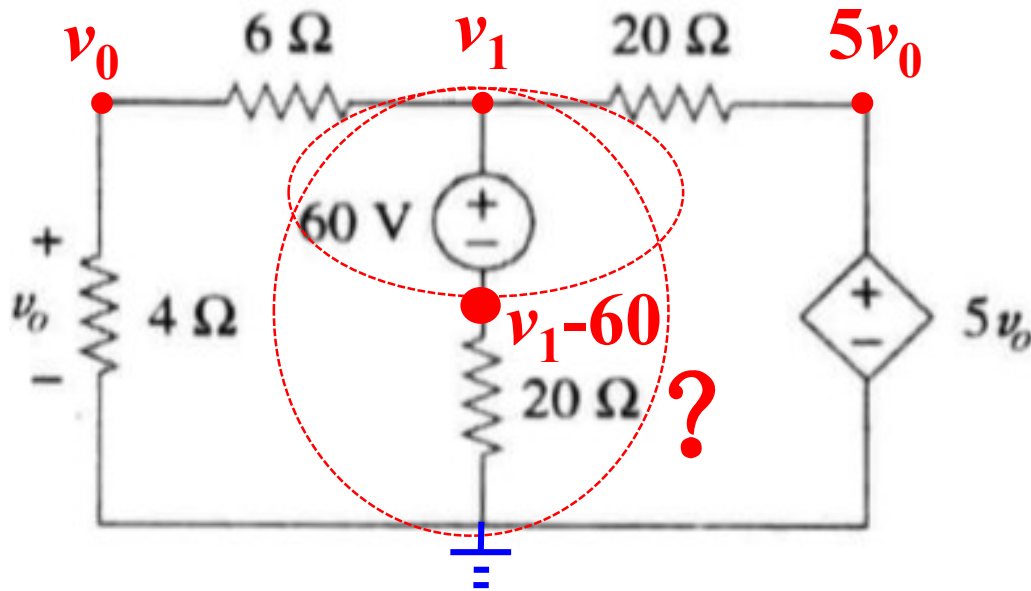3.8 P115

A supernode is formed by enclosing a voltage source (dependent or independent) connected between two non-reference nodes and any elements connected in parallel with it.

Using nodal analysis, find v_o in the circuit of Fig. 3.57.




What to do

$$\frac{v_0}{4} + \frac{v_1 - 5v_0}{20} + \frac{v_1 - 60}{20} = 0$$

$$\frac{v_0}{4} = \frac{v_1}{10}$$


解得 $v_0 = 12V$.

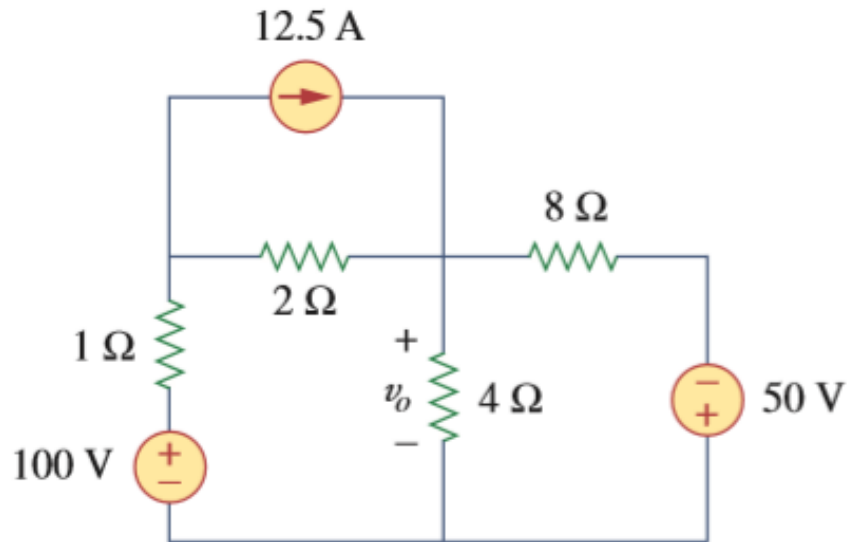3.14 Using nodal analysis, find v_o in the circuit of Fig. 3.63.




3.14

Solution:

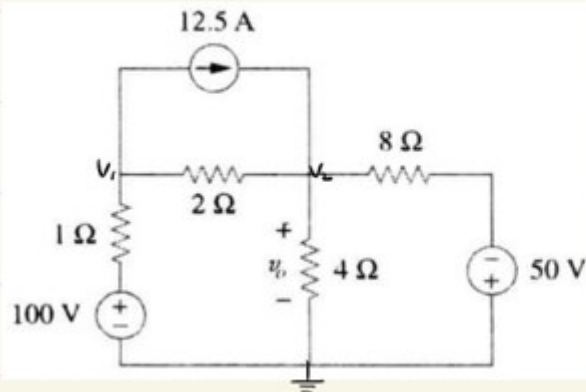

$$\left\{ \begin{array}{l} \frac{v_1 - 100}{1} + 12.5 + \frac{v_1 - v_2}{2} = 0 \\ \frac{v_1 - v_2}{2} + 12.5 = \frac{v_2}{4} + \frac{v_2 + 50}{8} \\ v_o = v_2 \end{array} \right. \Rightarrow v_o = 50 \text{ V}$$

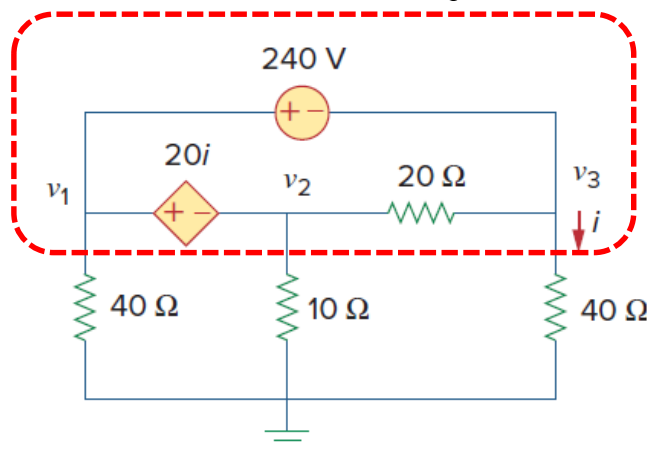3.20 For the circuit in Fig. 3.69, find v_1 , v_2 , and v_3 using nodal analysis.



Solution•

$$v_1 + v_2 + v_3: \frac{v_1}{40} + \frac{v_2}{10} + \frac{v_3}{40} = 0$$

$$v_1 - v_2 = 20i$$

$$v_1 - v_3 = 240$$

$$i = \frac{v_3}{40}$$




$$v_1 = -60V$$


$$v_2 = 90V$$

$$v_3 = -300V$$

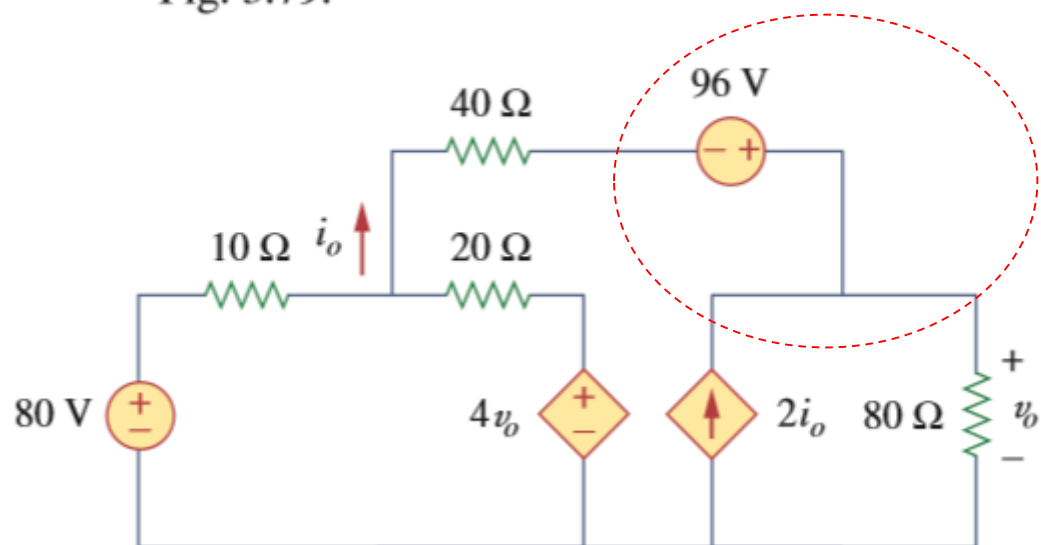3.30 Using nodal analysis, find v_o and i_o in the circuit of Fig. 3.79.




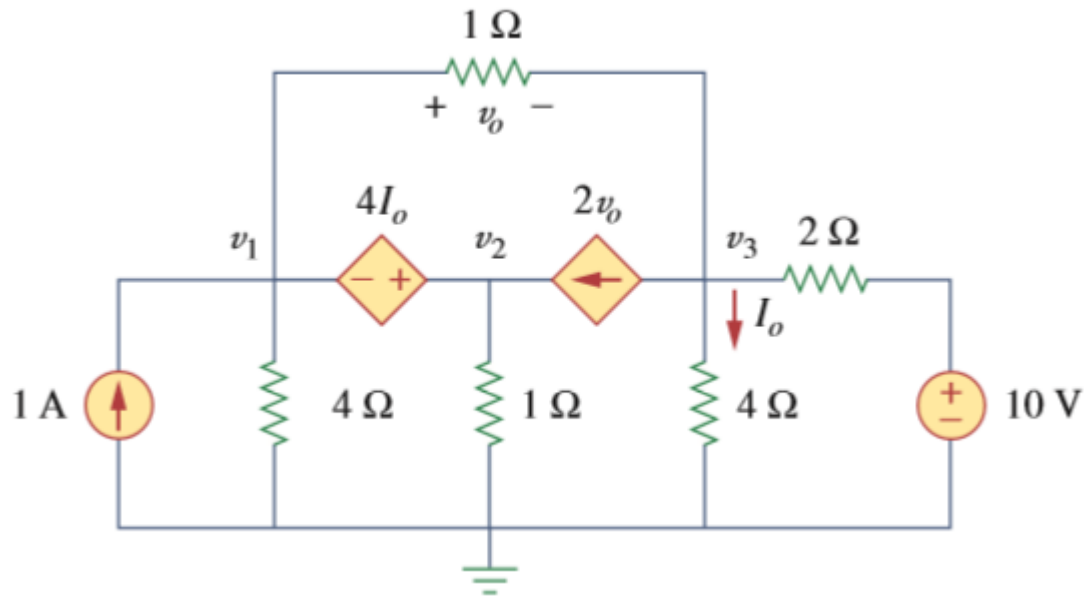3.31 Find the node voltages for the circuit in Fig. 3.80.




3.31

Solution:

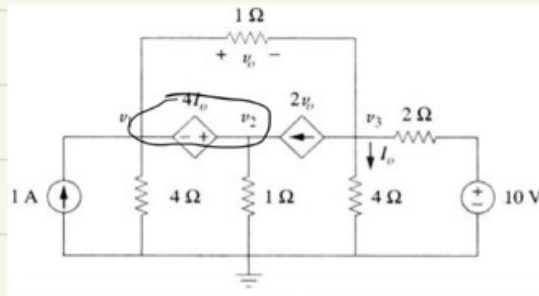


$$\left\{ \begin{array}{l} 1 + 2v_o = \frac{v_1}{4} + \frac{v_2}{1} + \frac{v_1 - v_3}{1} \\ \frac{v_1 - v_3}{1} + \frac{10 - v_3}{2} = 2v_o + \frac{v_3}{4} \\ v_o = v_1 - v_3 \\ v_2 - v_1 = 4I_o \\ I_o = \frac{v_3}{4} \end{array} \right. \Rightarrow \left\{ \begin{array}{l} v_1 = 4.97 \text{ V} \\ v_2 = 4.85 \text{ V} \\ v_3 = -0.12 \text{ V} \end{array} \right.$$

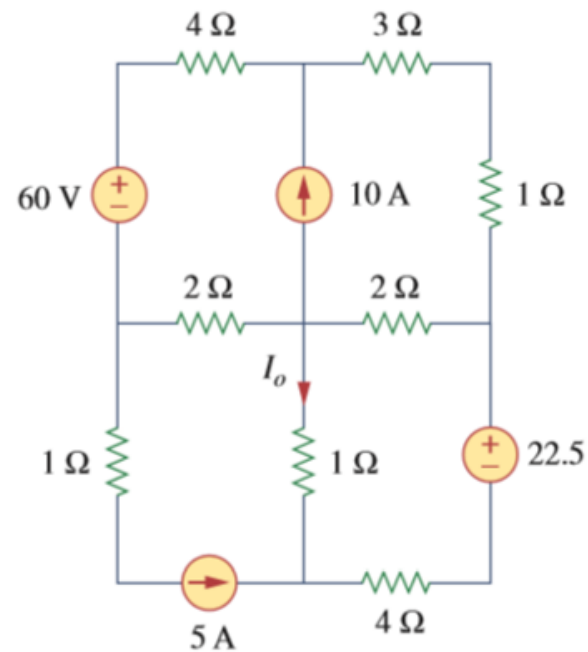3.38 Apply mesh analysis to the circuit in Fig. 3.85 and obtain I_o .



Solution:

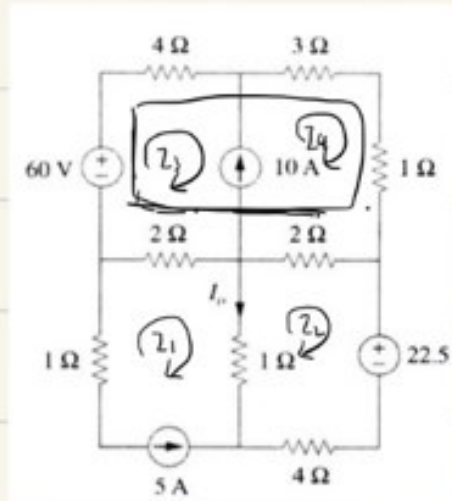

$$I_1: I_1 = -5A$$

$$I_2: 1(I_2 - I_1) + 2(I_2 - I_4) + 22.5 + 4I_2 = 0$$


$$\text{Super mesh: } -60 + 4I_3 + 3I_4 + 1I_4 + 2(I_4 - I_2) + 2(I_3 - I_1) = 0$$

$$I_{3,4}: I_4 - I_3 = 10A$$


$$I_o = I_1 - I_2$$

$$\Rightarrow I_o = -\frac{29}{8}A$$

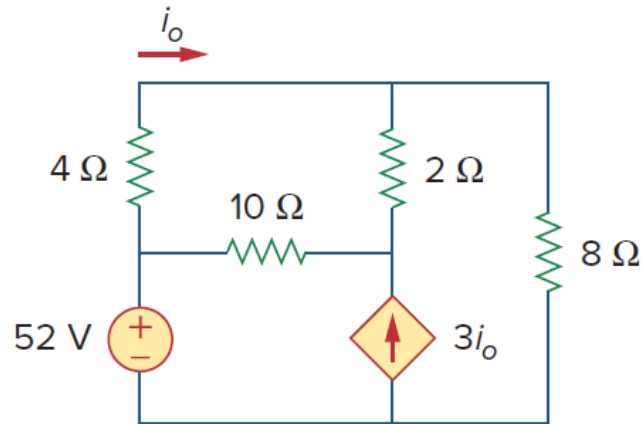3.50 Use mesh analysis to find the current i_o in the circuit of Fig. 3.95.




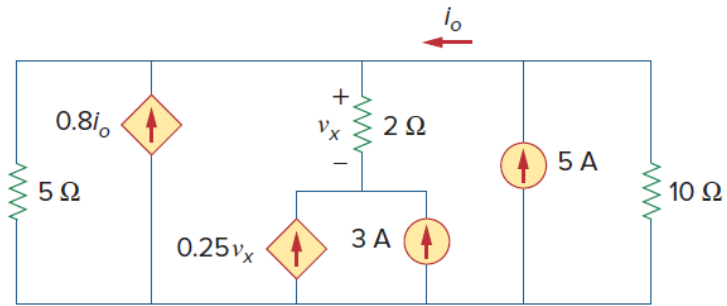3.63 Find v_x and i_o in the circuit shown in Fig. 3.107.



3.67 Obtain the node-voltage equations for the circuit in

Fig. 3.111 by inspection. Then solve for V_o .

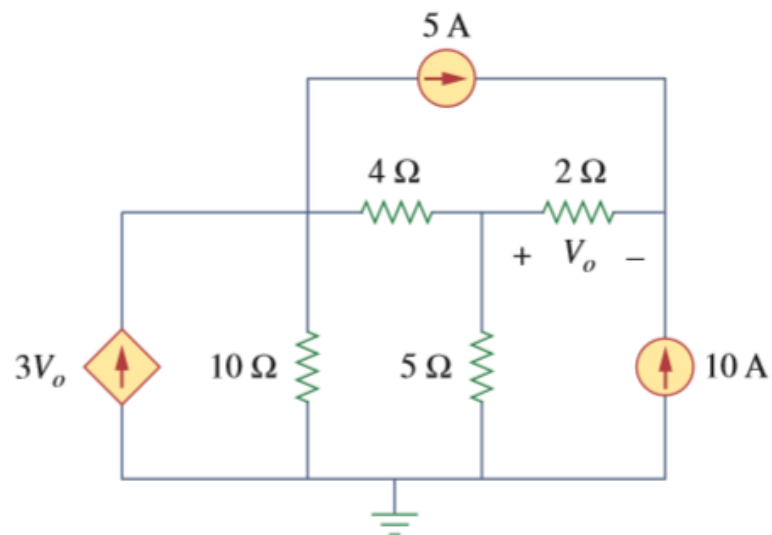

3.73 Write the mesh-current equations for the circuit in Fig. 3.117.

